
Studies on Programmable Charge Amplifier

GSI, FAIR FEE Workshop

Trampitsch Gerd CERN - PH/ED


Overview

- ◆ **Ways towards a programmable Analog Front End**
 - Programmable Analog Parameters
 - Input Charge Range
 - Gain
 - Feedback Resistance of the CSA
 - Peaking Time
 - Sensitivity to signals with positive and negative polarities
- ◆ **Design of a Charge Sensitive Amplifier and Shaper in the IBM 0.13um CMOS process**
 - Architecture
 - Schematic and Layout of the CSA
 - Characteristics of the Circuit


Changing the Conversion Gain

◆ Adopt Input Stage to different Charge Ranges

 - Different Detectors
- Calibration of Conversion Gain
- Calibration of imperfect Pole Zero Cancellation
- Input of an inverting Amplifier is held at constant Voltage → Constant On-Resistance of Switches



 Sensitivity to positive and negative signals



Limited Output Swing


- $V_{outmax} = V_{b3} + V_{th}$
- $V_{outmin} = V_{sat4}$
- Max Output swing
 - $V_{dd} - 3V_{dsat}$
- Gets less when designing for low Noise
- At 1.5V supply, only some hundreds of mV

Solution

- Design Rail to Rail Preamp → Allows more Gain in the first Stage → Less Feedback Capacitance
- Change DC Level of the Amplifier's Output according to the expected Input Signal (Ions or Electrons)

Sensitivity to positive and negative signals



$$I_{fb} = (V_{out} - V_{target})/R$$

 

- ◆ Transconductor sets the output dc level to the desired voltage (V_{target}) independently to the input dc Level
 - This architecture can handle both, positive and negative going signals
 - Effective Feedback Resistance is $100R$
 - I_{fb} gets divided by current mirrors with different aspect ratios

Changing or Adjustment of the Peaking Time

  
- ◆ Basic 1st Order Filter Cells allow to tune Gain and Time Constants Independently
- ◆ Build Higher Order filters by cascading of 1st Order Cells or Biquads
- ◆ RC Filter
 - Better Linearity
- ◆ Gm-C Filter
 - Wider Tuning Range of Time Constants



Design for low noise in CMOS 0.13um

- ◆ **Increased gm**
 - + Better ENC (Equivalent Noise Charge)
Should ideally improve by ca. 20% per CMOS Generation
- ◆ **Low Supply Voltage limits SNR**
 - Dynamic Range
 - Rail to Rail Design
 - Invest Power to improve SNR
 - ◆ Big Capacitors
 - ◆ Design Shaping Circuit for Low Noise
- ◆ **Reduced Gate Oxide Thickness**
 - Gate Tunneling Current
 - + Radiation Tolerance
- ◆ **Short Channel Effects**
 - Hot Carrier Stress – Reliability, Noise
 - Velocity Saturation

 Architecture – CSA & Semi Gaussian Shaper




- ◆ The Resistance of the Feedback Element is a function of its Gate to source Voltage
 - V_{gs} is the same for both Transistors
 - Neglecting mismatches between the two transistors the according resistance should track
 - The CSA's input dc level is equal to its output dc level
 - The Current Gain is -20

CSA and Shaper


◆ Characteristics of current Design

- ENC ca. 300 electrons_{rms} (@12pF Cin)
- Peaking Time 100ns
- 4th Order Semi Gaussian Shaper
- 9mW Power Consumption
- Charge Range 0 - 160fC input signal with negative polarity
- 30pF Driving Capability of the Output Stage
- Differential Output
- Feedback Resistance of CSA ca. 10 MOhm
- Designed in a modern Process(0.13um)
 - Gives the possibility to integrate the Digital and Analog Signal Processing on the same Chip

 Charge Sensitive Amplifier (Folded Cascode)



Charge Sensitive Amplifier (Layout)

 

- ◆ **The area is dominated by the size of the Capacitors**
 - IBM CMOS 8RF, 0.13 um
 - CSA Area = $50\text{um} \times 500\text{um} = 0.025\text{mm}^2$
 - Total Area per Channel = 0.075mm^2
 - 16 Channel Chip → 2.50mm^2