


Time measurement with differential ring oscillators

Peter Fischer, Michael Ritzert


Lehrstuhl für Schaltungstechnik und Simulation
Institut für Technische Informatik
Universität Mannheim

Talk Outline

 - Overview of common circuit concepts for time stamping
- Design issues
- Recent results with a ring oscillator test chip
- Summary and next steps




Overview of Circuit Concepts

 


...and mixtures of these concepts

Fast Counter

 

- Counter must use Gray coding or similar to avoid scrambled bits when latches jitter
 - + very simple concept
 - + stable and predictable bins
 - + low power
- may reach some GHz in $0.18\mu\text{m}$, i.e. bin widths of some $\sim 200\text{ps}$
- Improvement with staggering of several counters possible


Ring Oscillator: Principle

 


- Principle:
 - a ring oscillator generates thermometer code time stamps. Needs overall inversion!
 - a ('slow') coarse counter generates the MSBs
 - input signal is used to latch values
 - Ring oscillator can be locked to a reference clock with a PLL
- + fairly simple, 'digital' design
- + 'infinite' dynamic range
- + no calibration required (with PLL), guaranteed stability
- limited bin size (but several times better than with counter: only 'inverter' delay)

Ring Oscillator / DLL: Design variations

- Resolution can be increased by:
 - using multiple channels with delayed stop signals
 - running several phase coupled ring oscillators
 - ⇒ using slow / fast buffers between ring oscillator and latches
 - ...
- Can use ‘single ended’ CMOS logic (see H. Deppe, GSI)
 - simple
 - issues: supply sensitivity, ring oscillator frequency range, linearity (inversion!)
- Or can use differential logic
 - uncommon
 - more complex, if everything (also PLL etc.) is done differentially
 - trimming simpler (change bias current)

 


Pulse Shrinking

 


- Principle:
 - Pulse is circulated in an (ideal) delay line.
 - **One** pulse shrinking element makes pulse shorter by constant ε with every ‘turn’
 - Width is determined by counting ‘turns’ until pulse vanishes. $W = N \times \varepsilon$
- Delay line must be longer than max. pulse width W_{\max}
- + Very low power
- Conversion time is long and linked to resolution: $T = W_{\max} \times W_{\max} / \varepsilon$
- Difficult calibration
- Sensitive to matching and noise (?)

TAC + ADC

 

 
- Principle:
 - generate a linear voltage ramp during the strobe signal
 - convert the voltage to a digital value with an ADC
- Ramp can be generated with
 - constant current charging of a capacitor
 - an 'interpolating DAC' (see H. Flemming, GSI)
- + very high resolution
- needs ADC (space, power, calibration!)
- extra circuitry needed to generate MSBs
- Issues are calibration and stability




from CBM TSR

Differential Logic

- Current I_{bias} is steered to left or right load circuit with a differential pair
- The load circuit converts to current step to a voltage step
- 'ideal' load circuit:
 - The V_{hi} -level is fixed by the maximum possible input voltage to the switch block ($\sim VDD - V_{TP} - V_{DSat}$)
 - The V_{lo} -level is fixed by the voltage swing required to 'fully' switch current in the switch block.
 - The plateau at $\frac{1}{2} I_{bias}$ guarantees equal rise and fall times (C_{load} is charged/discharged with $\pm \frac{1}{2} I_{bias}$)
- If V_{hi} and V_{lo} are independent of I_{bias} , the speed of the gate can be varied significantly with I_{bias}

 




CML principle (inverter)

 

'ideal' load characteristic



Proposed Load Circuit ($I \rightarrow U$ converter)

   - Parallel connection of:
 - NMOS operated as a current source with adjustable source voltage VSS
 - diode connected NMOS (other solutions are possible)



Differential Gates

  
- Logic function is implemented in a switch tree
 - Complex functions can be implemented in one gate (saving current!)



Function	CMOS		Differential	
	PMOS	NMOS	PMOS	NMOS
and2	2	2	4+1	4
and3	3	3	6+1	4
xor2	5(3)	5(3)	6+1	4
mux2	3	3	6+1	4
latch	4	4	6+1	4
Latch w. input MUX	7	7	10+1	4


Design Issues

- Design goals are
 - minimal bin width = max. resolution
 - linearity
 - dynamic range
 - low dead time = high double hit rate
 - low power
 - easy calibration
 - stable operation (with temperature, power supply etc.)
 - multi-chip operation
- Watch
 - matching between devices:
better for larger devices, but that costs power and/or speed...
 - radiation hardness
 - technology scaling (this favors ‘digital’ designs)

 


AMS 0.35μm Test Chip ‘TC3’

 - Block diagram shows only relevant parts
- Note that the differential inputs have an additional (analog) discriminator on this chip




Test Setup

 - We have developed a very compact USB based test setup.




Measurements: Ring Oscillator Speed

 - 16 stage Ring oscillator speed can be measured accurately on a scaled down digital output
- Speed can be tuned in a wide range as a function of the bias current (per stage)
- Standard operation point: **150 ps / bin @ 250 μ A per stage**




Hit bins for two different delays

 - Inject in the **two channels** with a constant (cable) delay
- VCO speed: **150ps / bin** $\Rightarrow \sigma_{\text{ideal}} = 43.3 \text{ ps}$
- Plot time **difference** (here in bins) for two delays (**red**)
- Also plot fine grain result using (uncalibrated) 'slow' buffers (**green**)
- Note that measured **coincidence sigma** = $\sqrt{2} \times \text{single channel sigma}$



Bin occupancies (i.e. relative bin width)

 
- Generate hits at random moments. Display counts for both channels
 - Equal time bin widths would give homogeneous bin occupancy
 - Shorter bins have lower occupancy



- This measurement can be used to **correct for bin size**
- Note: variations are from transistor mismatch and stable in time – a chip ‘fingerprint’

Bin width correction

 
- Use bin width information (fast / slow / mixed) for correction
- Maybe this result can still be optimized by adjusting the delay of the slow buffer...



- Note that any non-linearities are included in this measurement!

Next Test Chip: UMC 0.18μm (GSI Submission)

 - 16 stages
- 2 groups of latches
- VCO with or without delay trim
- VCO: $260 \times 30 \mu\text{m}^2$
- Trim: $260 \times 120 \mu\text{m}^2$



Summary and outlook

- We pursue a **ring oscillator** approach using **differential logic**
- Single channel resolution $\sigma \sim 35\text{ps}$ already reached in $0.35\mu\text{m}$ technology
- Advantages of the ring oscillator are:
 - stability (if locked to reference frequency with a PLL)
 - ‘infinite’ dynamic range (with wide ‘coarse’ counter)
 - very small dead time
- Is power consumption acceptable ? ($<15\text{mA} @ 2\text{V}$ per channel + VCO...)
- Expect factor ~ 2 improvement in $0.18\mu\text{m}$, i.e. $\sigma \sim 25\text{ps}$ (test chip has only fast bins).
- Next steps:
 - Test UMC chip (is back, but not tested yet due to bonding problems...)
 - Increase speed, linearity, resolution – work is in progress

