

**XXXV PANDA Collaboration Meeting**  
**29<sup>th</sup> November 2010, GSI**

# **ToPix3 Analog Cell Design & Simulation**



**Thanushan Kugathasan - Panda GE Torino Group**  
*INFN Sezione di Torino, Italy - Università di Torino, Italy;*



# Pixel Readout Cell Specification

Pixel Size	100 $\mu$ m x 100 $\mu$ m
Input charge range	$\approx$ 1fC to 50fC
Noise (ENC)	$<$ 200 e <sup>-</sup>
Power consumption	15 $\mu$ W
Input polarity	Selectable
Leakage compensation	Up to 50 nA
Average Hit Rate	$\approx$ 10 <sup>3</sup> hits/s
Trigger	Self triggering
Radiation tolerance	10 Mrad

Simultaneous time stamping (12bit) and charge measurement

Good time resolution  $\approx$ 2 ns rms (at 155 MHz clock) with  $2 \cdot 10^7$  ann/s


**Technology CMOS 8RF 130nm**

# Time Over Threshold

Constant Current Feedback

$$V_{out}(t) = \frac{Q_{in} - I_{dis}t}{C_f}$$

$$ToT = \frac{Q_{in}}{I_{dis}}$$

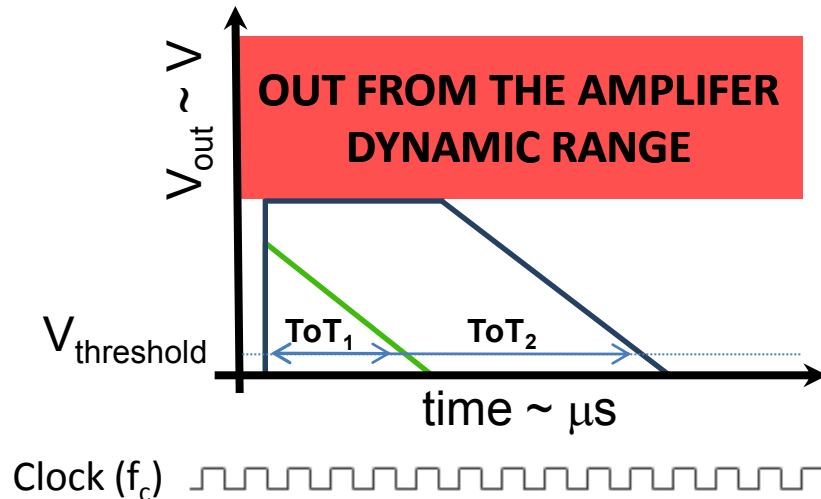


$$\delta Q = \frac{1}{f_c} \frac{\partial Q}{\partial t} \frac{1}{\sqrt{12}} = \frac{I_{dis}}{f_c} \frac{1}{\sqrt{12}}$$

With  $I_{dis} = 5\text{nA}$  and  $f_c = 155\text{MHz}$  the resolution in charge digitization is  $\delta Q = 59 e^-$

The ToT allows us to achieve good linearity and excellent resolution even when the preamplifier is saturated, thus making room for an high dynamic range.

# Analog Front-End

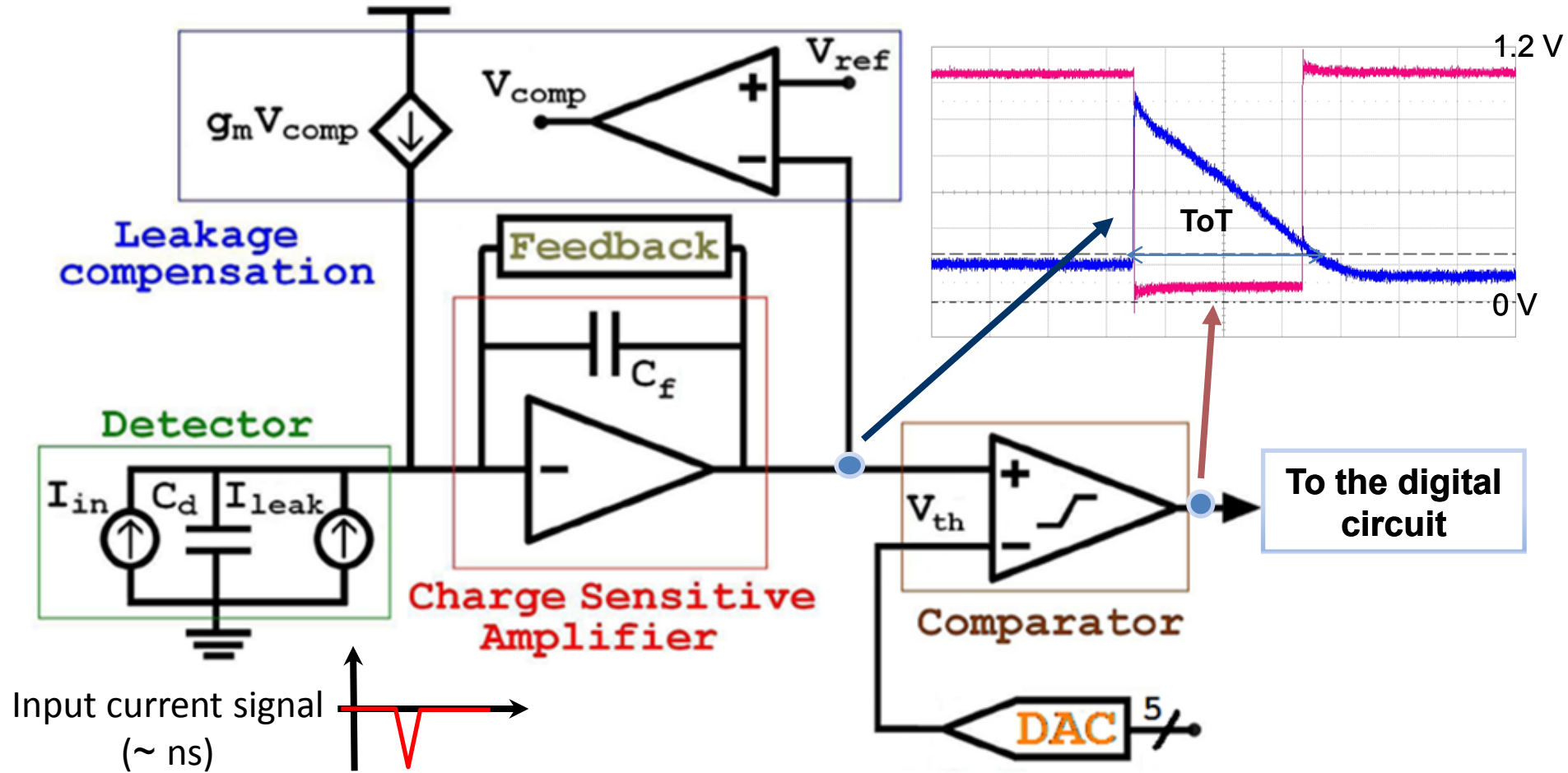


The Analog Front-End generates a pulse whose width is proportional to the injected charge by the sensor.

# Analog Cell Upgrades

- Increased gain by 2x ( $C_f = 24\text{fF} \rightarrow C_f = 12\text{fF}$ )
- Reduced size of the analog part (70% $\rightarrow$ 50%)
- Cut-off circuit for large signals ( $>50\text{fC}$ )
- Improved Baseline Holder for a better stability
- Test charge injection circuit bug corrected (charge up to  $35\text{fC}$ )

$$V_{out,peak} = \frac{Q_{in}}{C_f}$$

# Analog Cell Layout

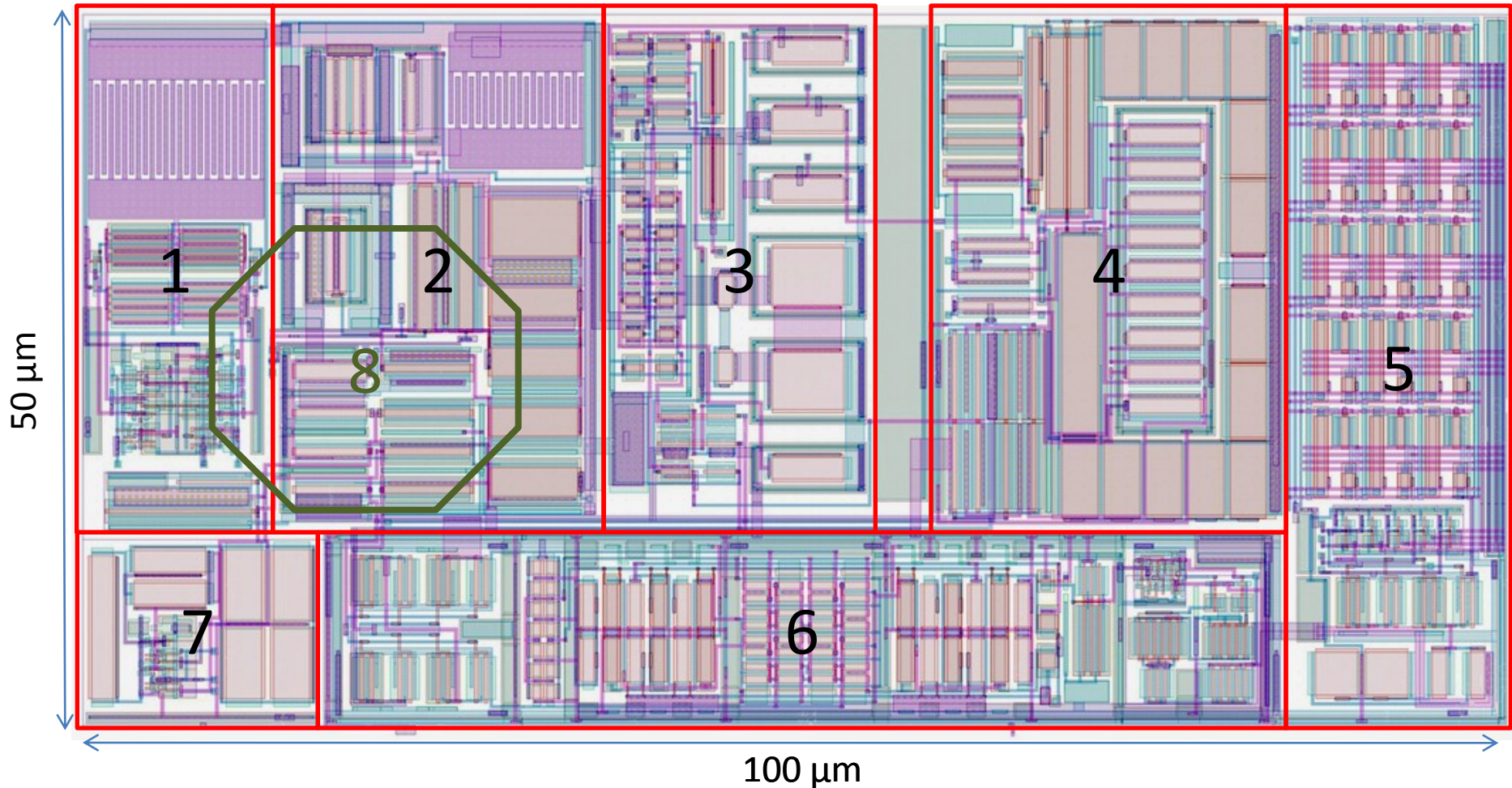

1. Test Pulse Injection

2. Preamplifier

3. Constant Current Feedback

4. Baseline Holder

5. 5 bit DAC for the threshold correction


6. Comparator

7. Large charge cut-off circuit

8. Bump bonding pad


# Post Layout - Monte Carlo Simulation

$Q_{in} = 1fC$   
200 Simulations

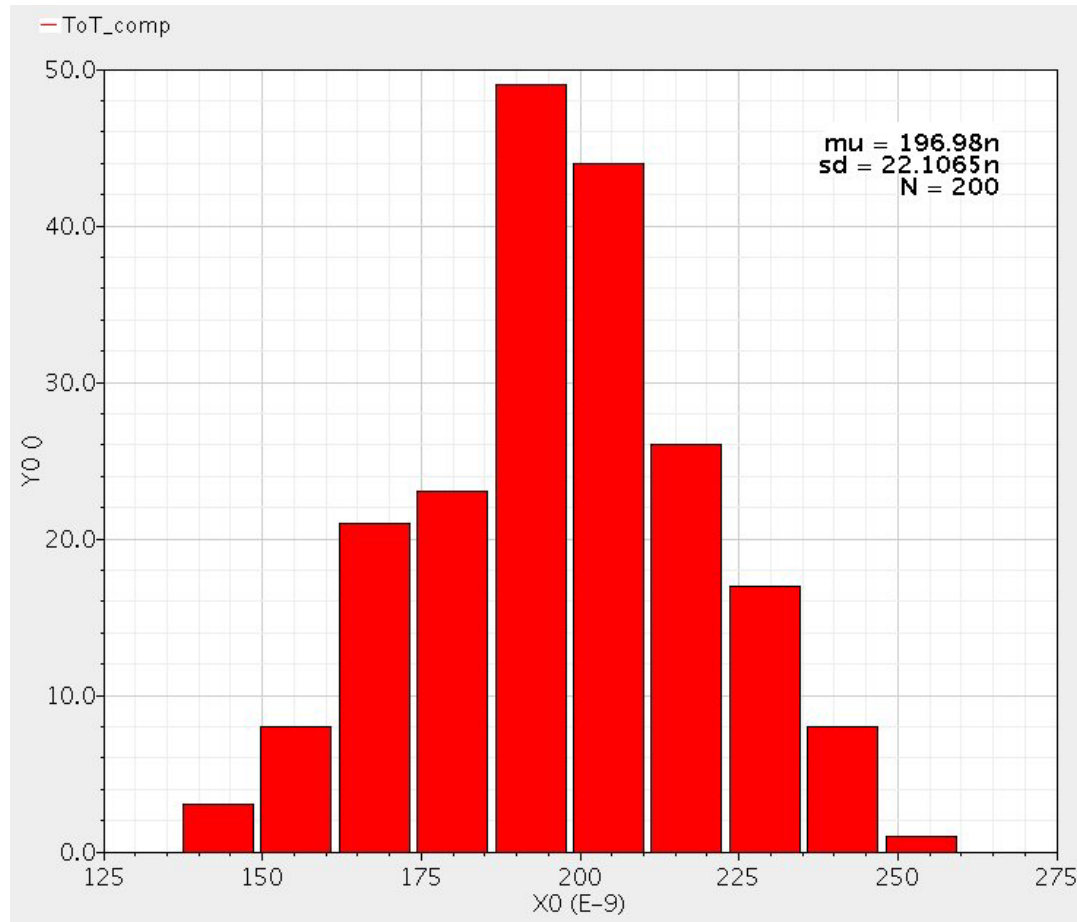


	Min	Max	Mean	Sigma
ToT (ns)	136.9	259.8	197.0	22.1

# Baseline dispersion

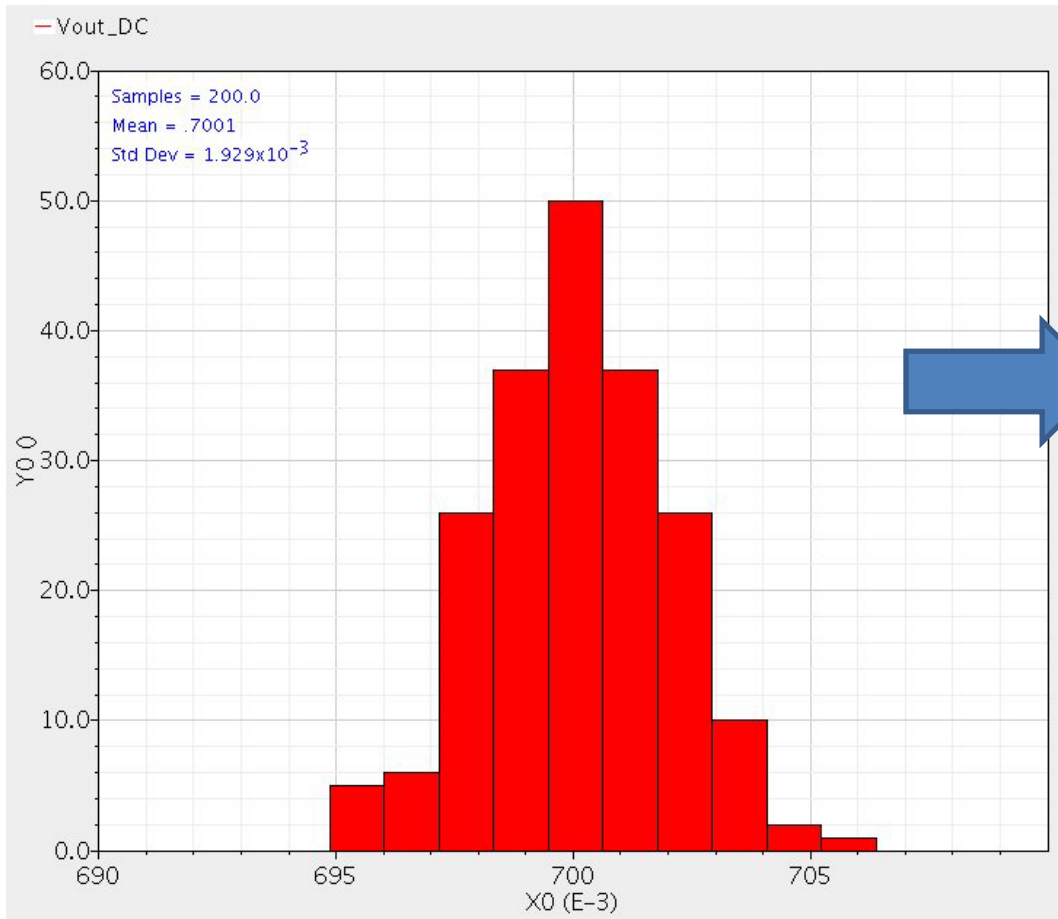

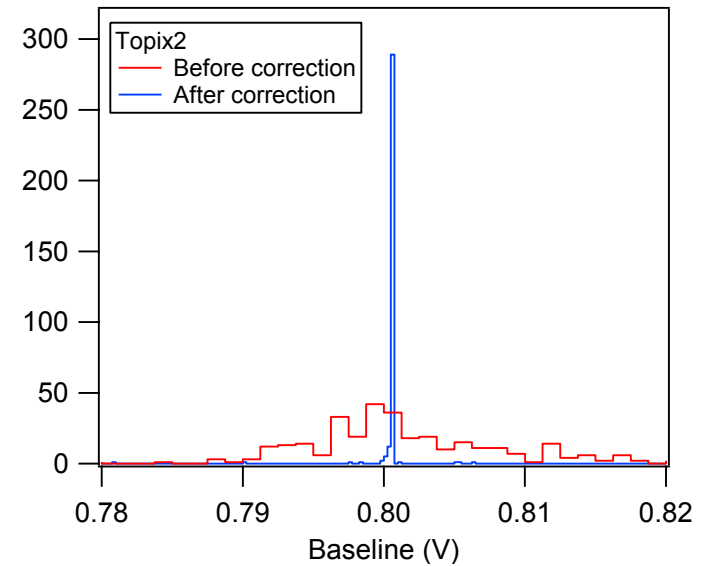ToPix2 - Threshold tuning on pixel by pixel basis




dispertion reduced to 2 mV


	Min	Max	Mean	Sigma
V <sub>out_DC</sub> (mV)	695.5	707.7	700.1	1.9



# Transient Noise Simulation

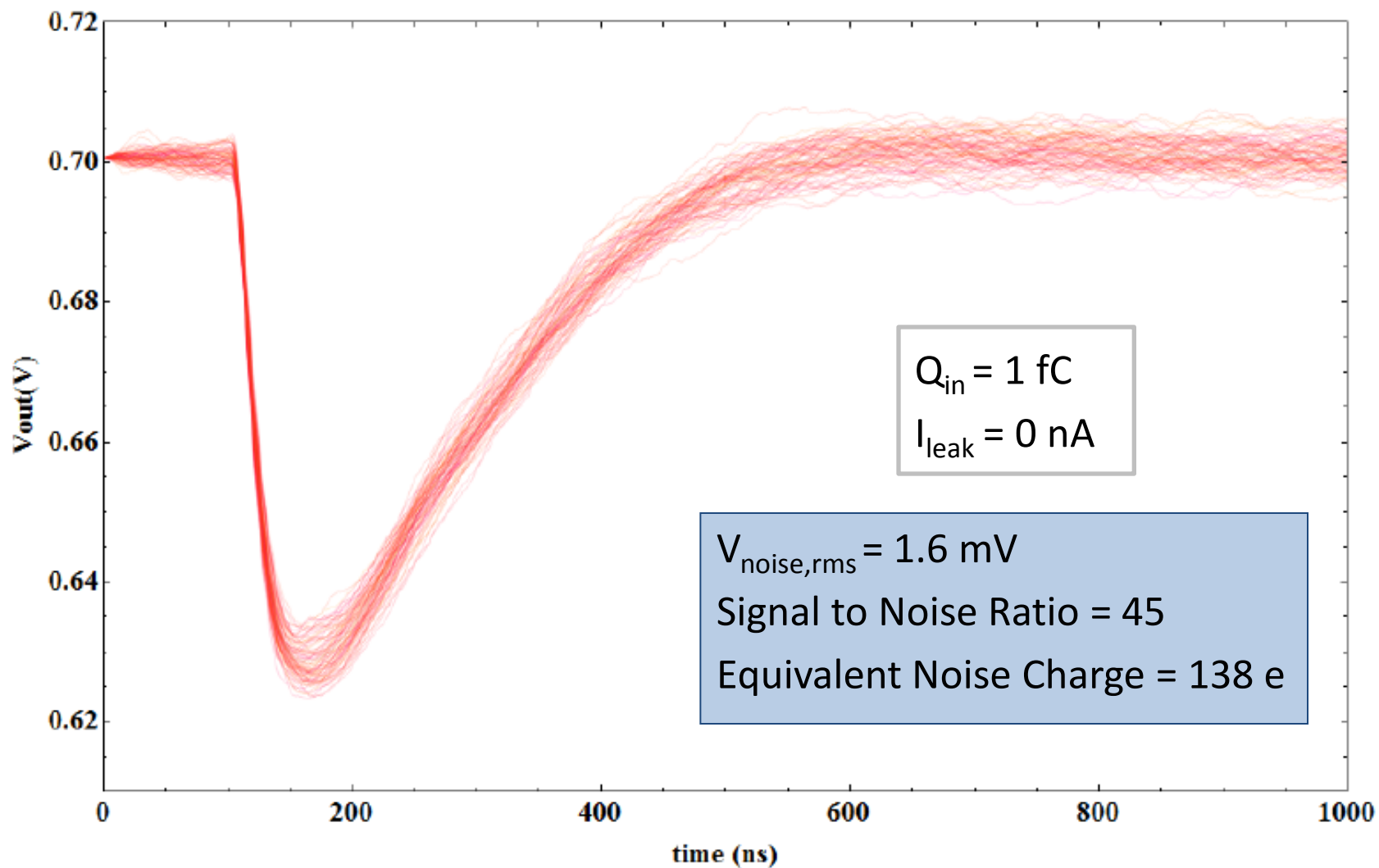


# Noise dependence from leakage current

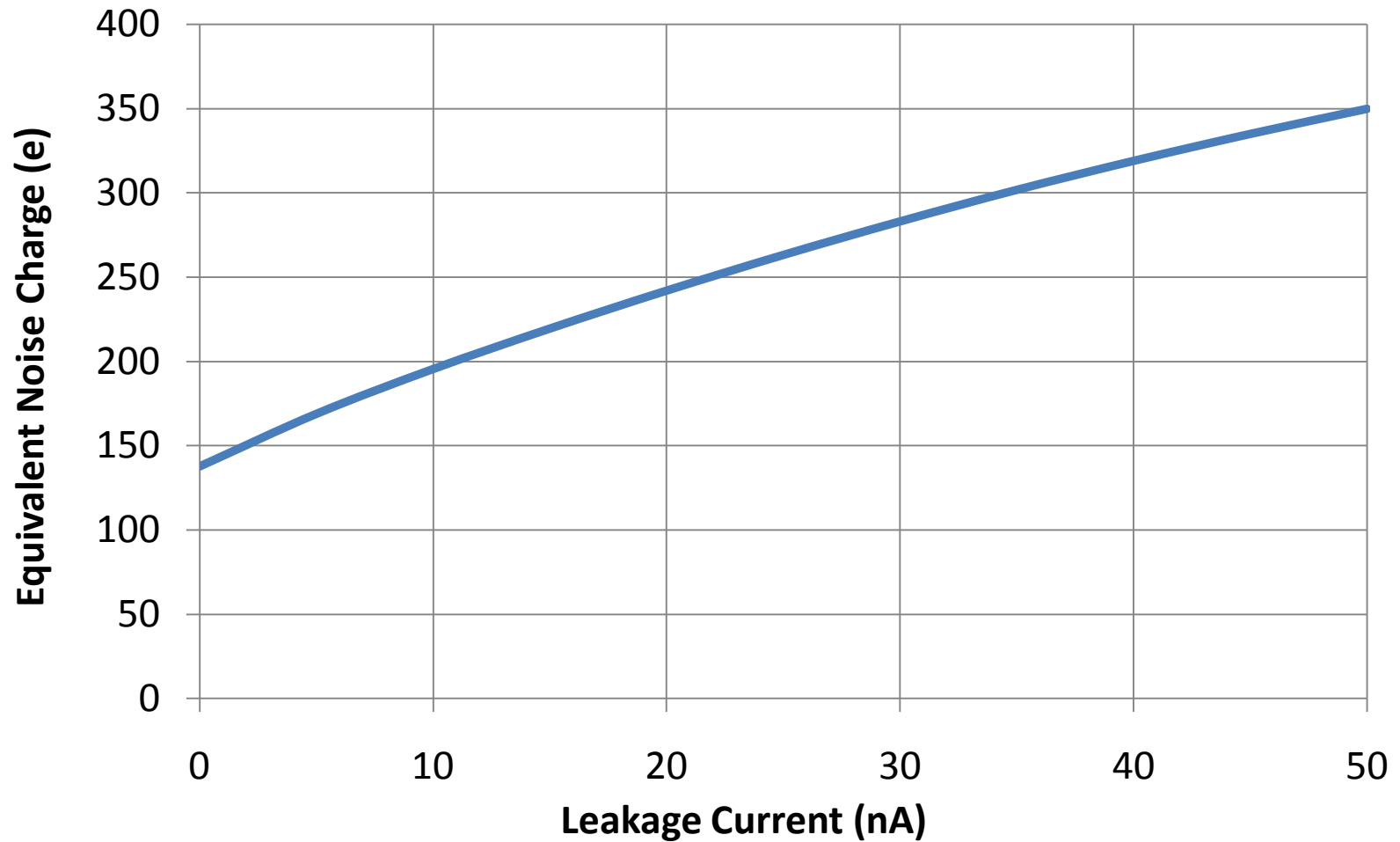


# Noise and Baseline



Noise

 

 Channel to channel  
baseline variation with  
no compensation




baseline variation  
+  
noise

  


# Comparator Threshold



Baseline + Noise < Comparator Threshold

 

# Linearity up to 50 fC

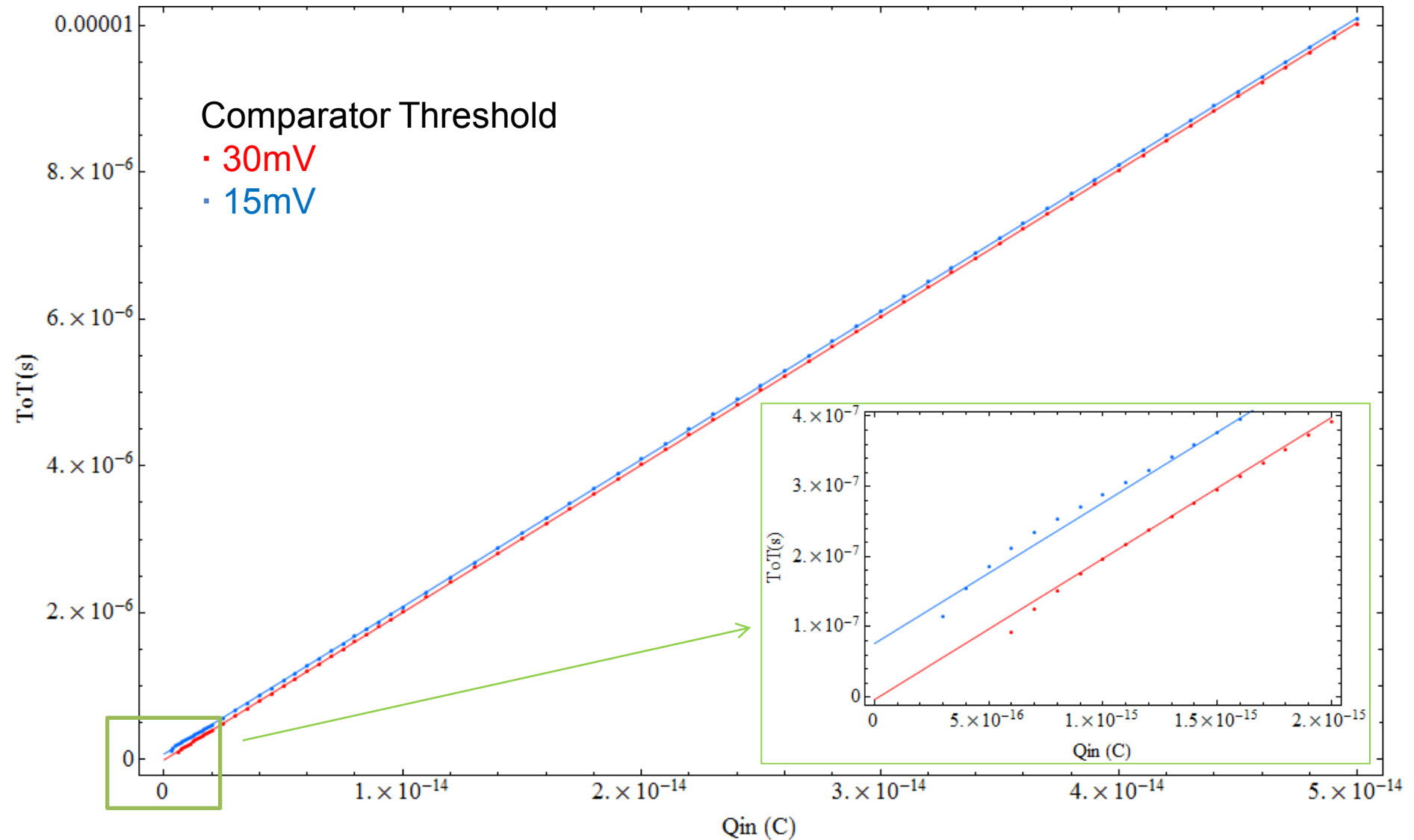


# Deviation from linearity

  

Comparator Threshold	Minimum charge	Error
• 30 mV	0.6 fC	-0.12 fC
• 15 mV	0.3 fC	-0.11 fC
 
# Clipping Circuit

A clipping circuit has been designed in order to protect the front-end when a large charge is presented at the input node, thus avoiding long dead times.




# Conclusion

ToPix3 - Prototype chip for the hybrid pixel sensors in CMOS 130nm.

- Based on Time over Threshold readout
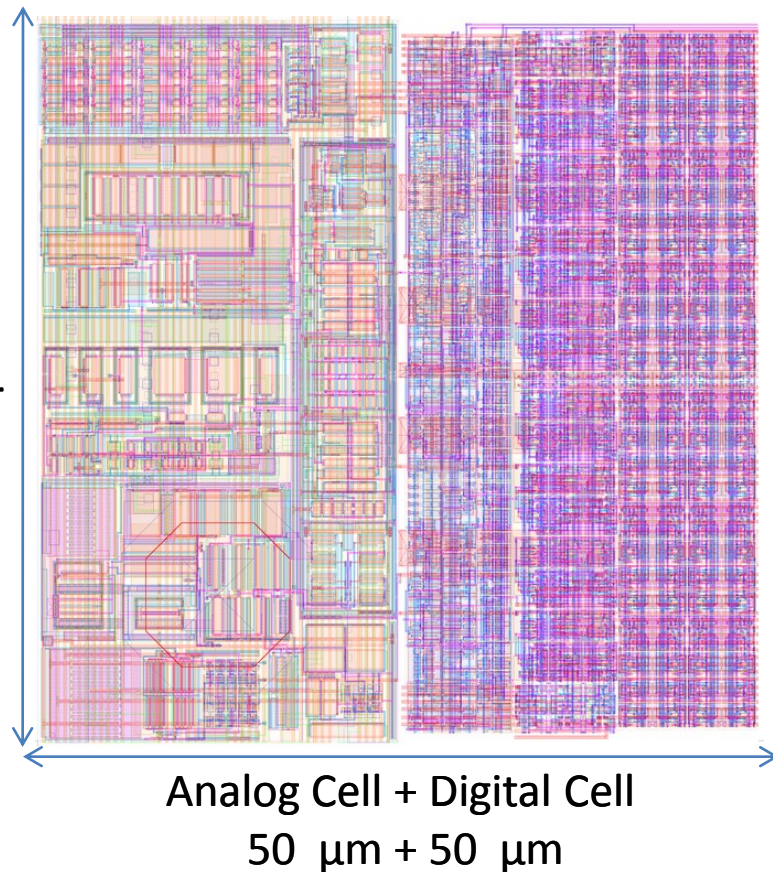
## Features



- Increase of the CSA gain ( $1/12fC$ ) and improvement of the loop stability
- A more compact leakage compensation stage
- Key Features:
  - Analog Cell Size:  $50\mu m \times 100\mu m$
  - Power Consumption:  $15\mu W/cell$
  - Equivalent Noise Charge:  $<200e^-$






# BACKUP SLIDES

# First Prototype

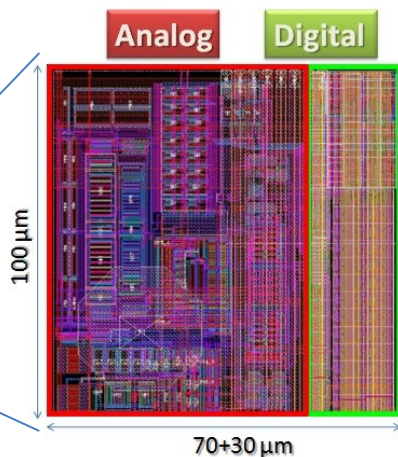 

Each cell incorporates the analog and digital electronics necessary to amplify the detector signal and to digitize the charge information.


## P-Type sensors ToT Linearity

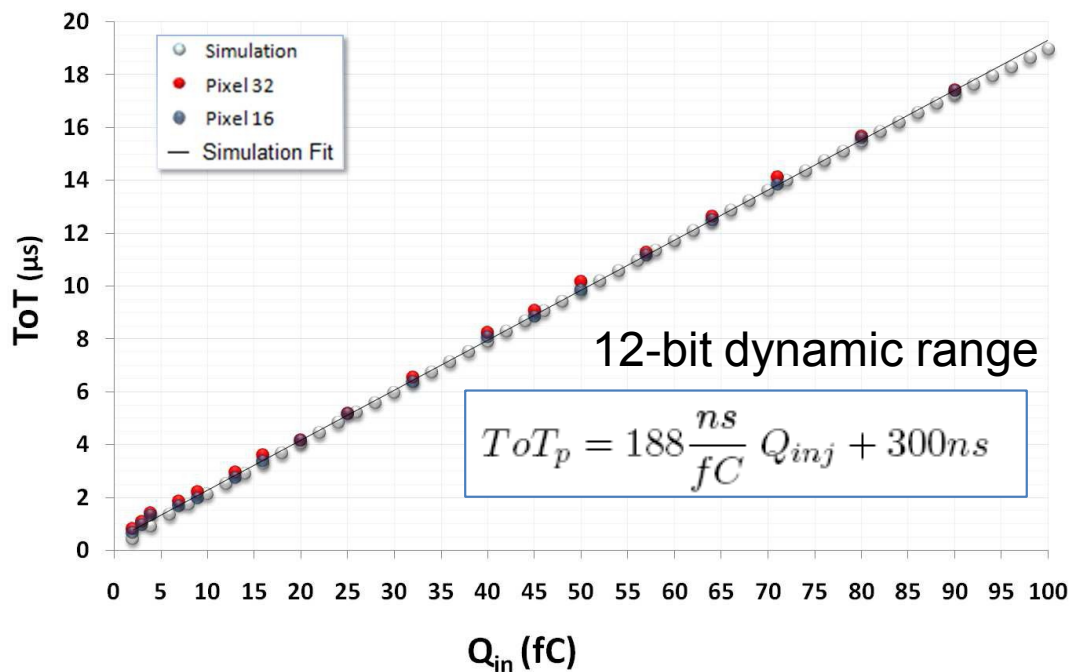

Reduced scale prototype chip (320 cells)

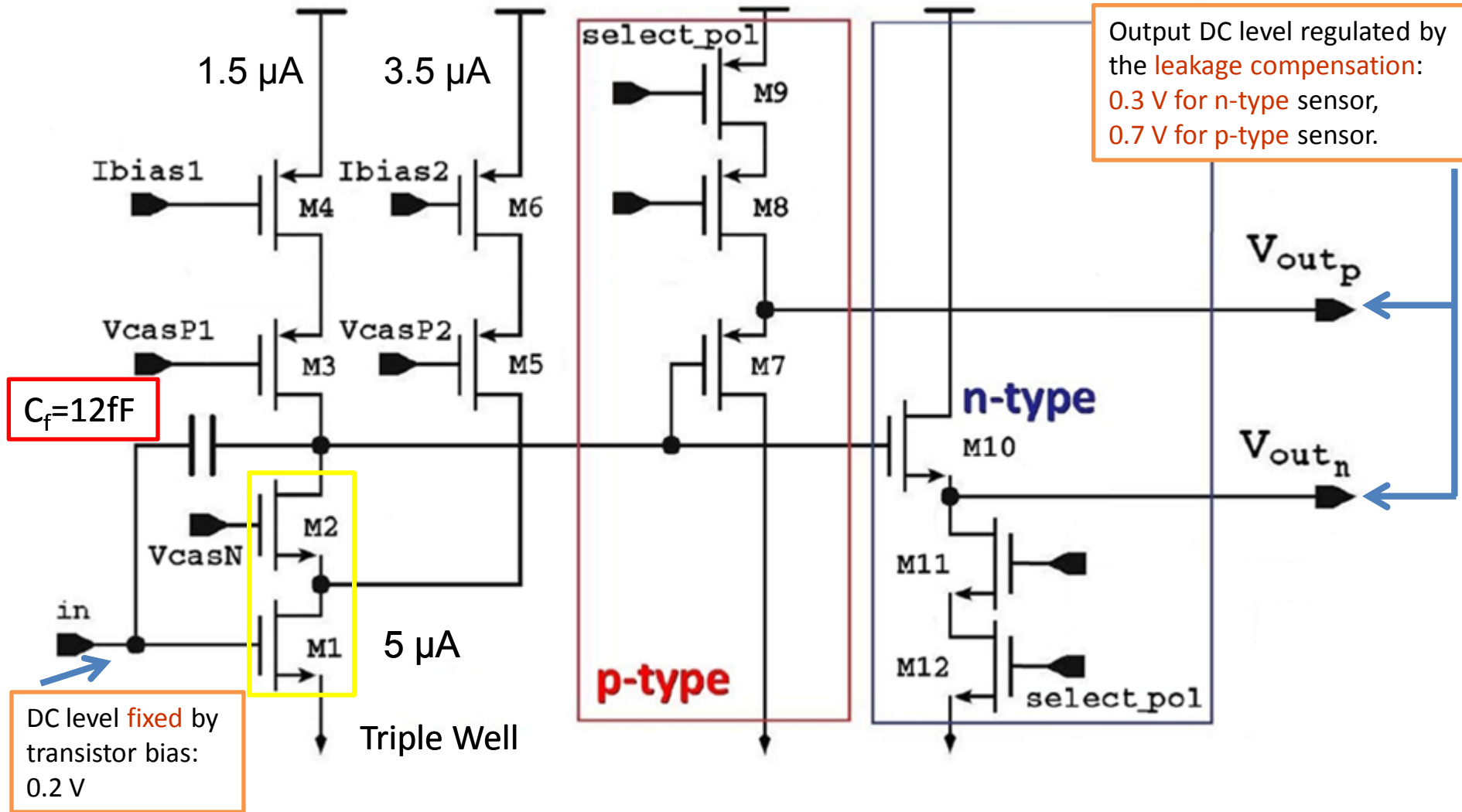
# CSA Schematic

Selectable source follower: 1  $\mu\text{A}$



# Baseline Holder

## Compact Low-Frequency Feedback Filter

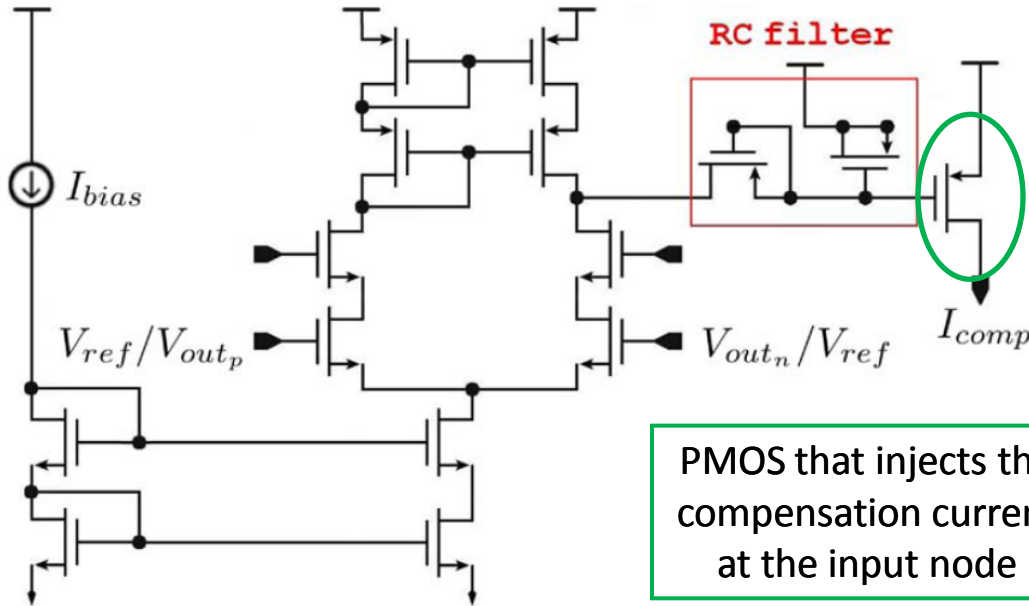

ToT signals can be very long (< 20us)

In order to preserve the signal a very low cutoff frequency ( $\approx 10\text{Hz}$ ) is required.

The leakage current depends on the Total Ionizing Dose. It may be up to 50nA.

$$f_p = \frac{1}{2\pi R_0 C_0} \approx 10\text{Hz} \Rightarrow R_0 C_0 \approx 1\text{s} \quad C_0 \approx 1\text{pF} \Rightarrow R_0 \approx 10^{12}\Omega$$

In CMOS technology in an area of few hundreds of  $\mu\text{m}^2$  it is possible to implement a capacitor of few pF


R: Gate-Source shorted MOS

C: Source – Drain shorted MOS
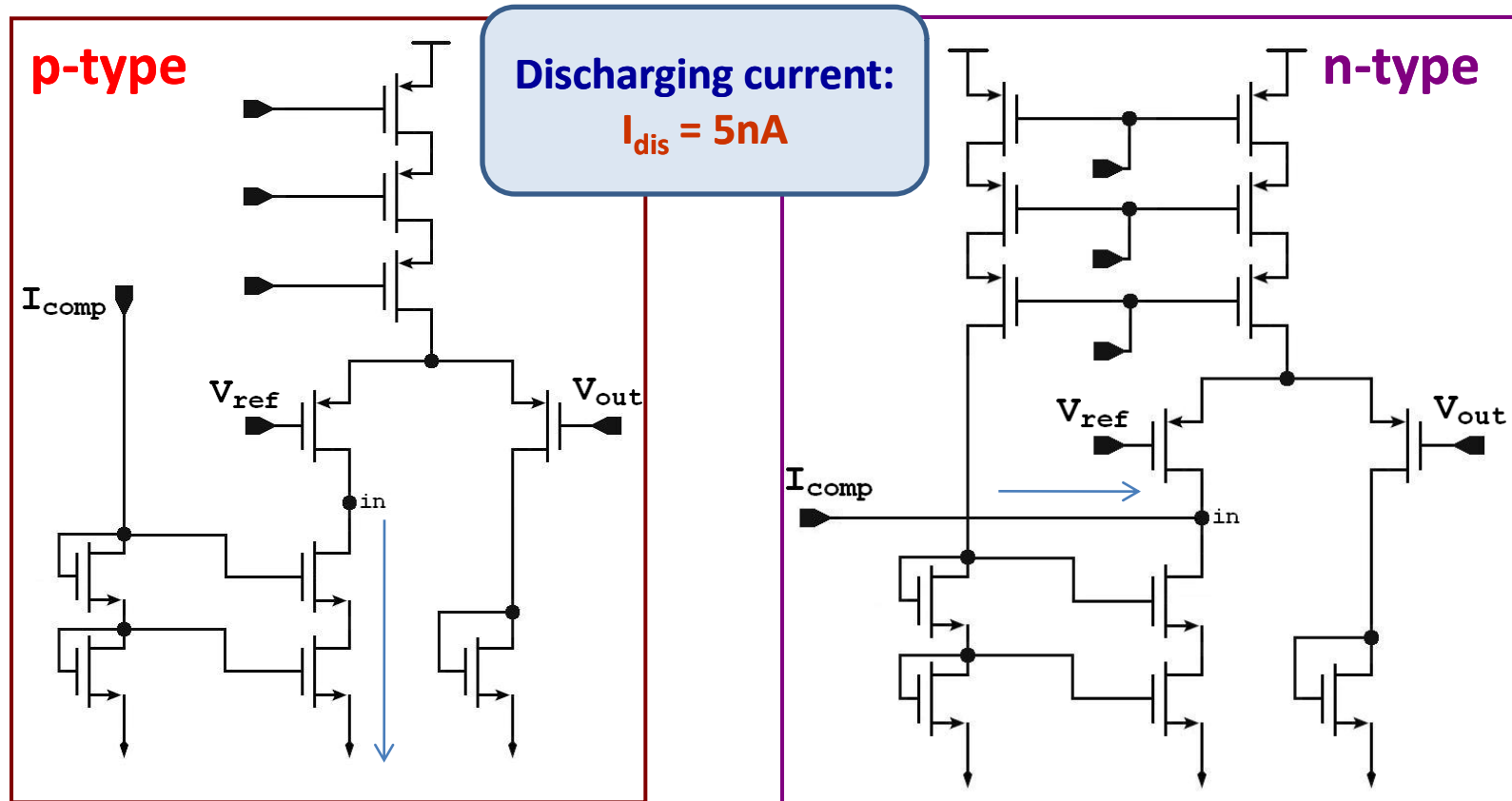
# Feedback Circuit

It keeps the output at the reference voltage, discharging the charge deposited on the input node.

This stage provides also the injection of the leakage compensation current at the input node.



Compensation current injected trough current mirror

Compensation current injected directly