

Efficient Powering of Inner Layer LHC Detector Electronics

SLDO & HF-DCDC

Michael Karagounis

GSI Darmstadt


28.01.2026

Power Demand of Pixel Detectors

- Hybrid-Pixel detectors are power hungry devices


Chip	Pixel Area	Current per Pixel	Current Density
FE-I3	50 x 400 μm^2	47 μA	1400 A/m ²
FE-I4	50 x 250 μm^2	16 μA	1280 A/m ²
RD53	50 x 50 μm^2	7 μA	2800 A/m ²

 - Increased current consumption caused by
 - parasitic detector capacitances
 - additional digital functionality
- ITkPix quad-module expected to consume 4.5-7.5 A of current
 - Exact current consumption depends module position e.g. layer




Need for Low Mass

 - detector mass influences the tracking and calorimeter resolution
 - multiple-scattering, Bremsstrahlung, photon conversion
- limited material budget
 - affects available number and diameter of supply lines
 - no sense lines
- long supply lines
 - power supplies are outside the active area
 - assuming c.a. 200m aluminum of 5 mm² diameter gives 1Ω cable resistance



 Power Efficiency of Conventional Power Scheme




- Modules are connected in parallel
- Powered by constant voltage source
- Total supply current scales with the number n of modules
- Large supply currents affect efficiency
- IR drops on power cables

$$\eta = \frac{1}{1 + n \frac{R_C I_m}{V_m}}$$

$$\eta = \frac{1}{1 + 16 \frac{1\Omega \cdot 6A}{1,2V}}$$

$$\approx 1.23 \%$$

DC / DC Conversion

 

- power is distributed at k-times higher supply voltage
- supply voltage is converted down close to the load
- supply current is reduced by k

$$\eta = \frac{1}{1 + \frac{n R_C I_m}{k^2 V_m}}$$


$$\eta_4 = \frac{1}{1 + \frac{16 \cdot 1\Omega \cdot 6A}{16 \cdot 1.2V}}$$

$$\approx 16.7 \%$$


$$\eta_8 \approx 44.4 \%$$

$$\eta_{16} \approx 76.2 \%$$

Special Conditions in HEP Experiments

 


 - 1 Grad (10 Msvt) of Total Ionizing Dose
- significant radiation induced threshold voltage shifts for gate-oxide thickness larger than 5nm



- High magnetic field to measure momenta and charge
- ferromagnetic materials saturate
- only air coils applicable
- air coils have larger dimensions than coils with core

Serial Powering

 

- modules are connected in series
- powered by constant current source
- total supply current is defined by maximum load current of a single module
- total supply voltage across the chain scales with the number of powered modules

$$\eta = \frac{1}{1 + \frac{R_C I_m}{n V_m}}$$

- regulator circuitry required to generate constant supply voltage out of constant current


$$\eta = \frac{1}{1 + \frac{1\Omega \cdot 6A}{16 \cdot 1.2V}}$$

$$\approx \frac{1}{1 + \frac{1\Omega \cdot 6A}{16 \cdot 1.2V}}$$

$$\approx 76,2\%$$


Efficiency of Different Power Supply Concepts
 
$$\begin{aligned} V_m &= 1.2V \\ I_l &= 4.5 A \\ R_c &= 1 \Omega \\ k_1 &= 4 \\ k_2 &= 2.5 \end{aligned}$$




The Serial Powering Commandments

 
- You shall prevent the break of the serial powering chain
- You shall avoid hot spots
- You shall distribute power equally across the chips and the module
- You shall avoid single point of failure
- You shall introduce redundancy
- You shall operate several regulators in **parallel** on module level



Shunt Regulator Operation Principle

 


 - Voltage regulation by current steering
- Current flow through load defines V_{out}
- Referenced voltage $V_{out} = \left(1 + \frac{R_1}{R_2}\right) V_{ref}$
- Excess current I_{shunt} is shunted by M1
- $I_{in} > I_{load} \rightarrow \eta = \frac{I_{load}}{I_{in}}$




- Very steep voltage to current characteristic
- → Small voltage source output impedance 😊
- → Unbalanced current distribution across parallel placed regulators ☹️
- Parallel placed regulators generate different V_{out}
 - voltage reference variations
 - error amplifier offset
 - resistor mismatch
 - ground shifts
- Current will flow through regulator with small V_{out}
- Regulator may be destroyed due to overload cond.

 Known Methods to Combat Unbalanced Shunt Current Distribution




 
- Distributed shunt transistors but single control circuitry
- Balances shunt current across the module
- Achilles heel → control circuitry
- Malfunctioning control circuit leads to loss of module or even loss of complete chain
- Module parasitics complicate design



- Trimming of voltage reference
- Fraction of the shunt current is mirrored and compared with a current reference
- Current difference ΔI is read out by transimpedance amplifier
- Transimpedance amplifier voltage output is fed back to the error amplifier as reference
- Effective reference voltage rises with ΔI
- V_{out} increases → I_{shunt} decreases 😊
- V_{out} depends on load current ☹️
→ Bad output impedance

simplified design don't try at home → won't work


FE-I3 Regulator Approach

  


- Resistor R_{slope} is added to the current input
- R_{slope} decreases the IV-slope of V_{in} (not V_{out})
- R_{slope} helps distributing the shunt current between parallel placed regulators 😊
- Output impedance is not affected 😊
- R_{slope} decreases power efficiency ☹️
- Additional supply voltage is generated by LDO
- **Design Idea of Shunt LDO Regulator:**
- **Move shunt transistor M_1 to LDO load**
- **Replace R_{slope} by LDO pass transistor M_2**

Design Concept

 
- The Shunt-LDO regulator combines the functionality of an LDO voltage regulator with the capability of a shunt regulator to drain a constant current
- Two control loops: 1) constant output voltage 2) constant current flow through the regulator



V/I Characteristic

 

 
$$V_{in} = V_{ofs} + \frac{R_3}{k} I_{in}$$




Measurements Line & Load Regulation

 
- Line Regulation = $\frac{\Delta V_{out}}{\Delta I_{in}} = 25mV/A$




 
- Load Regulation = $\frac{\Delta V_{out}}{\Delta I_{load}} = 11.5mV/A$



 
Lessons Learned Outer Barrel Demonstrator



  - FE-14 quad module based serial chain
- Overload current situation reduces module (SLDO input) voltage
- Other modules in chain see overvoltage
- PSPP chip triggers and generates even more overvoltages




Protection Feature: Overload Protection

 


- With RD53A overload currents lead to collapse of regulator input voltage
 - This lead to overvoltages at other modules in the serial chain
- RD53B protects against overloads which are considered as undershunt current scenarios
 - high load current reduces shunt current
- In undershunt current case Vout is reduced
 - Vout is lowered by lowering Vref
- Activation Threshold $I_{shunt} < 10 \text{ mA}$
- Vout minimum value 700mV → Vref minimum value 350 mV

Measurement of Overload/Undershoot Protection


Enabled

 


Disabled

 

 Protection Feature: Overvoltage Protection Voltage Clamp




 - voltage clamp implemented as shunt regulator
 - operated in parallel to SLDO
- takes all excess current in case $V_{in} \Rightarrow 2V$
- limits the voltage to 2V
- can absorb up to 2A additional current per chip
- OVP threshold defined by untrimmed bandgap
 - voltage limit can vary +/- 5%




Startup Optimization

 - Startup should not depend on too many bandgaps circuits





 - SLDO must be in high-impedance during startup




On-Pixel-Chip Monitoring

 
 
- Monitored SLDO properties
 - input/output voltage
 - shunt and total current
 - Vref and Vofs reference voltages



Monitoring of Pixel System


 


MOPS Chip

  


Negative Bias Generator

  - „preferred“ options for generation of negative voltages
 - inductive Buck-Boost converter
 - Cross-Coupled Charge Pump
- Radiation-hard implementation
 - challenging but feasible




High-Frequency DCDC Buck Converter

 - Cascode switching stage
 - 4 NMOS (Mn1 - Mn4)
 - 4 PMOS (Mp1 - Mp4) Operation
- with quadruple nominal transistor voltage
- Voltage-controlled pulse width modulation (PWM)





Specification	
Input voltage	4.8V
Output voltage	1.2V
Switching frequency	100MHz
Max. load current	1A
Required inductance	22nH
Required capacitance	100nF
Efficiency @400mA	70%
Technology	TSMC 65nm (core Transistoren)
Nominal outout voltage	1.2V
Maximum voltage	1.32V

Cascoded Power Switch Stage

 


- 4 PMOS and 4 NMOS transistors each
- Core transistors (nominal voltage: 1.2V, max. voltage 1.32V)
- Circuit switches between HIGH state (red) and LOW state (blue)
- Control signals from Mp1 and Mn8 determine the state of the circuit
- Driver network ensures safe operation of the stacked transistors
- Network monitors the drain potentials of the stacked transistors and provides the required gate voltage
- Ensures that the transistors are within their voltage limits
- Auxiliary voltages VDD, 2VDD and 3VDD required



 
 
Decoupling Capacitors for High Frequency Operation



 - Ultra large band **W**ire bondable **S**ilicon **C**apacitor **U**WSC
 - Murata
 - 10nF
 - 0202 (0.5 x 0.5mm)
 - Für Frequenzen bis 26GHz



    *Testchip mit On-Chip capacitors
(2.2 x 2 mm)*




Conclusion

- Power Aspects are always relevant and challenging
 - Especially due to additional constraints in HEP experiments
- Conventional parallel/voltage based powering scheme is not viable
 - Radiation hard custom made DC/DC converters are an option for outer layers
 - Serial Powering with SLDO are used in inner layers
- Hybrid/Resonant Converters may allow DC/DC conversion in hybrid-pixel detectors
 - e.g. as an alternative to short serial chains with 3D sensors


SPARE SLIDES

Pole und Nullstellen des LDOs:

- Verstärkerpol p1: $\omega_{p1} \approx \frac{1}{R_E[C_{GS1} + (1 + g_{m1} \cdot r_{LG})C_{GD1}]}$
- Ausgangspol p2: $\omega_{p2} \approx \frac{1}{r_{LG} \cdot C_{out}}$
- RHP-Nullstelle z1: $\omega_{z1} = \frac{g_{m1}}{C_{GD1}}$
- Mit $r_{LG} = R_{load} || R_1 + R_2 || r_{ds1}$
- R_E : Ausgangswiderstand des Verstärkers A1
- Für die Stabilität ist eine Phasenreserve $> 60^\circ$ im offenen Regelkreis erforderlich
 - Kompensationsnullstelle für Phasenhebung
- Konventioneller Ansatz: Kompensation durch ESR-Nullstelle
 - Große On-Chip Kapazität ($\approx 300\text{nF}$) $\rightarrow$ ESR-Kompensation nicht möglich
 - Neues Kompensationsschema erforderlich

 


LDO mit Position der Pol/Nullstellen

 

Kapazitive Last des LDO-Reglers


$$O(s) = \frac{1 + sR_{ESR}C_{out}}{s(C_{int} + C_{out}) \left[1 + sR_{ESR} \frac{C_{int}C_{out}}{C_{int} + C_{out}} \right]}$$

- **Kompensationsnetzwerk:**
 - R_s/C_s erzeugen Nullstelle für Phasenanhebung
 - Stromspiegel: $M_1 \rightarrow M_2$
 - C_s koppelt Spannungsabfall an R_s über R_1/R_2 ein
- M_4 verbindet R_s mit Ausgangsspannung
 - Stellt sicher, dass M_2 in Sättigung bleibt
- Referenzpfad durch Stromspiegel M_3 stellt Stromfluss durch M_5 ein
- Verstärker A_2 stellt Stromspiegelgenauigkeit zwischen M_1 und M_3 sicher

 

SLDO Stabilization Strategy Bode Plots
 
$$\omega_{z,comp} = \frac{1}{\sqrt{2}C_{out}R_{LG}} \sqrt{-1 + \sqrt{1 + \frac{R_{LG}^4 g_{m1}^2 C_{out}^2}{g_{m2}^2 R_0^2 C_s^2 R_x^2}}}$$



Amplitudenantwort der Ausgangsstufe des LDOs (orange),
Kompensationsschaltung (blau), beide Kombiniert (gelb)

