 


The HADES RPC Frontend Readout System

D. Belver ⁴, J. A. Garzon ⁴, A. Gil ², D. Gonzalez ⁴,
J. S. Lange ³, J. Marin ¹, N. Montes ⁴, P. Skott ³,
M. Traxler ³, W. Koenig ³



¹ CIEMAT, Madrid

² IFIC, Valencia

³ GSI, Darmstadt

⁴ Univ. Santiago de Compostela




1st FAIR-FEE Workshop, GSI Darmstadt, 11-13.10.2005

Content




- The Daughterboard (DB)
 - 2nd iteration (STEP2)
 - 3rd iteration (STEP3)
 - 4th iteration (STEP4) – pre-final
- The Motherboard (MB)
- The Power Supply Board (RPS)
- Test results from 2 Santiago tests and 2 LIP/Coimbra tests
- Note: this talk covers everything in front of the TDC board (see talks by K. Korcyl, M. Palka)

The HADES Resistive Plate Chamber (RPC) Detector.

 - Area 8 m², 6 sectors
- construction 2005-2008
- 1024 detectors
- 2-sided
- **TOF**
(time-of-flight)
TOT
(time-over-threshold)
into same TDC channel
(multi-hit TDC)
- TDC bin width
 $\Delta t = 100$ ps
sufficient for 3σ
lepton/ π separation
(flight path factor ~ 2
larger than FOPI)




The HADES RPC Detector

   


4 gaps

An RPC signal.

 

RPC Signals with different amplitudes.

 

Frontend Design Considerations.

- high frequency boards

<1 kHz / cm² RPC area

x 100 cm² = 100 kHz


x 31 channels = 3.1 MHz firing

power-to-ground has GHz components
due to switching $\Delta t \leq 1$ ns


requirements:

- fast risetime
 - high frequency design rules (no sharp edges etc.)
 - many filter capacitors
-
- all signals = LVDS = low voltage differential signal

 DB STEP2 (Previous Iteration until 12/2004)



 DB STEP2 (previous iteration until 12/2004)



2-ch / 1 FEE

From STEP2 to STEP3


▪ STEP2

- long dead-time (1 us)
- start/stop LVDS signal (flip-flop) by 1 signal (non-differential)
→ difficult if noise
- concept of flip-flop + delay was adjusted
to standard TDC concept
but obsolete by choice of CERN HPTDC
(free-floating adjustable fire-window
even before external trigger)

▪ STEP3


- use comparator with latch-enable
- advantageous side effect: 3 components less
(more space available > 4 channels / 1 DB became feasible)

 DB FEE STEP3 (Previous Iteration until 08/2005)




DB STEP4 (now) (minor changes)

 comparator
hysteresis
now $\Delta V = 8 \text{ mV}$



RC of TOT 2 ns (keep short to avoid ionic tail)
RC of Latch 20 ns

DB FEE STEP4 (now)

 

Pre-Amplifiers


- impedance mismatch amplifies signal in a „natural“ way
~factor 2.5 ($20\Omega/50\Omega$)
- STEP4
only 1 pre-amp is sufficient
 - not 2 (HADES pre-final version)
 - not 3 (FOPI)
- choice: GALI-S66 by Mini-Circuits (same as FOPI)

	BGA2712	GALI-S66
▪ wideband	≤ 3.2 GHz	≤ 8 GHz
▪ noise figure	2.7dB (factor 1.86)	3.9dB (factor 2.54)

noise figure = ratio of amplification of noise output/input

- operate @ gain 15

The Motherboard (MB)

 


top/bottom appears empty, but it is not:
8-layers, in 3-dim (with vias) completely full (<6 cm not possible)

note: 8 DB per 1 MB, but only 31 channels
because TDC needs 1 channel for START

4 Main Tasks of the MB

 - 1. supply stable voltage to DB
+5 V
+3.3 V
-5 V
- 2. get logical signals (TOF and TOT) from 8 daughterboards
and concentrate to 1 connector
(then twisted pair HITACHI cable to TDC board)
- 3. generate multiplicity signal for trigger
- 4. set thresholds on DB
for TOF and TOT
use programmable DAC chips
- And a few minor tasks:
multiplex/fan-out test signals 1→16 (from TDC board),
invert polarity of TOT thresholds,
LVDS repeaters etc.



8-layer total thickness d=1.438 mm


TTL Test Signals

GND
differential pair


+3.3 V
+5 V

differential pair
GND

-5 V

 

 Layer 3 (from top): signals, differential routes



150 μm in-pair trace-to-trace
450 μm pair-to-pair
130 μm trace thickness

Special Board Features #1: 100 Ω Impedance Matching

Edge-coupled Surface Microstrip

Edge-coupled Coaxial Microstrip


Edge-coupled Embedded Microstrip

Edge-coupled Symmetrical Stripline

Edge-coupled Offset Stripline

Broadside-coupled Stripline

Edge-coupled Offset Stripline

 

Notes

Add your comments here

Units

- ☐ Mils
- ☐ Inches
- ☒ Microns
- ☐ Millimetres



Design and Test Tools for Controlled Impedance and Signal Integrity

Polar

Height	H	398
Height1	H1	200
Width	W	110
Width1	W1	130
Separation	S	150
Thickness	T	18
Dielectric	Er	3.9
Diff. Impedance	Zo	100.75


avoid reflections for signals (if impedance mismatch)

Special Board Features #2: Plugged Vias

 
 


quite new (~ 1 year), only 2 PCB manufacturers in Europe
makes 6 cm MB width possible
(otherwise PCB and RPC would overlap)

DB and MB


 


  RPC Gas Box
(LIP-Coimbra,
P. Fonte et al.)



Special Board Features #3: The SAMTEC connector

  
- between DB and MB
- small pitch 0.635mm
- right-angle 90° on MB side
DB „hanging“
- differential
every 3rd pin missing
- „high-speed“ series
@2 GHz
impedance mismatch <10%
crosstalk <3.6%




TOF/TOT A low	2	1	TOF/TOT B low
TOF/TOT A high	4	3	TOF/TOT B high
-5 V	6	5	+5 V
-5 V	8	7	+5 V
mult-4	10	9	Test Signal A/B
GND	12	11	GND
Threshold TOF A	14	13	Threshold TOF B
Threshold TOT A	16	15	Threshold TOT B
Threshold TOF C	18	17	Threshold TOF D
Threshold TOT C	20	19	Threshold TOT D
GND	22	21	GND
(mult-4)	24	23	Test Signal C/D
+5 V	26	25	+3.3 V
+5 V	28	27	+3.3 V
TOF/TOT C low	30	29	TOF/TOT D low
TOF/TOT C high	32	31	TOF/TOT D high

Special Board Features #4: The MURATA super filters

 
- NFM18PC
- multilayer ceramic
- 0603 size
but unusual layout
- 2A high current
- low residual ESL
i.e. factor ~ 10 smaller than
comparable monolayer ceramic



二端子コンデンサを使用
チップ積層コンデンサ ($1 \mu\text{F}$)

 


三端子コンデンサを使用
NFM21P ($0.22 \mu\text{F}$)

 


Trigger

inverting op-amps, summing in 3 stages

 

 note: all resistors are on PCB top
→ easily exchangeable (if necessary)




The Santiago Test Setup (May and August 2005)

RPC

SPI Control


MB

DB

 

Slow Control

 - SPI (serial peripheral protocol)
62 kBit/s
- 1 DAC per 1 DB
- all DACs in daisy chain
- for Santiago test:
connected to laptop
(USB-SPI interface
plus TTL-LVDS converter)
- plan for Nov test:
by ETRAX chip
(= single chip LINUX PC)
on TDC board



Results

- Time jitter
42-48 ps FWHM
(factor $\sqrt{2}$ due to
start/stop with same signal)
- Crosstalk
 - 20 ns pulses
 - 450 mV (higher than nominal)
 - 2 μ s puls-to-puls
 - neighboured channels
on DB and MBno other channel fired
in ~ 6.5 Mill. Events
- Propagation delay
 ≤ 5 ns


 


Fig.11- Time Jitter con pulser STEP3 vs. STEP2.


TOT results from LIP test

- TOF+TOT
(= length LVDS signal)

 

charge (a.u.)

TOT only

 

charge (a.u.)

The RPC Power Supply Board (RPS)

- former concept (e.g. HADES drift chambers)
LV (e.g. +5V) from power supply over long cable (10 m)
to LDOs at the detector
common ground
- new concept:
point-of-load
supply +48 V with low current over 10 m cable
then use DC-DC converters with wide input voltage range (35-70 V)
(and get high current)
- LDOs ?
recent DC-DC converters have comparable ripple and stability
~20-50 mV
- ground loops ? No.
Use galvanic separation.
- Use MURATA filters
- Use MURATA ferrit beads


The RPC Power Supply Board (RPS)

- input +48 V
- output -5, +3.3, +5 V
- ripple


DATEL ULE-5/12-D48P
48V $\rightarrow$ +5 V, -5 V (12 A)
 ± 50 mV ripple peak-to-peak

POLA PME5218T
+5 V $\rightarrow$ +3.3 V
 ± 20 mV ripple peak-to-peak

 - shielding box
- between chip and shielding:
Bergstrom material
(electric conductivity zero,
heat conductivity high)




The RPC Power Supply Board (RPS)

 

Outlook

 - Test in Beam at GSI in Nov 2005 (800 MeV/c ^{12}C)
24 detectors, full chain readout (DB+MB+TDC Board)
- Supported by EU under FP6 program (#515876)



Acknowledgements:


LIP/Coimbra Detector Group: P. Fonte et al.

GSI DVEE: G. Eidmann, M. Wiegand


FOPI RPC Group: M. Ciobanu, K. Koch, A. Schüttauf

Additional Slides

DB schematics #1 (Pre-Amp)

 



DB schematics #2 (Comparator)

 

CAEN TDC (used for Santiago Test)



- 128-ch in 1 slot VME module
- multi-hit (pipe-lined)
- 100 ps bin width
- same CHIP as TRB: HPTDC
- VME readout:
self-written stand-alone
- TDC can fire **before** trigger
(adjustable windows
by registers through VME)
→ delay cable obsolete

RIO-2 LynxOS

  

The RPC Power Supply Board (RPS)

  - filtering noise
- MURATA filters
(see above, MB,
we had to buy
4000 anyway)
- in addition:
MURATA ferrit beads
inductance at low frequencies
resistor at high frequencies
($1\text{k}\Omega$ at 100MHz)
resistor = „real“ part of impedance
= dissipates high frequency noise as heat
high current 1.5A = O.K.



How to measure time jitter.




Measurement of Jitter (DB+MB) with RPC Signals


2 LVDS signals

- from RPC near end
- from RPC far end

 (both measured
at MB output =
signal propagated
through full chain)



 Measurement of Jitter (DB+MB) with RPC Signals



Trigger on MB

- RPC multiplicity signal
- inverting op-amp's for summing
- design:
 - use the fact that high level of last pnp stage on DB (+3.2 V)
 - and also close to +3.3V supply on DB
- 3 stages:

		low (zero fired)	high (all fired)	
stage #1	4-ch	+2.4 V	+3.2 V	on DB
stage #2	16-ch	+3.2 V	+4.0 V = pECL	on MB
stage #3	31-ch	0 V	-3.2 V = nTTL	on MB

- LEMO out
- op-amp's on stage #2 are on GND, but on stage #3 on -5 V

Test with Pulser

100 ns




10 ns



- „full chain“
(DB+MB+TDC+VME),
but pulser (not RPC)
- 10 ns pulses
100 ns puls-to-puls
→ multi-hit TDC multi-fires
for 8-9 subsequent pulses
- $\Delta t \sim 160$ ps FWHM
incl. 100 ps TDC bin width

leading edge
of 1st puls

leading edge
of 2nd puls

 

TDC can fire before trigger signal

- windows must be adjusted by writing registers through VME (opcodes = hex number sequences)
- delay cables obsolete

1st case: the trigger matching window precedes the trigger arrival:

