

THMP Calibration

Miriam Kümmel

Ruhr-Universität Bochum
Institut für Experimentalphysik I


LVII. $\bar{\text{P}}\text{ANDA}$ -Collaboration Meeting
June 2016

RUHR
UNIVERSITÄT
BOCHUM

RUB




Latest Design of the THMP \bar{P}

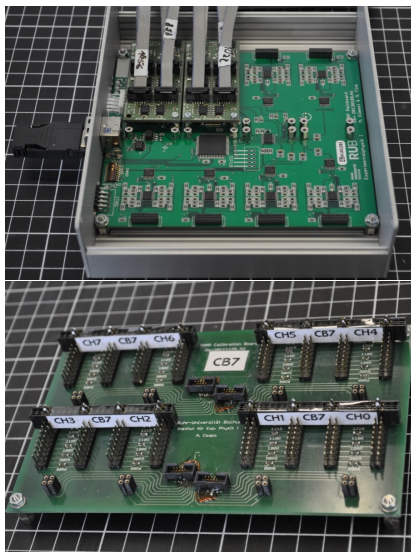

- Using type A USB connectors, still using the CAN-bus protocol!
 - Temperature sensor integrated on mainboard
 - Change of plugs and cables, which connect the THMP \bar{P} with the sensors, in order to match patch panel PCB
- Modified the calibration boards

Why and How Do We Measure Temperatures?

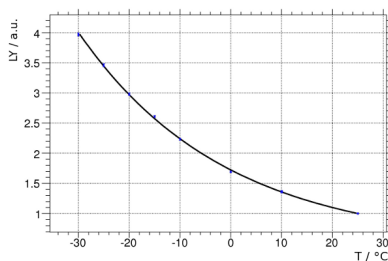PWO-II: LY depends on T with $\frac{d(LY)}{dT} = 3\%/^{\circ}\text{C}$ at -25°C




- Goal for $\overline{\text{PANDA}}$: $\Delta T < 0.1^{\circ}\text{C} \rightarrow$ sensors with $\sigma_T < 0.02^{\circ}\text{C}$
- R vs T relation of platinum quite linear

$$R(T) \approx R(0^{\circ}\text{C})(1 + \alpha_{\text{Pt}} \cdot T), \quad \alpha_{\text{Pt}} = 3.89 \cdot 10^{-3} \text{K}^{-1}$$

- Accuracy for temperature sensors translates to accuracy for the THMP: $\sigma_R \approx \frac{\partial R(T)}{\partial T} \cdot \sigma_T \approx 7.8 \text{ m}\Omega$

How Do We Measure Resistances?

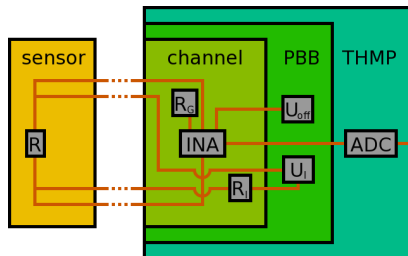- 4-wire measurement
- constant current $I = \frac{U_I}{R_I}$
- gain $G = 5 + \frac{200 \text{ k}\Omega}{R_G}$
- offset voltage U_{off}
- ADC conversion factor C




$$(R \cdot I \cdot G + U_{\text{off}}) \cdot C = R \cdot \underbrace{I \cdot G \cdot C}_m + \underbrace{U_{\text{off}} \cdot C}_n = N$$

→ σ_R corresponds to 3.5 ADC channels for optimized values of U_I , R_I , R_G and U_{off}

How Do We Measure Resistances Accurately?

! Electronic components vary within their production accuracy
all readout channels k on a PBB are different!

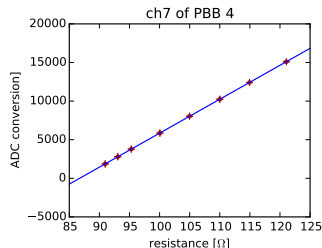- constant current $I_k = \frac{U_I}{R_{I,k}}$
- gain $G_k = 5 + \frac{200 \text{ k}\Omega}{R_{G,k}}$
- offset voltage U_{off}
- ADC conversion factor C




$$R_k \cdot \underbrace{I_k \cdot G_k \cdot C}_{m_k} + \underbrace{U_{\text{off}} \cdot C}_n = N_k$$

→ Calibrate each channel by fitting a 1st order polynomial to pairs of known resistors and ADC conversions!

How Do We Measure Resistances with Respect to the T?

! behaviour of diodes and resistors depends on T
 for $R_{I,k}$, $R_{G,k}$ is $(\Delta R/R)/\Delta T = 10 \text{ ppm/K}$ the best available

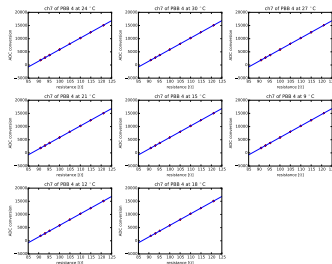- constant current $I_k(T) = \frac{U_I(T)}{R_{I,k}(T)}$
- gain $G_k(T) = 5 + \frac{200 \text{ k}\Omega}{R_{G,k}(T)}$
- offset voltage $U_{\text{off}}(T)$
- ADC conversion factor C




$$R_k \cdot \underbrace{I_k(T) \cdot G_k(T) \cdot C}_{m_k(T)} + \underbrace{U_{\text{off}}(T) \cdot C}_{n(T)} = N_k$$

→ Perform fits (prior slide) at different temperatures,
 describe dependency on T & monitor $\overline{\text{THMP}}$ temperature!

How Do We Measure Resistances with Respect to the T?

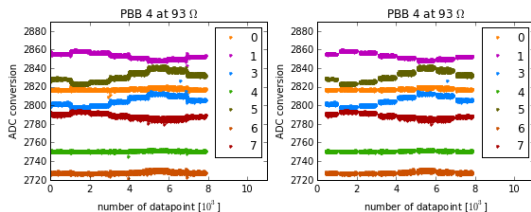
- Measure with varying temperature for each resistance value
- Analyse the data from periods with stable temperature



- The temperature dependency is fairly linear

How Do We Measure Resistances with Respect to the T?

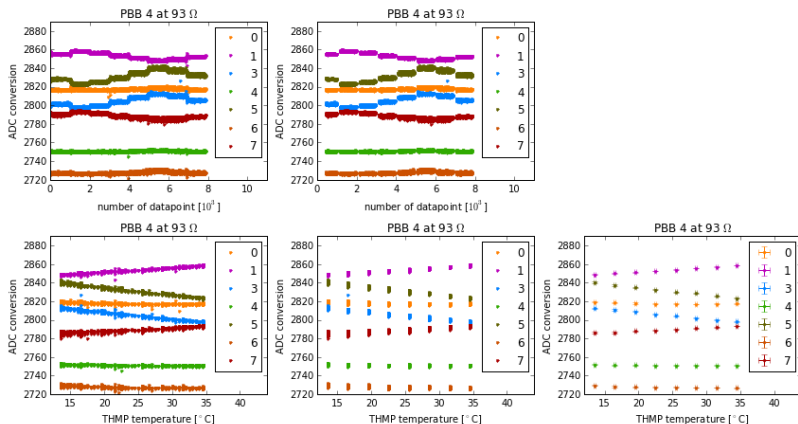
- Measure with varying temperature for each resistance value
- Analyse the data from periods with stable temperature



- The temperature dependency is fairly linear

How Do We Measure Resistances with Respect to the T?


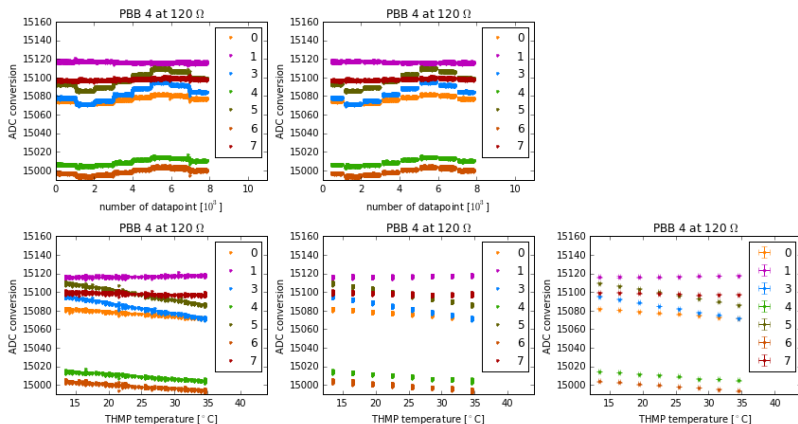
- Measure with varying temperature for each resistance value
- Analyse the data from periods with stable temperature



- The temperature dependency is fairly linear but differ for individual channels and different resistances

How Do We Measure Resistances with Respect to the T?

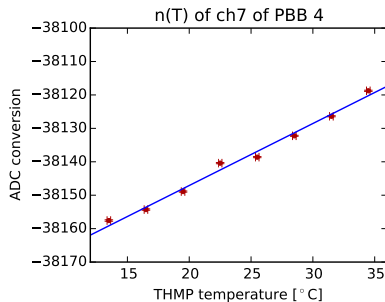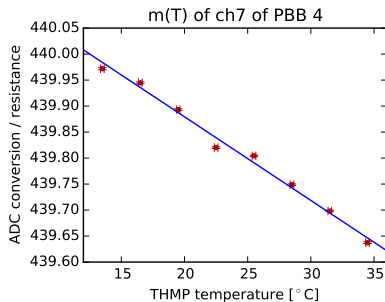
- Consequently $m_k(T)$ and $n(T)$ depend linearly on T



How Do We Measure Resistances Reliably?

! There is an additional PBB-wide drift of unknown origin (t)!

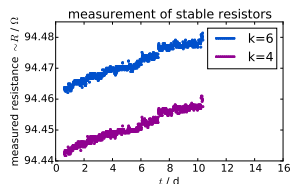- constant current $I_k(T, t) = \frac{U_I(T, t)}{R_{I, k}(T)}$
- gain $G_k(T) = 5 + \frac{200 \text{ k}\Omega}{R_{G, k}(T)}$
- offset voltage $U_{\text{off}}(T, t)$
- ADC conversion factor C




$$R_k \cdot \underbrace{I_k(T, t) \cdot G_k(T) \cdot C}_{m_k(T, t)} + \underbrace{U_{\text{off}}(T, t) \cdot C}_{n(T, t)} = N_k(T, t)$$

- Use a reference resistor on each PBB!
- The 10 THMPs foreseen for the fwd. endcap are still sufficient.

Choosing Best Configuration

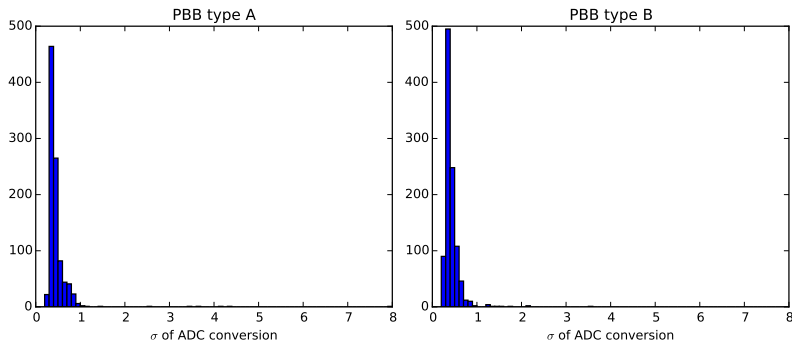- Two similar options for R_G and diodes which generate the offset voltage U_{off} have been considered and were tested.



- The temperature dependency has to be dealt with anyway.
- The second option seems to be electronically more stable.

Summary and Outlook

- ! The resistance of resistors depends on T .
The effect has already been minimized,
but has still to be compensated.
- ✓ A temperature dependent calibration is done.
- ✓ The THMP temperature is monitored by a temperature sensor
which is included in the final THMP design.
The temperature dependency is quite linear.
- ! Additionally, a slow drift has been observed.
- The source of the drift will be determined
by a long-term measurement.
- ✓ The drift can be compensated by using a reference resistor.
- ! If you want a well calibrated THMP ,
you will have to adjust the cabling.
- ✓ The setup for the temperature sensor calibration is updated,
mimicking the endcap instead of the prototype design.

Questions? Comments?

How to Take the Reference Resistor Into Consideration?

- Two possible sources have been identified: U_I and U_{off}
- Determine the impact of each source

$$\begin{aligned}
 m_k(T, t) &= \frac{U_I(t)}{R_{I,k}(T)} \cdot G_k(T) \cdot C = m_k(T) \alpha(t) \\
 \Rightarrow R_k \cdot m_k(T) \cdot \alpha(t) + n(t) &= N_k(T, t) \\
 \Rightarrow \frac{N_k(T, t) - N_j(T, t)}{R_k m_k(T) - R_j m_j(T)} &= \alpha(t)
 \end{aligned}$$

- Long-term measurement with known resistors of different resistances for each channel

case 1 U_I stable: $n(t) = N_{\text{ref}}(T, t) - R_{\text{ref}} \cdot m_k(T)$

case 2 U_{off} stable: $R_k = \frac{N_k(T, t) - n}{N_{\text{ref}}(T, t) - n} \frac{m_{\text{ref}}(T)}{m_k(T)} R_{\text{ref}}$

case 3 Both unstable: Best ansatz with only one reference sensor:

$$\frac{N_k(T, t) - n(0)}{N_{\text{ref}}(T, t) - n(0)} \frac{m_{\text{ref}}(T)}{m_k(T)} R_{\text{ref}} = R_k \left(1 - \frac{n(t) - n(0)}{N_{\text{ref}}(T, t)} \left(1 - \frac{R_{\text{ref}} m_{\text{ref}}(T)}{R_k m_k(T)} \right) \right)$$