

***Readout Electronics for  
LumiCal Detector at ILC  
possible applications in PANDA...?***

**Marek Idzik**

K. Świentek, T. Fiutowski, Sz. Kulis, D. Przyborowski



AGH-UST Kraków

# *Outline*

- ❑ LumiCal Architecture and Readout
- ❑ LumiCal Front-end electronics
- ❑ ADC design and measurements
- ❑ General purpose DAC design
- ❑ Other designs
- ❑ Summary
  
# LumiCal architecture


Si/W sandwich calorimeter,  
2 half barrels, each 30 layers



- Signal: from 2 fC - 10 pC
- Occupancy: up to ~20%
- Sensors:  $C_{det}$  10-100 pF
- leakage current ?
- Inter bunch time ~ 350 ns
- Low average power dissipation

Each layer consists  
of 0.35cm thick  
tungsten  
and 300 $\mu$ m thick Si  
sensor

 
Single detector layer  
48 azimuthal sectors,  
each sector ~96 radial pads







AGH

# LumiCal Readout System

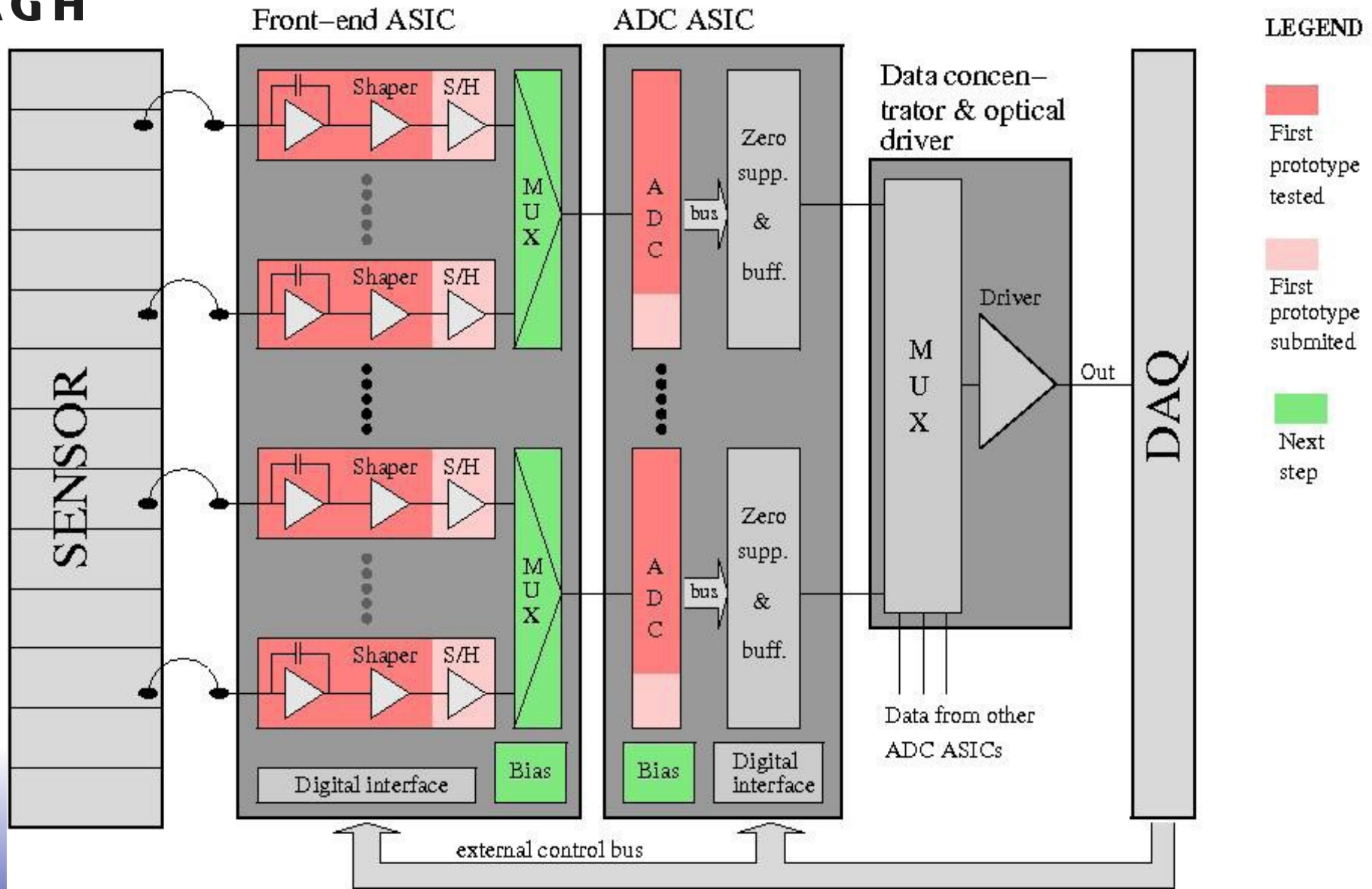

# Front-end architecture

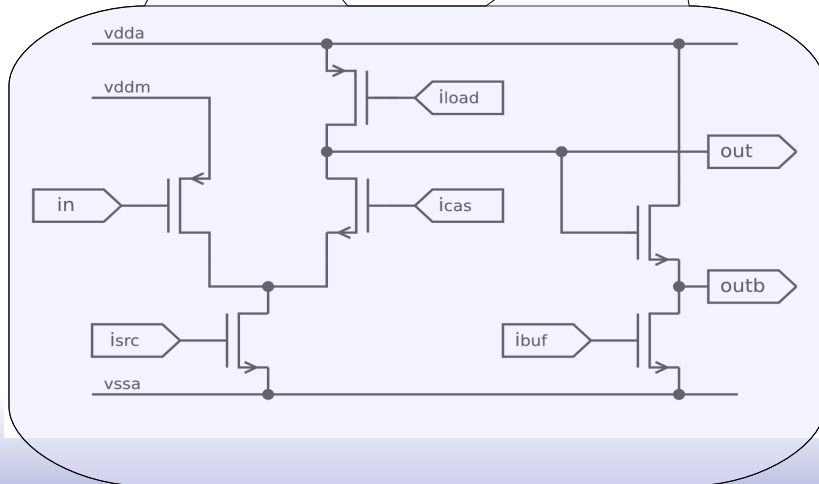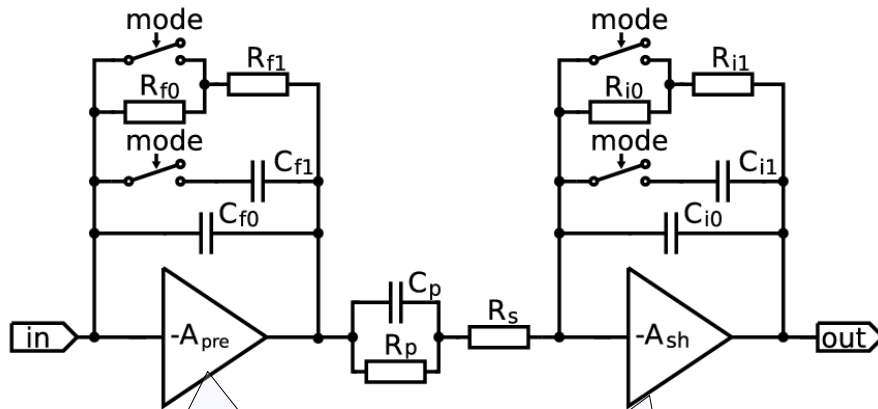

## Components


- Charge amplifier
- Pole zero cancellation
- CR-RC Shaper

## Specifications (old):

- $C_{det} = 10 - 100 \text{ pF}$
- $T_{peak} \sim 60 \text{ ns}$
- Variable gain: physics and calibration mode
- Physics mode:  $Q_{max} \sim 10 \text{ pC}$  ( $C_f = 10 \text{ pF}$ )
- Calibration mode:  $S/N > 10$  for MIP
 
# *Front-end prototype*



- AMS 0.35  $\mu\text{m}$  technology
- 8 channels
  - 4 channels with MOS feedback
  - 4 channels with passive  $R_f$  feedback
- Power dissipation  $< 9\text{mW/channel}$





AGH


# Pulse shape

 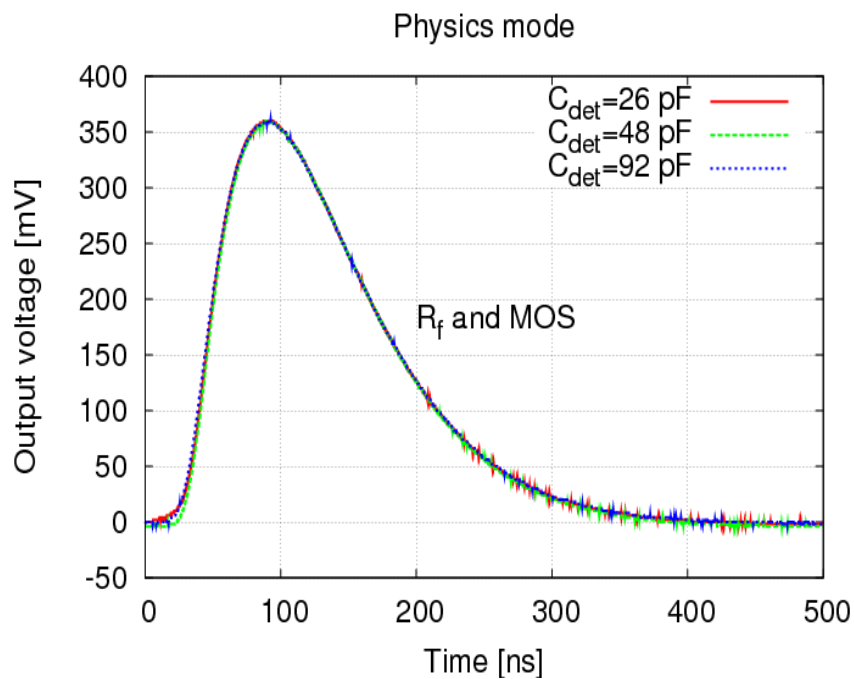


*Very good charge sensitivity in physics mode (same for MOS and passive  $R_f$  feedback)*

*Slight sensor capacitance dependence in calibration mode (gain for MOS and  $R_f$  feedback different by design)*

# Gain

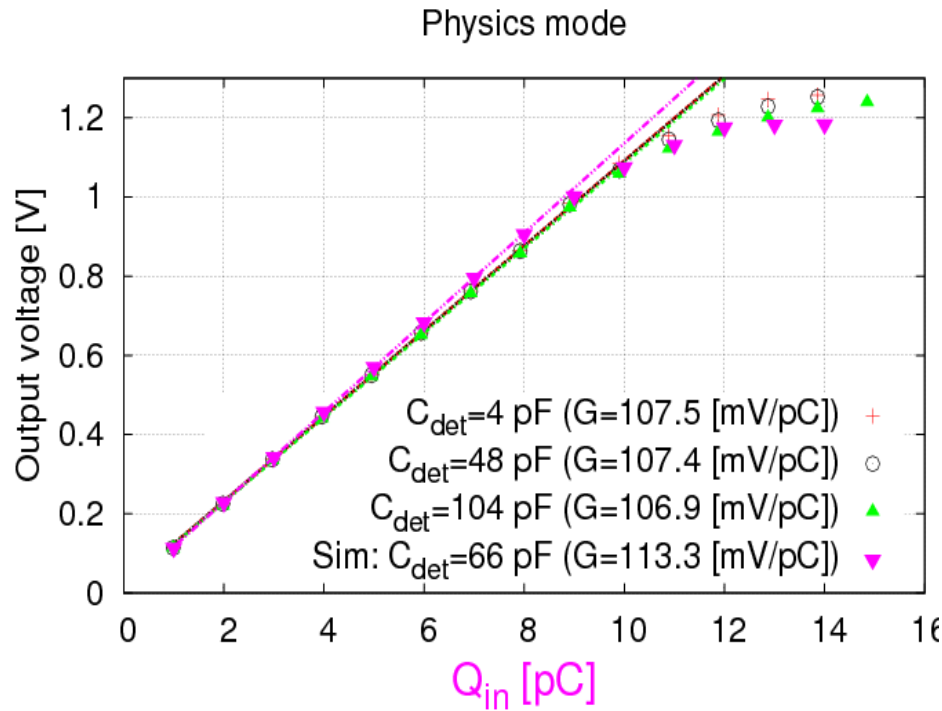

**Constant gain in physics mode**


 


**Slight gain decrease with growing sensor capacitance in calibration mode**



# Noise


# Pulse rate

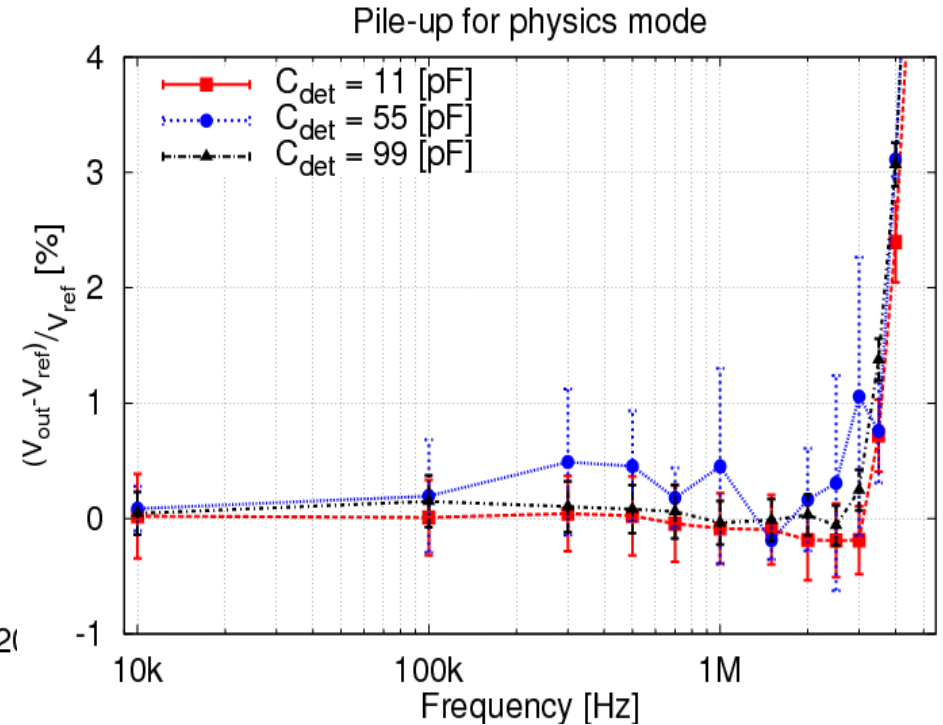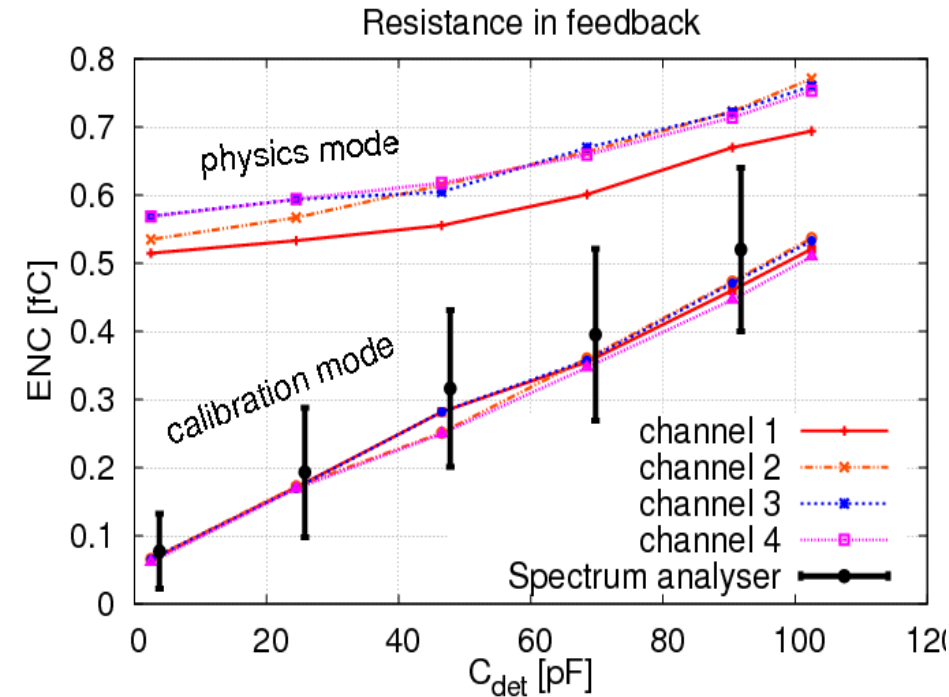

- Noise measurements done with external capacitance and generator. Need to be confirmed with sensor and particles
- In calibration mode noise  $< 0.4$  fC - good MIP sensitivity ( $SNR > 10$ )
- Front-end works well up to  $\sim 3$  MHz continuous input rate

# *LumiCal front-end with straw tubes*


ASIC output connected to external ADC

 


Connection between detector and preamplifier through RC decoupling filter

First Measurements taken by P.Salabura and J. Smyrski Group at Jagiellonian University

 Systematic investigations and comparison with Carioca front-end in progress!



# ADC architecture


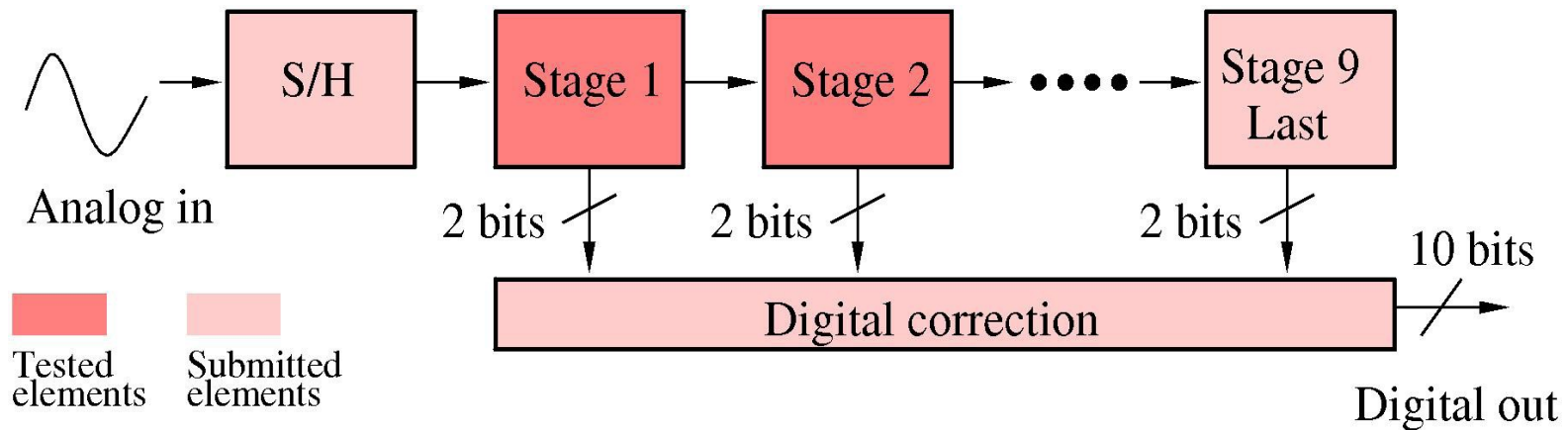


- Pipeline architecture (fully differential)
- 10 bits resolution (1.5 bit per stage)
- Input dynamic range 2 V
- Maximum sampling rate 35 MHz
- Power efficient & small area




# 1.5 bit stage architecture

AGH

  


Differential amplifier with boosted gain

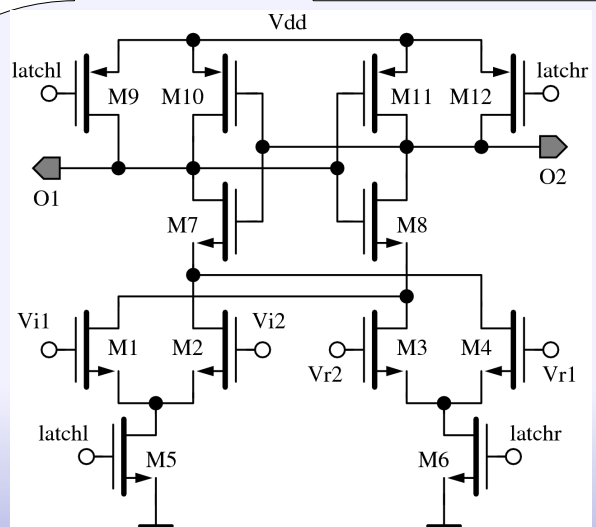


Dynamic latch comparators
 
# *ADC 2nd prototype*

- AMS 0.35  $\mu\text{m}$  technology
- Channel area about  $330\mu\text{m} \times 2950\mu\text{m}$
- All 9 stages and Sample&Hold
- Digital correction implemented
- Biasing and Reference voltages applied externally



# ADC test setup (FPGA based)

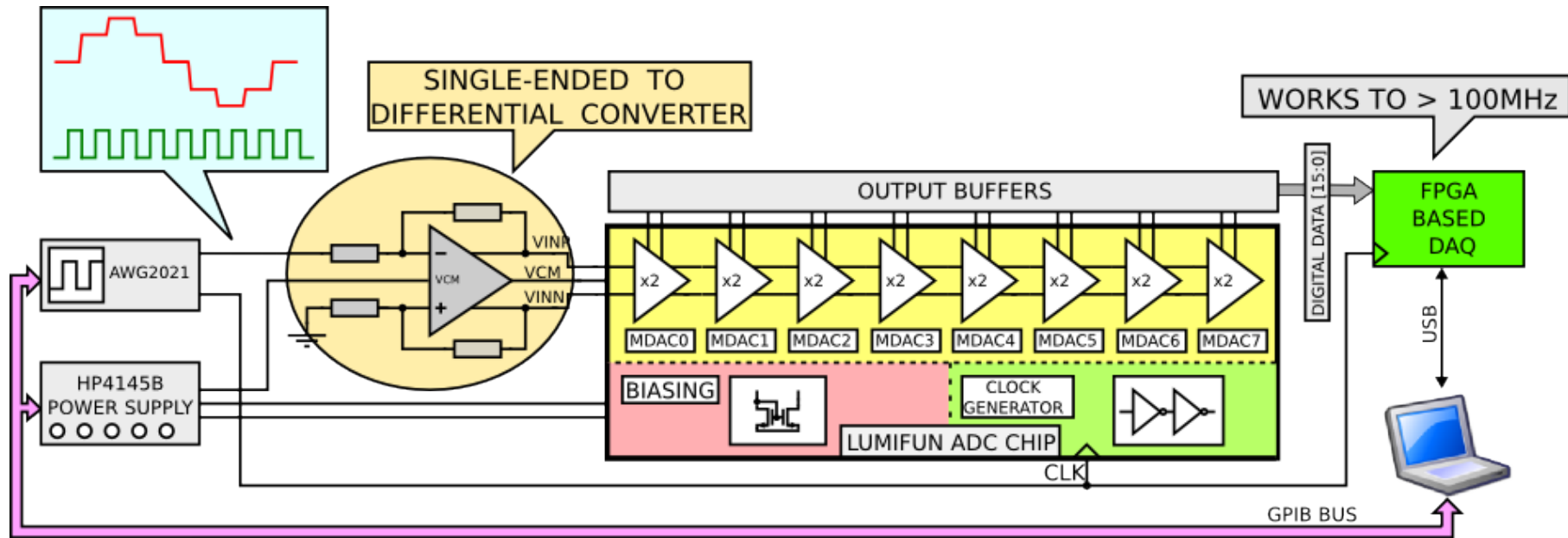

## □ Static measurements


- INL, DNL, ENOB

## □ Dynamic FFT measurements

- SNHR, THD, SFDR, SINAD, ENOB

# *ADC measurements*



## *Very preliminary!*

 

- Power consumption at 30MHz
  - Analog 8-14mA x 3.3V
  - Digital 6mA x 3.3V

# *Static ADC tests*

## *Very preliminary!*

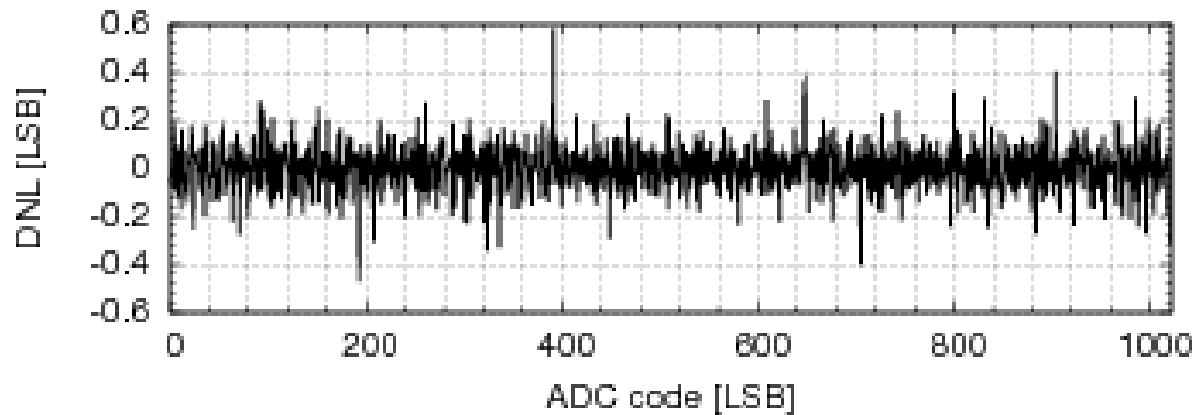 


- Maximum Integral Nonlinearity  $INL < 1$  LSB
- Maximum Differential Nonlinearity  $DNL < 0.6$  LSB



# Dynamic FFT ADC tests

## Very preliminary!

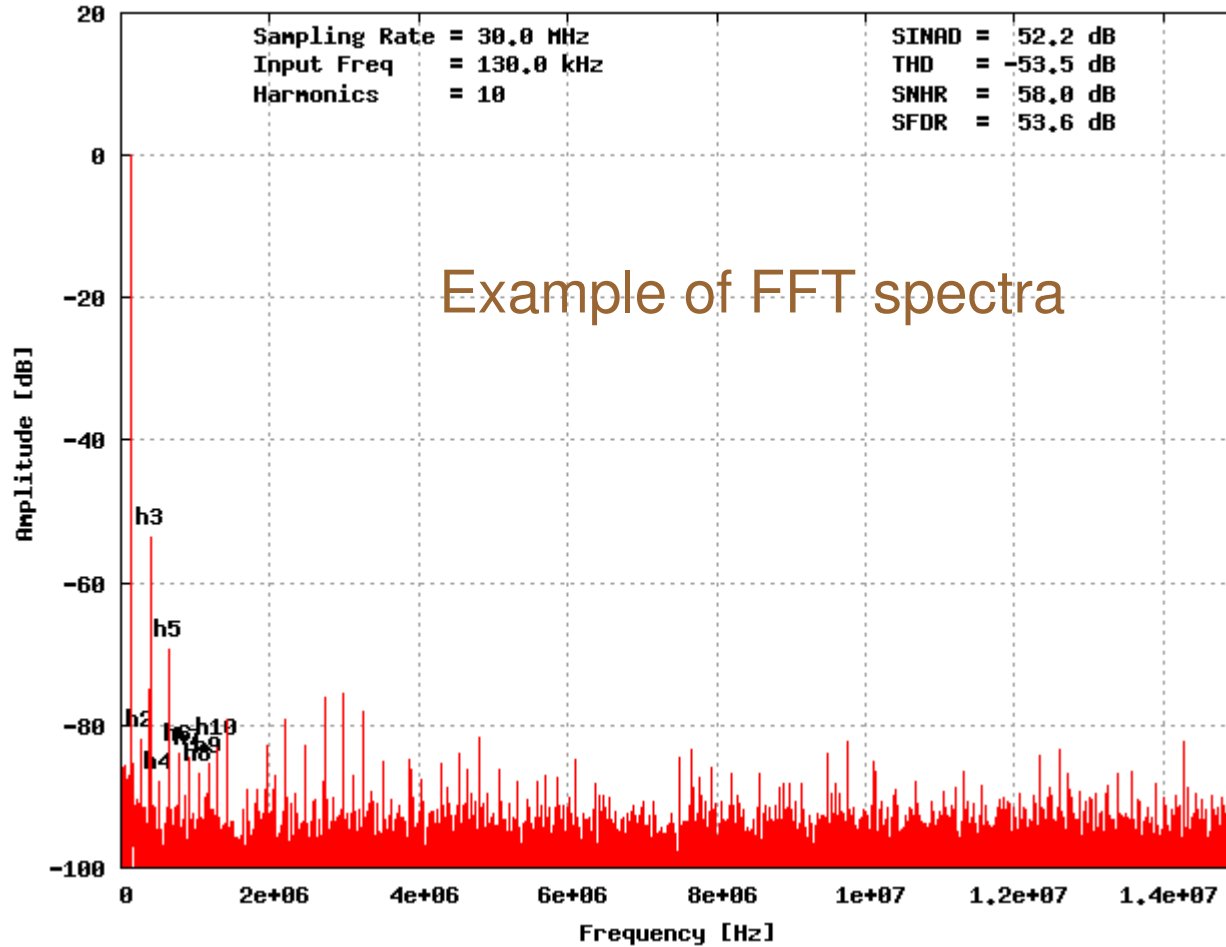


- Good S/N (SNHR), resolution slightly worse than from static measurements, but 3<sup>rd</sup> harmonic might come from the setup


# General purpose DAC
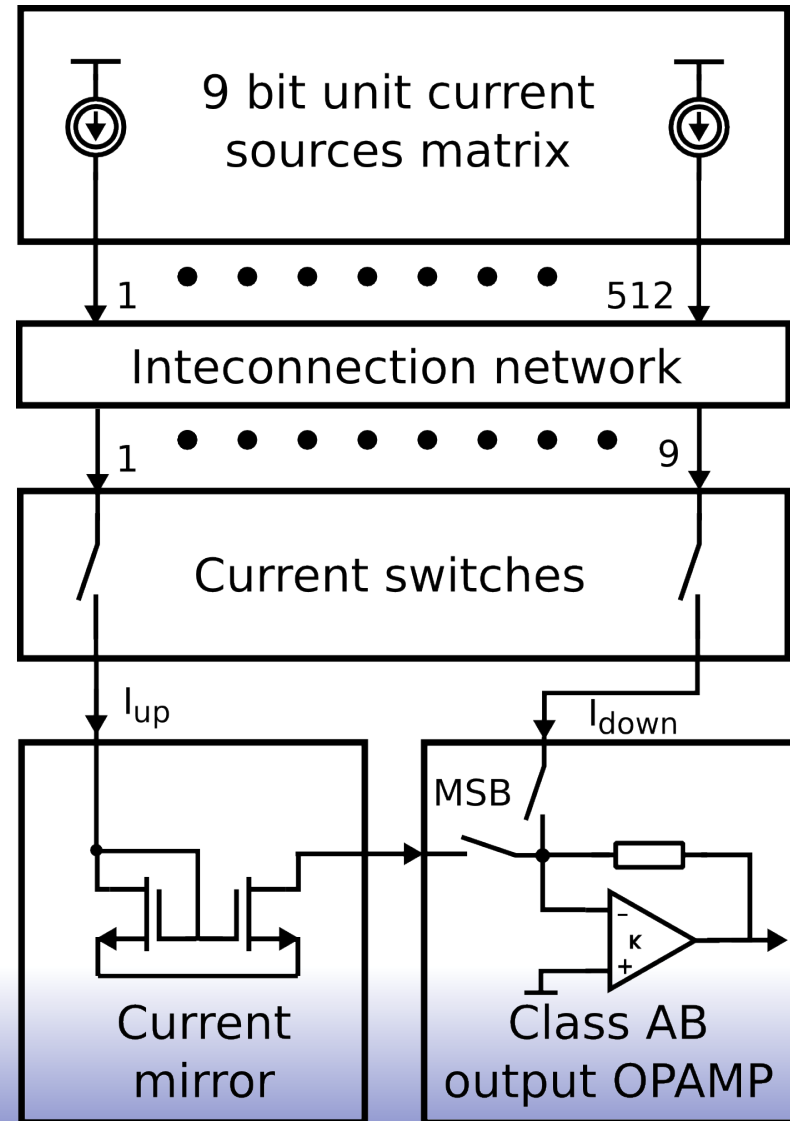
## □ DAC specifications:

- 10 bits
- Voltage output
- High swing
- Low power (<1mW)
- Small area
- No high rate request




# *I-steering 10 bit DAC design*

 

9 bit  
current  
DAC



Current  
mirror

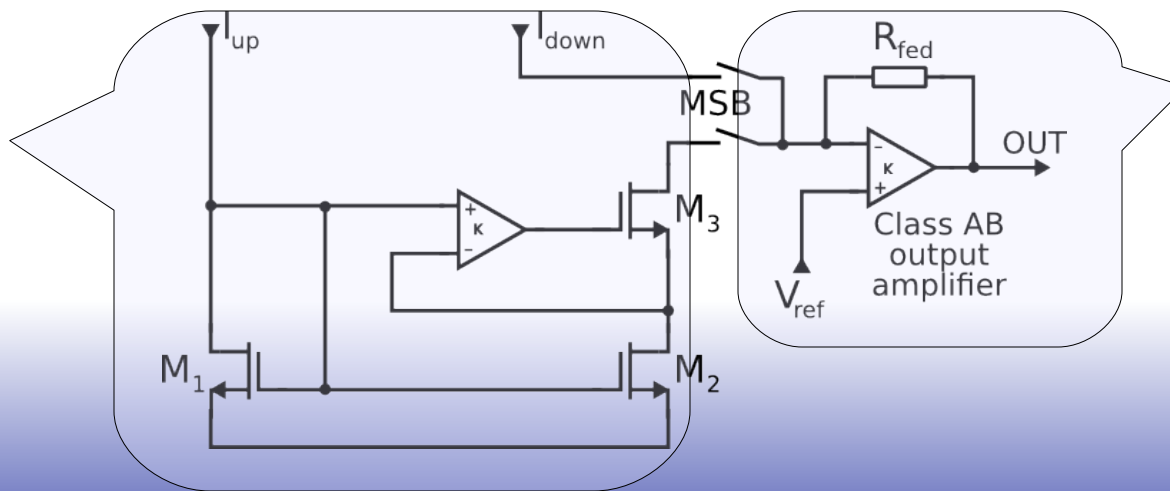

I-V converter  
with class  
AB output  
amplifier


# DAC measurements

Transfer function

 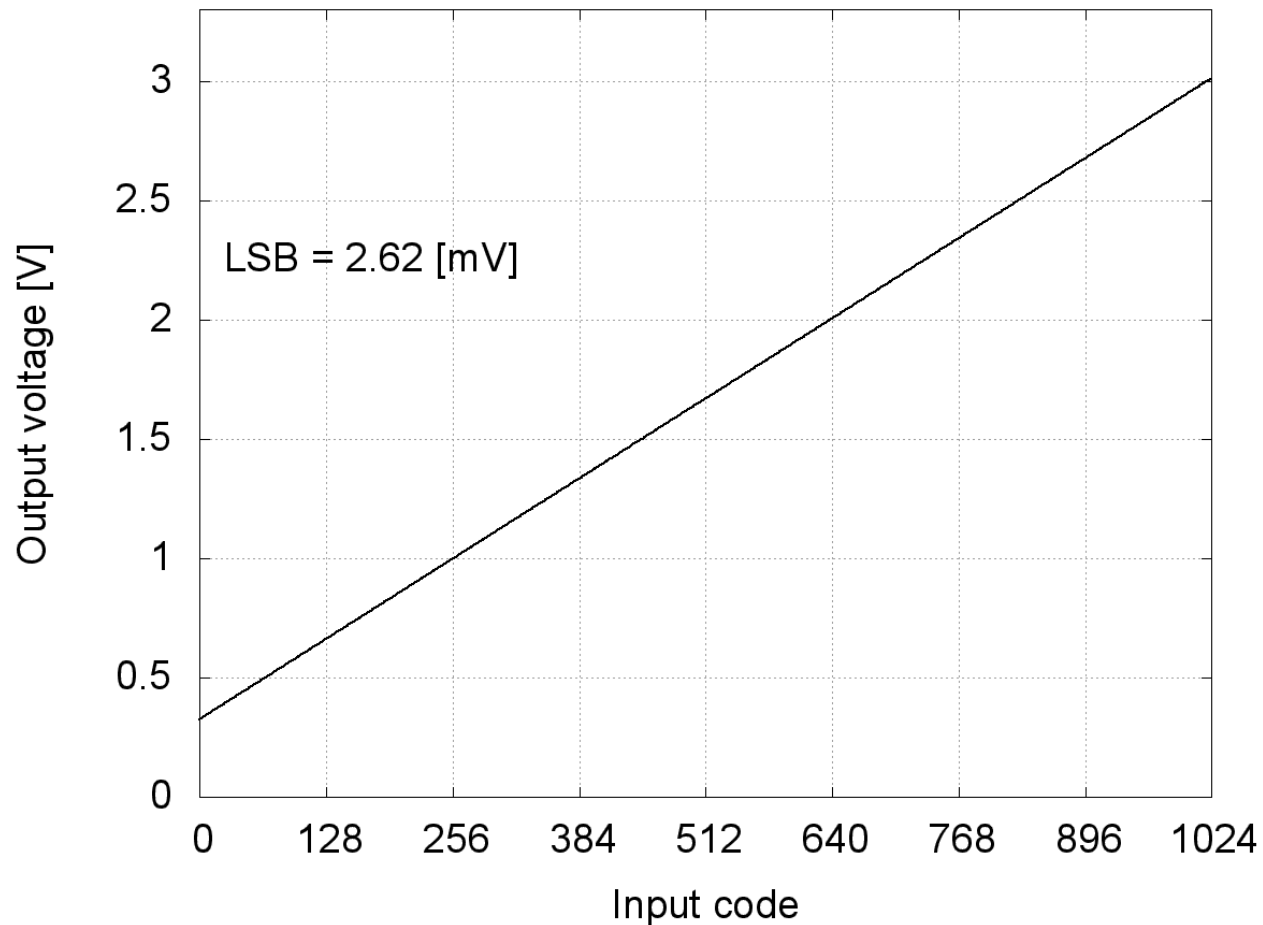

- 0.35 $\mu\text{m}$  CMOS
- Area 0.18mm<sup>2</sup>
- Power <0.6mW

# Static measurements

 

- INL measurements OK
- DNL generally OK, for few points worse than 0.5 LSB

# *Other designs in progress...*

- Bandgap based reference voltage and thermometer circuits ready for submission
- Fast LVDS driver ready for submission
- Fast LVDS receiver ready for submission

# *Summary*

- Development of LumiCal Redout electronics in progress
  - Front-end prototypes tested
  - 10 bit ADC prototypes ready, first tests promising
  - 10 bit DAC prototypes tested
  - Other designs (Bandgap, LVDS) ready for submission
- Readout for PANDA straw tubes under study, real design work should start in the second part of 2009
- If possible components of LumiCal readout will be used in PANDA