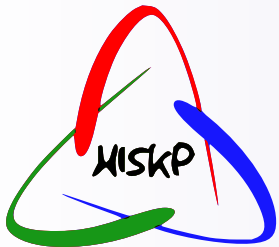





HV regulation board for the forward endcap - Status -

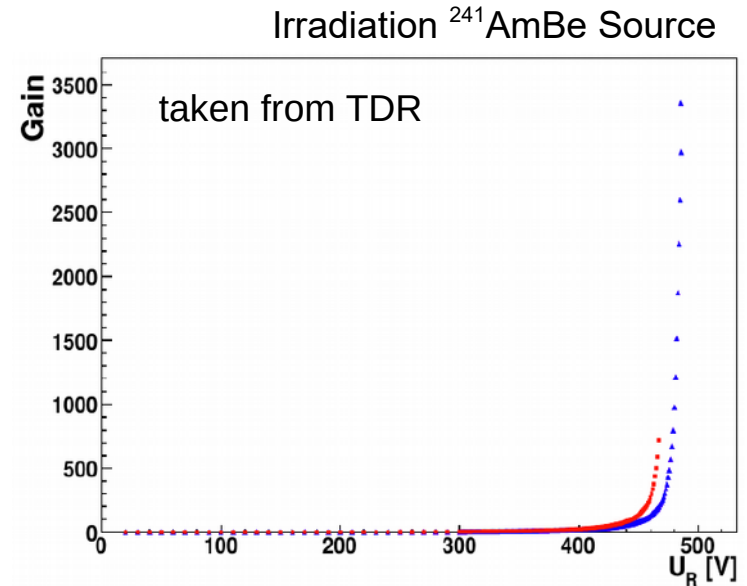F. Grifka, C. Schmidt, U. Thoma



Motivation

- Reach gain spread of max. 1%
- More freedom in matching procedure (less strict), $G(U)$ very steep @200
- Be able to compensate different gain drifts of APDs due to radiation damage on long term




Original idea voltage distribution

Due to very limited cross section for HV cables

—→ One HV is fed to 8 APDs


Power distribution concept

Voltage distribution

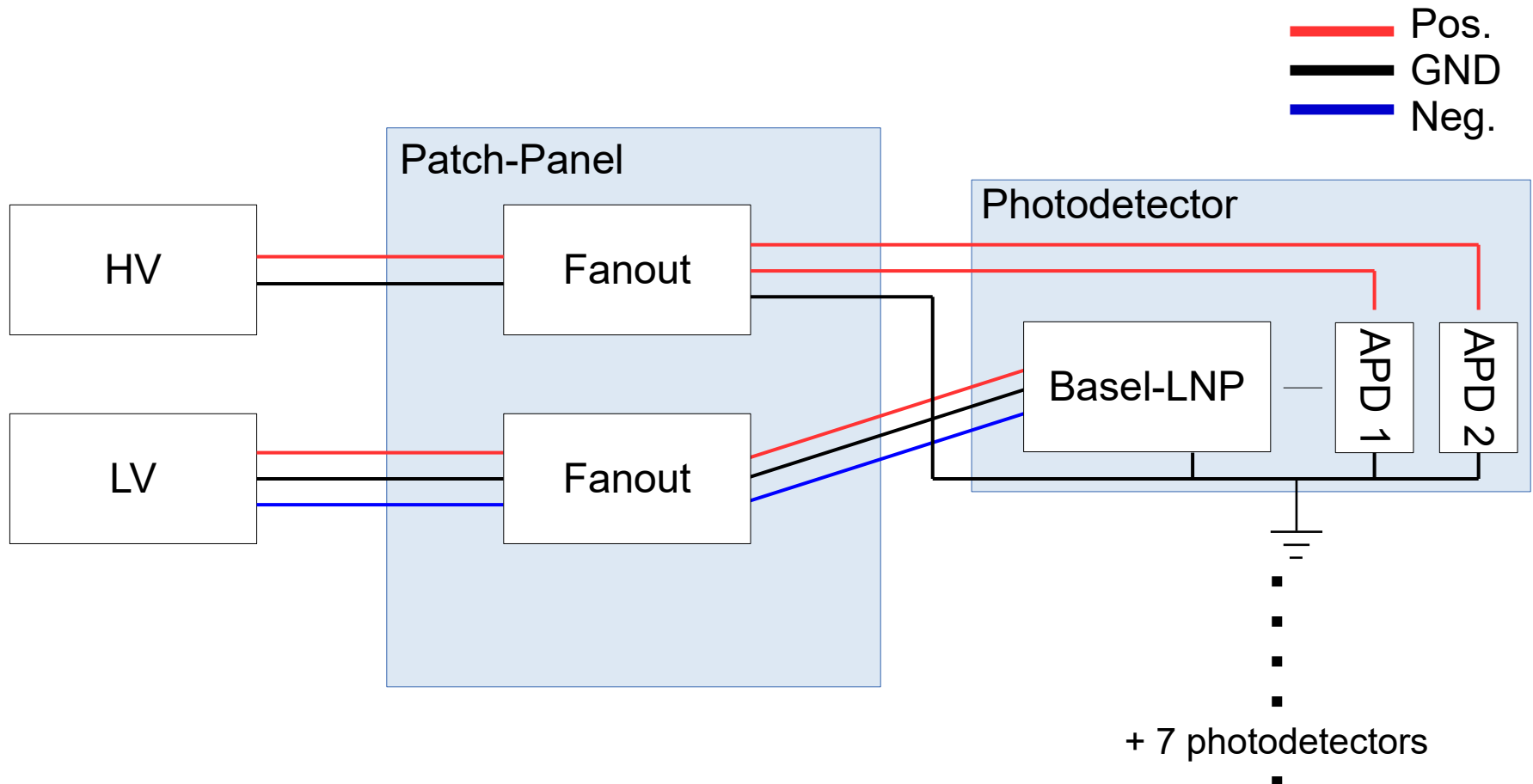

Power distribution concept

Voltage distribution

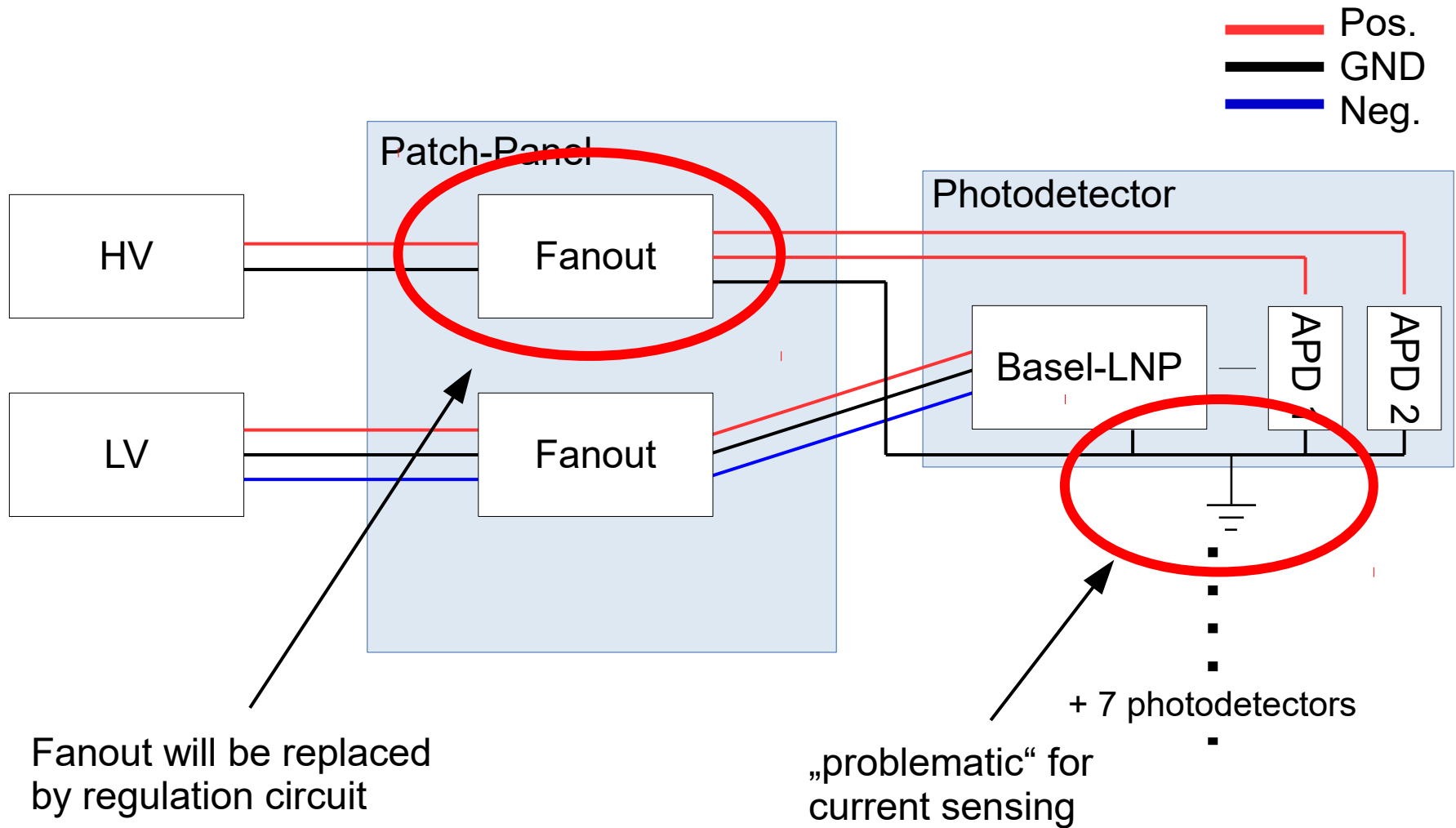

Reuse HV regulation circuit from the Crystal Barrel Exp.@ELSA
(also used in the barrel part)

- Regulation range 10Bit (100-500V)
- Temp. compensation
- I²C controlled

Special adaption for forward endcap

- 8%/V @ gain 200 → ~ 0,1V Voltage resolution
- Reasonably regulation span (~25-40V)
- Accurate HV voltage measurement
- (Current measurement)

Mechanics – space constraints




Extrem dense situation behind the backplate

- All cables have to fit in a depth of 3.3cm
- Patch panel is interconnection of alveole to „outside“ cables

Add piggyback board


- As close as possible to existing patch panel
- Adds space for components of about 73 cm²

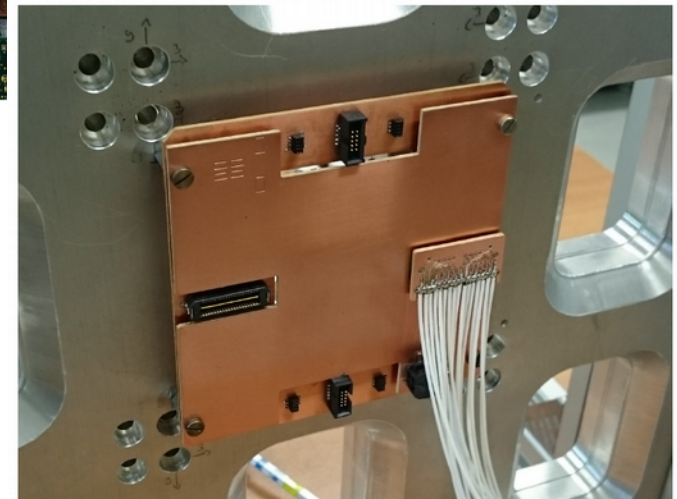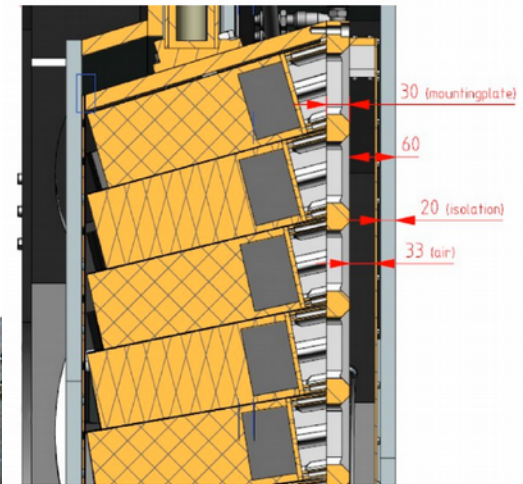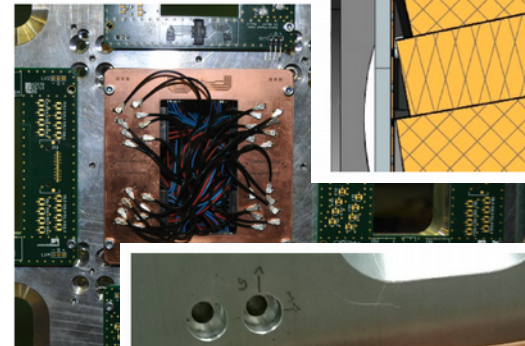Piggyback board helps in mounting procedure




Voltage regulation

Schematic of basic circuit

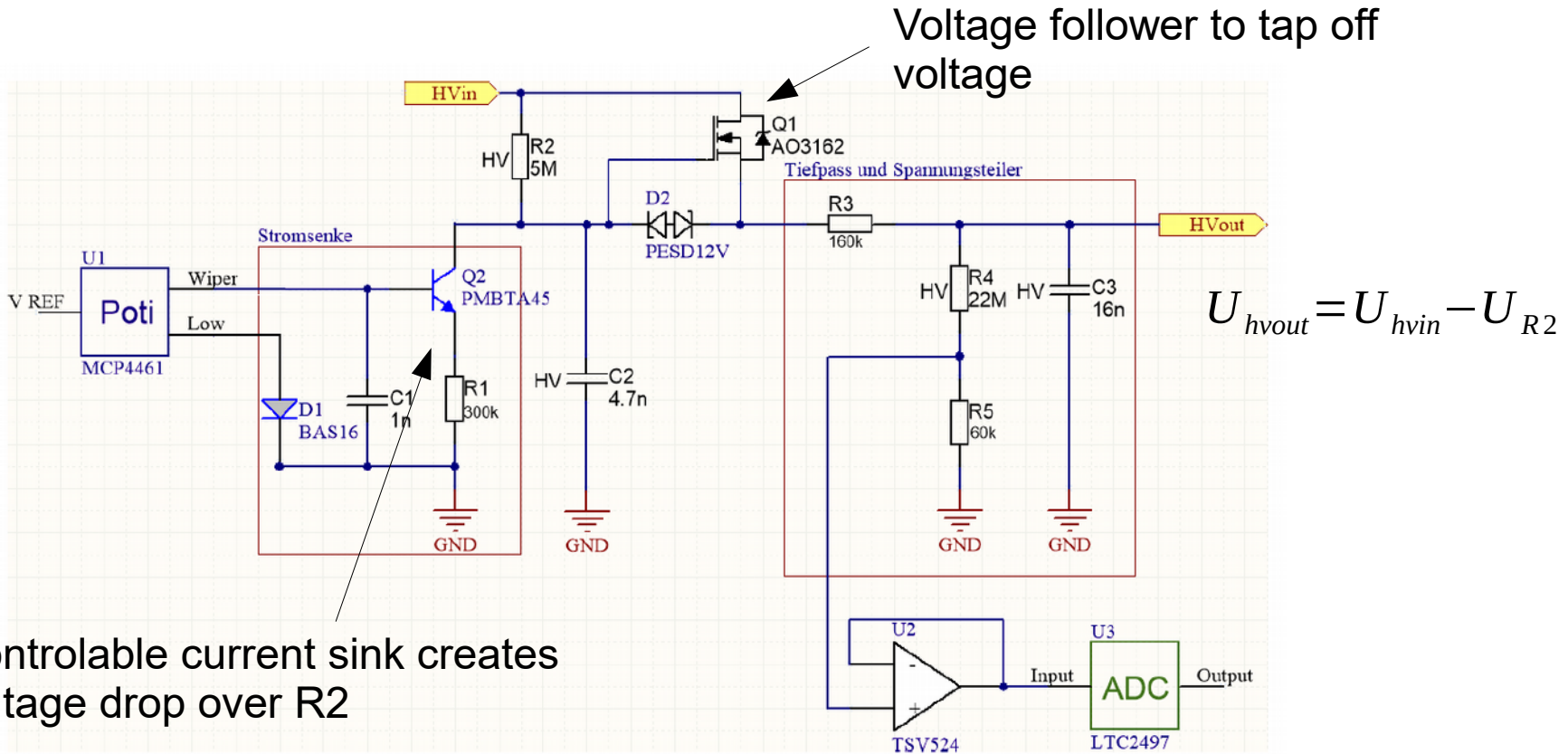

Whole basic circuit is needed 32x for 16er and 16x for 8er alveole

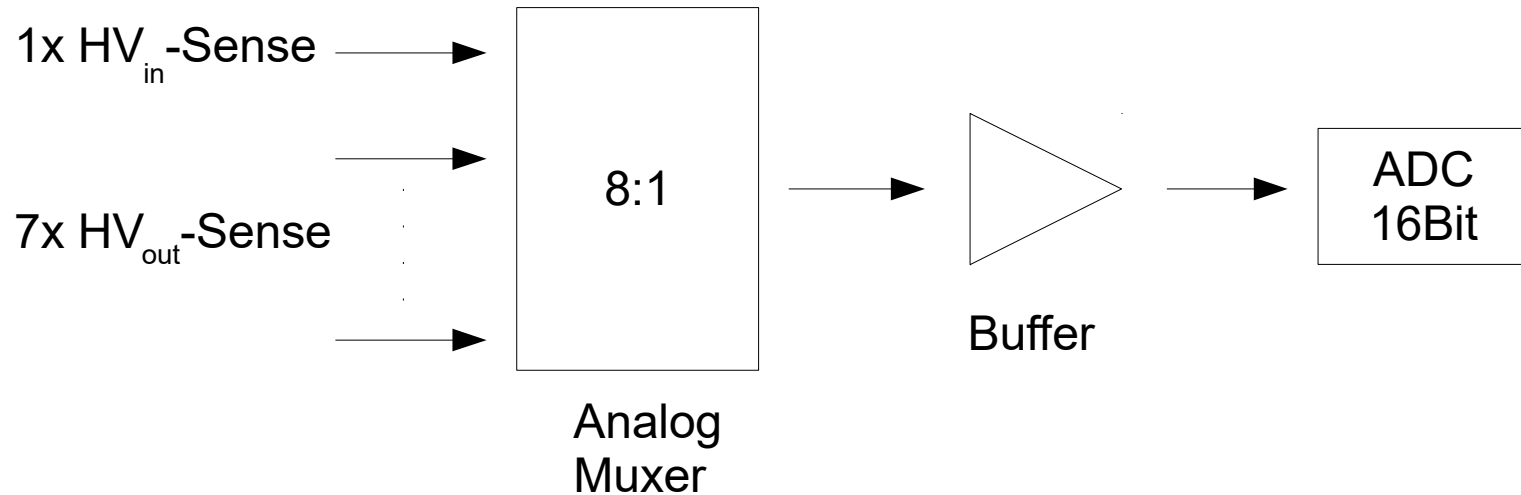Instead of 32 OP-amps and 2 ADCs, sense voltages switched by muxer



Pros


- Monitoring of input voltage
- Recalibration of ADC channels possible after mounting

Cons

- Only 4/5 channels can be converted at once

Space constraints

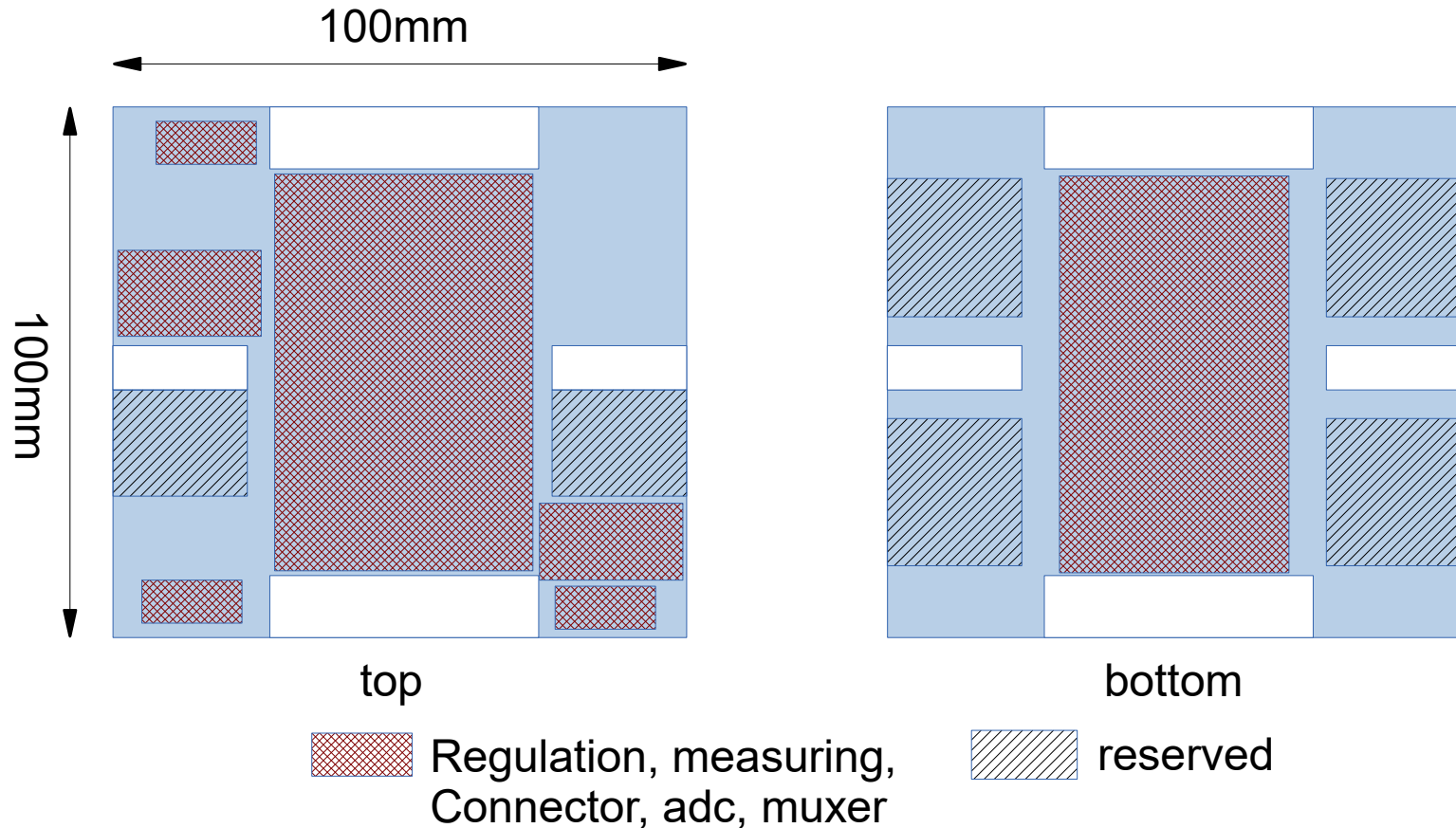
Almost all space used by regulation, measurement and connectors
high side current sensing needs more components




Not enough space → omitted current measurement

Board layout

Current design

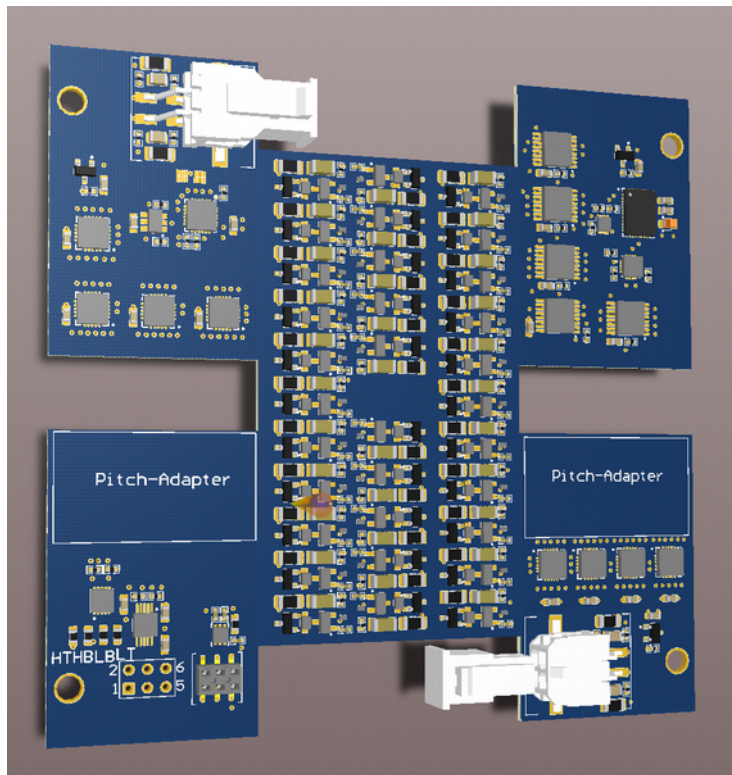


Top side

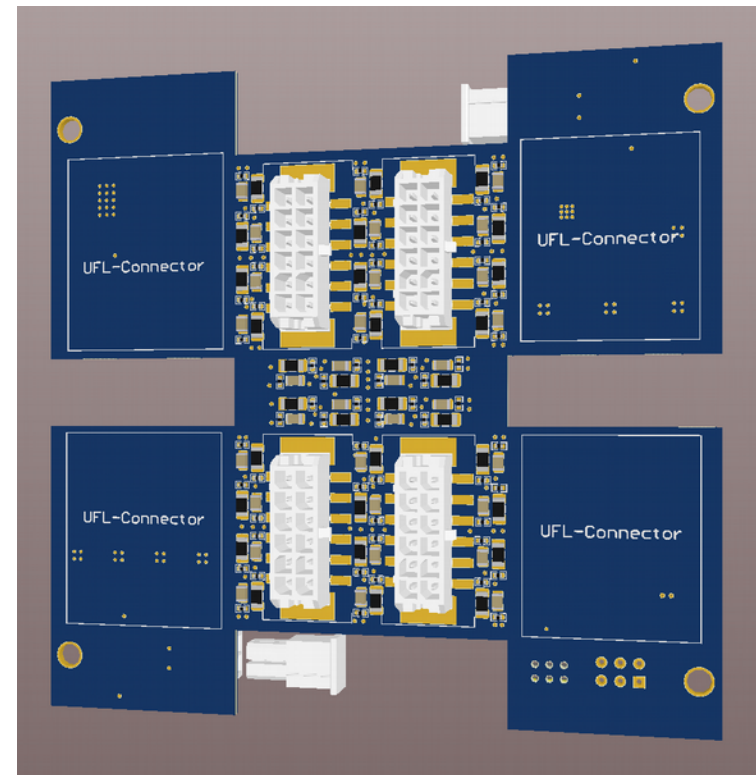

Bottom side

Board layout

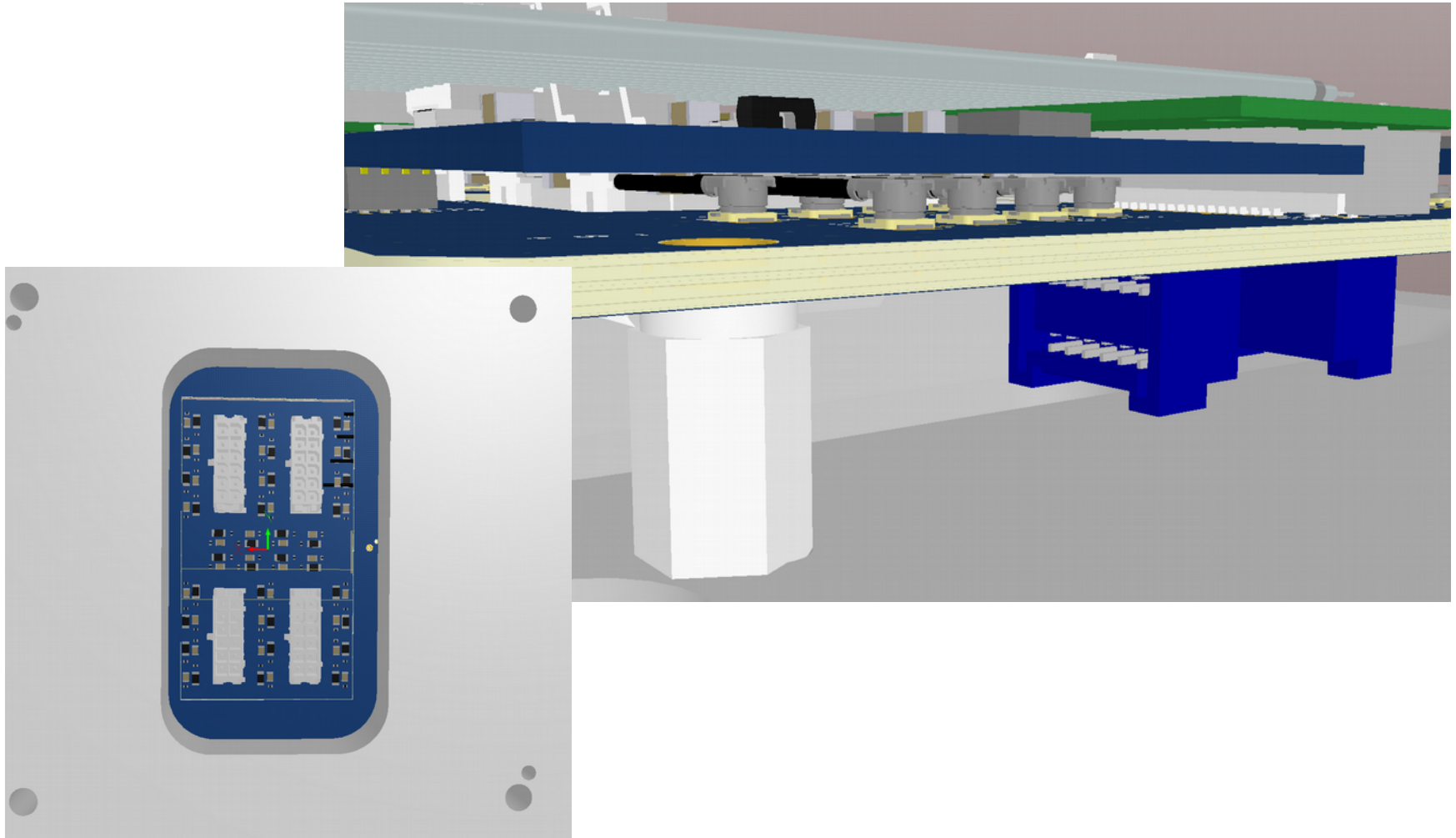

Cable „problem“

264 patch panel boards (16er/8er size) on each, one HV board

No room for 264 cables from available cross section.

—————▶ In maximum ~32 cables possible

I²C

- 2 pairs via differential I²C (Data, CLK)
- chainable

SPI

- 4 single ended lines (SS, MOSI, MISO, CLK)
- chainable

To reduce cable count boards needs to be cascaded

16 boards → ~ 16 cables

8 boards → ~ 32 cables

Dangerous:

If data- or clock-lines get stuck, one loses control of connected boards


Due to different chip selection (dig. Poti, ADC) from original design, tests are needed

Test parameter of chips under different conditions

- Radiation
 - Test chips (I²C, ADC, Poti,...) up to a radiation dose of 500Gy
 - 4 runs of 125 Gy
- Temperature-cycles / dependence
- Longterm stability of voltage

1-Channel
prototype

I2C components
test board

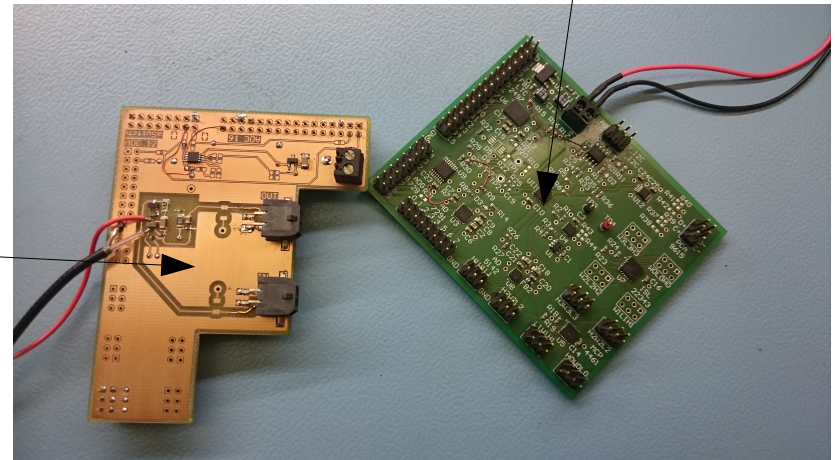

Radiation tests

Test of digital potentiometer by measuring Resistance by 6,5digit multimeter





MCP444X/446X

7/8-Bit Quad I²C Digital POT with
Nonvolatile Memory

Comparing the voltage divider factor for different radiation doses:

$$r_T(ch) = \frac{R_T(ch)}{R_T^{max}}$$

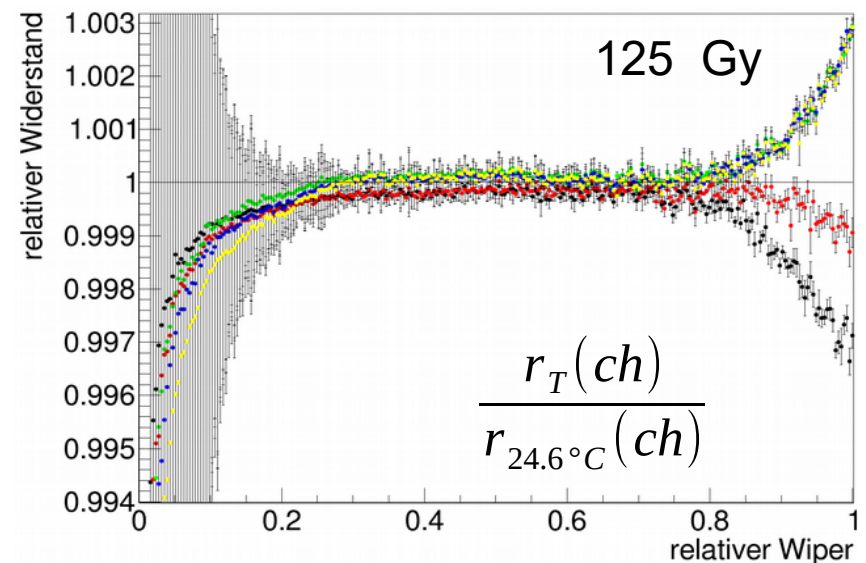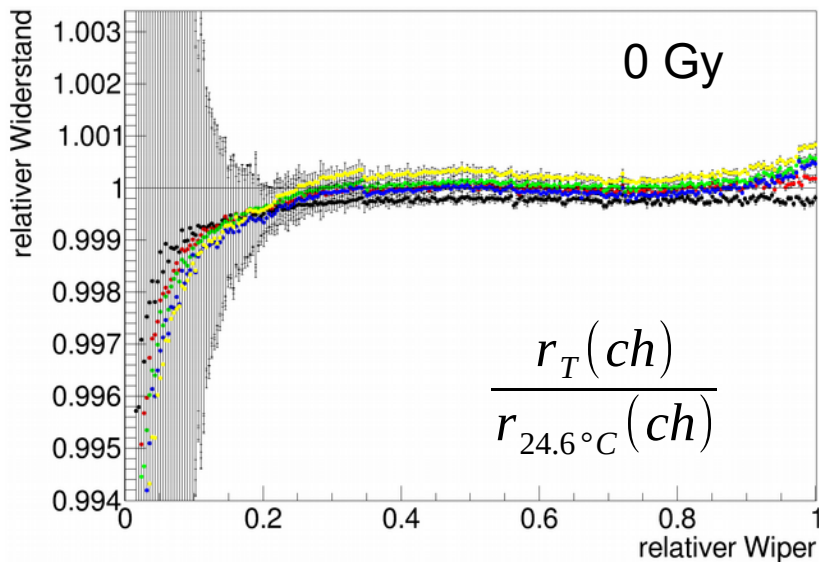- 24,6 °C
- 9,8 °C
- 0,2 °C
- -10,2 °C
- -20,2 °C
- -29,8 °C




Radiation tests

Test of digital potentiometer by measuring
Resistance by 6,5digit multimeter



MCP444X/446X

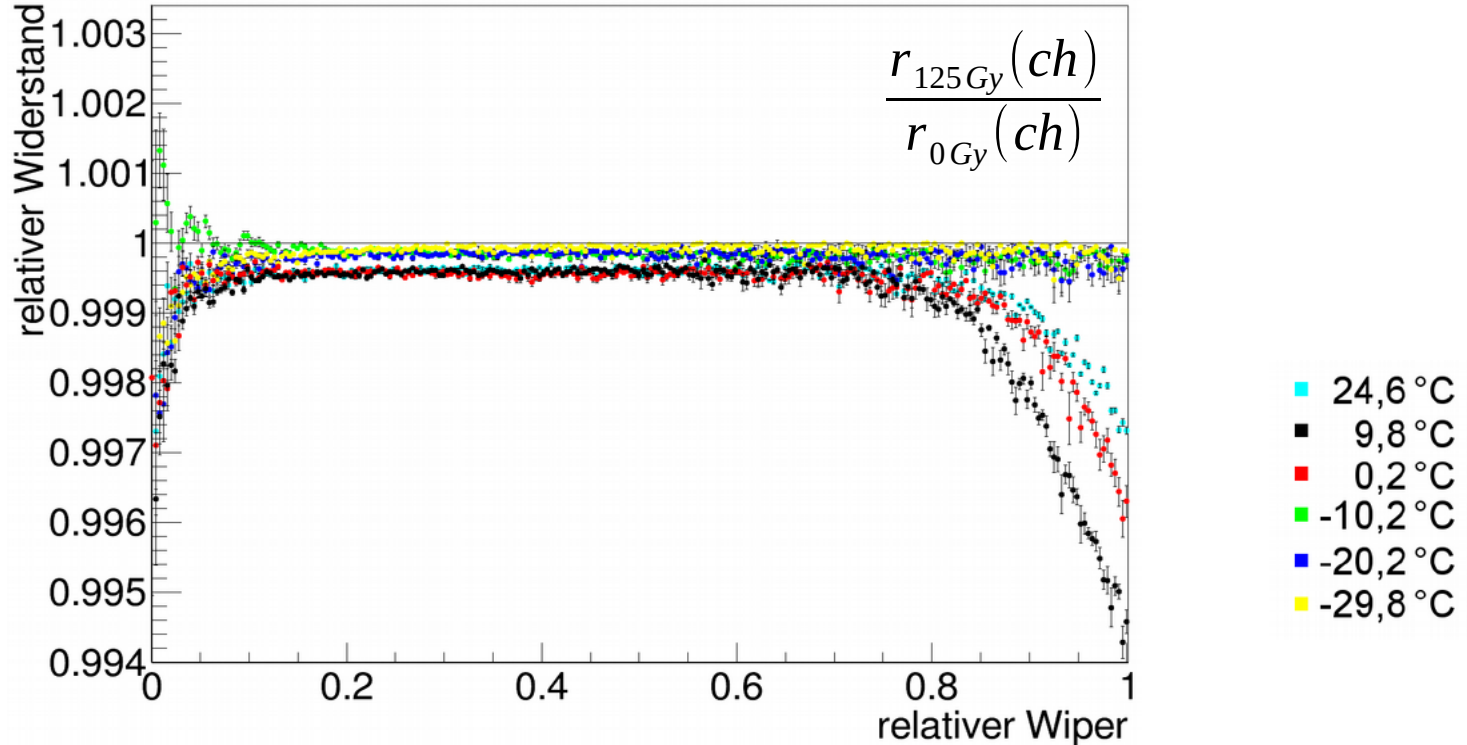7/8-Bit Quad I²C Digital POT with
Nonvolatile Memory





Stimulate ADC input with external voltage source (0-1.5V)




LTC2497

16-Bit 8-/16-Channel


Fit of $U_T(c) = o + g_T \cdot c$

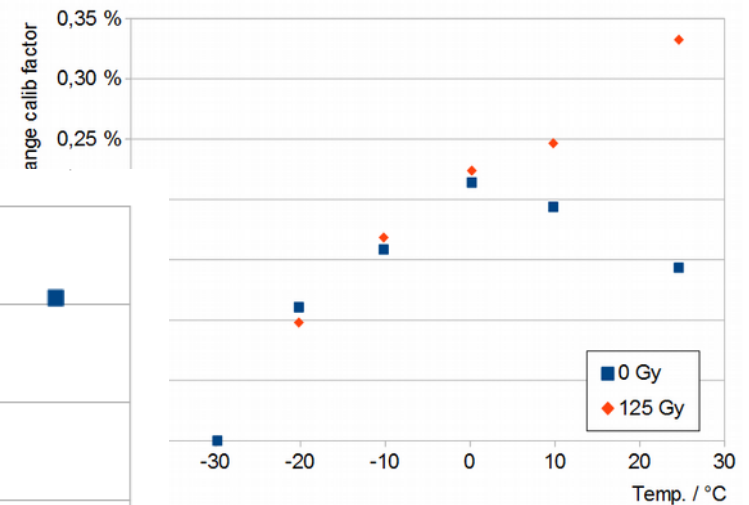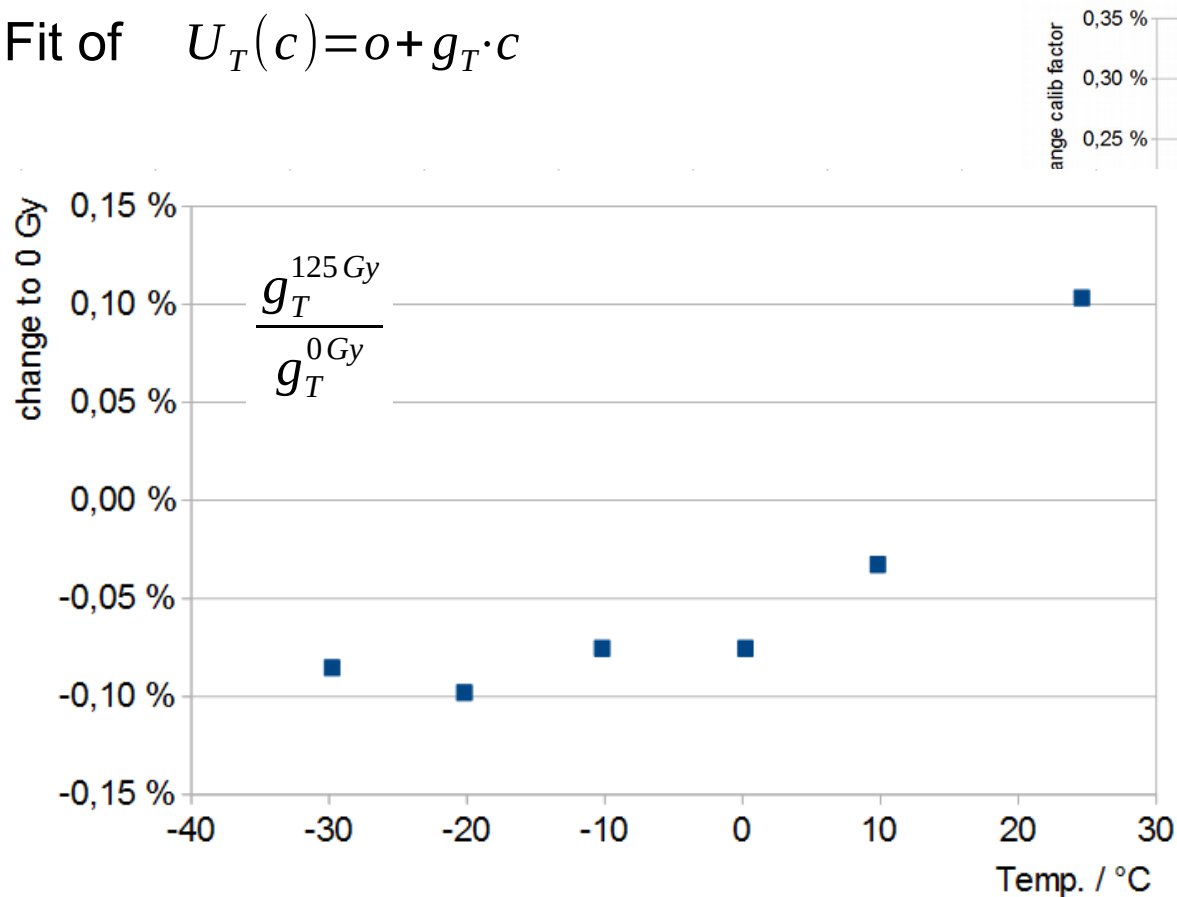

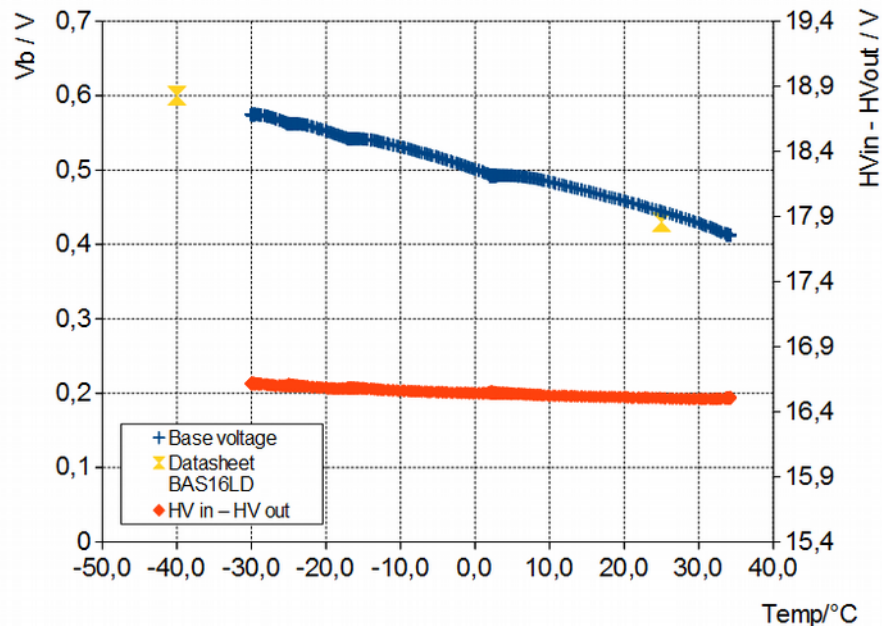High voltage output - temperature dependence



~ 2mV/°C drift @Wiper=0

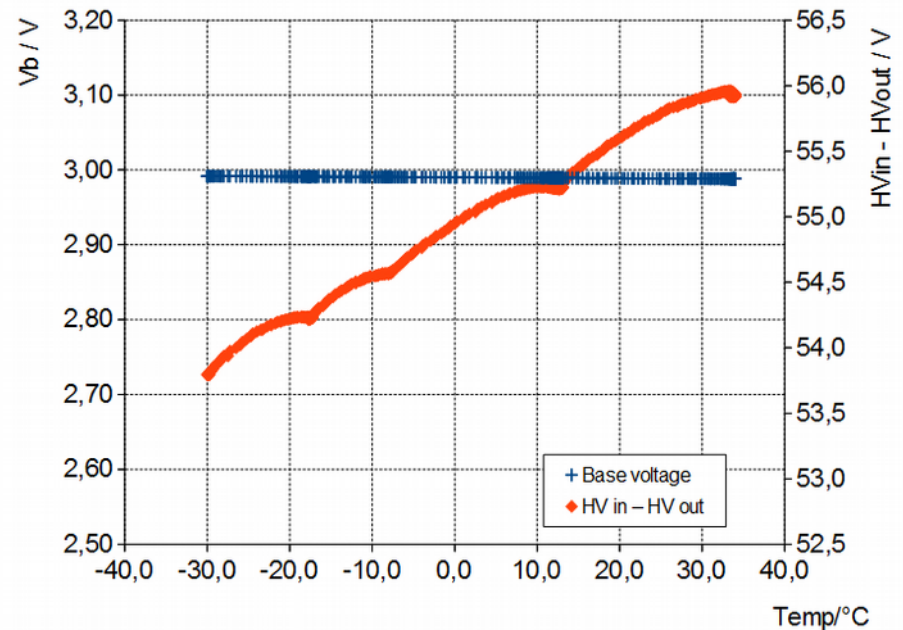

~ 33mV/°C drift @Wiper=255

- Current design compensates temp. dependence only partly
- If temp. is stable below 0.5°C, temp. dependence will be max. 16mV

Ref. Voltage 3V


~ 60μV/°C temp. dependence (datasheet max. 80ppm/°C)

1-Channel Prototype

High voltage output - step size (LNB)

Digital potentiometer (MCP446X) with 8Bit resolution

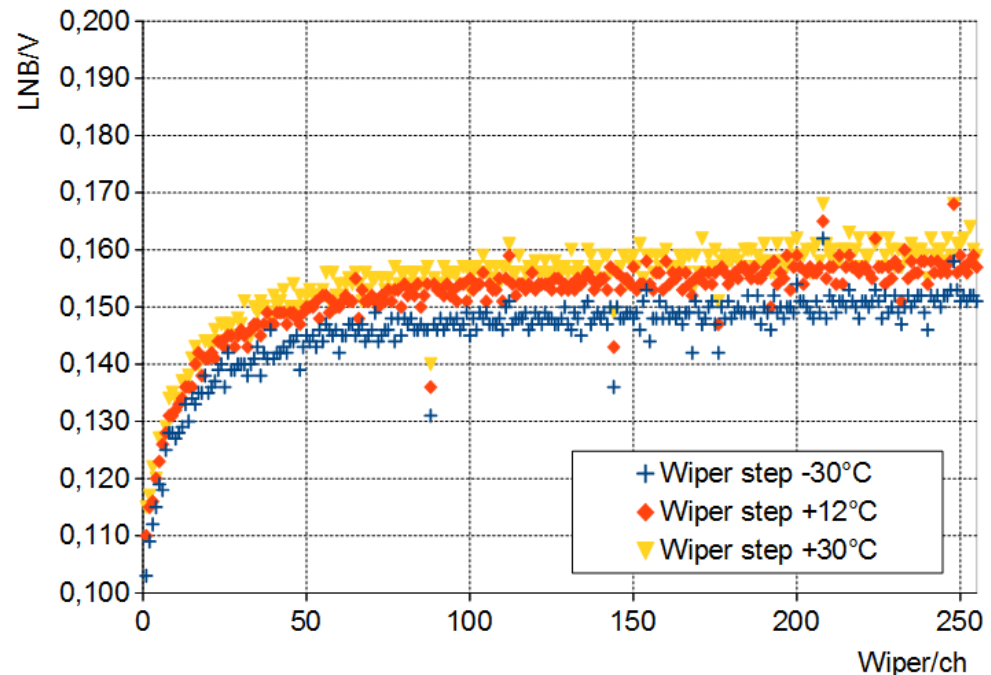@40V → 100 – 160 mV
(8%/V: ~1%)
@20V → 50 – 80 mV
(8%/V: ~0,5%)



Alternative to MCP 446x:

Serial adapter chip (integrated 10bit DAC)

can increase the range by factor of 3 → 40V to 120V

or the resolution by factor 3 → 150mV to 50mV

see talk H. Flemming

1-Channel Prototype

High voltage output - long term stability

Measurement at a fixed temperature in comparison to a 6,5digit multimeter (Keysight 34465A)

HV_{in} , HV_{out}

6,5digit DMM

ADC calib


onboard ADC

To be independent of HV_{in} fluctuations use difference

Std. deviation:

$HV_{in} - ADC \rightarrow 25mV$

$HV_{in} - HV_{out} \rightarrow 10mV$

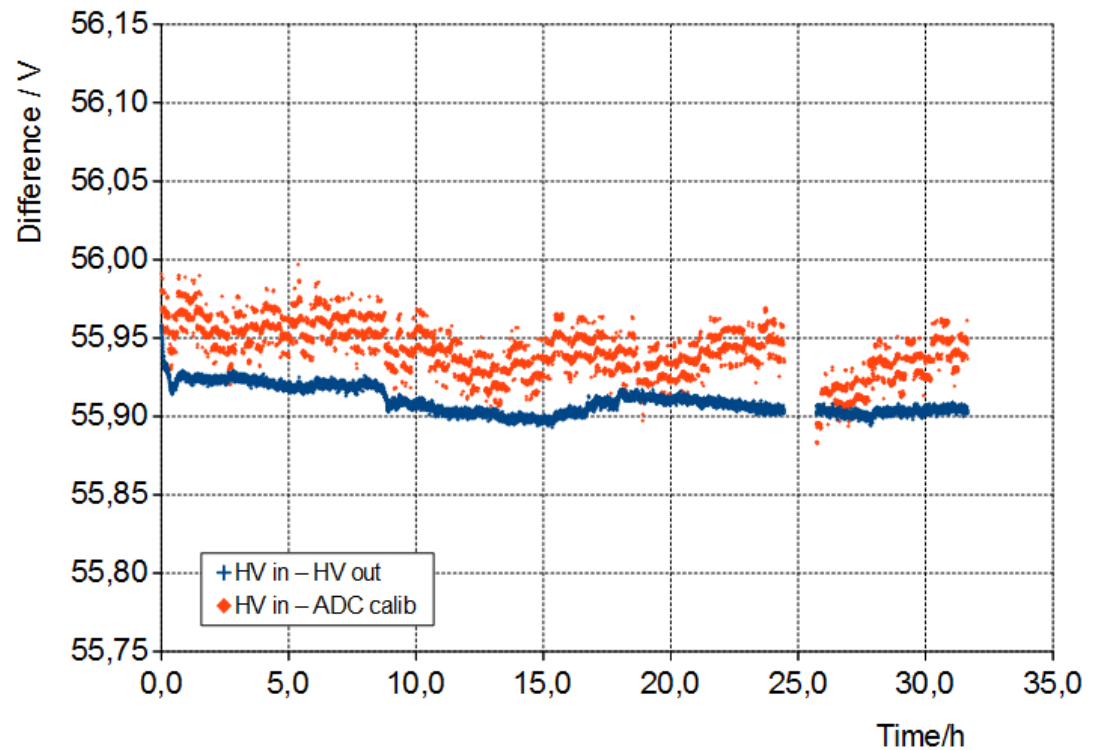

1-Channel Prototype

High v

Measu
(Keysig

Hvin, H

ADC ca


To be in
fluctuat

Std. de

HV_{in} - A

HV_{in} - H

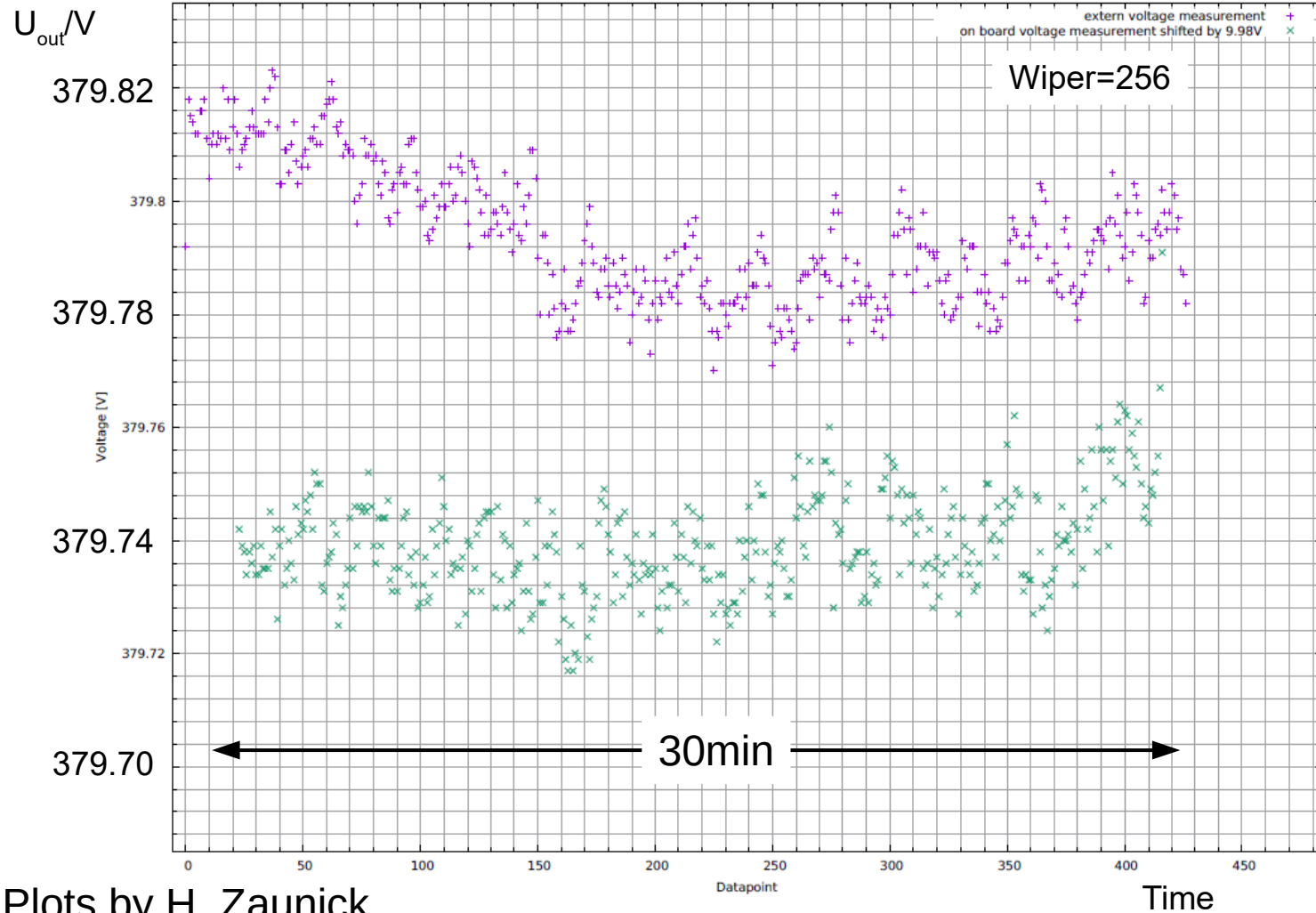Test with Barrel-Prototype (original chip set)



Plots by H. Zaunick

1-Channel Prototype

High v

Measu
(Keysi

Hvin, I

ADC c

To be i
fluctua

Std. de

$HV_{in} - I$


$HV_{in} - I$

Test with Barrel-Prototype (original chip set)



Next steps


Rough Time schedule

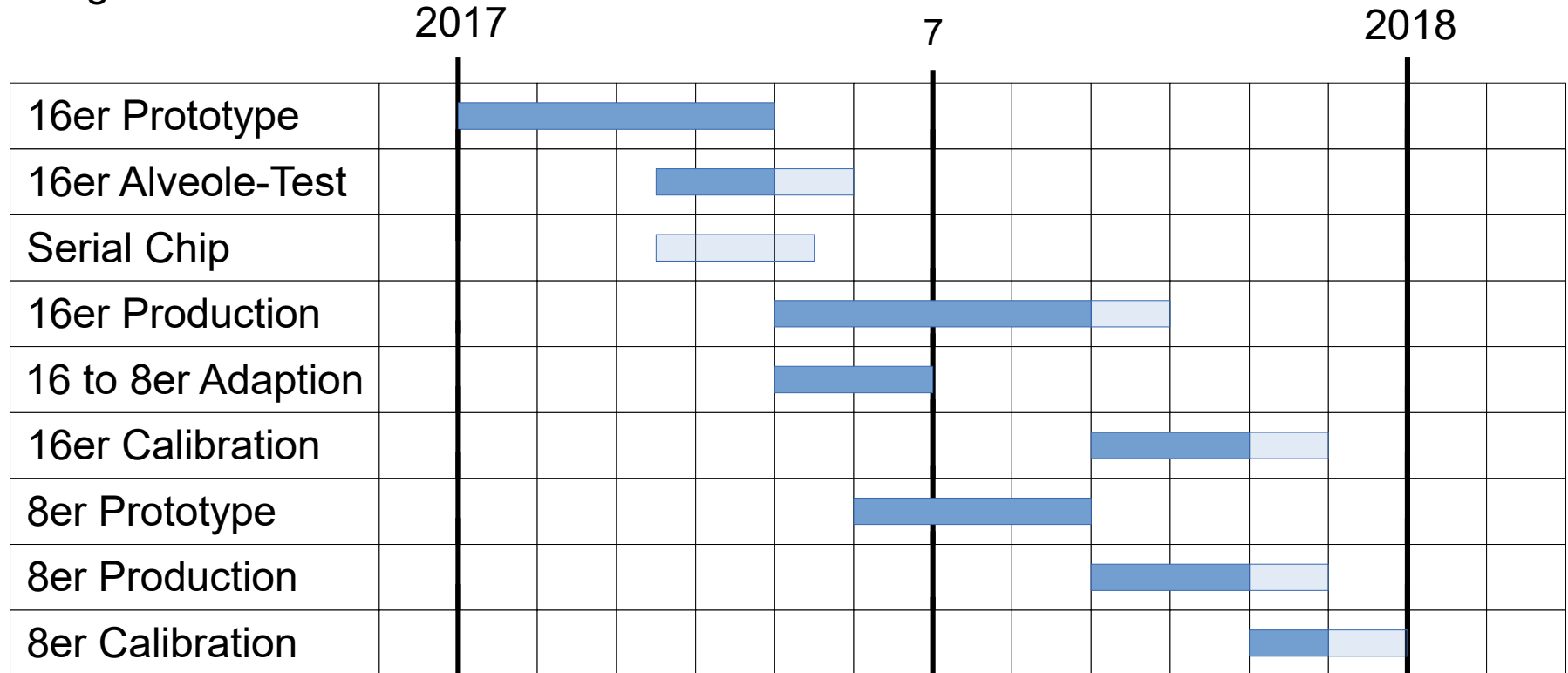


Near future steps

- Finalize layout 16er
- Build prototype
- Test 16er with APD Alveole

Thank you for your attention

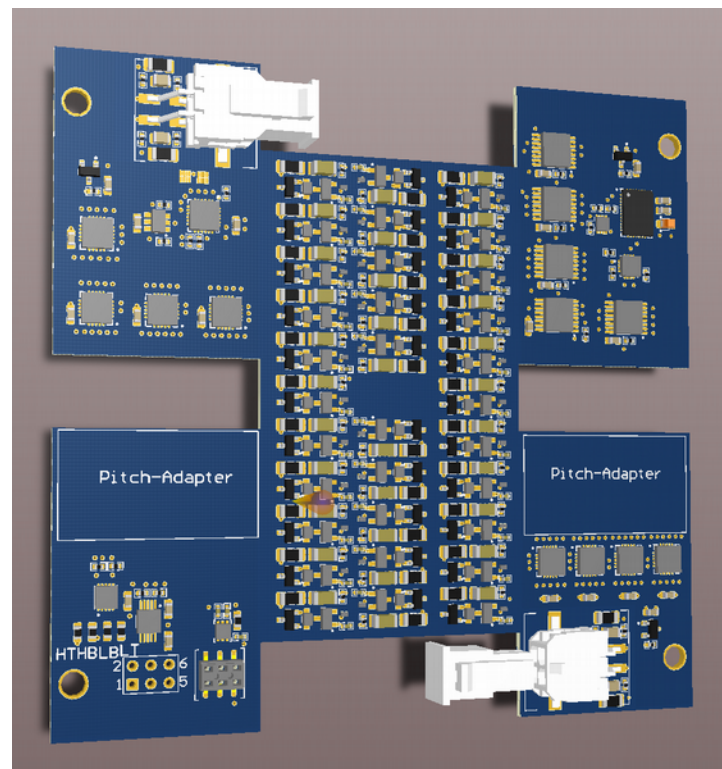


Backup slides

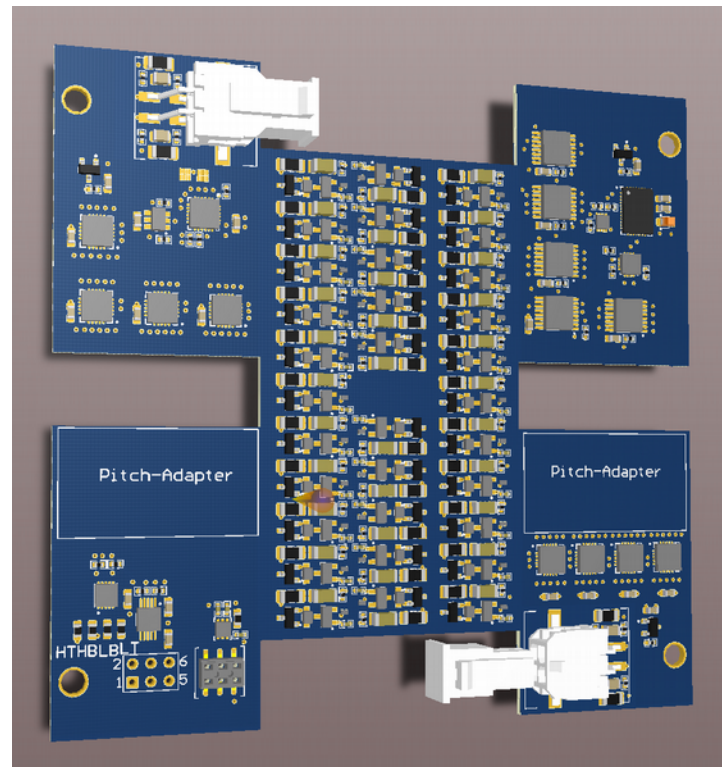

Space consumption

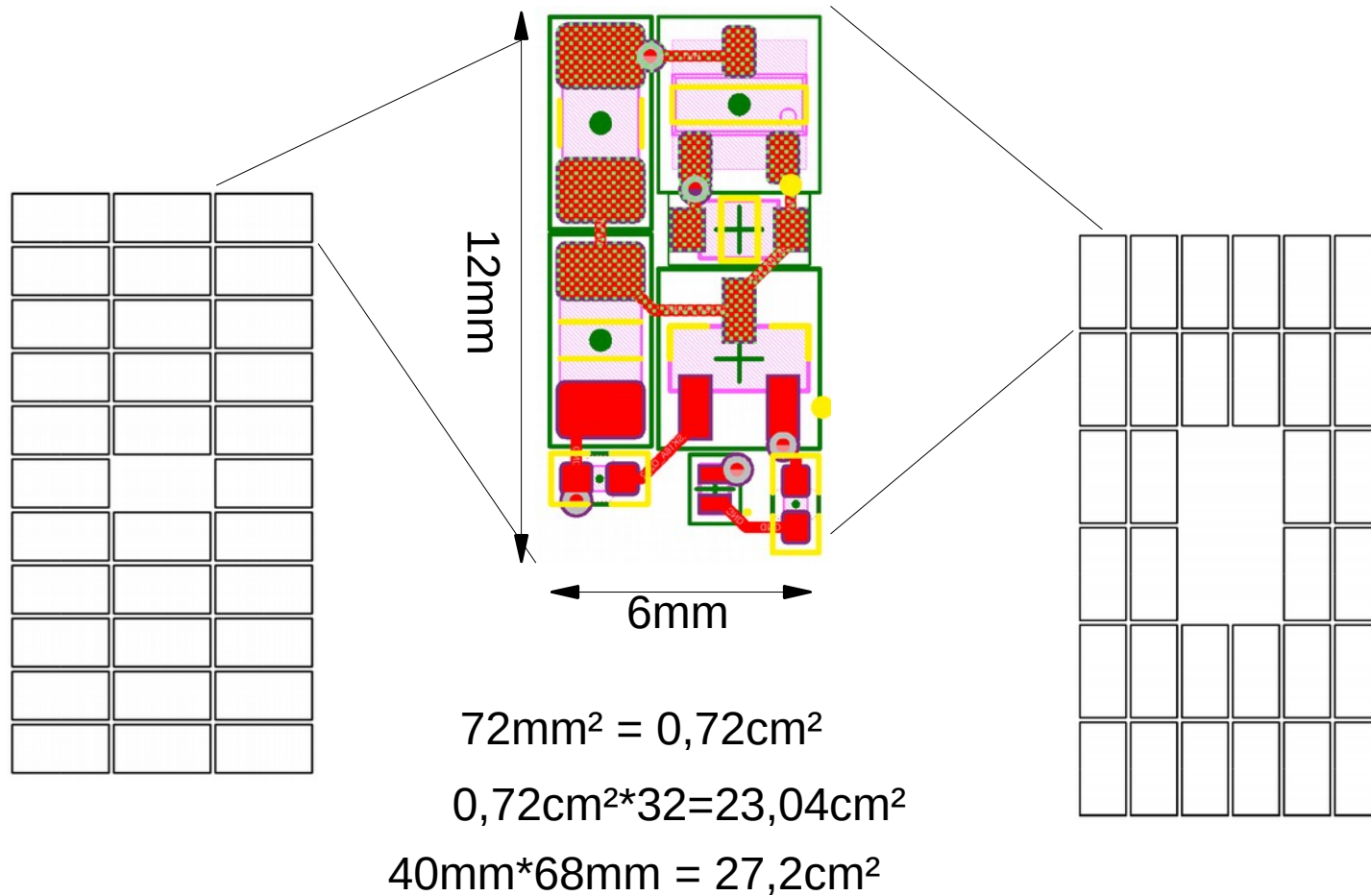Current sink and voltage follower on top, Voltage divider near connector on bottom




Current measurement circuit

Grounding concept in photodetector needs a highside current measuring circuit

Wilson Current Mirrors

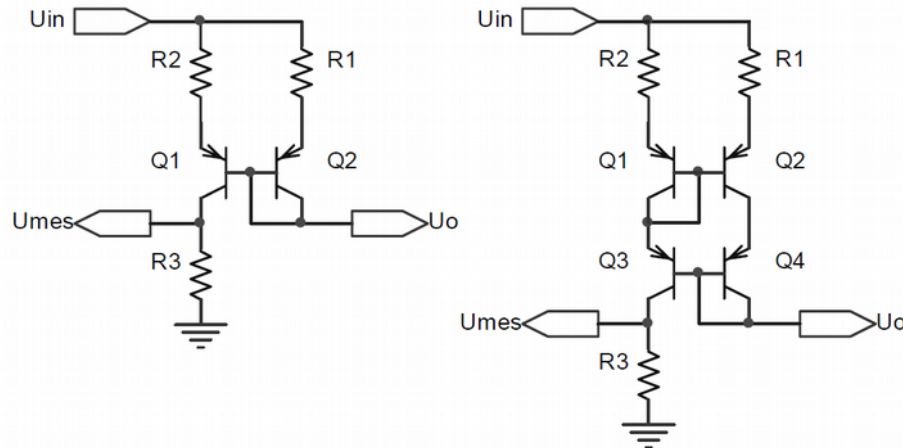mirrors current from the high side to a low side, where measuring can be done via a shunt resistor



Problems


Find FETs that can with stand 500V on U_{DS}

Needs much space (+additional parts to convert digital)

—————▶ Current sensing omitted

High voltage output - voltage measurement


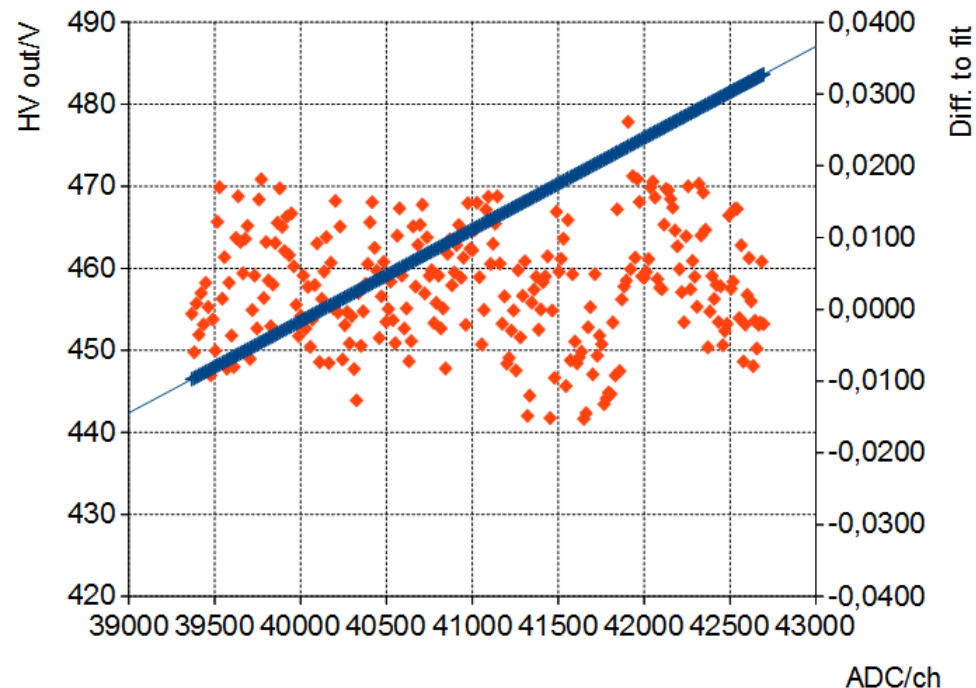
Output measured by 6,5digit DMM and sweep of potentiometer from 0 to 255.
3mV over Calibration




Maximal variation from a linear calibration $\sim \pm 20\text{mV}$

Space constraints

 reserved

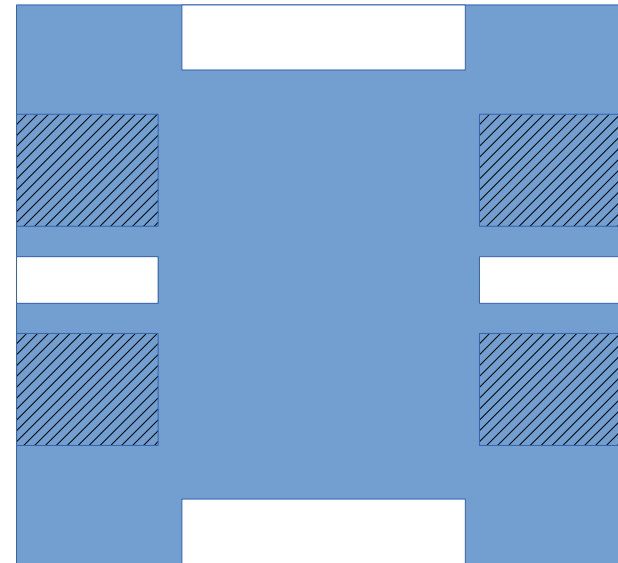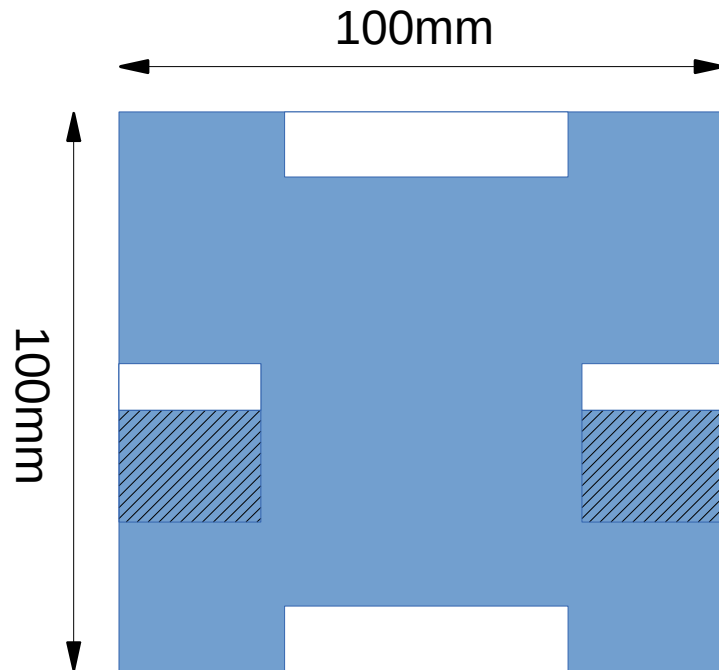

I²C structure

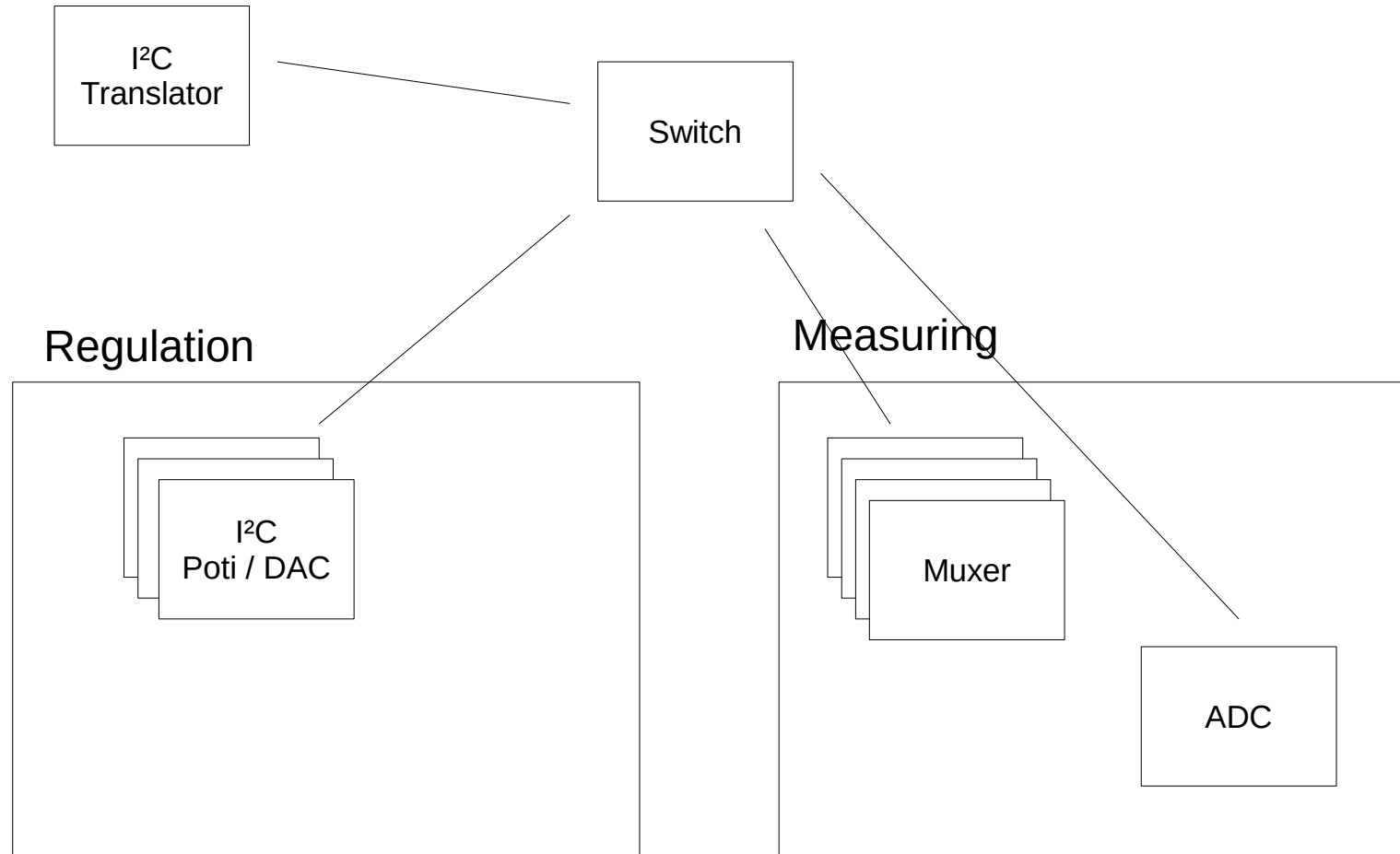

I²C standard allows 7 or 10 bit adr.

- 7 bit commonly used, 10 bit not on every chip
- $128 - 16 = 112$ adr.
- I²C switches, adr. translation
- Diff. I²C

Chip selection for current sink control

- Microchip MCP4464, 8Bit dig. Poti
- GSI chip, 10Bit DAC