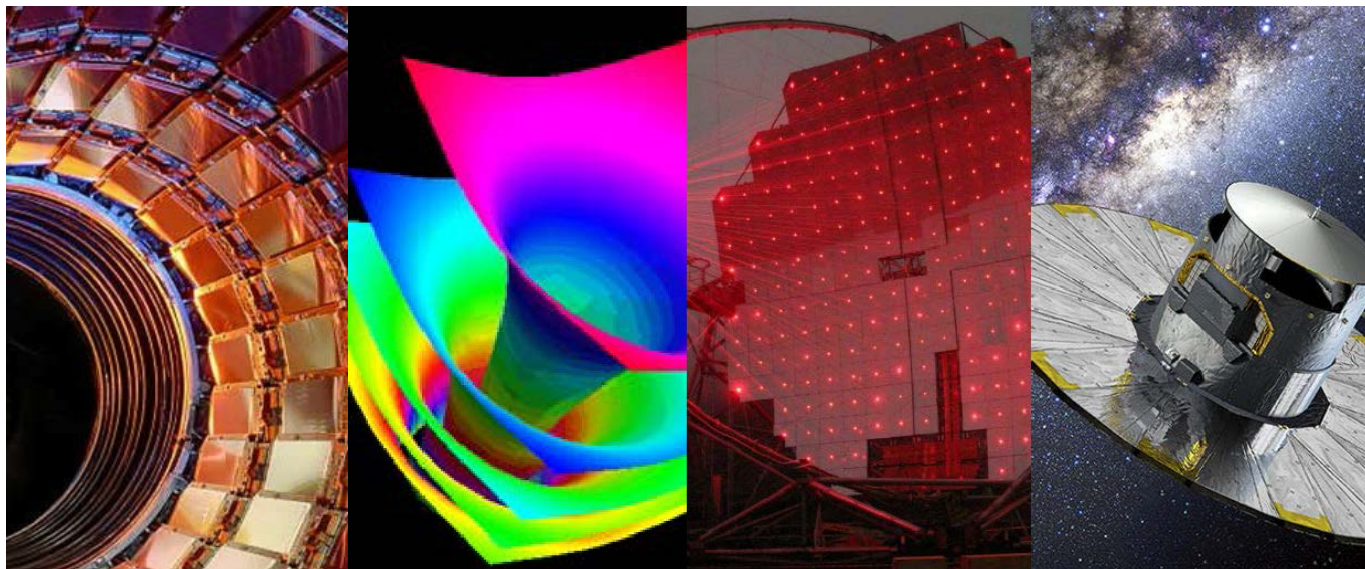




EXCELENCIA
MARIA
DE MAEZTU

Institute of Cosmos
Sciences



Review of SiPM readout circuitry

D. Gascon, S. Gomez (ICCUB)

R. Ballabriga, J. M. Fernandez (CERN)

ICASiPM

14/06/2018

- I. Introduction**
- II. SiPM electrical parameters
- III. FE circuits stage
- IV. ASIC examples
- V. Conclusions

I. Introduction

- Many different ASICs
 - Many possible classifications as well !
- According the input impedance
 - Current mode versus voltage mode
- According the complexity / functionality
 - Pure analogue front-end
 - Section III
 - Mixed-mode including digitization and readout
 - Section IV
- According the application
 - Many applications: PET, LIDAR, vision, life-sciences, particle physics, astrophysics, etc
 - Fast timing is a must in many of them

I. Introduction

- Disclaimers: what this talk will **not** be
 - A comprehensive review of SiPM read out chips
 - We would need hours !
 - How to measure SiPM electrical parameters
 - Some references at the end
 - Recommendation for model fine tuning and validation:
 - Compare measurements to simulations including model of the electronics!
- What we will talk about:
 - Review SiPM electrical parameters impact on signal shape and readout
 - Include effect of load (“amplifier”) input impedance and interconnect
 - Review basic input stages and analog signal processing
 - Present some examples of ASICs for different applications
 - Projects in which I am involved: the ones we know better ☺

Outlook

- I. Introduction
- II. SiPM electrical parameters**
- III. FE circuits
- IV. ASIC examples
- V. Conclusions

II. SiPM electrical model

Vacuum Photomultipliers

$$G = 10^5 - 10^7$$

$$C_d \sim 10 \text{ pF}$$

$$L \sim 10 \text{ nH}$$






Silicon Photomultipliers

$$G = 10^5 - 10^7$$

$$C = 10 - 400 \text{ pF}$$

$$L = 1 - 10 \text{ nH}$$

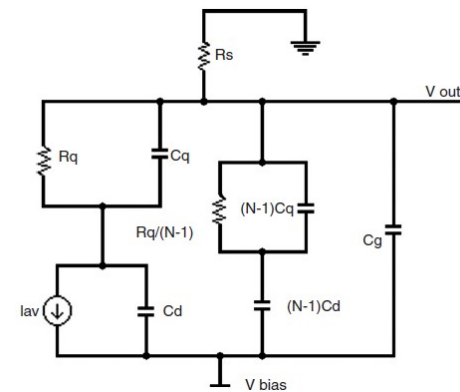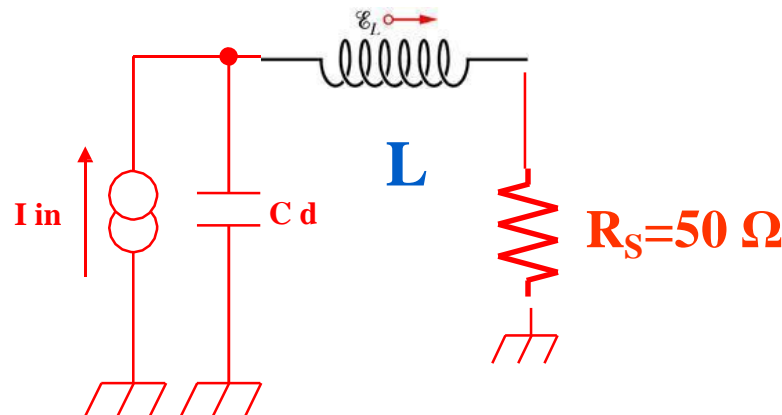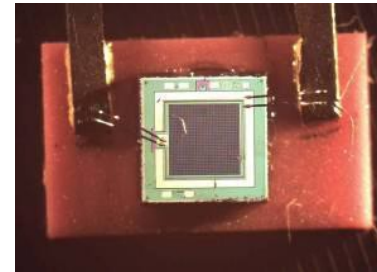


II. SiPM electrical model

Single cell model $\rightarrow (R_d || C_d) + (R_q || C_q)$

SiPM + load $\rightarrow (|| Z_{cell}) || C_{grid} + Z_{load}$


Signal = **slow** pulse (τ_d (rise), τ_{q-slow} (fall)) + **fast** pulse (τ_d (rise), τ_{q-fast} (fall))

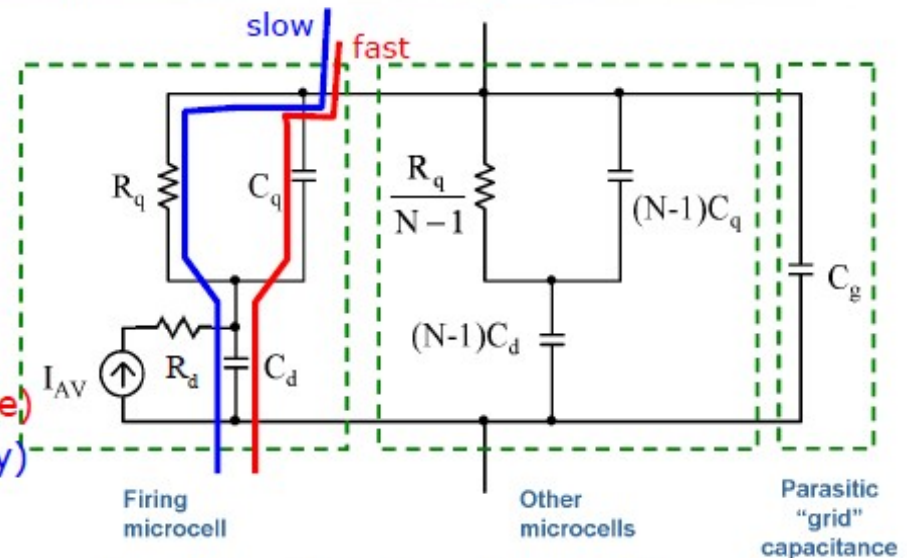- τ_d (rise) $\sim R_d (C_q + C_d)$
- τ_{q-fast} (fall) = $R_{load} C_{tot}$ (fast; parasitic spike)
- τ_{q-slow} (fall) = $R_q (C_q + C_d)$ (slow; cell recovery)



Pulse shape
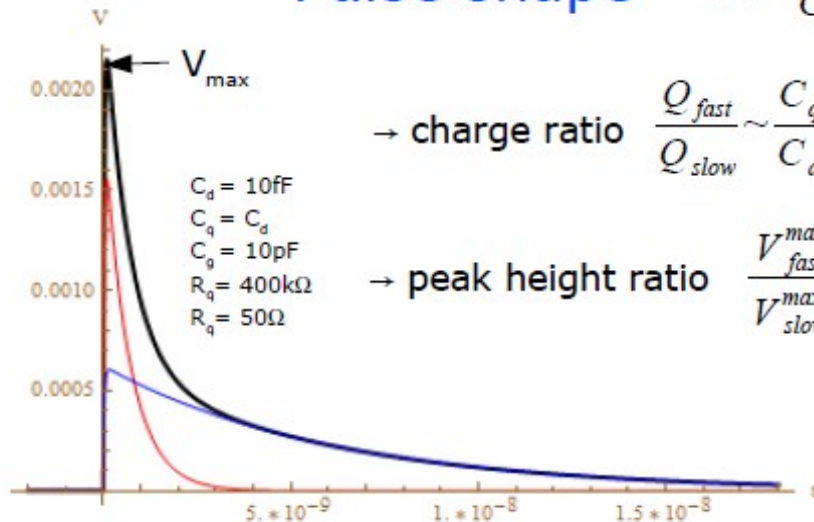
$$V(t) \approx \frac{Q}{C_q + C_d} \left(\frac{C_q}{C_{tot}} e^{\frac{-t}{\tau_{FAST}}} + \frac{R_{load}}{R_q} \frac{C_d}{C_q + C_d} e^{\frac{-t}{\tau_{SLOW}}} \right)$$



→ charge ratio $\frac{Q_{fast}}{Q_{slow}} \sim \frac{C_q}{C_d}$

→ peak height ratio $\frac{V_{fast}^{max}}{V_{slow}^{max}} \sim \frac{C_q^2 R_q}{C_d C_{tot} R_{load}}$

1) Peak V/I signal goes with C^{-1}

2) Peak I signal goes with R^{-1}


increasing with R_q and $1/R_{load}$
(and C_q of course)

Increasing C_q/C_d or/and R_q/R_{load}
→ spike enhancement
→ better timing


3) Fast vs slow component

ii: Equivalent input network: Series and parallel resonances

Current sensing

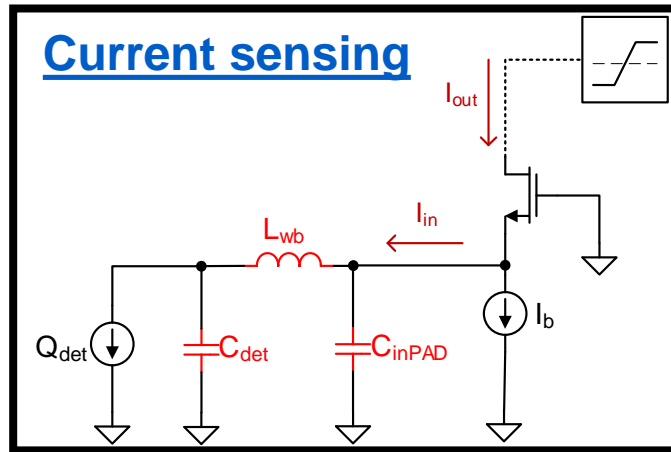


Series resonance: $C_{in} \rightarrow 0$

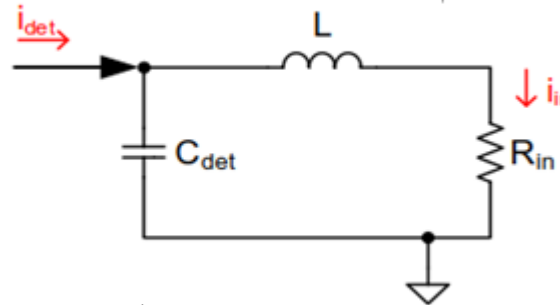


2nd order system

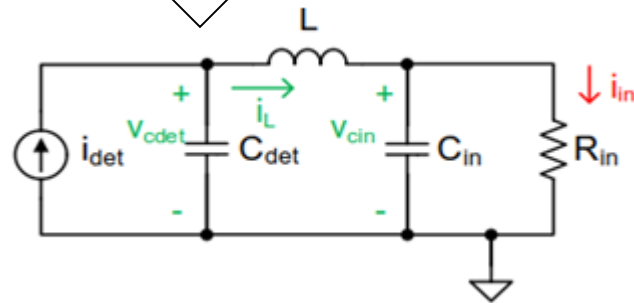- $\omega_{n,s} = \frac{1}{\sqrt{L C_{det}}}$
- $Q_s = \frac{\omega_{n,s} L}{R_{in}} = \frac{1}{R_{in}} \sqrt{\frac{L}{C_{det}}}$
- $R_{in,cr} = 2 \sqrt{\frac{L}{C_{det}}}$



Parallel resonance: $C_{in} \neq 0$

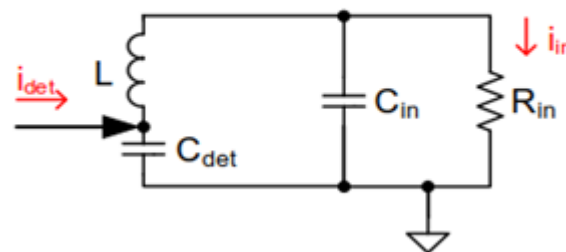

3rd order system

- $\omega_{n,p} = \frac{1}{\sqrt{L (C_{det} || C_{in})}}$
- $Q_p = \frac{C_{in}^2 R_{in}}{\sqrt{(C_{det} || C_{in})^3 L}} \approx R_{in} \sqrt{\frac{C_{in}}{L}}$
- $R_{in,p} = \frac{1}{2} \frac{\sqrt{L (C_{det} || C_{in})^3}}{C_{in}^2} \approx \frac{1}{2} \sqrt{\frac{L}{C_{in}}}$

Similar analyses in "Interfacing a SiPM to a Current-mode Front-End, F. Ciciriello et al.", and "SiPM readout electronics overview, CNRS/IN2P3, C. de la Taille, 2012"

II: Dynamics of the input signal

For oscillation-free input current:

$$R_{in,cr} \leq R_{in} \leq R_{in,p} \rightarrow 2 \sqrt{\frac{L}{C_{det}}} \leq R_{in} \leq \frac{1}{2} \frac{\sqrt{L(C_{det} || C_{in})^3}}{C_{in}^2} \quad \&\& \quad C_{det} \geq 18.7 C_{in}$$

Corners: L = 5 nH (Small) / 25 nH (Large), Cdet = 10 pF (Small) / 1 nF (Large)


L / C _{det}	R _{in} range for C _{in} = 0.1 pF	R _{in} range for C _{in} = 0.5 pF	R _{in} range for C _{in} = 1 pF
Small / Small	44.72 Ω ≤ R _{in} ≤ 110.15 Ω	44.72 Ω ≤ R _{in} ≤ 46.47 Ω	44.72 Ω ≤ R _{in} ≤ 30.64 Ω
Small / Large	4.47 Ω ≤ R _{in} ≤ 111.78 Ω	4.47 Ω ≤ R _{in} ≤ 49.96 Ω	4.47 Ω ≤ R _{in} ≤ 35.3 Ω
Large / Small	100 Ω ≤ R _{in} ≤ 246.29 Ω	100 Ω ≤ R _{in} ≤ 103.91 Ω	100 Ω ≤ R _{in} ≤ 68.52 Ω
Large / Large	10 Ω ≤ R _{in} ≤ 249.96 Ω	10 Ω ≤ R _{in} ≤ 111.72 Ω	10 Ω ≤ R _{in} ≤ 78.93 Ω

Oscillatory response:

- **Below 5 Ω**
- **Above 250 Ω**

Example (Cdet = 380 pF, L = 25 nH, Cin = 0.5 pF)

■ Ipulse||Cdet ■ SiPM model

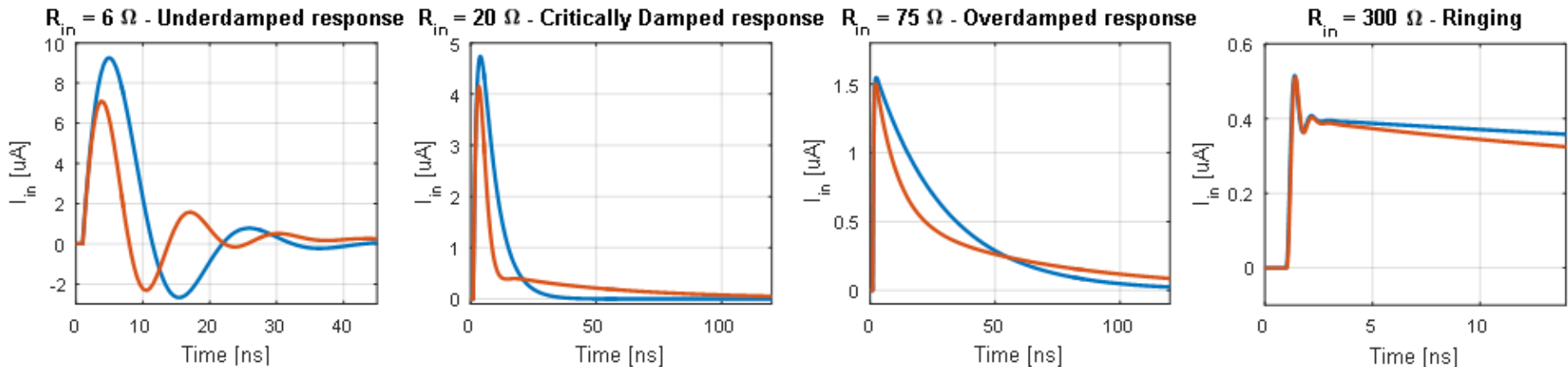


Condition for oscillation-free input current also valid for SiPM model!

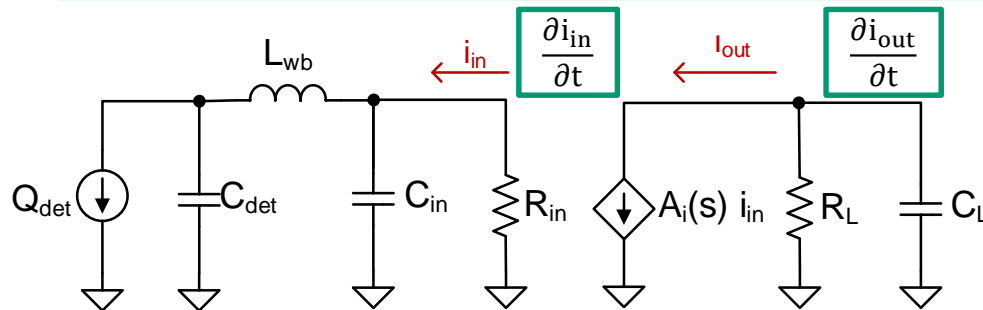II. Slew-rate degradation with bandwidth in current sensing

Convolution between the input slope and the electronics bandwidth (time domain):

$$SR = \frac{\partial i_{out}}{\partial t} \propto \left(\frac{\partial i_{in}}{\partial t} \right) * (BW \cdot e^{-t \cdot BW})$$





Optimum bandwidth for connecting inductances
5 nH – 25 nH and C_{det} = 10 pF – 1 nF

L_{wb} / C_{det}



5 nH / 10 pF	5 nH / 1 nF	25 nH / 10 pF	25 nH / 1 nF
1.3 GHz	270 MHz	560 MHz	81 MHz

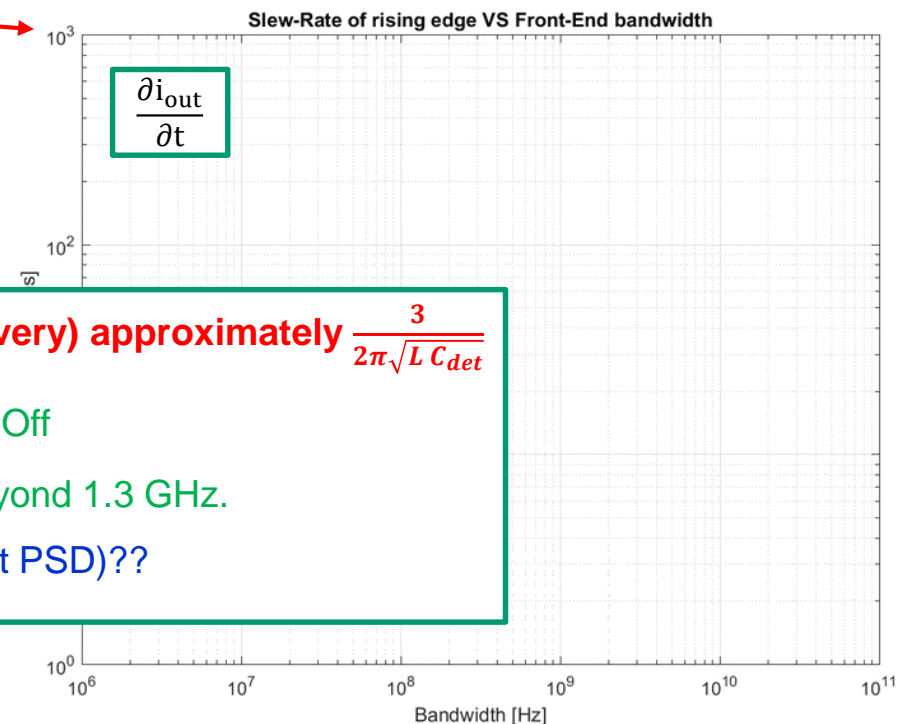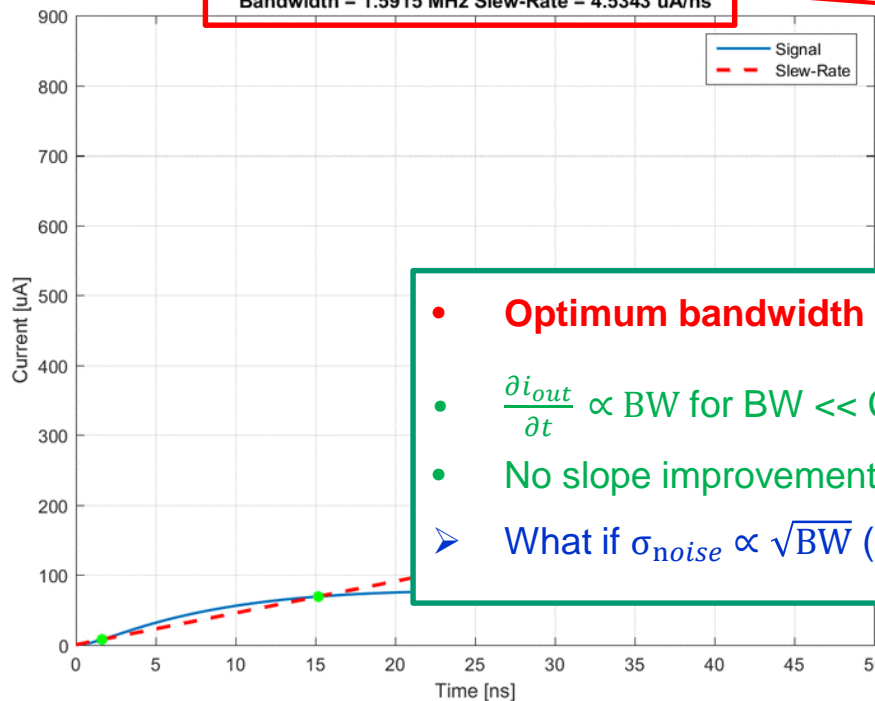Bandwidth = 1.5915 MHz Slew-Rate = 4.5343 uA/ns





- Optimum bandwidth is (very) approximately $\frac{3}{2\pi\sqrt{L} C_{det}}$
- $\frac{\partial i_{out}}{\partial t} \propto BW$ for $BW \ll \text{Cut-Off}$
- No slope improvement beyond 1.3 GHz.
- What if $\sigma_{noise} \propto \sqrt{BW}$ (~flat PSD)??

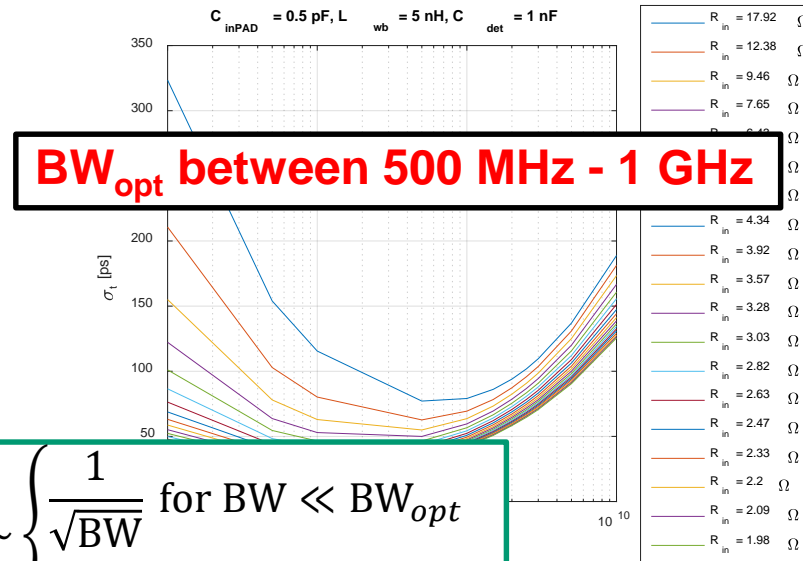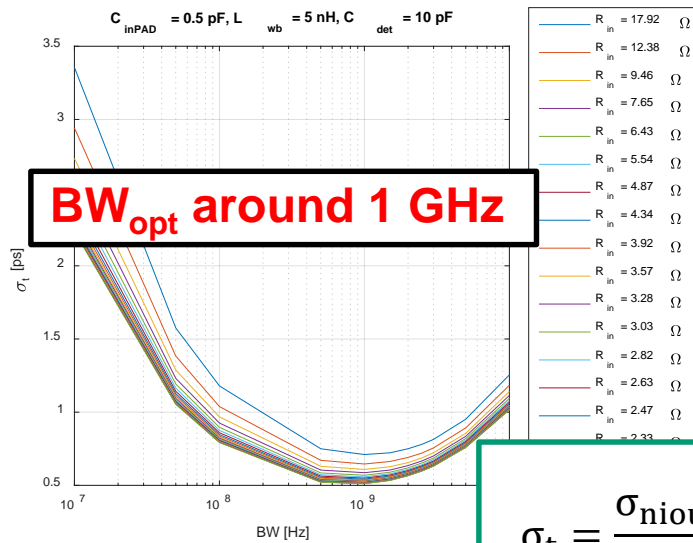II. Example of Slew-rate versus bandwidth in current sensing (assuming leading edge discrimination)



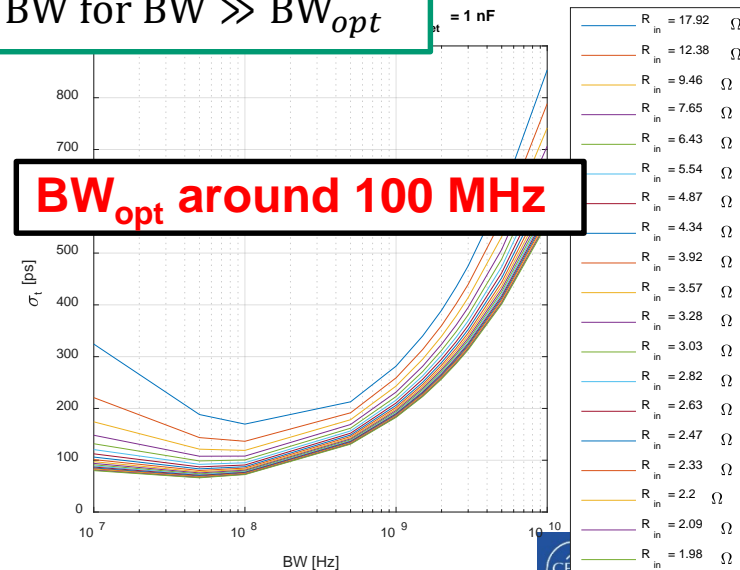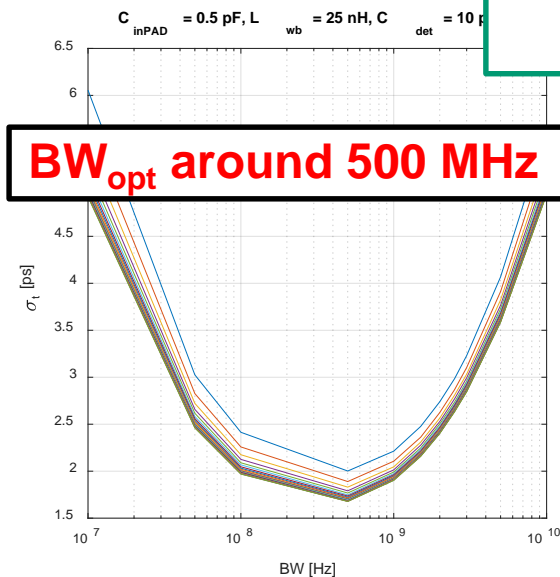
$$\sigma_t = \frac{\sigma_{niout}}{\frac{\partial i_{out}}{\partial t}} \sim \begin{cases} \frac{1}{\sqrt{BW}} & \text{for } BW \ll BW_{opt} \\ \sqrt{BW} & \text{for } BW \gg BW_{opt} \end{cases}$$



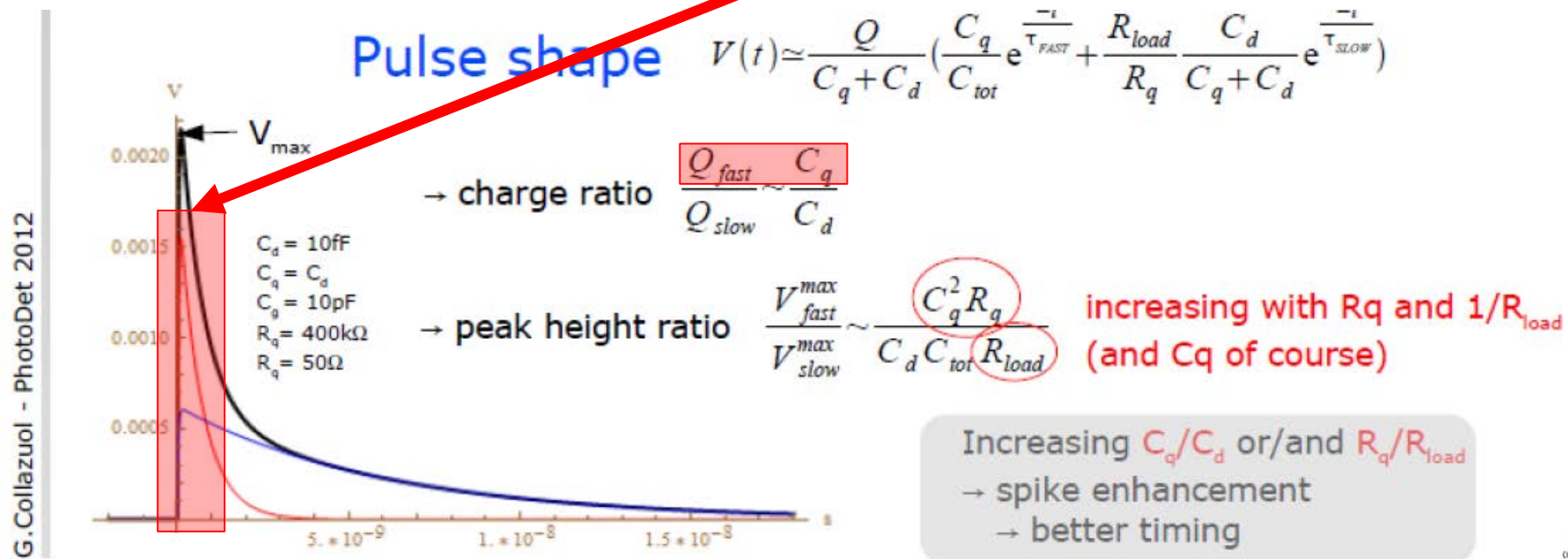II. SiPM electrical model

- Front end electronics for SiPM is needed to:
 - Preamplify for SNR optimization
 - Even if “nominal” gain is in the order of 10^6 only a fraction of the charge is used for fast read-out systems
 - The “effective” gain for a fast system can be between 2 and 10 times lower than the nominal gain




Outlook

- I. Introduction
- II. SiPM electrical parameters
- III. FE circuits**
- IV. ASIC examples
- V. Conclusions

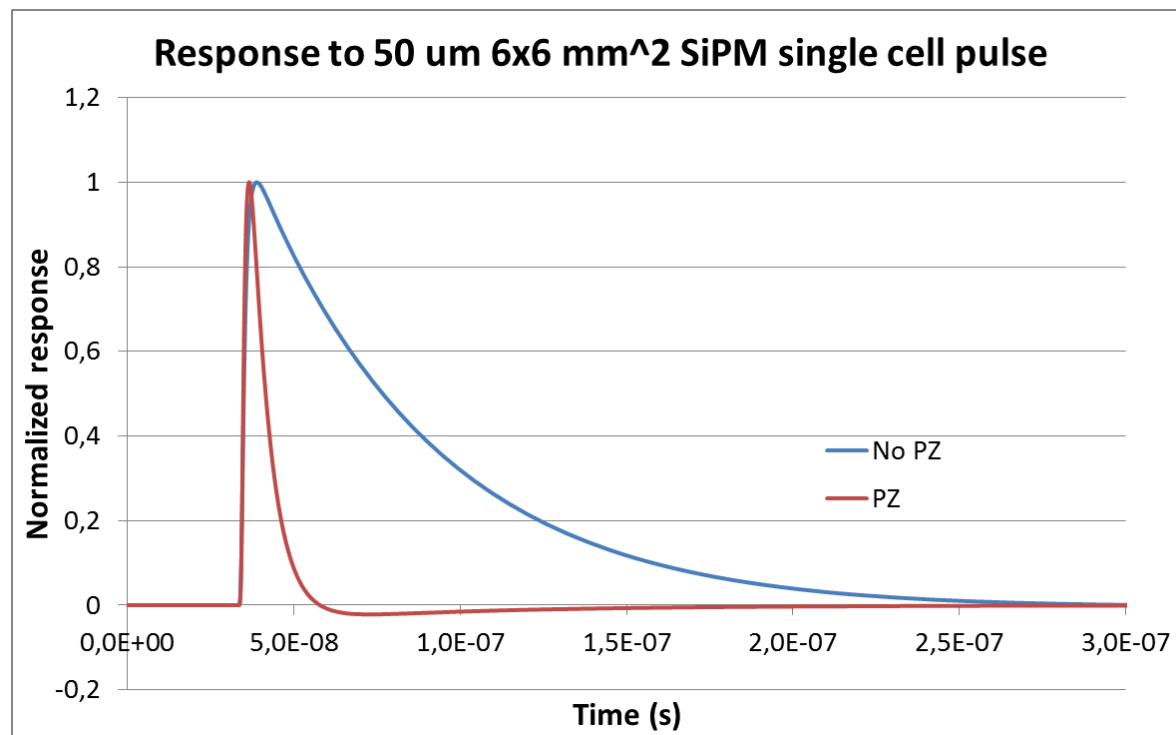III. FE circuits: Pole-Zero cancellation


- Pole-Zero (PZ) cancellation of the SiPM recovery long time constant (τ_{slow})
- The PZ shaping has an effect in the signal to noise ratio (SNR)
 - A $\text{SNR} > 5$ is required for photopeak identification
 - Can be seen in 2 different ways:
 - 1) Attenuation of slow frequency components of the signal
 - 2) Increase of the input referred noise ($\text{ENC} = \text{Equivalent Noise Charge}$)



Simulation with a
model obtained from
3x3 mm device

II FE circuits: effect of capacitance and shaping in noise

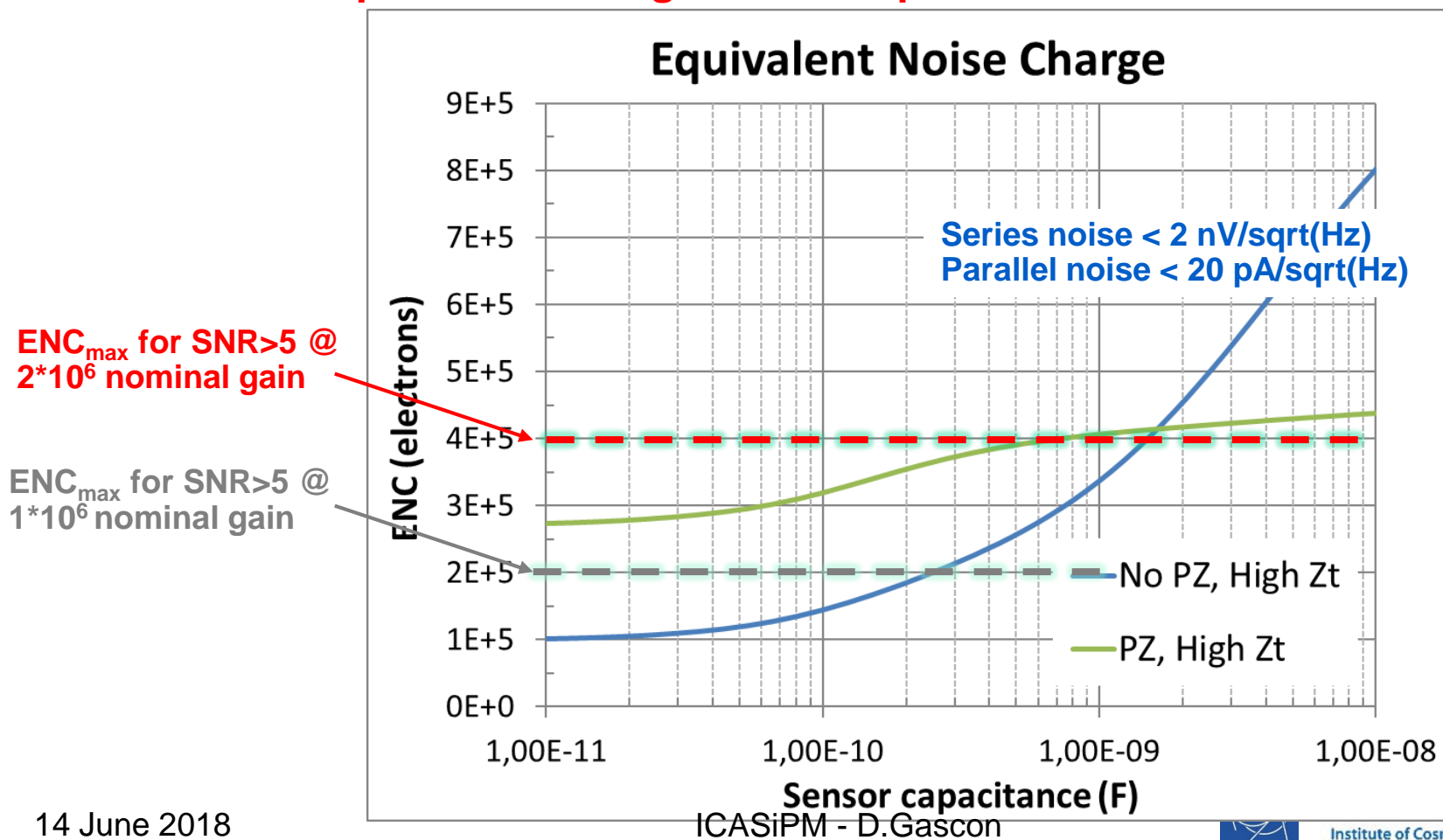
- Front end electronics for SiPM is needed to:
 - Low noise front end is required for large SiPMs
- SiPM capacitances range from 10s pF to more than several nF**



III. FE circuits: current versus voltage mode

- Typical photo-sensor front end circuit configurations:

Charge preamplifier

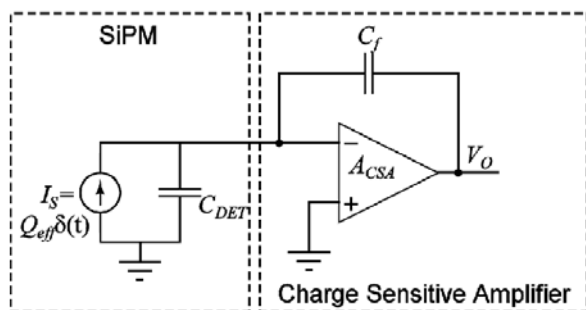

Voltage preamplifier


Current preamplifier

- | | | |
|--|--|---|
| <ul style="list-style-type: none"> <input type="checkbox"/> Best noise performance <input type="checkbox"/> Best with short signals <ul style="list-style-type: none"> ➤ Long tails: pile-up! ➤ Need to discharge C_f <input type="checkbox"/> Best with small capacitance <ul style="list-style-type: none"> ➤ $BW = C_f / C_{det} * GBW$, with $C_f \ll C_{det}$ typically... | <ul style="list-style-type: none"> <input type="checkbox"/> E.g. common-emitter/source configuration <input type="checkbox"/> Large Z_{in} // Large Z_{out} <input type="checkbox"/> Current conversion with R_{in} <input type="checkbox"/> High power budget for high speed systems <input type="checkbox"/> But can exploit RF technologies | <ul style="list-style-type: none"> <input type="checkbox"/> E.g. (super) common-base/gate <input type="checkbox"/> Low Z_{in} // Large Z_{out} <input type="checkbox"/> Current conversion with R_{in} <input type="checkbox"/> Potential stability issues <input type="checkbox"/> Best for high rate applications <input type="checkbox"/> Good power/BW trade-off⁰ |
|--|--|---|


F. Ciciriello et al., "Time performance of voltage-mode vs current-mode readouts for SiPM's," */WASI/*, 2015

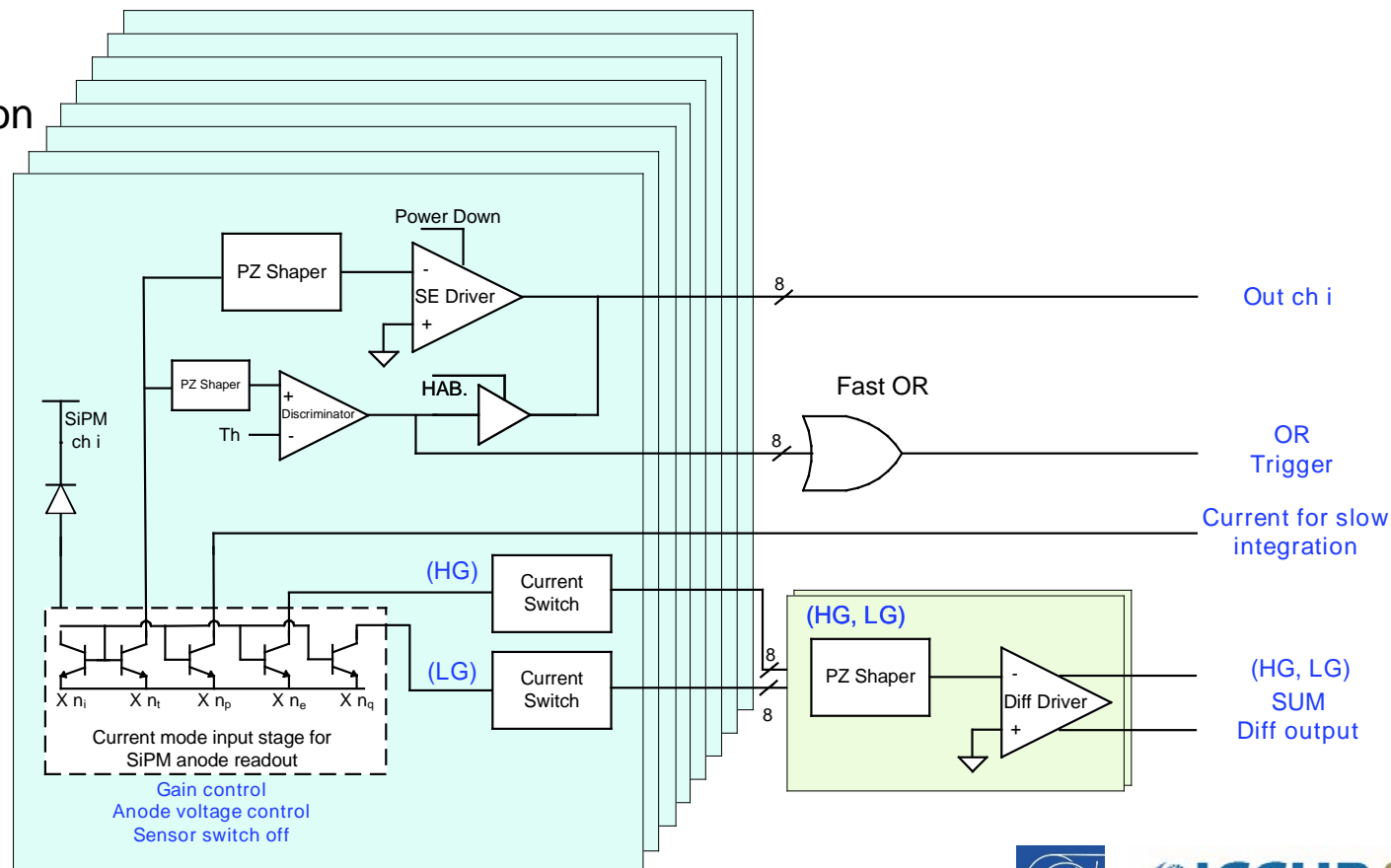III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- MUSIC: current mode, analog (binary) and designed for astroparticle (CTA) but multipurpose
 - Amplification / impedance adaptation
 - Pole zero cancellation
 - Summation
 - Discrimination



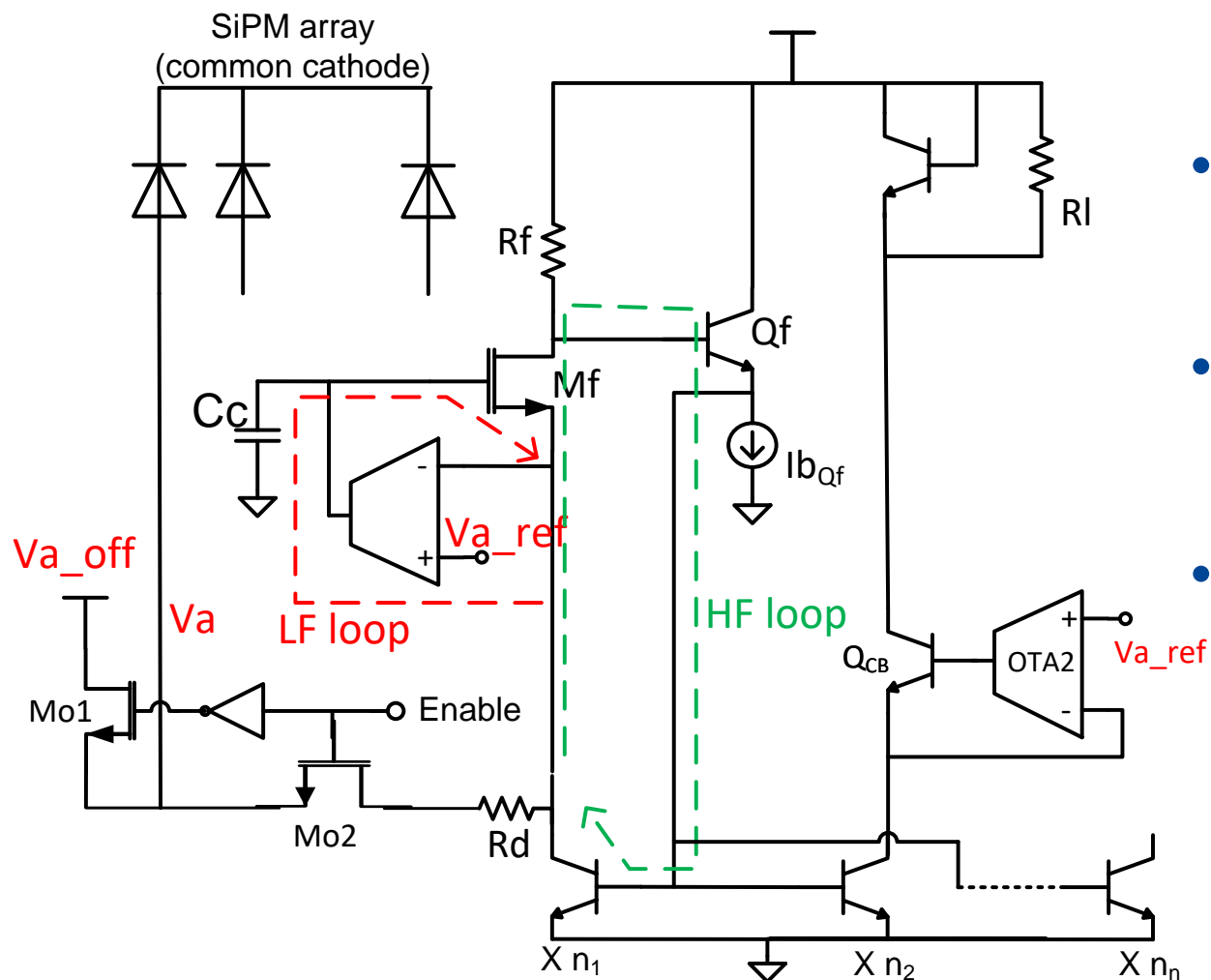III. FE circuits: MUSIC: Multipurpose SiPM RO chip




- Possible to disable each input reducing overvoltage to Va_{off} .
- Double feedback loop
 - Low input impedance
 - Anode voltage control
- High bandwidth

Series noise $< 2 \text{ nV}/\sqrt{\text{Hz}}$
 Parallel noise $< 20 \text{ pA}/\sqrt{\text{Hz}}$

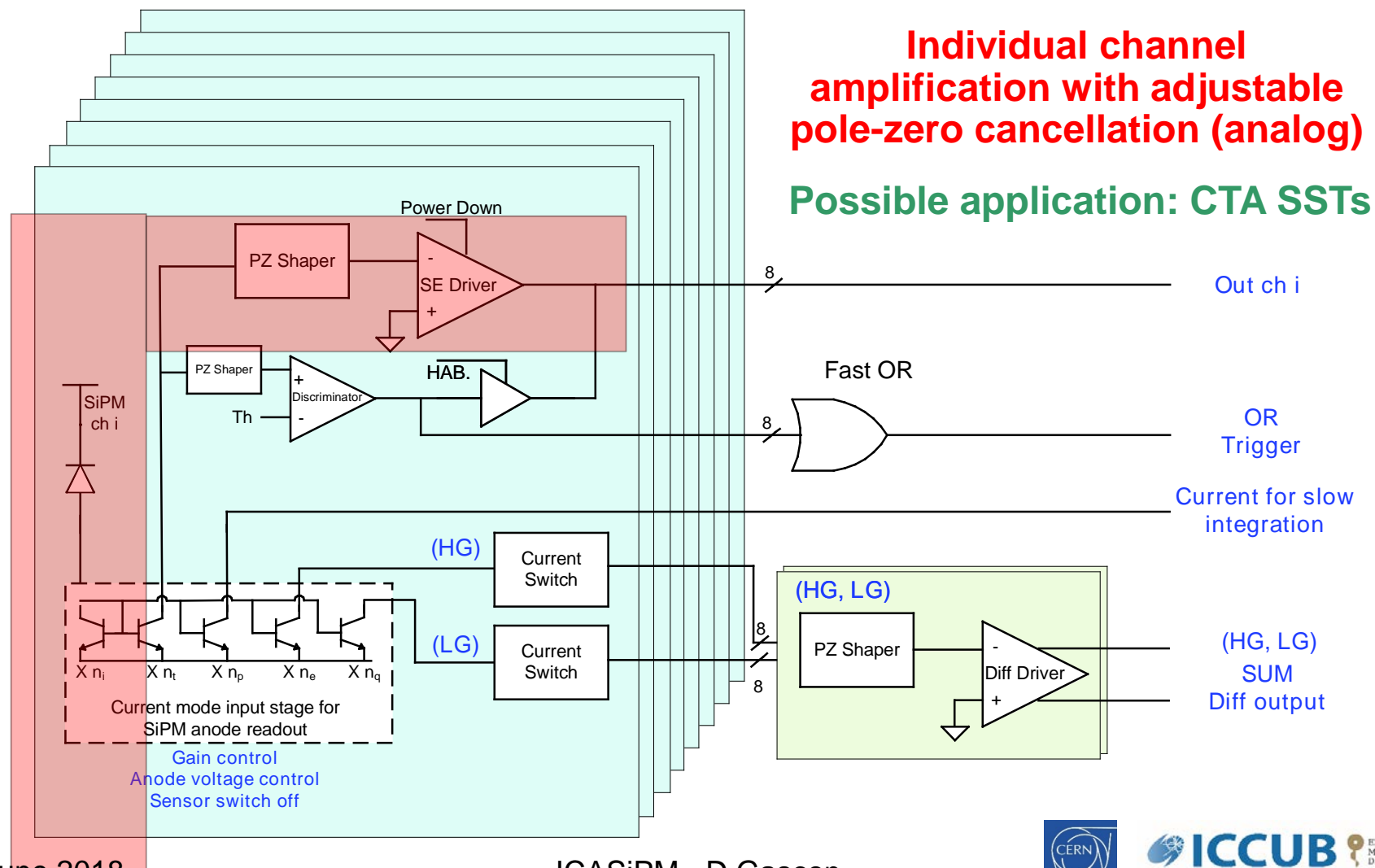
III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- MUSIC 8 ch ASIC integrates all those functionalities




III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- Output for a LCT4 MPPC (3x3 mm²)

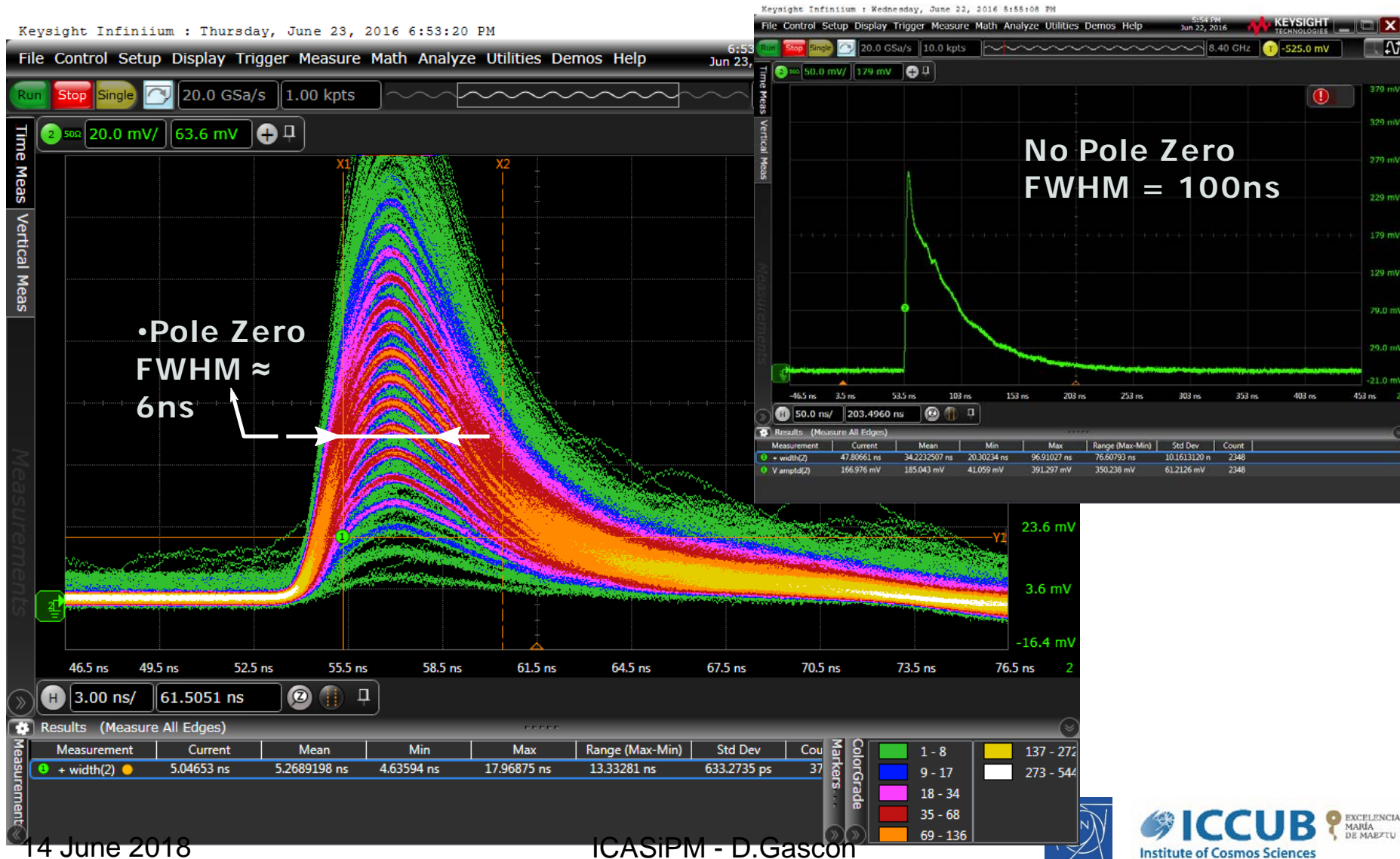

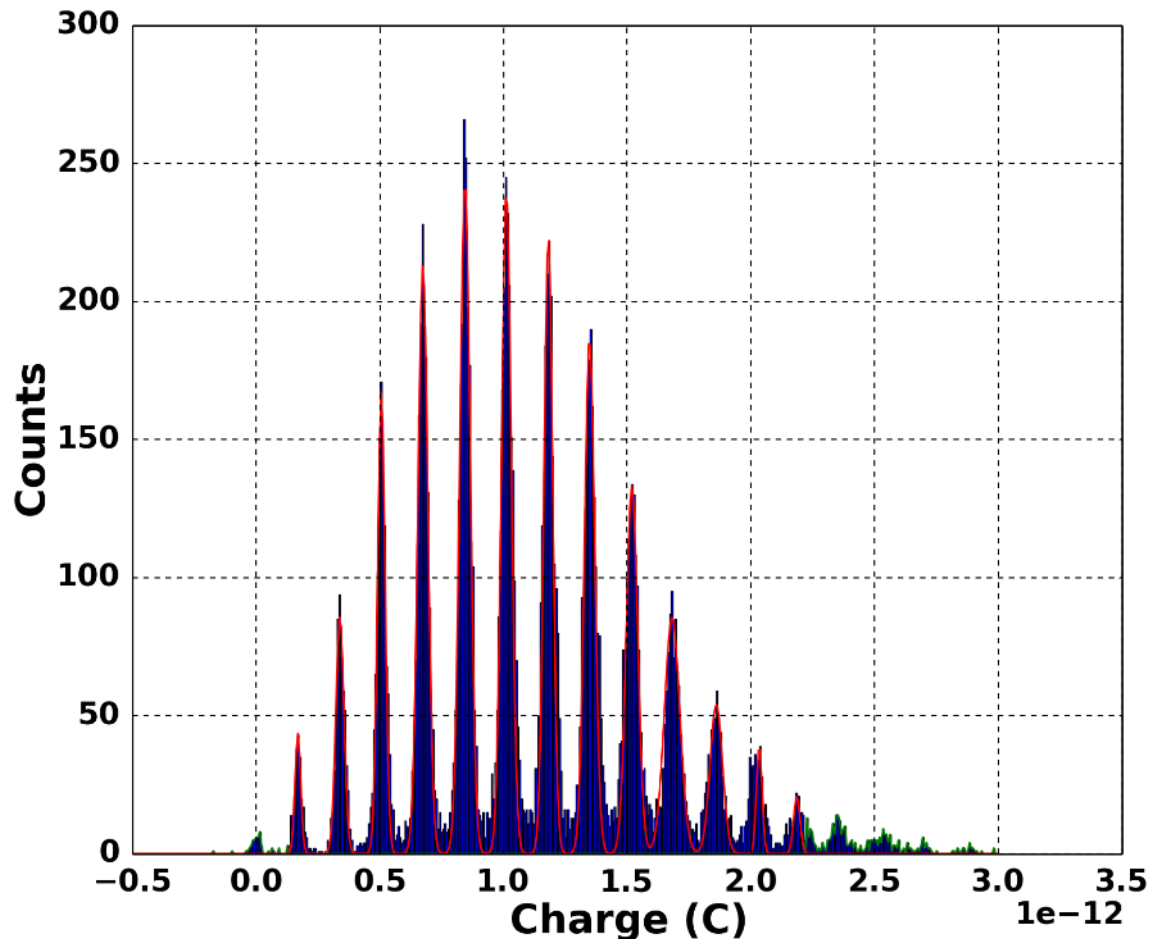III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- Charge spectrum for a LCT4 MPPC (3x3 mm²)
- Pole-zero cancellation
- Excellent resolution with FWHM of 5 ns




III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- Active summation to build large area detectors
- Why active summation?
 - Total noise for active and passive summation can be similar
 - If series noise dominates...
 - But signal (peak) is much higher !
 - Provided high summation BW

Series noise $< 2 \text{ nV}/\sqrt{\text{Hz}}$
 Parallel noise $< 20 \text{ pA}/\sqrt{\text{Hz}}$

7 x SiPM
6x6 mm² each


1 x PMT
18 mm diameter

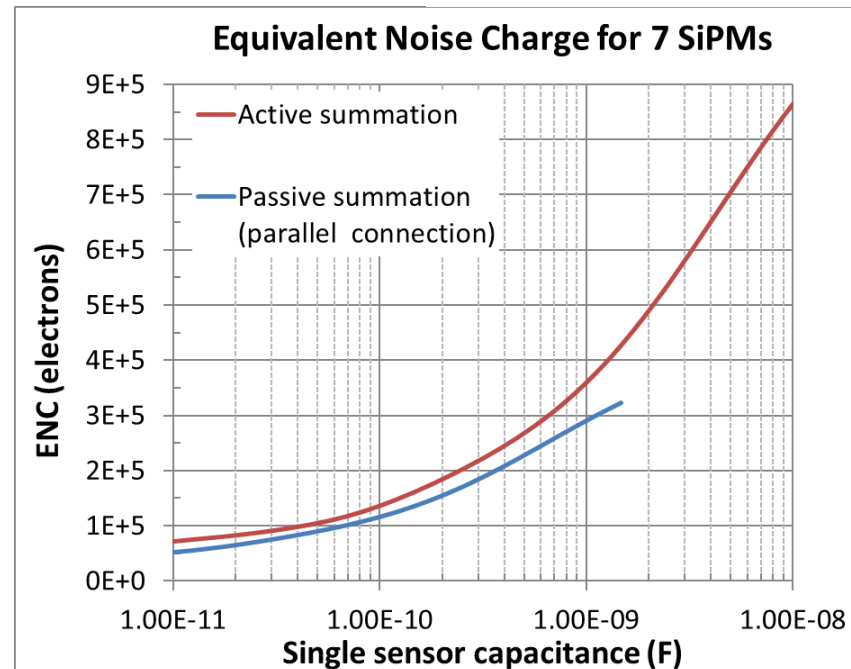

* 7x7mm² and some custom larger SiPMs exist


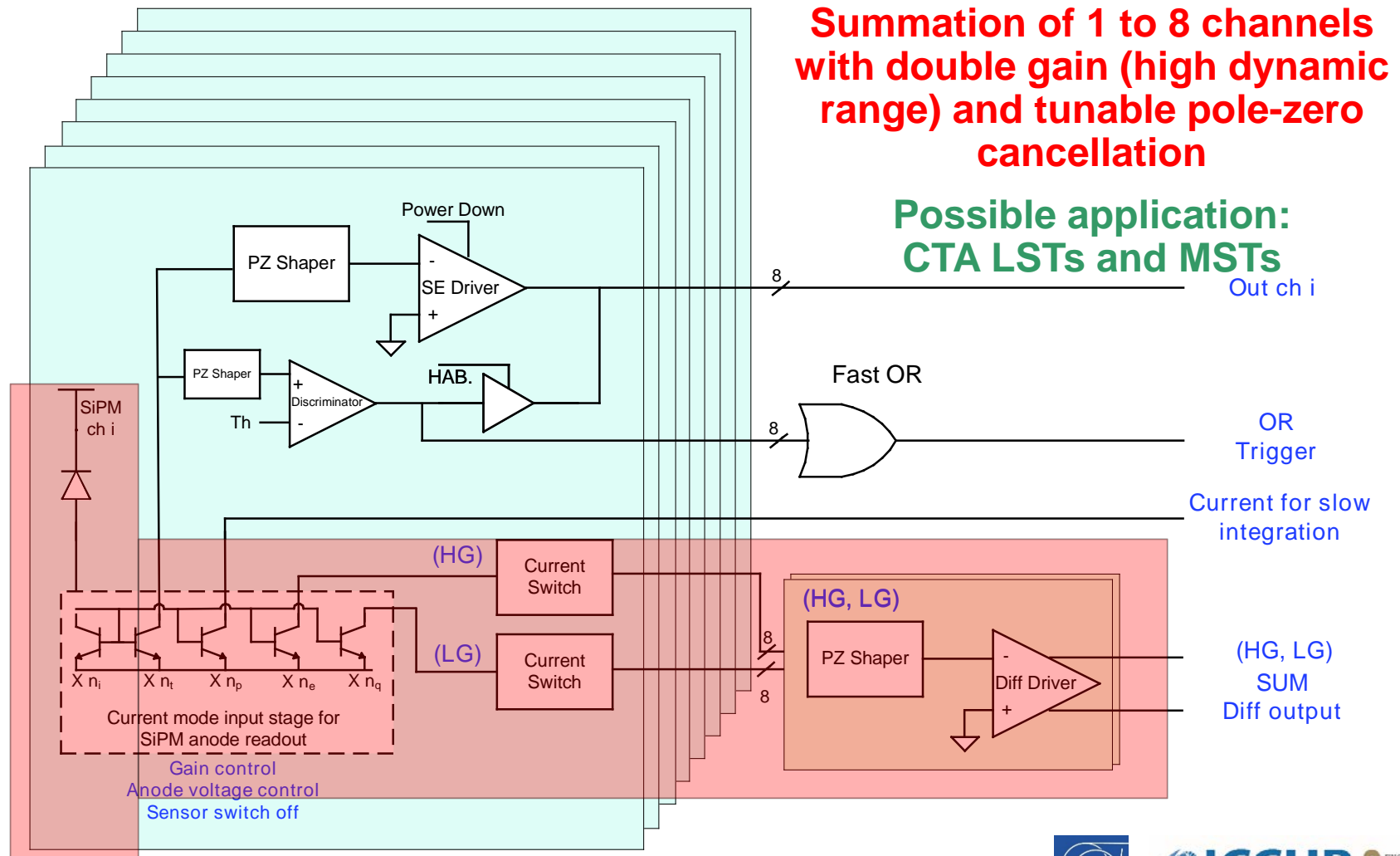
III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- MUSIC 8 ch ASIC integrates all those functionalities



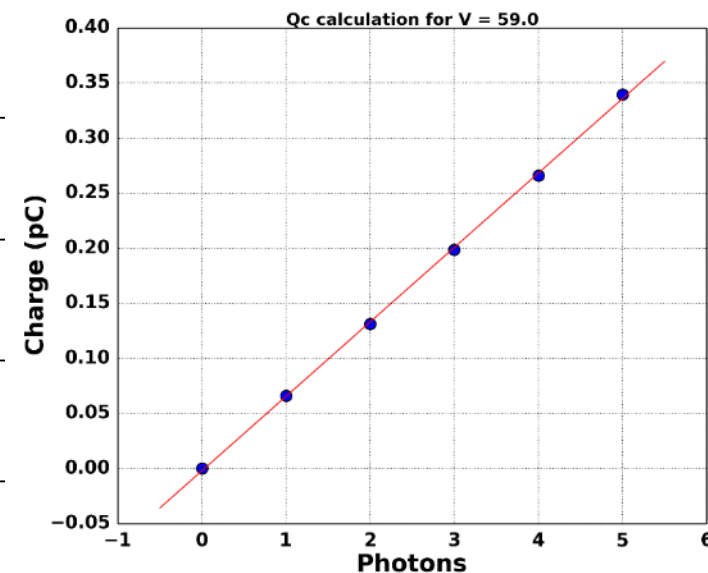
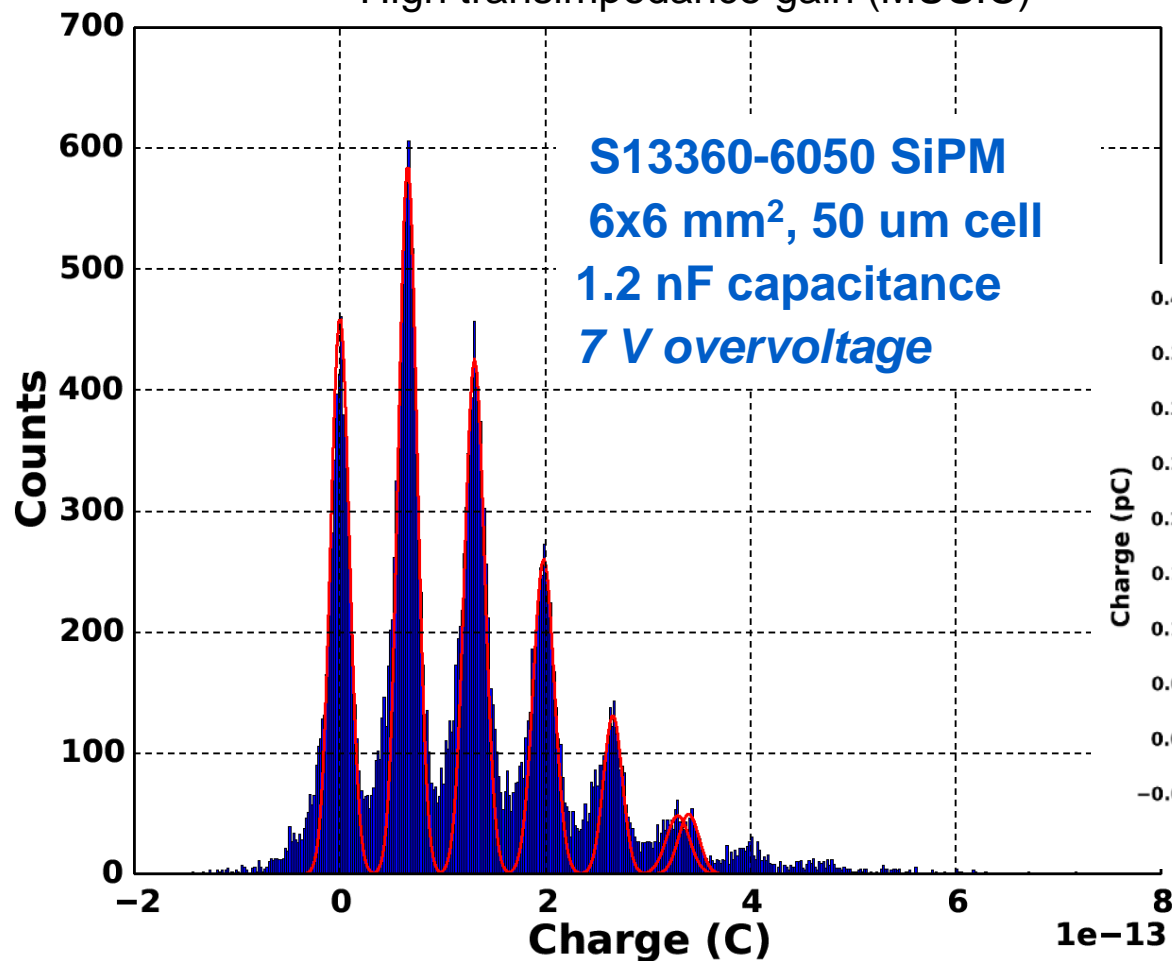
III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- MUSIC configuration: the adder takes only 1 channel
 - Pole-zero cancellation: trade-off between resolution and speed
 - High transimpedance gain (MUSIC)




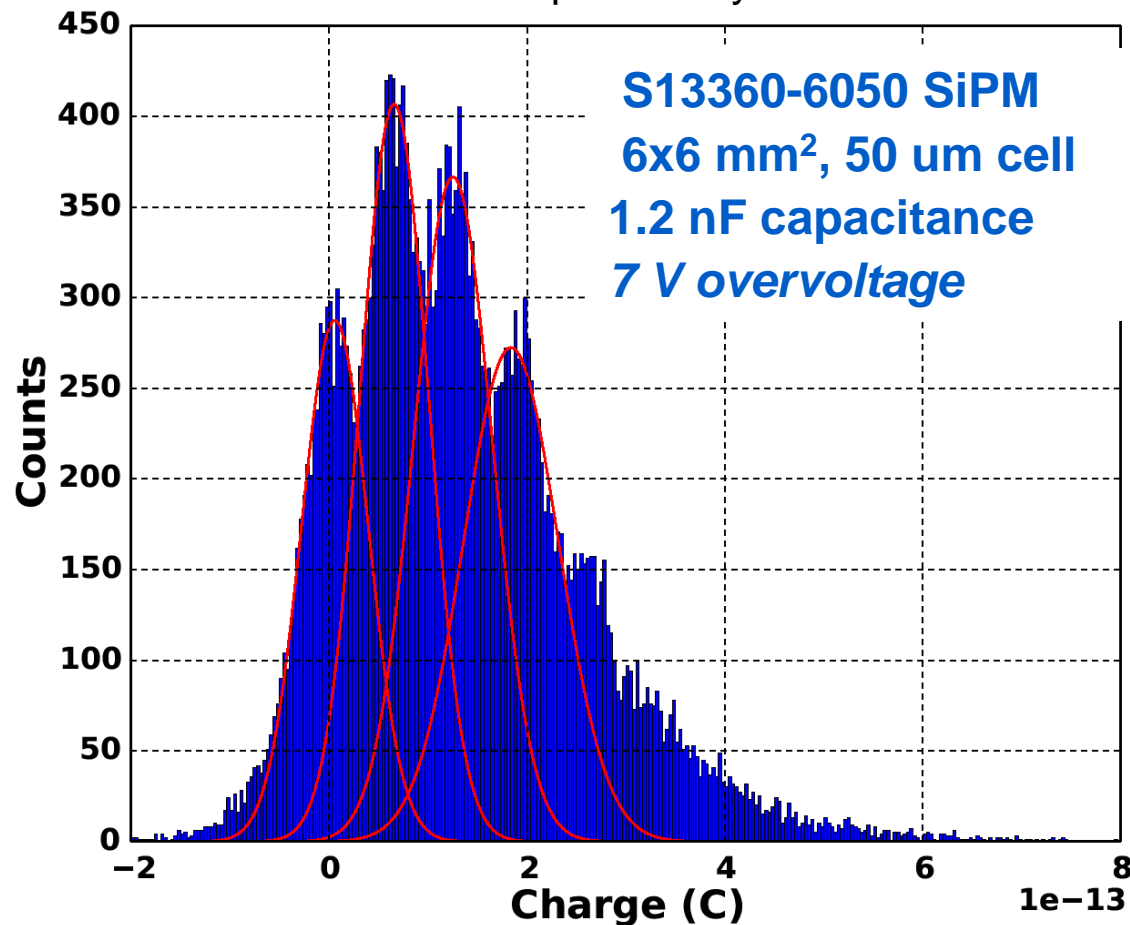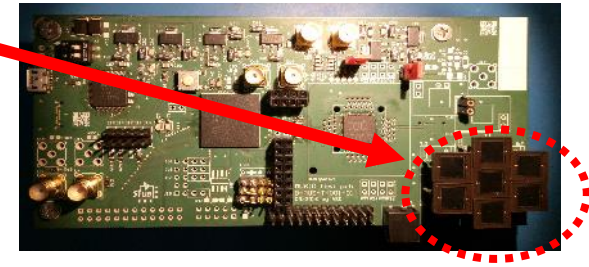III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- MUSIC configuration: the adder takes 7 channels
 - Noise is much higher ($\sqrt{7}$)
 - But pe (cell) peaks can still be identified
 - Channels have been equalized by MUSIC anode ctrl voltage



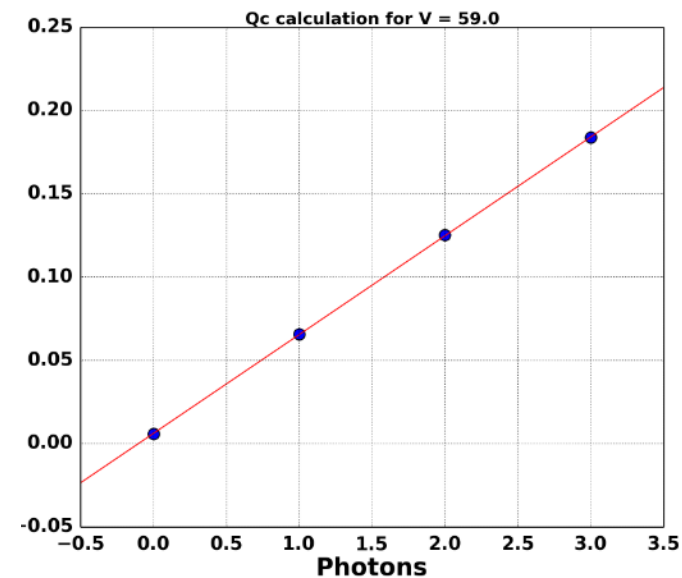1 x PMT \approx 7 x SiPM
 18 mm diameter \approx 6x6 mm² each




III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- SHIP experiment is a new general-purpose beam dump facility at the SPS (CERN) to search for hidden particles
 - Predicted by a very large number of recently elaborated models of Hidden
 - Dark matter, neutrino oscillations, and the origin of the full baryon asymmetry




- Reconstruction of the HNL decays in the final states: $\mu^- \pi^+$, $\mu^- \rho^+$ & $e^- \pi^+$

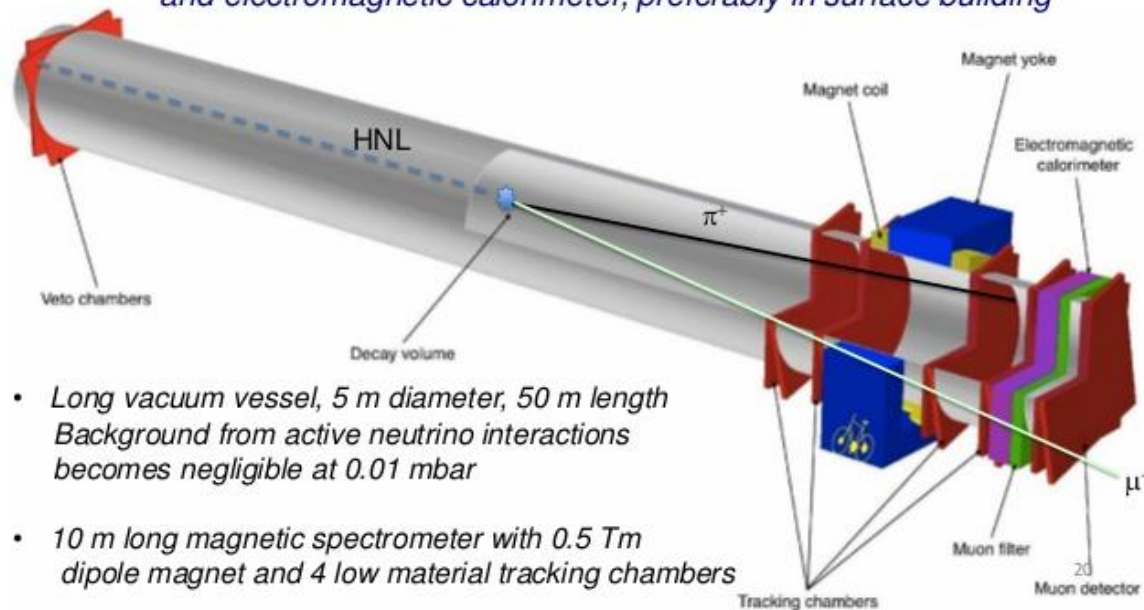Requires long decay volume, magnetic spectrometer, muon detector and electromagnetic calorimeter, preferably in surface building




- Long vacuum vessel, 5 m diameter, 50 m length
Background from active neutrino interactions becomes negligible at 0.01 mbar
- 10 m long magnetic spectrometer with 0.5 Tm dipole magnet and 4 low material tracking chambers

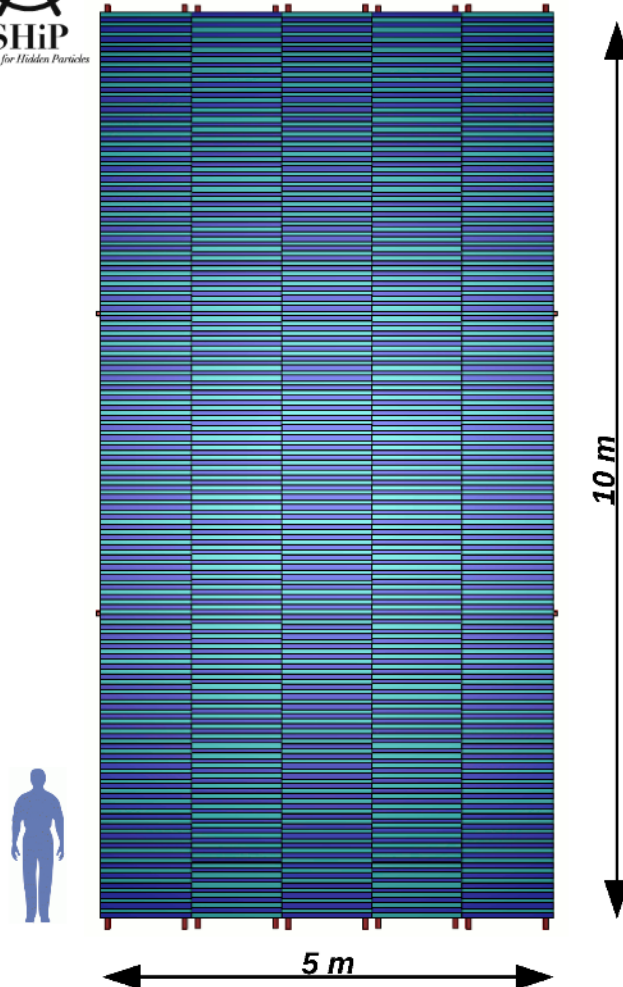
III. FE circuits: MUSIC: Multipurpose SiPM RO chip



Timing Detector in SHiP

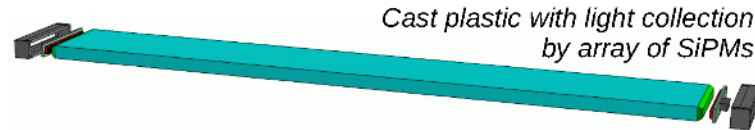

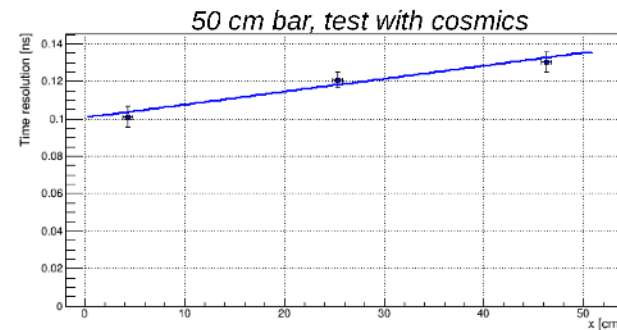- For the TD of size 5 m x 10 m with a bar **100 cm x 6 cm x 1 cm**
 - 5 col x 182 row = 910 bars =>
 - 910 bars x 2 = 1820 ch =>
 - 1820 x 8 = 14560 SiPMs
- The resolution at 50 cm is ~140 ps => we can use with 1 m bar and 2-side readout to be within 100 ps.






5

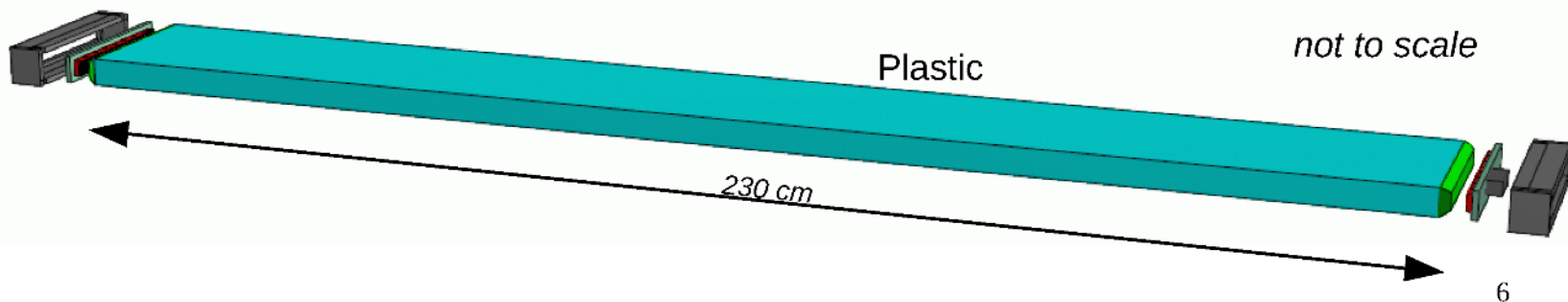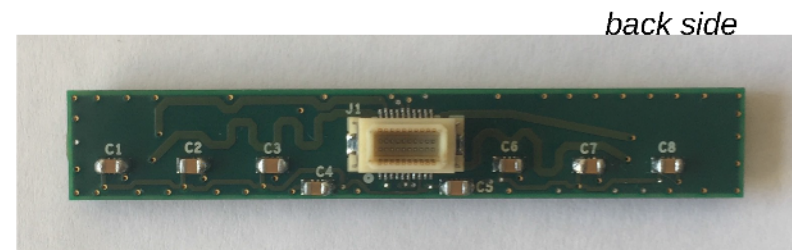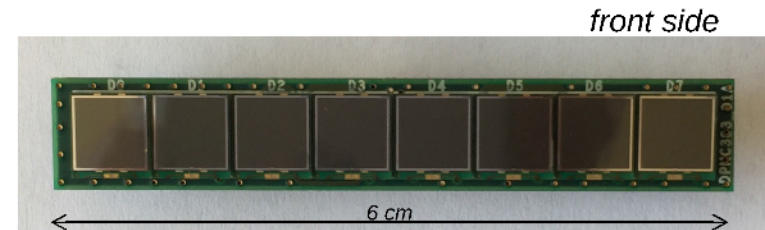III. FE circuits: MUSIC: Multipurpose SiPM RO chip

Bar and sensors for ToF/ND280



- Bar: 230 cm x 6 cm x 1 cm
- Plastic material:
 - EJ200 (BC408) or EJ208(BC412)
 - Attenuation length ~ 4 m
 - 1.42 kg/bar
- Readout from both ends
 - 8 sensors of 6 mm x 6 mm
 - Example: S13360-6050PE



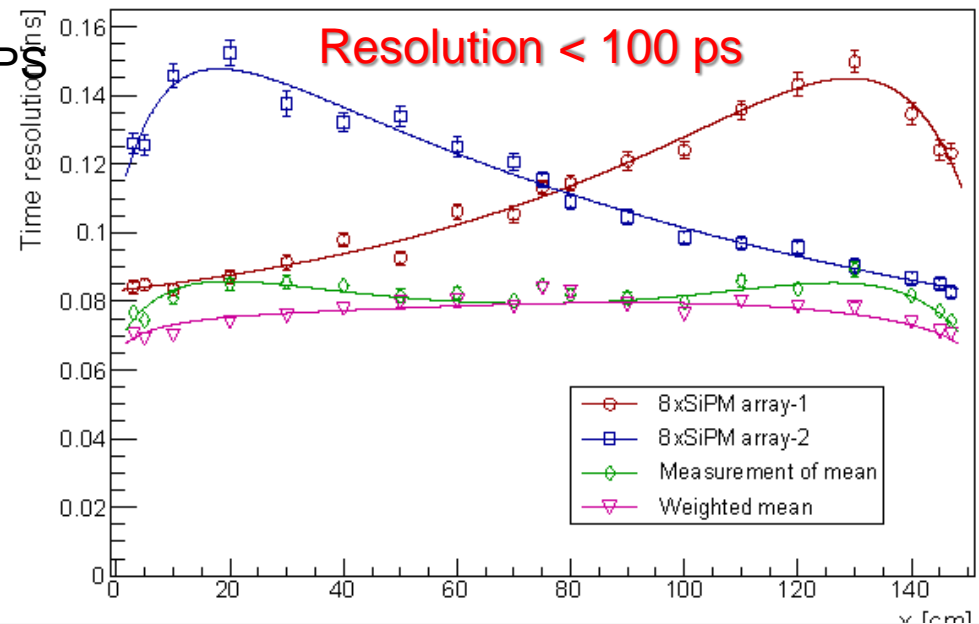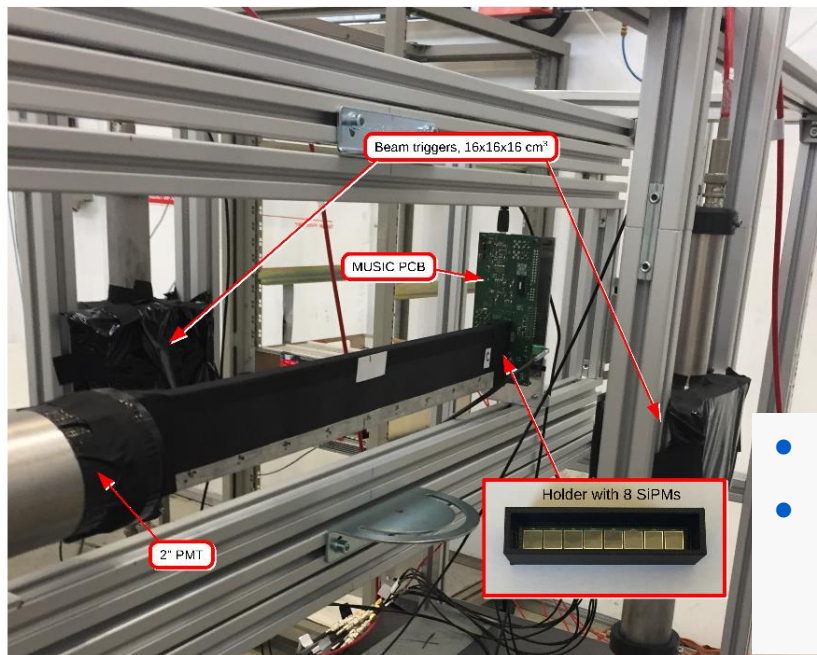III. FE circuits: MUSIC: Multipurpose SiPM RO chip

• Timing sub-detector test beam with MUSIC chip

- By Univ. Geneva & Univ. Zurich
- MUSIC in summation mode (8 $6 \times 6 \text{ mm}^2$ SiPMs)
 - Bar read-out at both ends
- 2.5 GeV/c muon beam at the CERN PS
- Readout with Wavecatcher
 - Fast analog memory (LAL & IRFU/CEA)



- Measurements with the 150 cm x 6 cm x 1 cm bar.
- Time resolution as measured by the SiPM arrays at both ends of the bar as a function of the interaction point along the bar.

© A. Kornezev (Univ. Geneva)

- I. Introduction
- II. SiPM electrical parameters
- III. FE circuits
- IV. ASIC examples**
- V. Conclusions

IV. ASICs for HEP: PACIFIC

SciFi - The New Scintillating Fibre Tracker for LHCb

Albert Comerma* on behalf of the SciFi tracker collaboration

*Physikalisches Institut, Universität Heidelberg



IEEE NSS-MIC, 26th October 2017

IV. ASICs for HEP: PACIFIC

Introduction
○○○

Mats construction
○○○


Readout electronics
○○○○○

Testbeam

Summary
○○

SciFi Overview

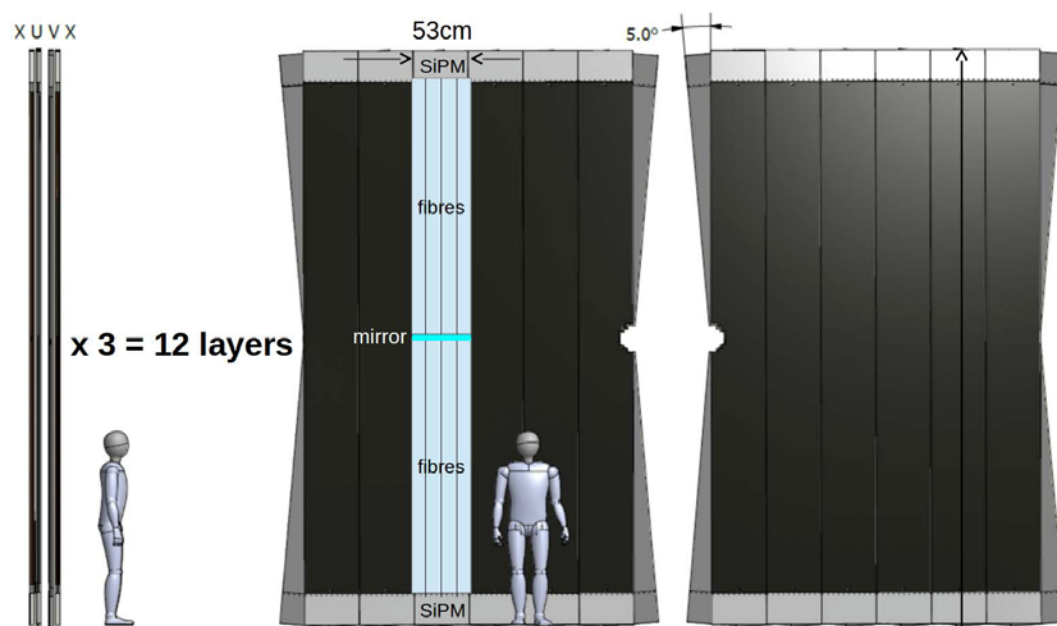- Scintillating Fibre Tracker:
 - Light detector, $< 1\% X_0/\text{layer}$
 - Large area, total of $6 \times 5\text{m}^2$
 - XUVX planes on each station
 - Full detector is 3 stations
 - Total radiation up to 35kGy
- Requirements:
 - Hit efficiency $\approx 99\%$
 - High granularity $250\mu\text{m}$
 - Hit resolution $< 100\mu\text{m}$



Albert Comerma (comerma@physi.uni-heidelberg.de)

SciFi - The New Scintillating Fibre Tracker for LHCb

2 / 14

IV. ASICs for HEP: PACIFIC

Introduction
○○●

Mats construction
○○○

Readout electronics
○○○○○

Testbeam


Summary
○○

SciFi Module

Total of **128 modules** of $0.5 \times 5m^2$.
Each module consists on eight fibre mats.
Each fibre mat is $240 \times 13cm^2$.
Mats constructed with 6 layers of fibres:



Fibres readout by SiPM array:

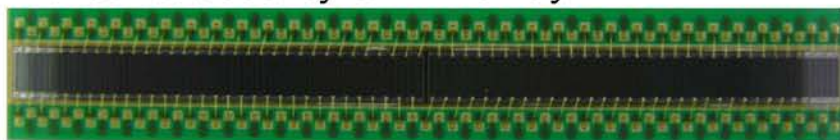


64 + 64 channels array (2 dies).
 $60 \times 60\mu m^2$ cells, 104 pixels / channel.



Albert Comerma (comerma@physi.uni-heidelberg.de)

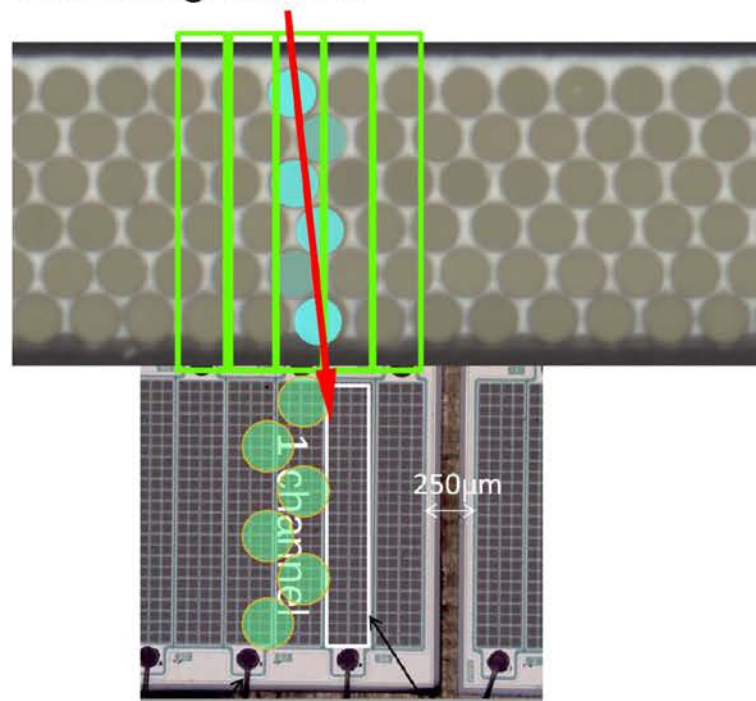Signal spread over channels, 16-20 phe.
Clustering needed:



SciFi - The New Scintillating Fibre Tracker for LHCb

3 / 14

IV. ASICs for HEP: PACIFIC

Introduction
○○○

Mats construction
○○○

Readout electronics
○○○●○


Testbeam
○○○

Summary
○○

PACIFIC

Collaboration: Heidelberg, ICCUB, LPC-Clermont, IFIC-Valencia

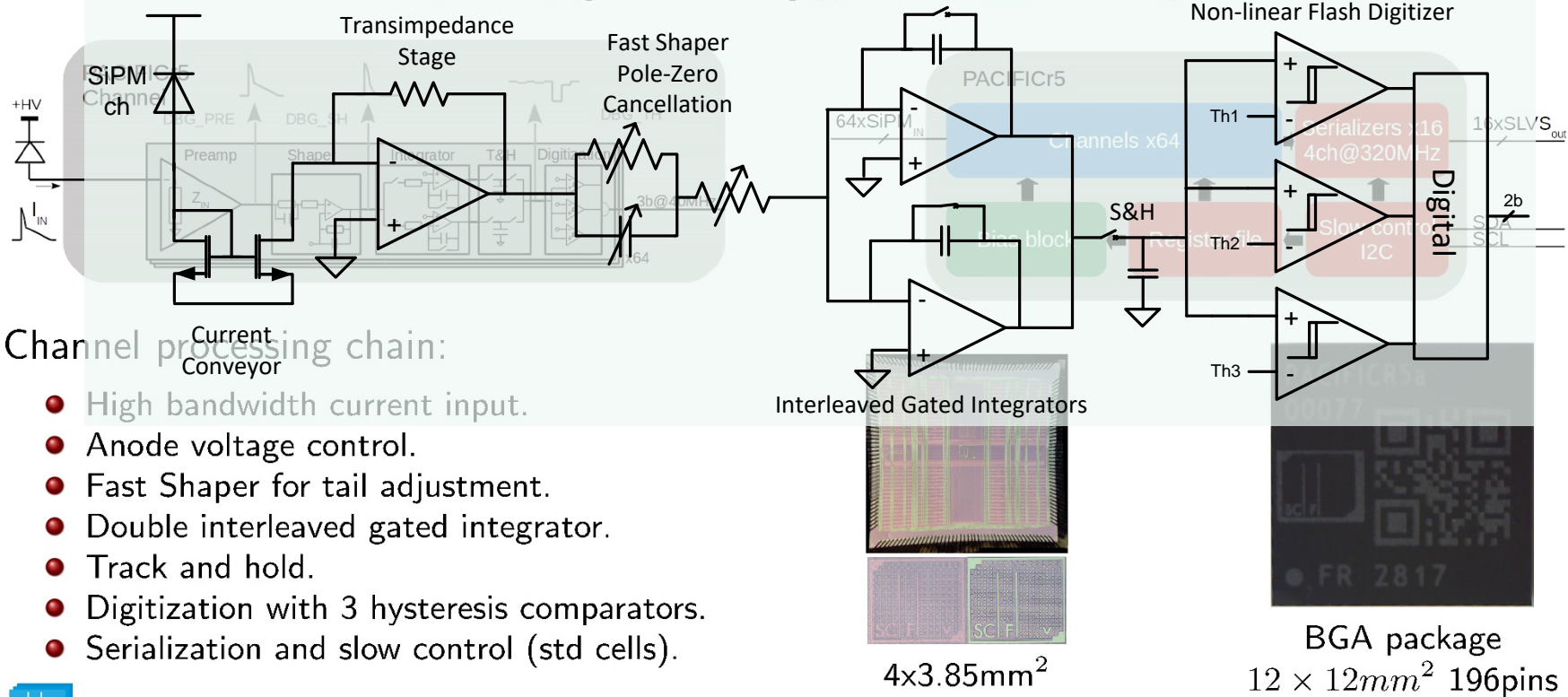Low Power ASIC for the SCIntillator Fibres tracker



Albert Comerma (comerma@physi.uni-heidelberg.de)

SciFi - The New Scintillating Fibre Tracker for LHCb

10 / 14

IV. ASICs for HEP: PACIFIC

Introduction
○○○

Mats construction
○○○


Readout electronics
○○○○●

Testbeam
○○○

Summary
○○


PACIFIC

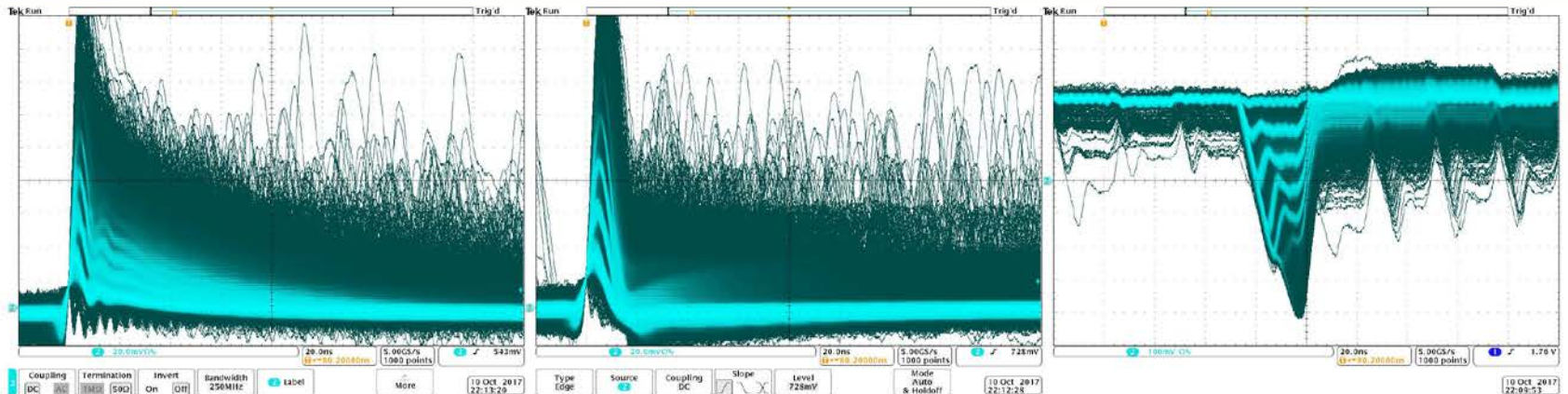Collaboration: Heidelberg, ICCUB, LPC-Clermont, IFIC-Valencia



SiPM connected to PACIFIC:

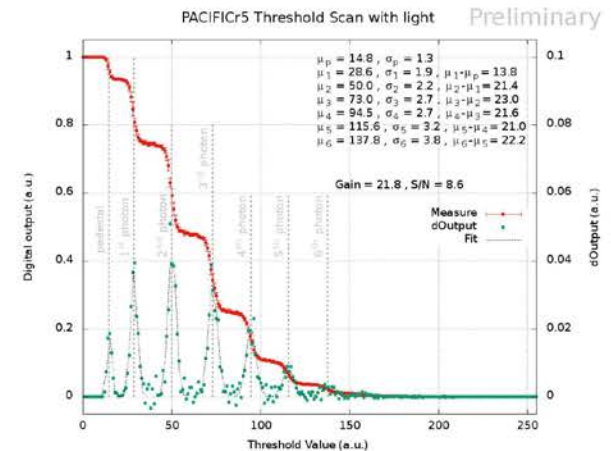- Analog DEBUG outputs for Preamplifier, Shaper and TH.
- Synchronous light triggered on front of array.
- Threshold scan of one comparator to measure photons.



Albert Comerma (comerma@physi.uni-heidelberg.de)

SciFi - The New Scintillating Fibre Tracker for LHCb

11 / 14




IV. ASICs for PET: FlexToT: linearized ToT RO chip

Collaboration: ICCUB and CIEMAT

• A Flexible ASIC for SiPM RO (PET, SPECT, Compton)


- Novel current mode input stage
- Time resolution for ToF
- Time over Threshold RO

▪ No ADC

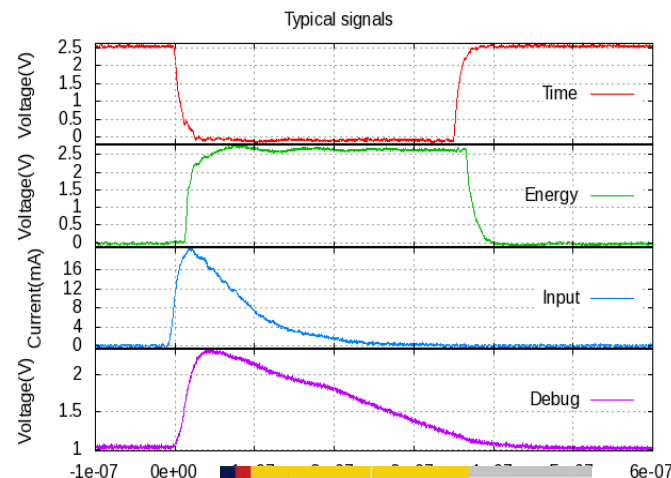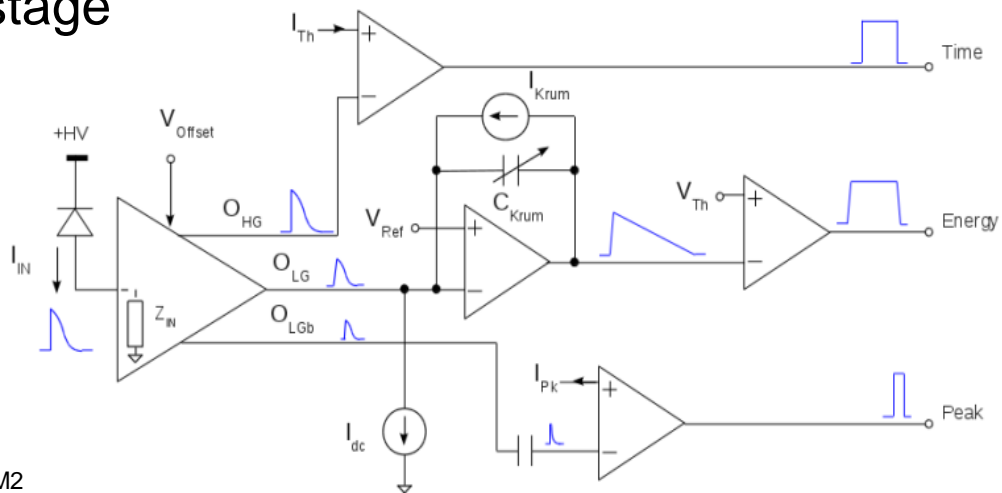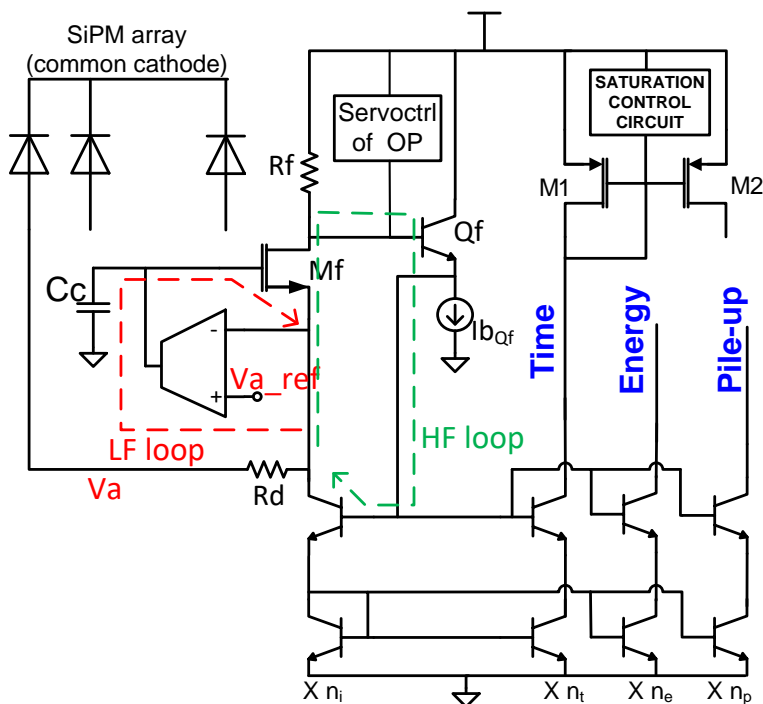

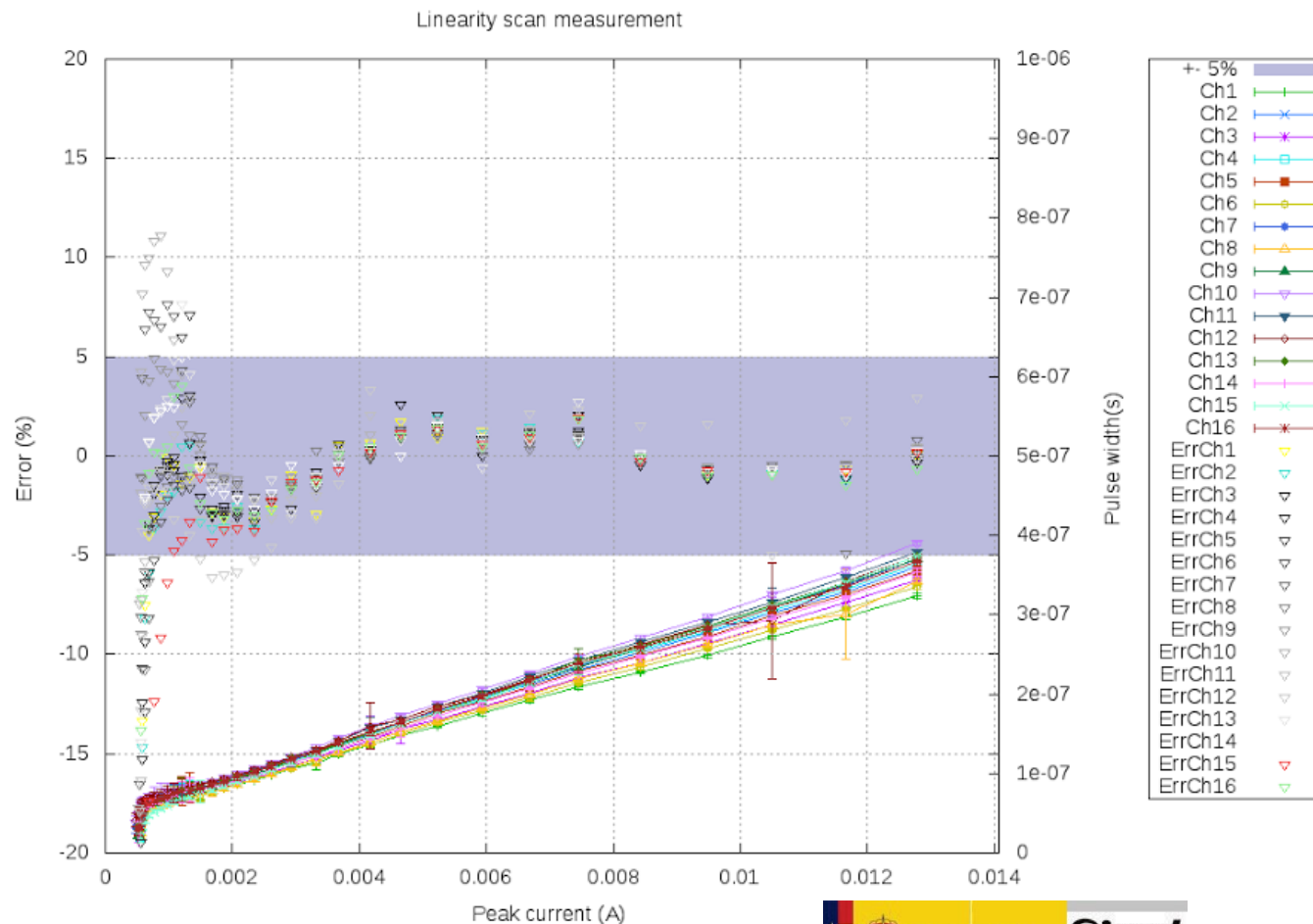IV. ASICs for PET: FlexToT: linearized ToT RO chip

- **Good linearity and uniformity**
 - With only comparator threshold offset equalization
- **Different operating ranges can be covered**





IV. ASICs for PET: FlexToT: linearized ToT RO chip

• Measured @ CERN:


- Single Photon Time resolution (SPTR)
- Coincidence Time Resolution (CTR)
- Supported by FAST COST ACTION
 - Many thanks to E. Auffray and S. Gundacker
- Similar results as for NINO but 3 times lower power consumption

Coincidence Time Resolution (CTR): 128 ps FWHM

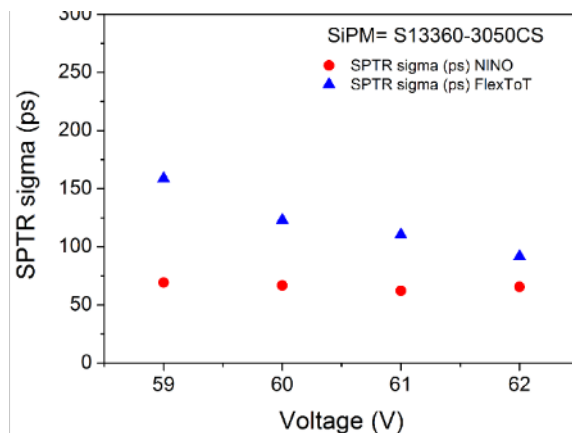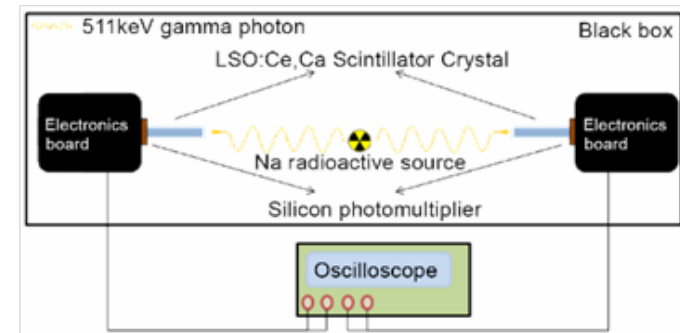- 2x2x5 mm³ LSO:Ce,Ca crystals.
- Measurements performed in a black-box at 15 °C.
- Coincidences corresponding to 511 KeV photopeak ($\pm 3\sigma$).




SPTR=90ps

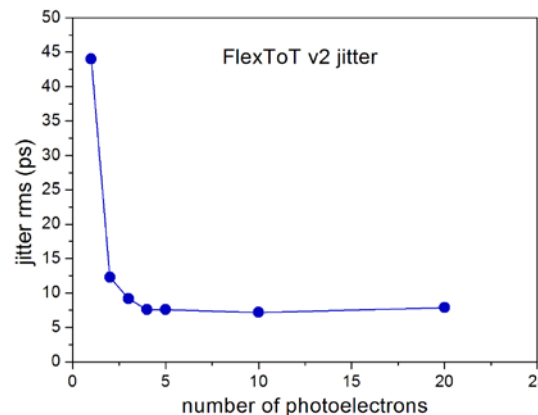

Jitter floor: 7 ps rms

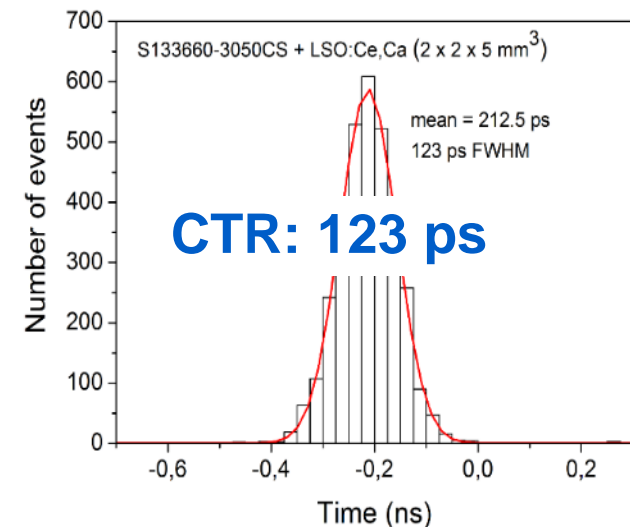Coincidence Time Resolution (CTR) test bench setup



IV. ASICs for PET: FlexToT: linearized ToT RO chip



• Pisa University has developped a FPGA based TDC readout for FlexToT

- Based on Arria 10 FPGA
 - TDC: 38 ps resolution
- System CTR: 116 ps FWHM !
- Energy resolution: 8 % FWHM @ 511 KeV
- Dead time < 5ns: event rate > 1 MHz !




P. Catra,
G. Sportelli

2 LYSO xtals 3x3x5 mm³
NUV-SiPM

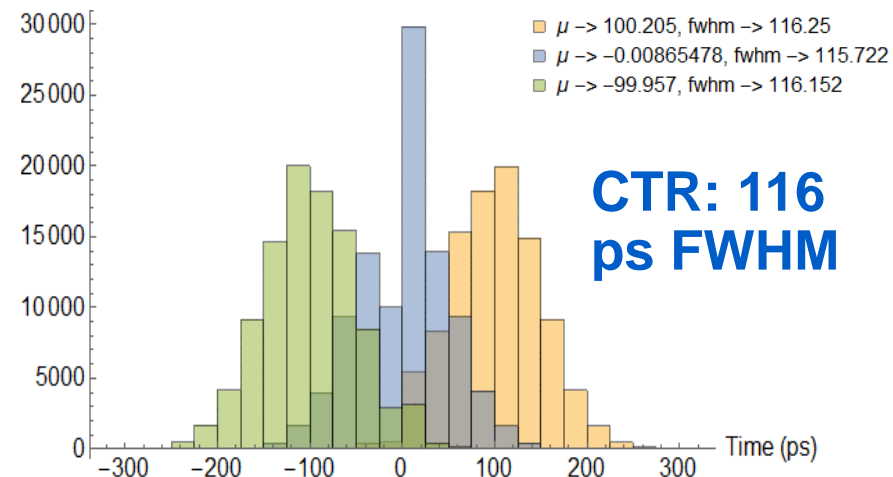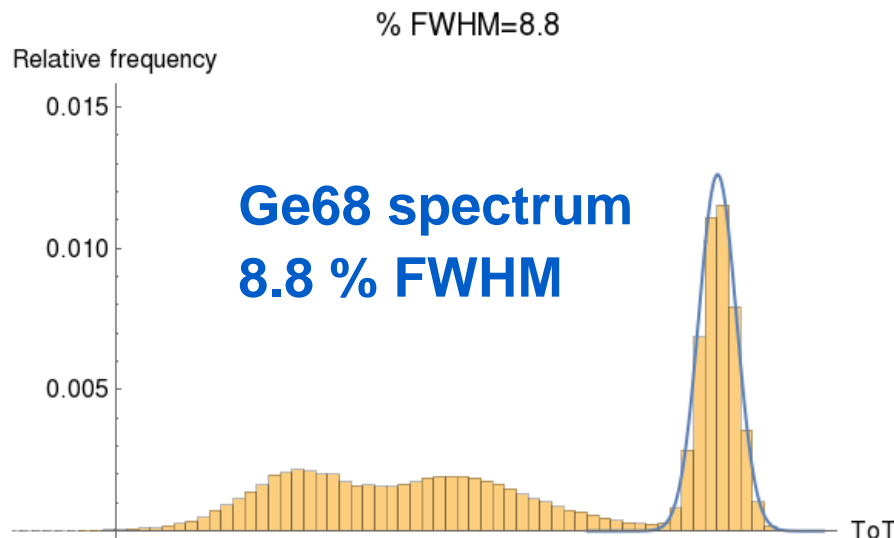


Timing distributions for different source positions

- # HRFlexToT
- ## 180 nm CMOS

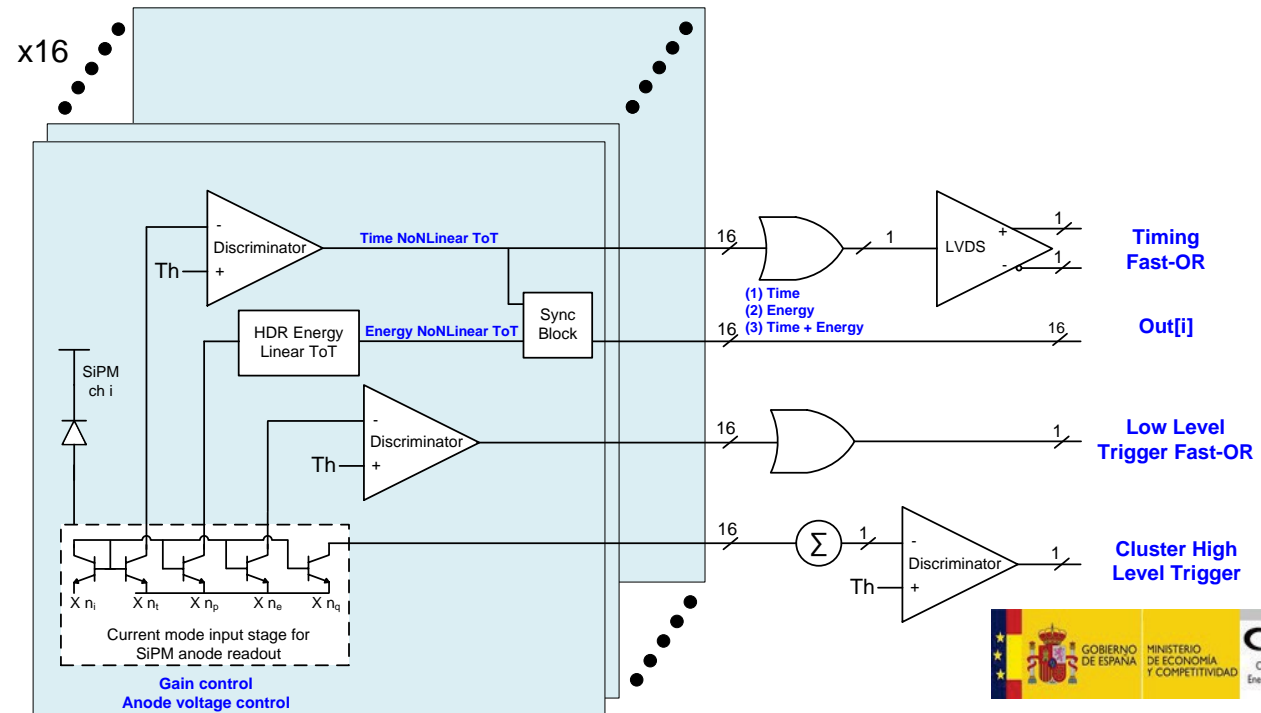


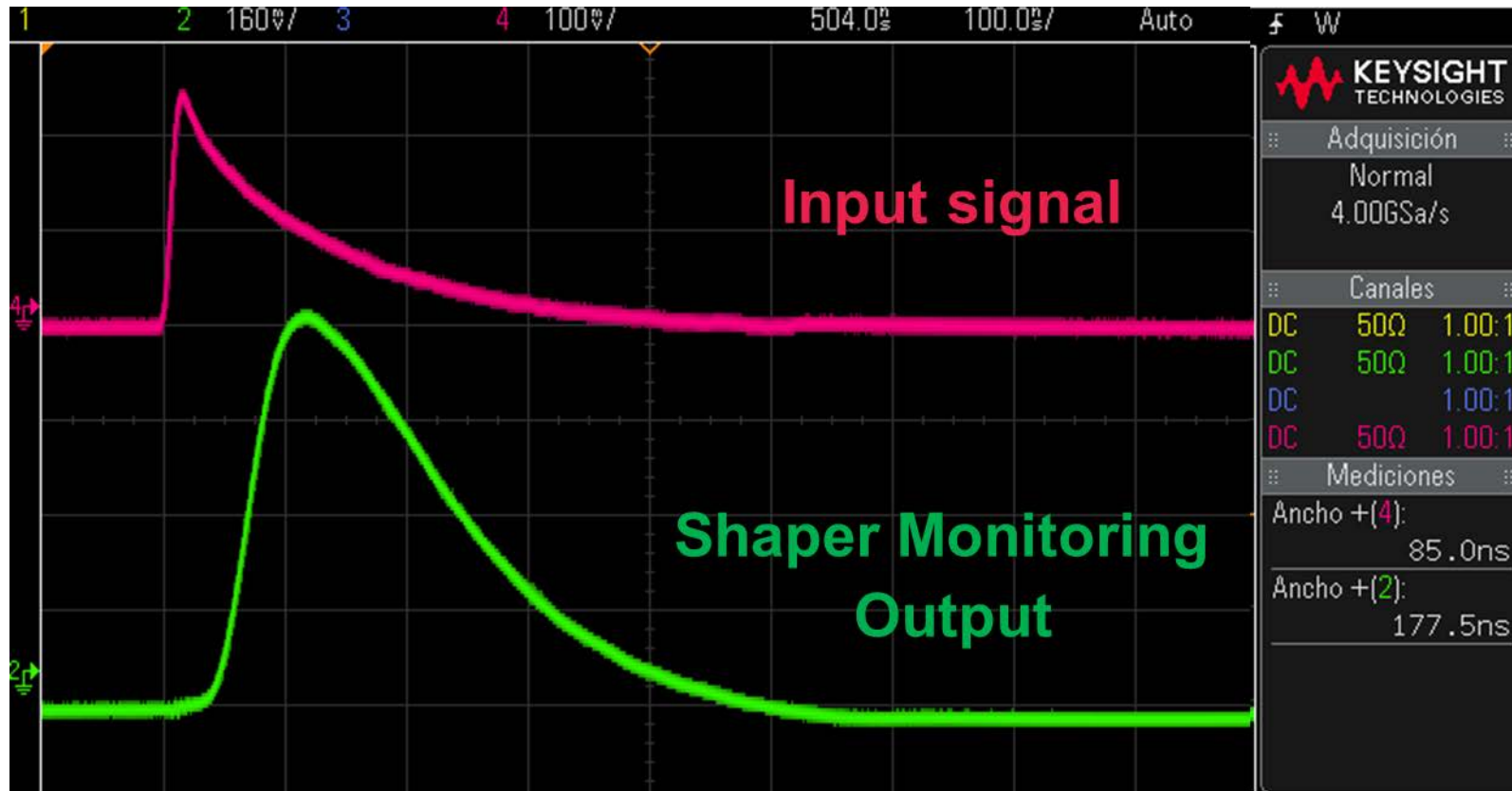
IV. ASICs for PET: HRFlexToT: linearized ToT RO chip

- Based on shaper and peak detector circuits



IV. ASICs for PET: HRFlexToT: linearized ToT RO chip


- Linearity and dynamic range

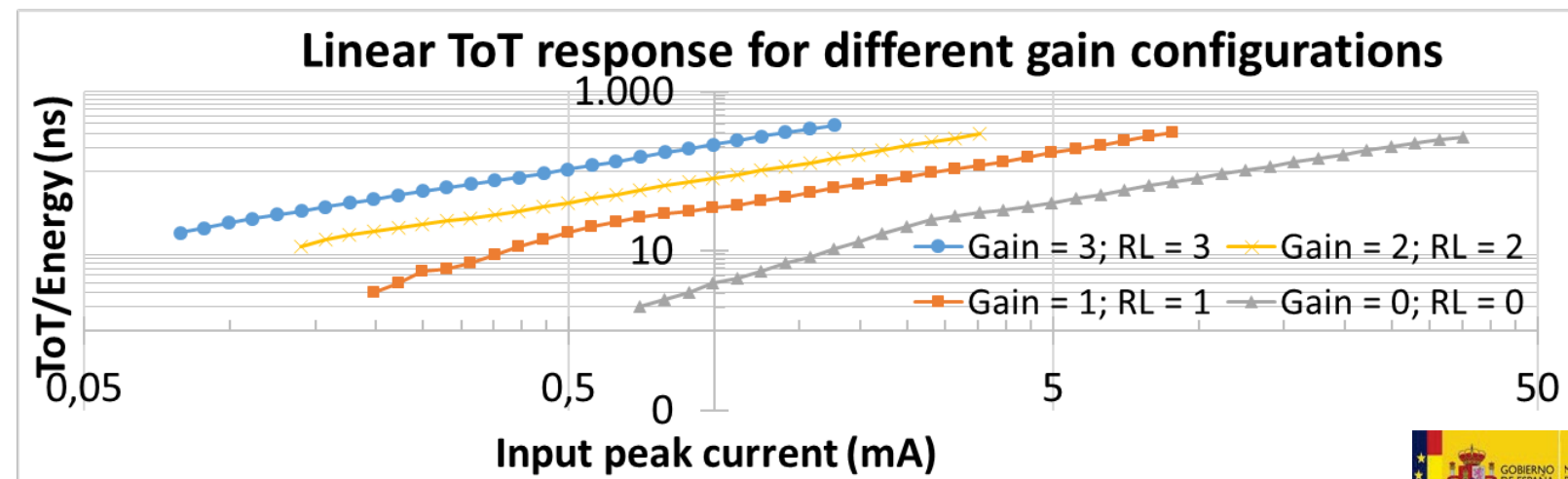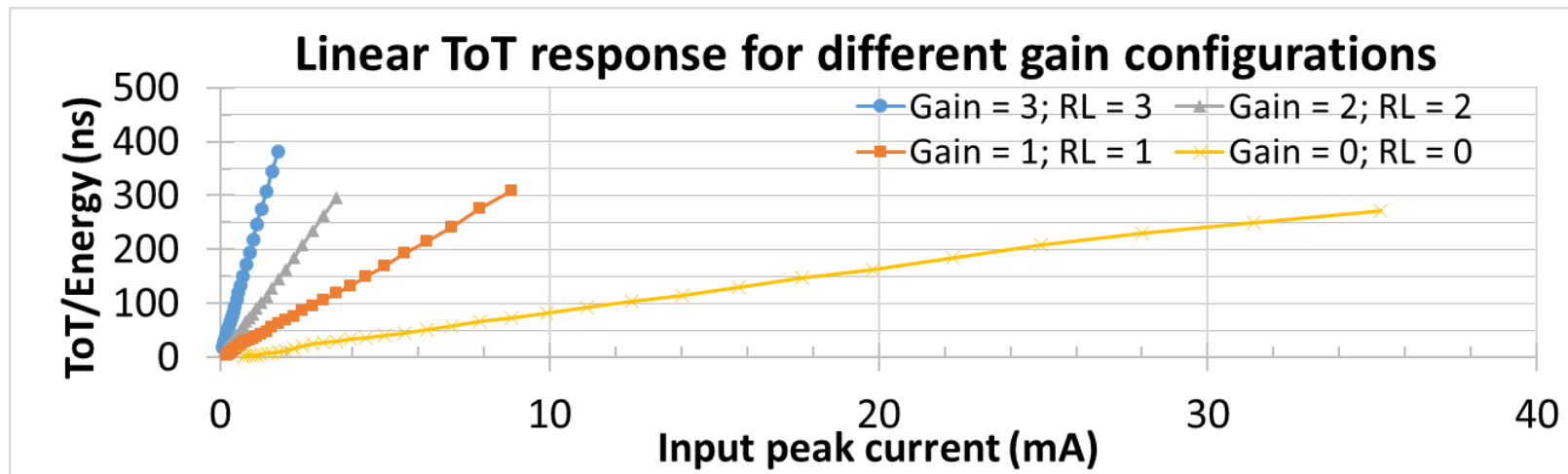

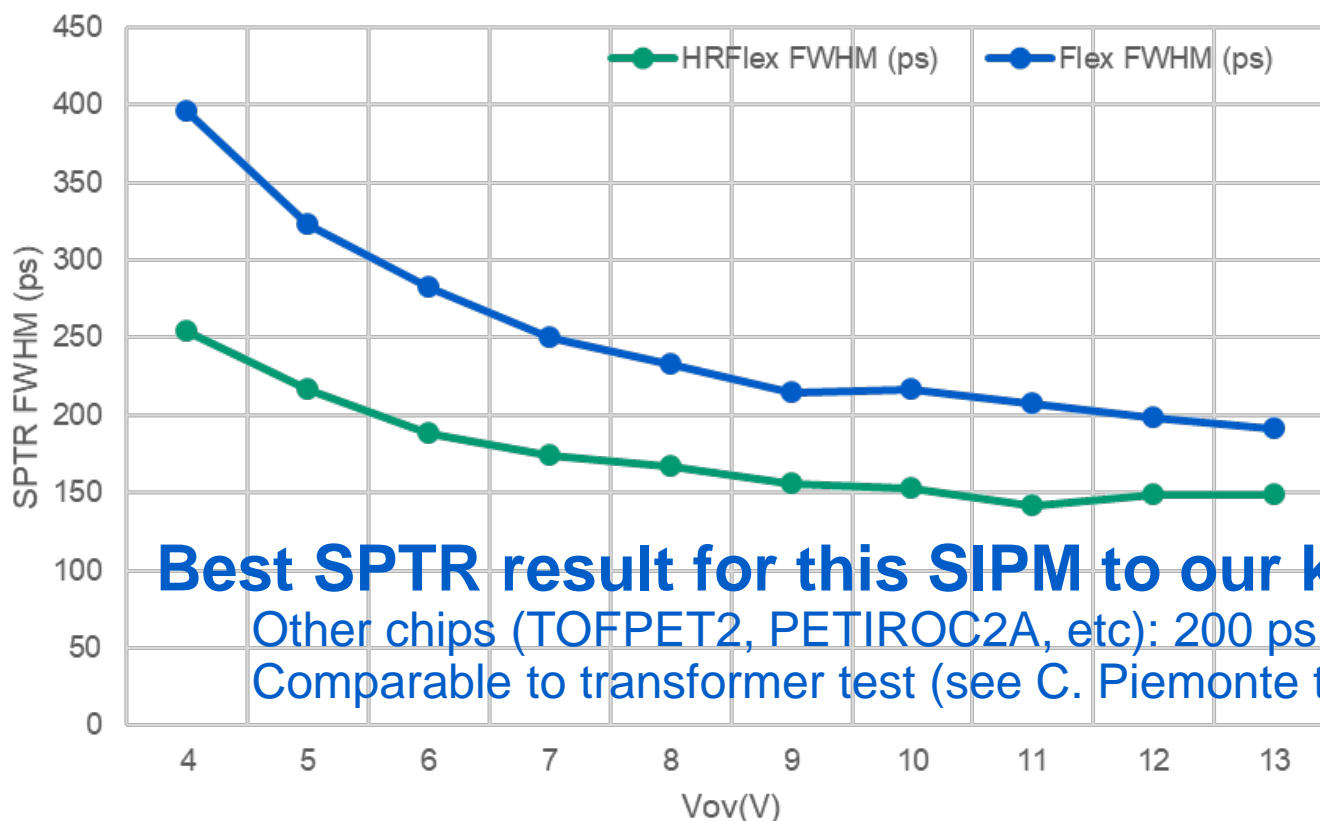IV. ASICs for PET: HRFlexToT: linearized ToT RO chip

- Preliminary results

- **3x3 mm²** HPKK device (50 um) cell, **S13660**.
- ***SPTR*** of about 60 ps rms (**<150 ps FWHM**) with 3.5 mW/ch




Best SPTR result for this SIPM to our knowledge:

Other chips (TOFPET2, PETIROC2A, etc): 200 ps FWHM for S13360
 Comparable to transformer test (see C. Piemonte talk).

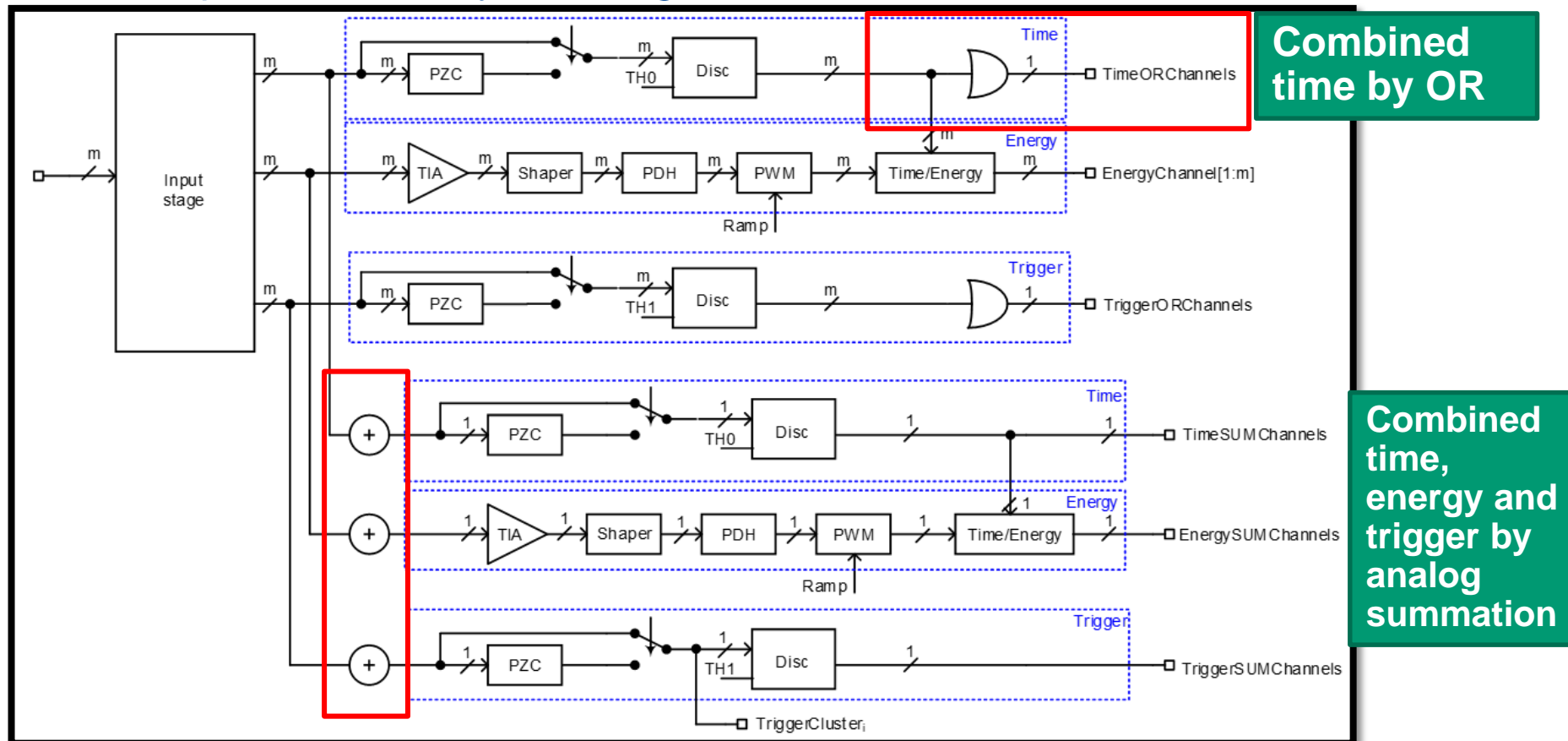IV. ASICs for fast timing: outlook

- New ASIC **FastIC** in 65 nm being developed by ICCUB and CERN
 - Very low power input stage, low input impedance, summation, < 10 ps TDC...
- First step towards a Hybrid Single Photon Pixel Detector



- I. Introduction
- II. SiPM electrical parameters
- III. FE circuits
- IV. ASIC examples
- V. Conclusions**

V. Conclusions

- SiPM pulse shape depends on readout amplifier and parasitic component of interconnects
- In current sensing, R_{in} should be minimized for best timing (improved di/dt)
 - But any value smaller than $R_{in,min} = 5 \Omega$ make the parasitic input network to resonate
- In voltage sensing, R_{in} should be maximized for best timing (better dv/dt)
 - This means large tails (PZ cancellation needed) and increasing series noise
- Optimum bandwidth in the signal path, prior to discrimination $BW_{opt} \sim 3 \frac{1}{2\pi\sqrt{L C_{det}}}$
 - No point in designing faster circuits, since only increases noises !
 - This limit can be below 100 MHz for large SiPMs with high interconnect inductance.
- For an accurate design we need to consider SiPM, readout circuits and interconnects together
 - Input impedance, electronics noise and shaping determine final performance: shape, effective gain, time resolution, energy resolution, etc
 - ***In my “dream” LLL: sensor sensor and electronics are optimized together:***
 - ***3D integration and hybrid approaches: not purely analog nor purely digital***

References on SiPM modelling and FE electronics

- G. Collazoul, "The SiPM Physics and Technology", Photodet 2012, https://indico.cern.ch/event/164917/contributions/1417121/attachments/198512/278663/PhotoDet12_-_collazuol_-_v3.pdf
- S. Seifert, "Simulation of silicon photomultiplier signals", IEEE Trans. Nucl. Sci., vol. 56, no. 6, pp. 3726-3733, Dec. 2009.
- F. Corsi et al., "Modelling a Silicon Photomultiplier (SiPM) as a Signal Source for Optimum Front-End Design", Nucl. Instr. and Meth. in Phys. Res., vol. A572, pp. 416-418, 2007
- F. Ciciriello, F. Corsi, F. Licciulli, C. Marzocca, G. Matarrese et al., "Accurate Modeling of SiPM Detectors Coupled to FE Electronics for Timing Performance Analysis", Nucl. Instr. and Meth. in Phys. Res., vol. A 718, pp. 331-333.
- F. Ciciriello, F. Corsi, F. Licciulli, C. Marzocca and G. Matarrese, "Design of Current Mode Front-End Amplifiers with Optimal Timing Performance for High-gain Photodetectors," in European Conference on Circuit Theory and Design, 2015.
- C. de la Taill, "SiPM readout electronics overview", Photodet 2012, https://indico.cern.ch/event/164917/contributions/1417117/attachments/198508/278657/1-cdlt_Photodet2012.pdf

Third Barcelona Techno Week

Course on semiconductor detectors

Institute of Cosmos Sciences, Barcelona
From 2nd to 6th July 2018

About ▾ Program ▾ Sponsorship ▾ Registration Meeting Point Outreach Activities ▾ Techno Week Editions


Barcelona Techno Week

Barcelona Techno weeks are a series of meeting point events around a technological topic of interest for both academia and industry. They include comprehensive multidisciplinary keynote presentations by world experts that are combined with networking activities to foster collaboration among participants.

Thanks a lot for your attention !!!

Questions ?

dgascon@fqa.ub.edu

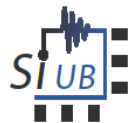

II: Input stage optimization

- In current sensing, R_{in} should be minimized for best timing (improved di/dt), **but any value smaller than $R_{in,min} = 5 \Omega$ make the parasitic input network to resonate.**
 - Low R_{in} trade-offs with power consumption; it can be reduced by means of feedback schemes, at the cost of compromising stability.
 - In practice, R_{in} in the range $15 \Omega - 20 \Omega$ are desirable in order to be compatible with detectors showing $C_{det} = 10 \text{ pF}$ (PMTs/MCPs) – 1 nF (Large SiPMs).
- In voltage sensing, R_{in} should be maximized for best timing (improved dv/dt). **Signal dynamics are favourable since underdamped response is not possible under such a case.**
 - The parallel resonance can boost the slew-rate even more, but one should rely on parasitics...
 - Large R_{in} results in degraded count-rate capabilities. PZ cancellation becomes compulsory.
- Optimum bandwidth in the signal path, prior to discrimination $BW_{opt} \sim 3 \frac{1}{2\pi\sqrt{L C_{det}}}$
 - The minimum LC_{det} product (5 nH short connection / 10 pF in PMT) already results in 1 GHz optimum bandwidth.

→ No point in designing current sensing circuits faster than 1 GHz , since only noise would be integrated, worsening σ_t !

I. Introduction: current IACTs cameras

- Even some CTA telescopes will still be based on PMTs

incoming photon



photoelectric effect PE
(generation of the primary electron)


electron multiplication chain

- production of secondary electrons
=> **measurable electric signal**

photomultiplier tube (PMT) - THE photodetector!

NO Si-based!

schematic view

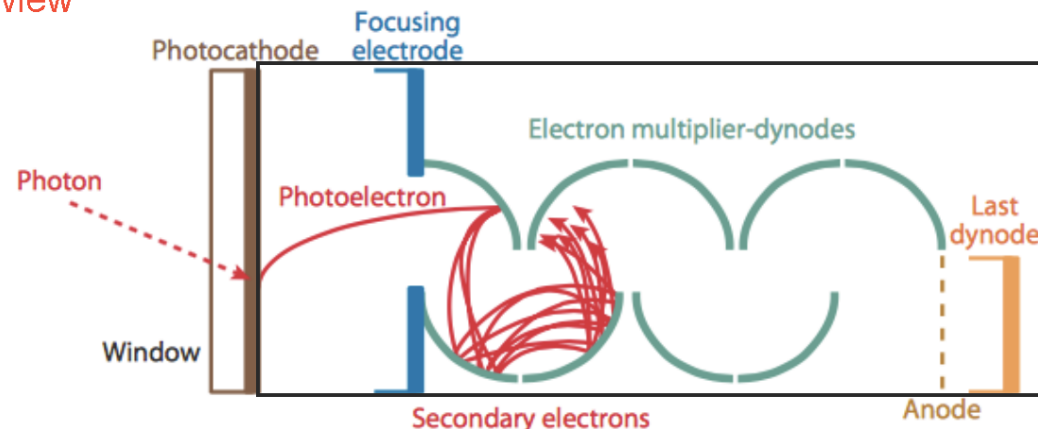


C. Casella, "Application of photosensors", ICCUB- Technoweeek, 2016.

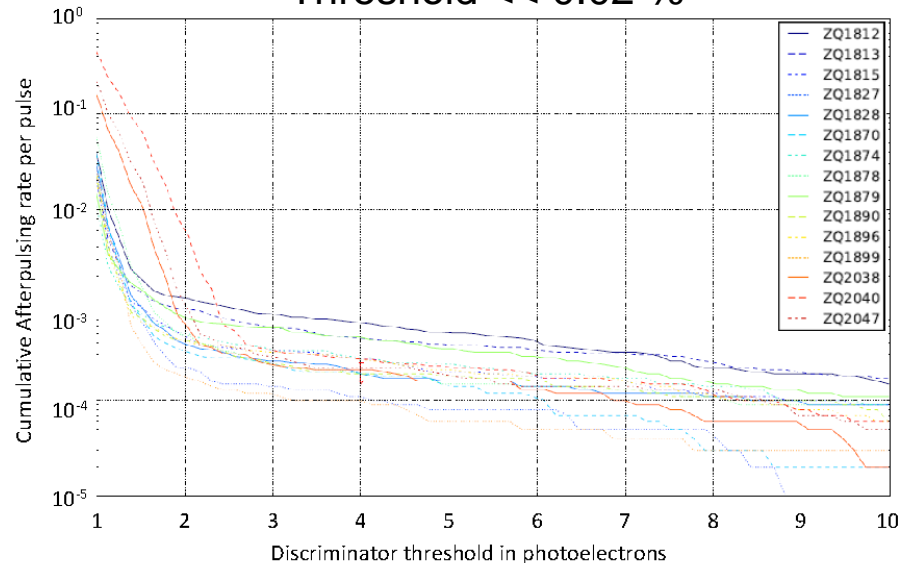
I. Introduction: current IACTs cameras

- Even some CTA telescopes will still be based on PMTs
- Amazing progress in last 10 years
 - PMTs developed for CTA

Afterpulsing at 4 ph.e.
Threshold $\ll 0.02\%$



Peak PDE > 35 %

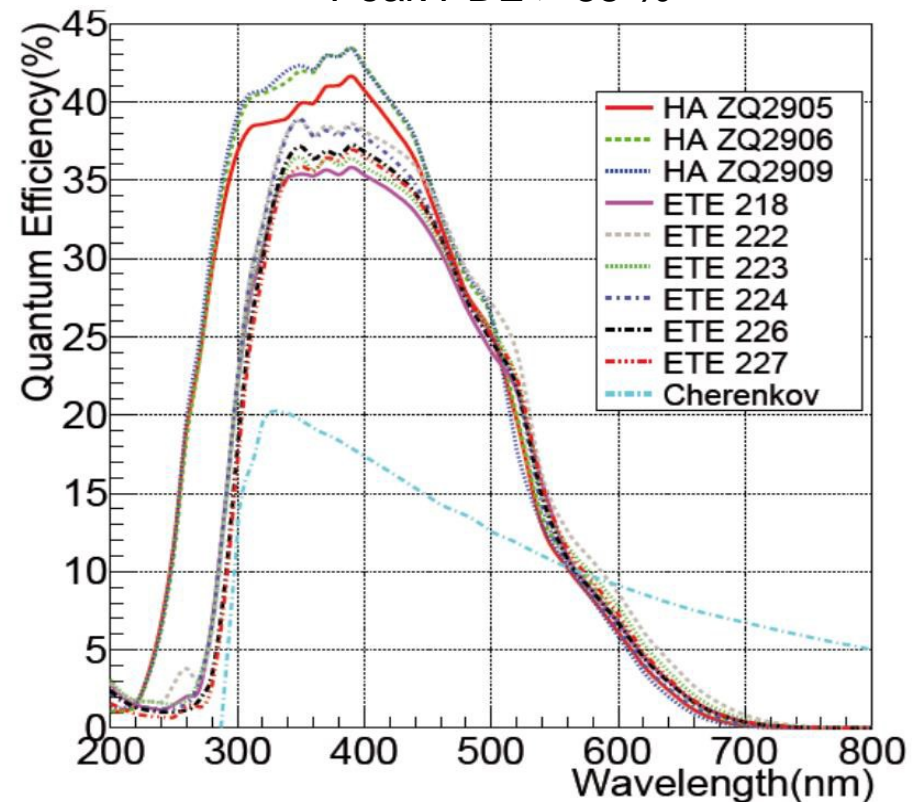



22.04.2015 APPEC TF,

Razmik Mirzoyan:

Recent Progress on PMT and SiPM, where we are going to

I. Introduction: SiPM based IACTs cameras

- SiPM principle

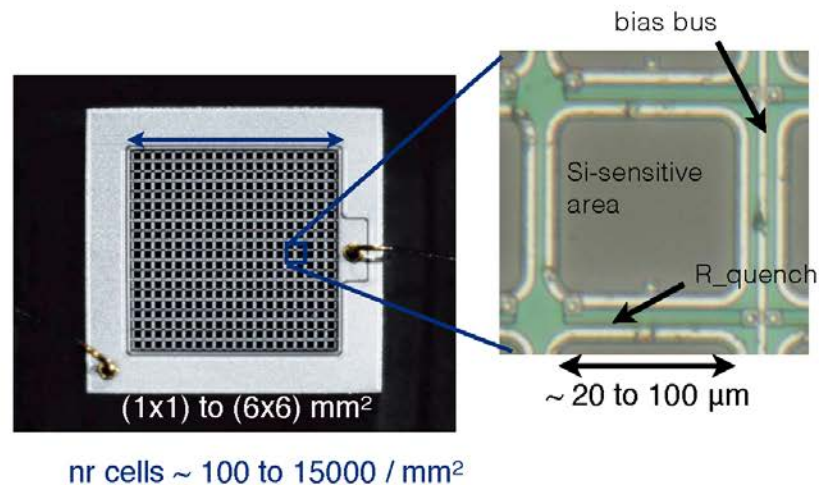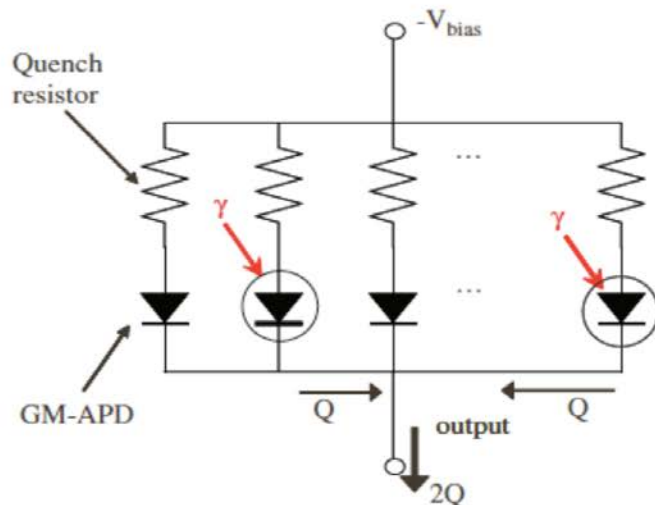

SiPM : array of micro-cells APD-like operated in G-mode connected to a **common bias** through **independent quenching resistors**, all integrated within a sensor chip.
The output is the **analogue sum of all cells**

individual cell (i.e. one diode, APD-like)

- $V_{bias} > V_{breakdown}$
- Gain $\sim 10^6 - 10^7$
- Geiger regime (fully saturated)
- **No analogue info at the single cell level !**

- when hit by 1(2,3...n) photon(s)
=> full discharge
=> $Q_{cell} = C_{cell} (V_{bias} - V_{breakdown})$
overvoltage

C. Casella, "Application of photosensors", ICCUB- Technoweeek, 2016.

I. Introduction: SiPM based IACTs cameras

- What is crosstalk in a SiPM?

43

Correlated Noise


Optical Cross Talk

During the avalanche a large nr of photons are produced { **$O(1\text{photon}/10^5 \text{ charge carriers})$** }
 => Reach neighbours pixels and start a second avalanche

correlated noise

contribution **added** to the primary signal
 stochastic process => contributes to ENF


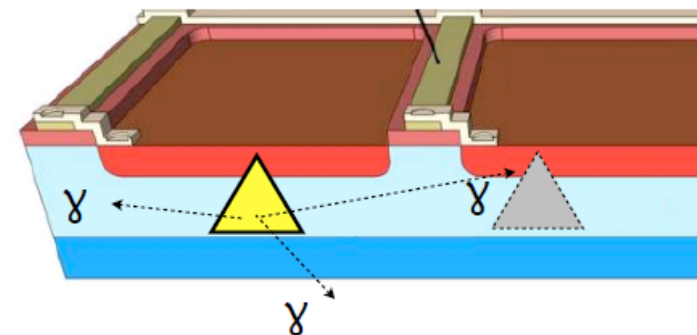
- **larger Vov => larger gain => higher P_XT**
- **smaller pixel size => higher P_XT**
- **XT ~ 30 - 40 % (w/o trenches)**
- **significant impact of trenches = optical separation**



C. Casella, "Application of photosensors", ICCUB- Technoweeek, 2016.

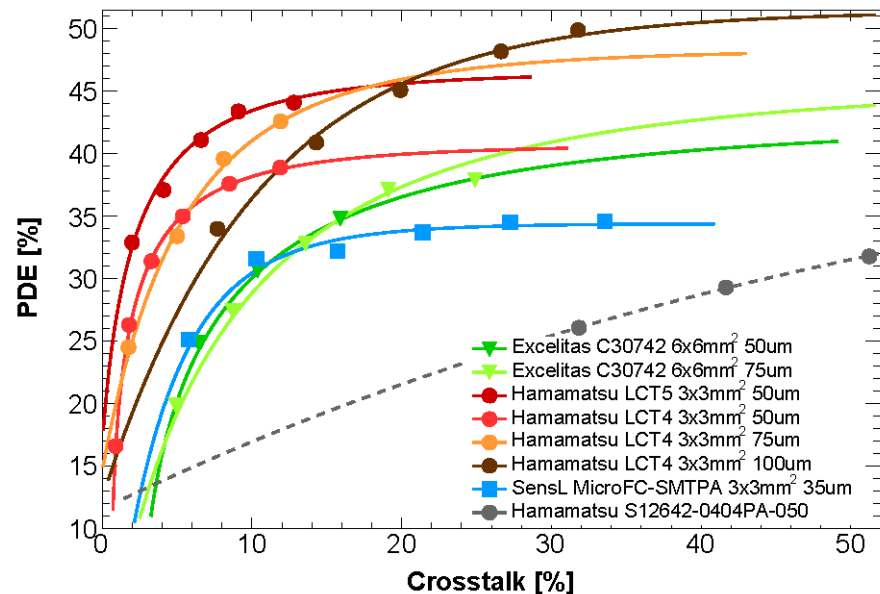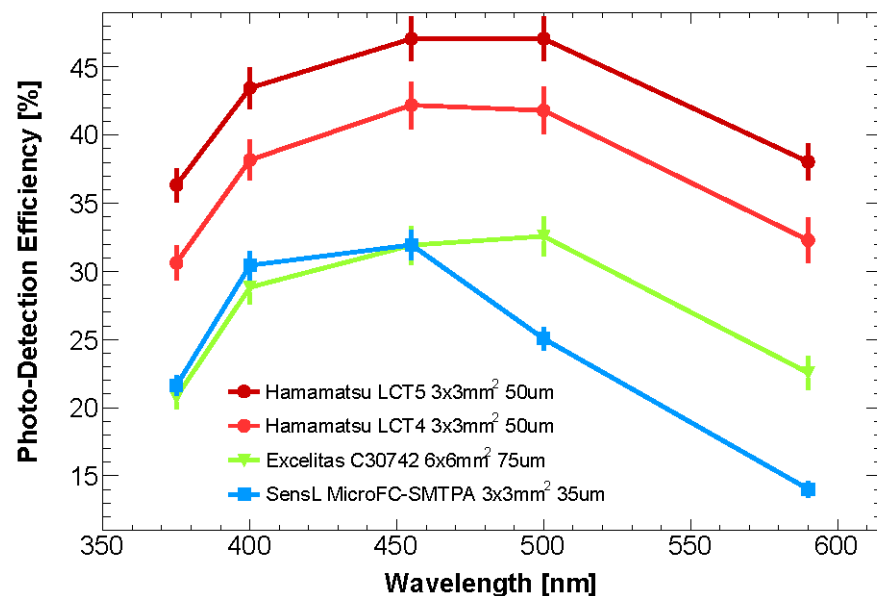I. Introduction: SiPM requirements for IACTs

- High PDE > 40 %
 - A higher PDE results in a higher reconstruction rate of Cherenkov photons and decreases the energy threshold
- Low crosstalk
 - Crosstalk degrades the single photon charge resolution
- Trade-off between PDE and crosstalk




J. Biteau et al. "Performance of Silicon Photomultipliers for the Dual-Mirror Medium-Sized Telescopes of the Cherenkov Telescope Array", ICRC2015

I. Introduction: SiPM based IACTs cameras


21

Solid state photodetectors (i.e. p-n junction)

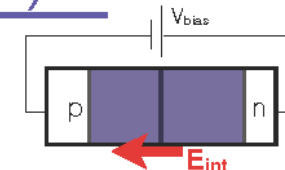Reversed bias pn junction - Different regimes



J. Haba, NIM A 595(2008) 154-160

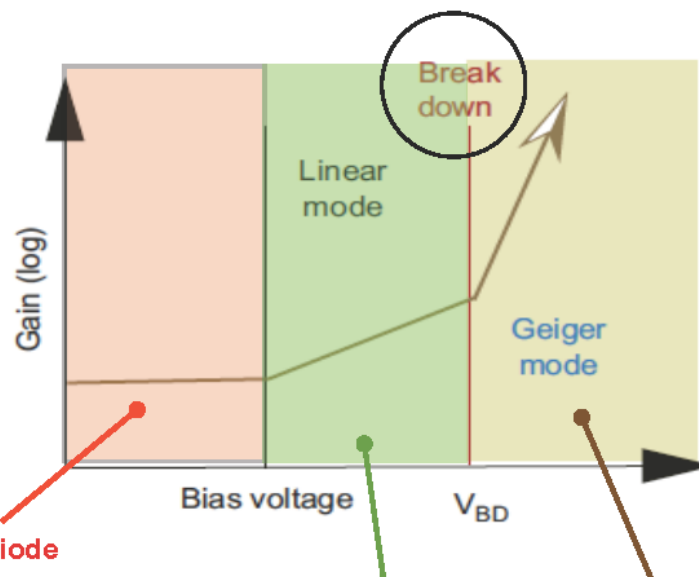

PIN Diode

- no bias
- no gain

AVALANCHE PHOTODIODE (APD)

- voltage
- secondary ionization from electrons
- avalanche
- linear regime

GEIGER MODE AVALANCHE (G-APD)


- $V > V_{\text{breakdown}}$
- secondary ionization from electrons and holes
- "broken" junction, avalanche
- Geiger regime, not linear anymore

SILICON PHOTOMULTIPLIER (SiPM) :

array of micro-cells operated in G-APD

V_{bias} :

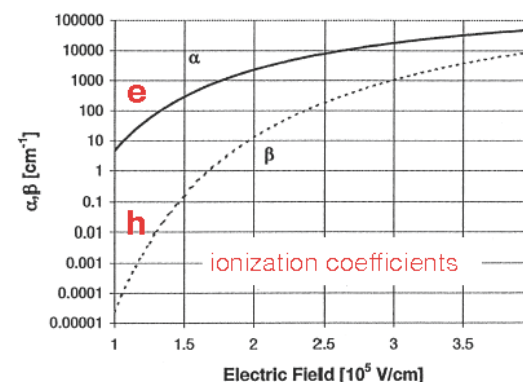- enlarge depletion region
- increase electric field
- secondary ionization




C. Casella, "Application of photosensors", ICCUB- Technoweeek, 2016.

I. Introduction: SiPM based IACTs cameras

36


SiPM properties : Photon Counting

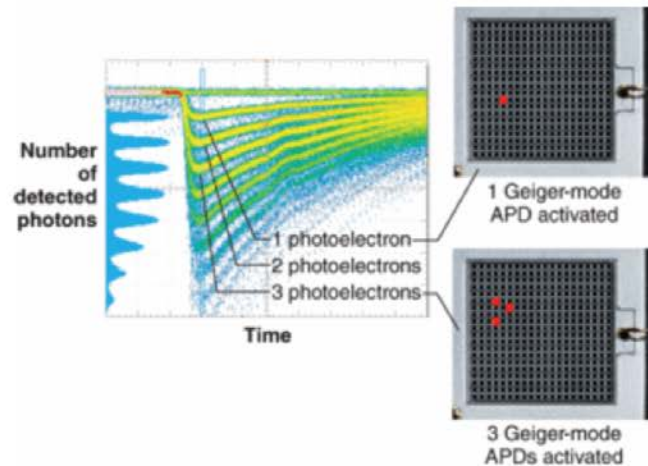

The output signal is 'quantized' and proportional to the Nr of fired cells



$$Q_{1\text{cell}} = C_{\text{cell}} V_{\text{ov}}$$
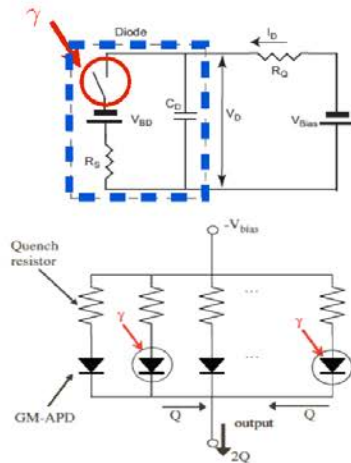
$$Q_{\text{total}} = N Q_{1\text{cell}}$$



Excellent single photon counting capability

D. Renker, 2009 JINST 4 P04004

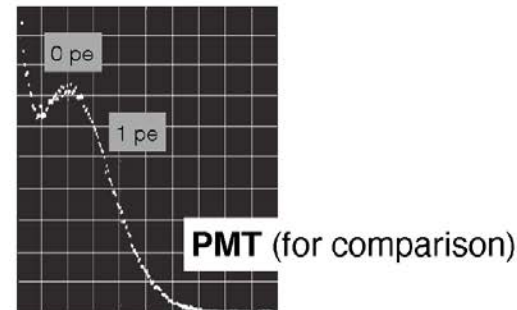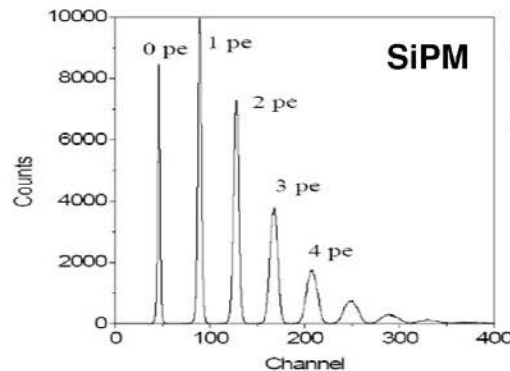



C. Casella, "Application of photosensors", ICCUB- Technoweeek, 2016.

14 June 2018

ICASiPM - D.Gascon

Basic pulse shapes

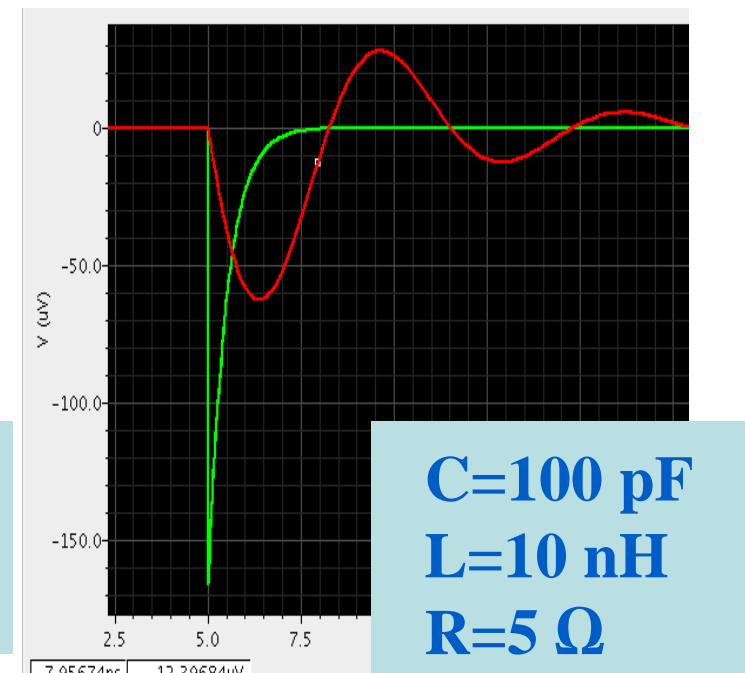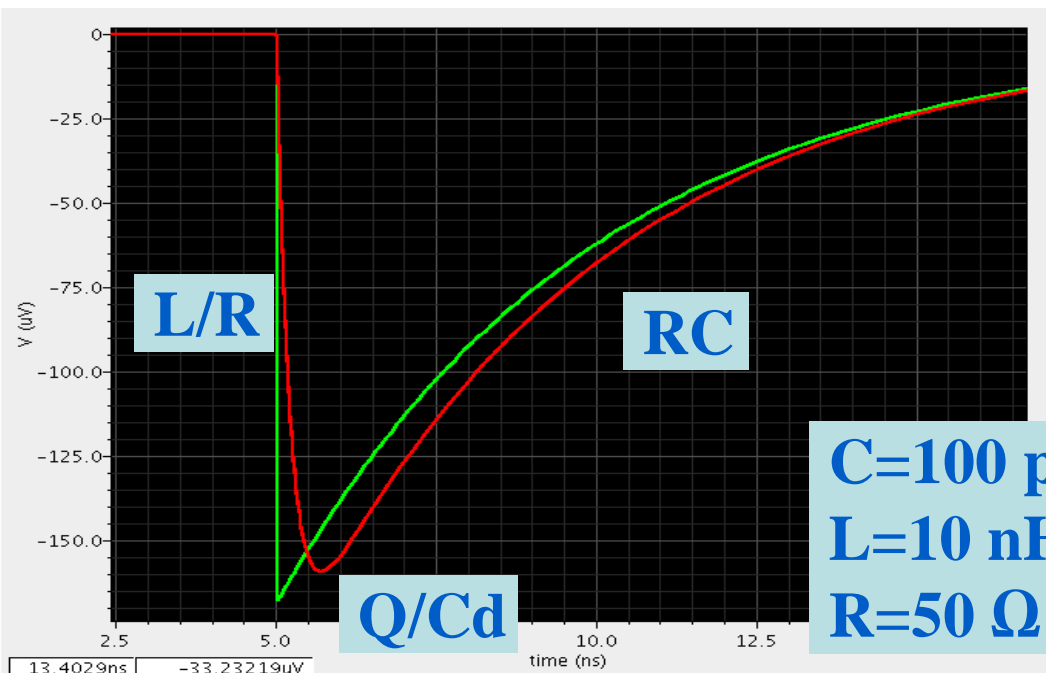
- Short pulse : $Q=16$ fC, $C_d=100$ pF, $L=0-10$ nH, $R_L=5-50$ Ω
- Smaller signals with SiPM (large C_d) \sim mV/p.e.
- Sensitivity to parasitic inductance
- Choice of R_L : decay time, stability
- Convolve with current shape... (here delta impulse)



SiPM modelization

- Modelization by Corsi et al [NIM A572 2007]

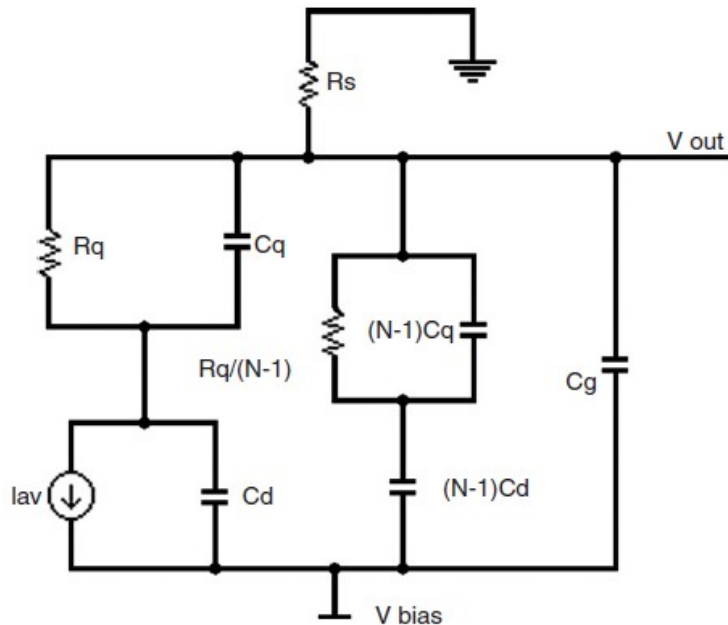SiPM IRST,
 $N = 625$,
 $V_{bias} = 35 \text{ V}$



[F. Corsi et al. NIM A572]

R_q (k Ω)	393.75
V_{br} (V)	31.2
Q (fC)	148.5
C_d (fF)	34.13
C_s (fF)	4.95
C_g (pF)	27.34


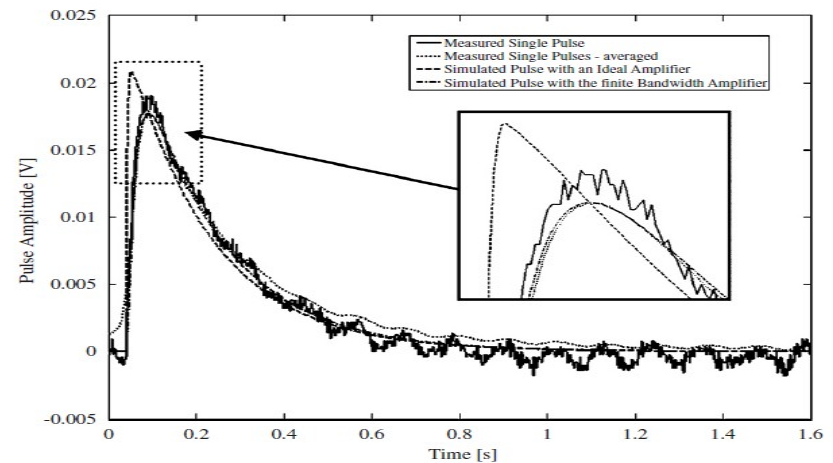
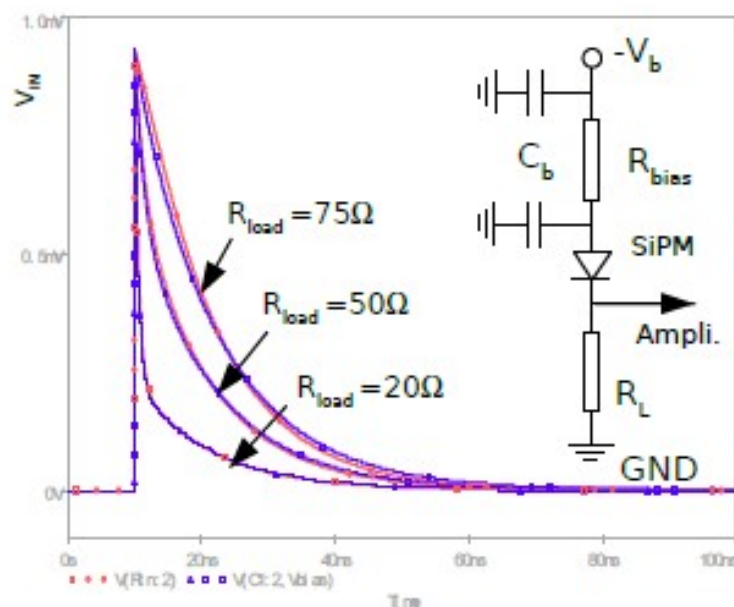


Fig. 2. Fitting of real data with the simulation results on the device model.

Electrical model of a SiPM

Collazuol
2008

- R_q : quenching resistor (hundreds of k Ω)
- C_d : junction capacitance (few tens of fF)
- C_q : parasitic capacitance in parallel to R_q (few tens of fF, $C_q < C_d$)
- I_{AV} : SiPM ~ ideal current source current source modeling the total charge delivered by a cell during the avalanche $Q = \Delta V(C_d + C_q)$
- C_g : parasitic capacitance due to the routing of V_{bias} to the cells (metal grid, few tens of pF)

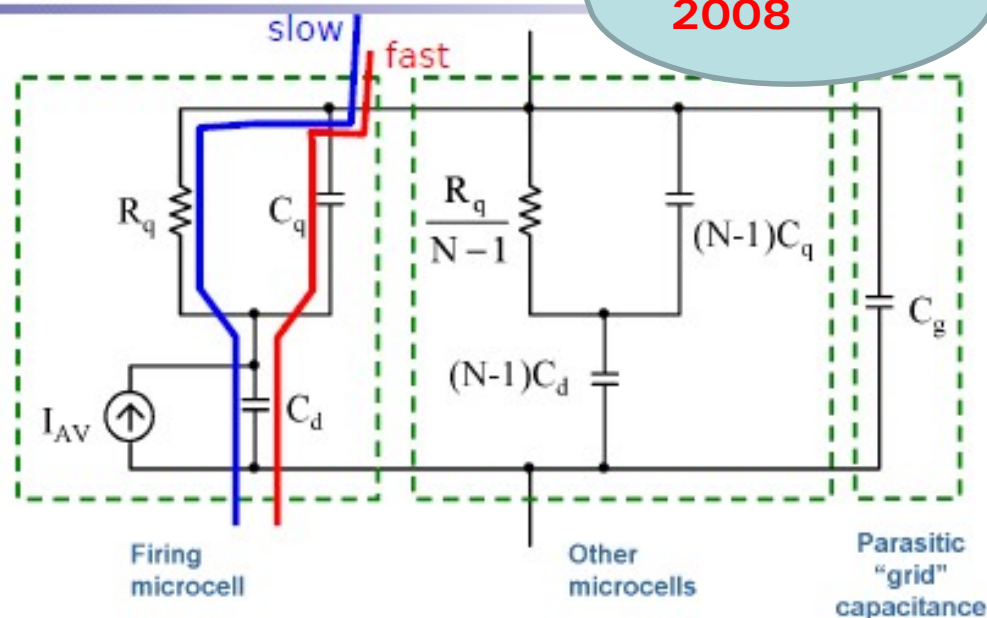

1) the peak of V_{IN} is independent of R_s

A constant fraction Q_{IN} of the charge Q delivered during the avalanche is instantly collected on $C_{tot} = C_g + C_{eq}$.

2) The circuit has two time constants:

- $\tau_{IN} = R_L C_{tot}$ (fast)
- $\tau_r = R_q (C_d + C_q)$ (slow)

Decreasing R_s , the time constant τ_{IN} decreases, the current on R_s increases and the collection of Q is faster

F. Corsi, C. Mazzocca et al.

SiPM equivalent circuit

Collazuol
2010



Single cell model $\rightarrow (R_d || C_d) + (R_q || C_q)$

SiPM + load $\rightarrow (||Z_{\text{cell}})||C_{\text{grid}} + Z_{\text{load}}$

Signal = **slow** pulse ($\tau_{d \text{ (rise)}}, \tau_{q \text{-slow (fall)}}$) +
+ **fast** pulse ($\tau_{d \text{ (rise)}}, \tau_{q \text{-fast (fall)}}$)

- $\tau_{d \text{ (rise)}} \sim R_d (C_q + C_d)$
- $\tau_{q \text{-fast (fall)}} = R_{\text{load}} C_{\text{tot}}$ (fast; parasitic spike)
- $\tau_{q \text{-slow (fall)}} = R_q (C_q + C_d)$ (slow; cell recovery)

F. Corsi, et al. NIMA 572(2007)

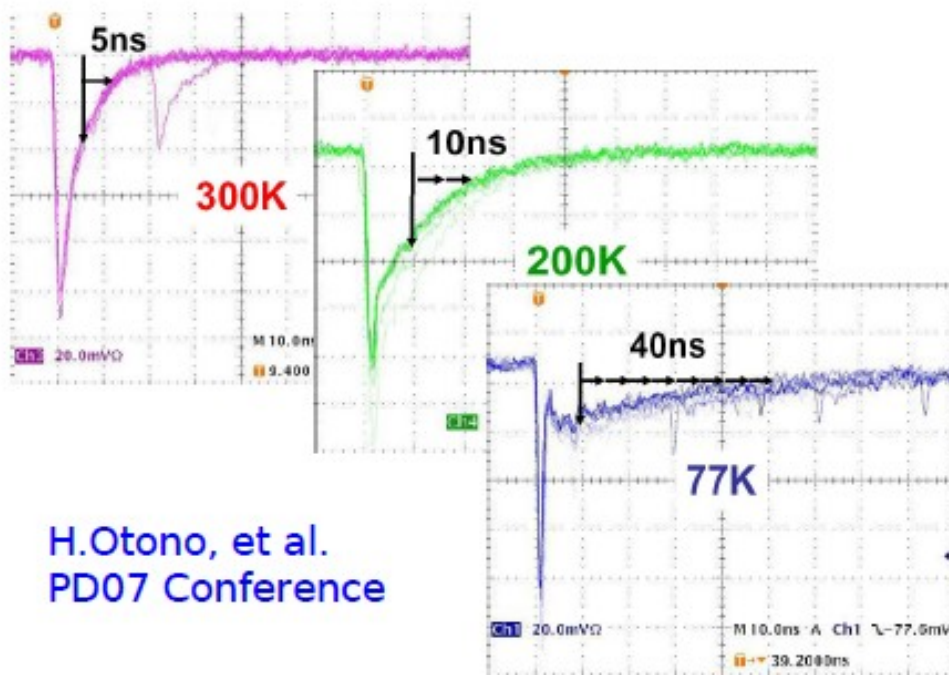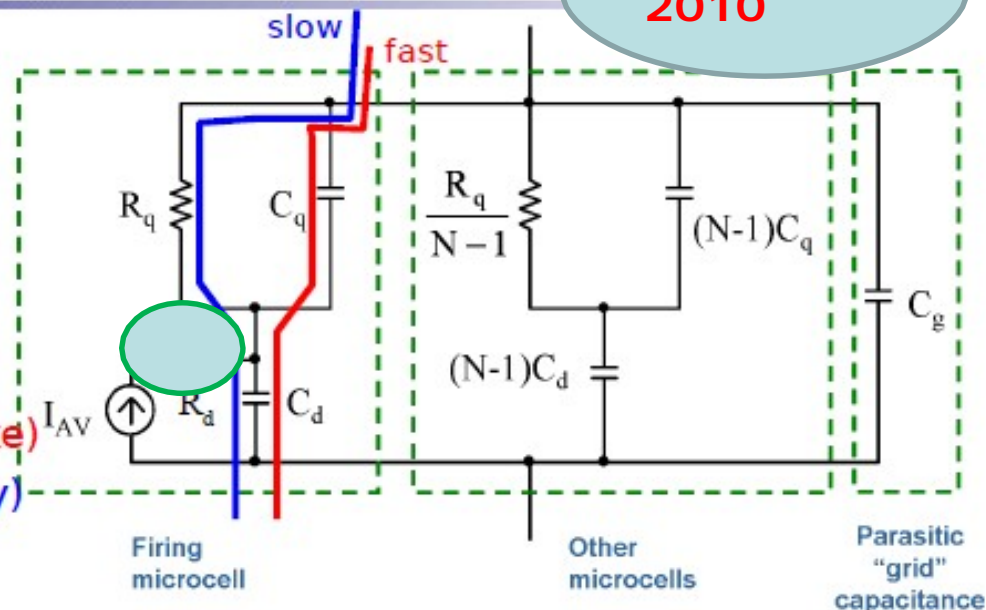

H.Otono, et al.
PD07 Conference

Pulse shape:

The two current components show different behavior with Temperature

\rightarrow fast component is independent of T because stray C_q couple with external R_{load} (no dependence on T) while R_q is strongly dependent on T

(we used low light level, BW filters against noise and AC coupling \rightarrow difficult to disentangle the two components)

Optimizing signal shape for timing


Collazuol
2012

Single cell model $\rightarrow (R_d || C_d) + (R_q || C_q)$

SiPM + load $\rightarrow (||Z_{\text{cell}}) || C_{\text{grid}} + Z_{\text{load}}$


Signal = **slow** pulse ($\tau_{d \text{ (rise)}}, \tau_{q \text{-slow (fall)}}$) +
+ **fast** pulse ($\tau_{d \text{ (rise)}}, \tau_{q \text{-fast (fall)}}$)

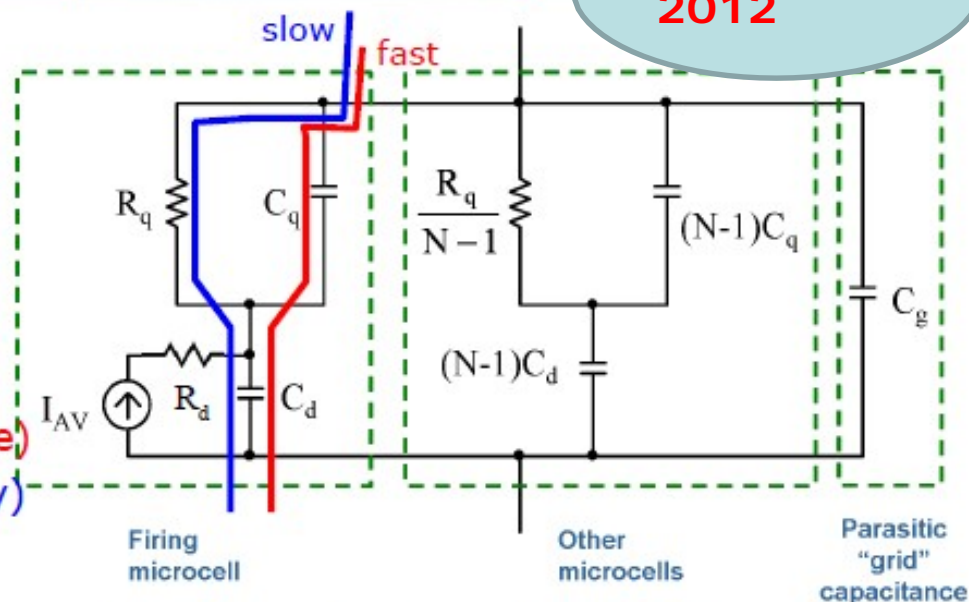- $\tau_{d \text{ (rise)}} \sim R_d (C_q + C_d)$
- $\tau_{q \text{-fast (fall)}} = R_{\text{load}} C_{\text{tot}}$ (fast; parasitic spike)
- $\tau_{q \text{-slow (fall)}} = R_q (C_q + C_d)$ (slow; cell recovery)



Pulse shape
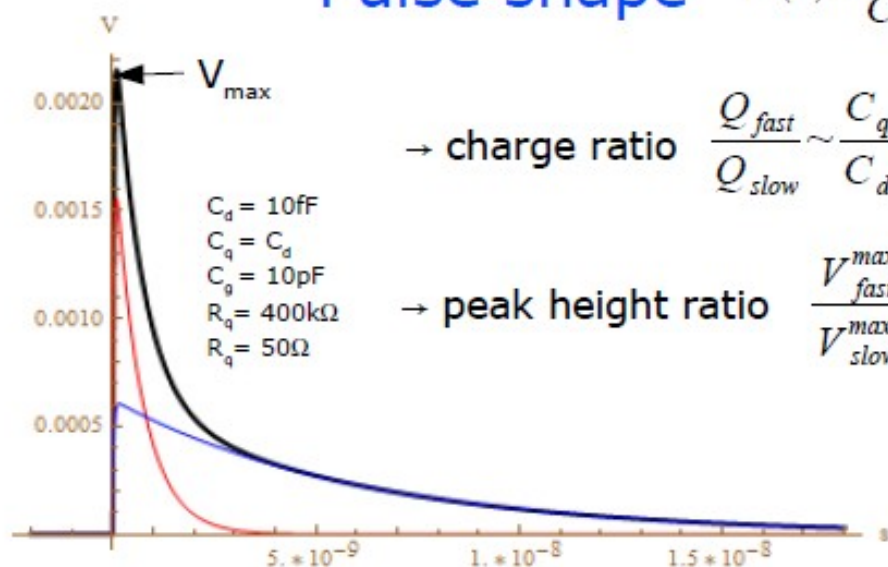
$$V(t) \simeq \frac{Q}{C_q + C_d} \left(\frac{C_q}{C_{\text{tot}}} e^{\frac{-t}{\tau_{\text{FAST}}}} + \frac{R_{\text{load}}}{R_q} \frac{C_d}{C_q + C_d} e^{\frac{-t}{\tau_{\text{SLOW}}}} \right)$$



→ charge ratio $\frac{Q_{\text{fast}}}{Q_{\text{slow}}} \sim \frac{C_q}{C_d}$



→ peak height ratio $\frac{V_{\text{fast}}^{\text{max}}}{V_{\text{slow}}^{\text{max}}} \sim \frac{C_q^2 R_q}{C_d C_{\text{tot}} R_{\text{load}}}$

increasing with R_q and $1/R_{\text{load}}$
(and C_q of course)

Increasing C_q/C_d or/and R_q/R_{load}
→ spike enhancement
→ better timing

II. Slew-rate in current and voltage sensing

Current sensing

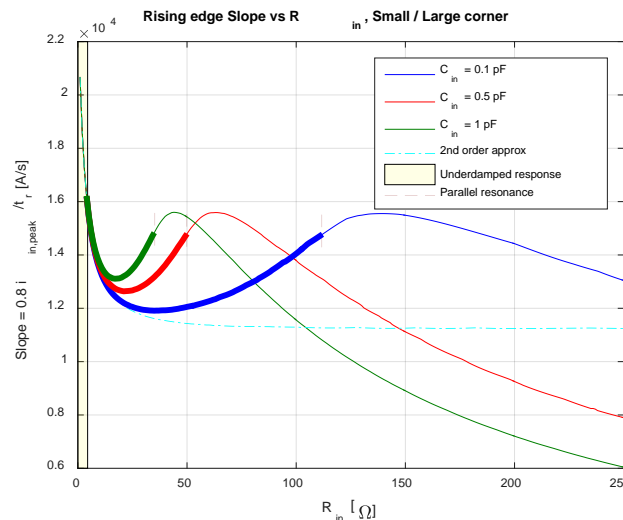
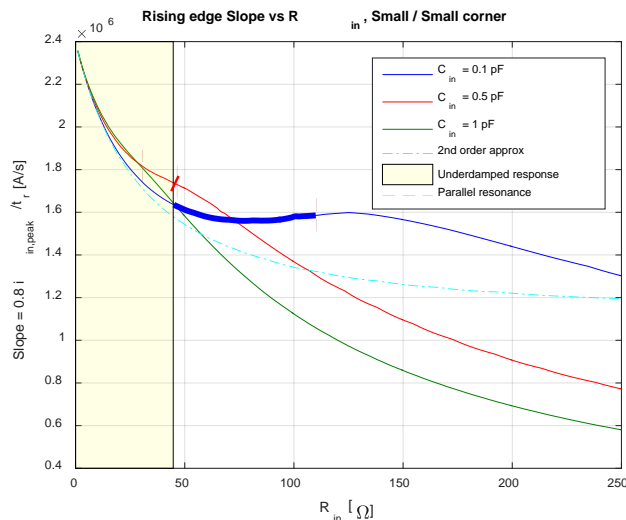


SR improves with small R_{in} :

$$\frac{\partial i_{in}}{\partial t} \propto \frac{Q_{det}}{L \cdot C_{det}}$$

- Specially true when entering in underdamped region.
- Underdamping can be problematic (multiple crossing in discrimination).
- Independent of R_{in} deep in overdamping regime. Parallel resonance enhances the SR.

Voltage sensing

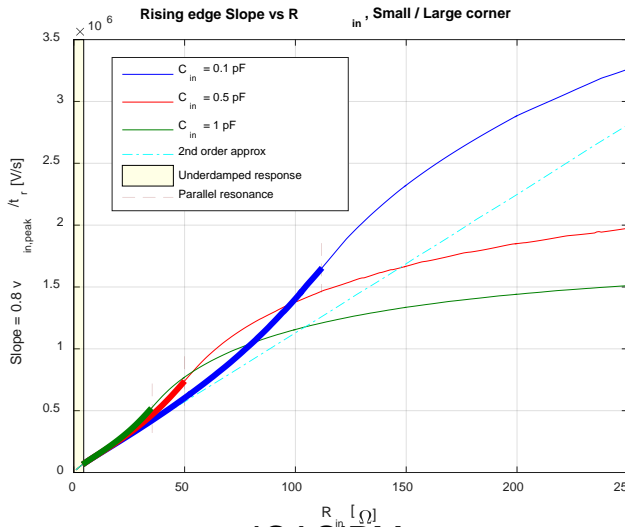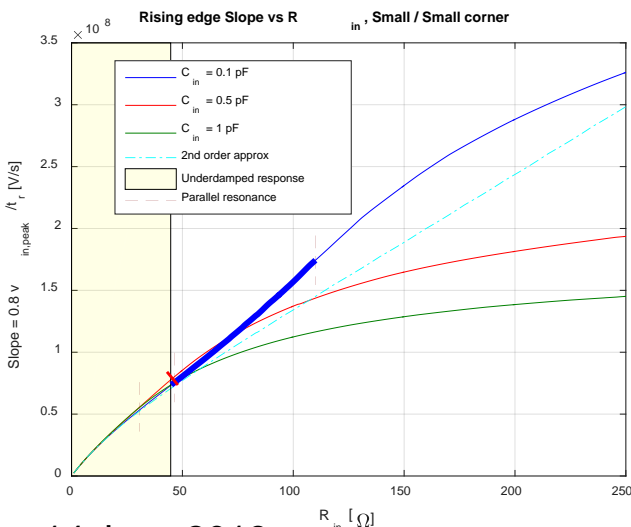



SR improves with large R_{in} :

$$\frac{\partial v_{in}}{\partial t} = R_{in} \cdot \frac{\partial i_{in}}{\partial t} \propto \frac{Q_{det} \cdot R_{in}}{L \cdot C_{det}}$$

- Almost linear relationship between SR and R_{in} .
- Parallel resonance can be exploited for peak enhancement.
- Problem: reduced count-rate for large R_{in} .

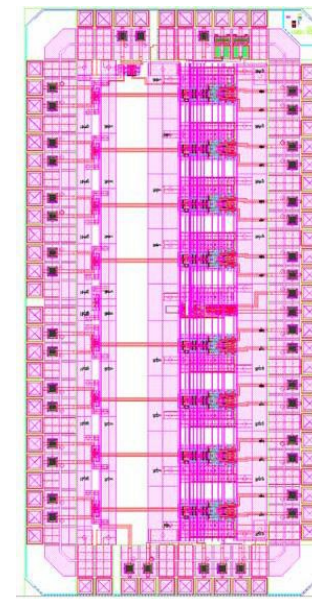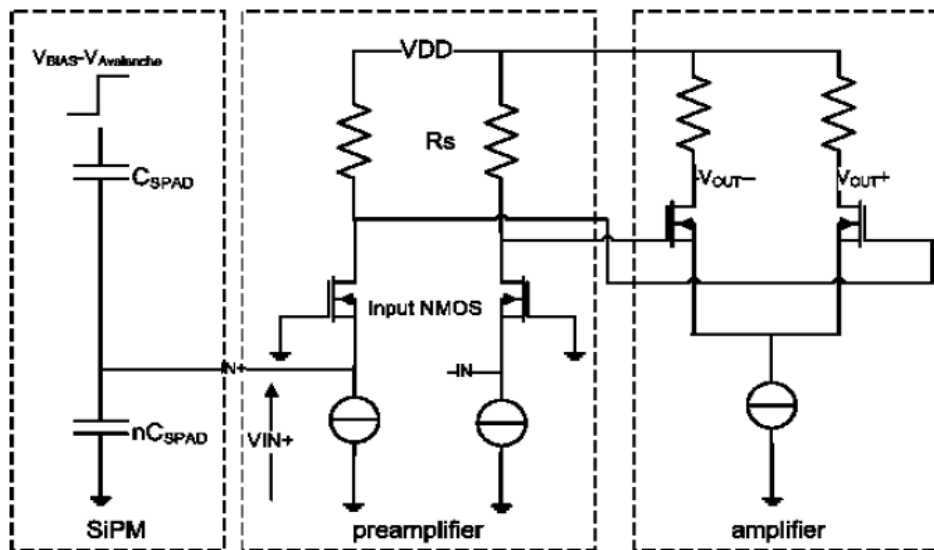III. FE circuits: NINO



- NINO: current mode, binary and quite generic
- Chip designed by CERN group for ALICE TOF RPCs but quite used for SiPM read-out
 - 8 channels amplifier and discriminator
 - Common grid current conveyor, high speed differential discriminator
 - High speed time measurement (10 ps),
 - $P_d = 25 \text{ mW/ch}$, Manufactured in IBM 0.25 μm



F. Anghinolfi, P. Jarron et al. NINO, NIM A, 2004, Vol. 533 page 183-187

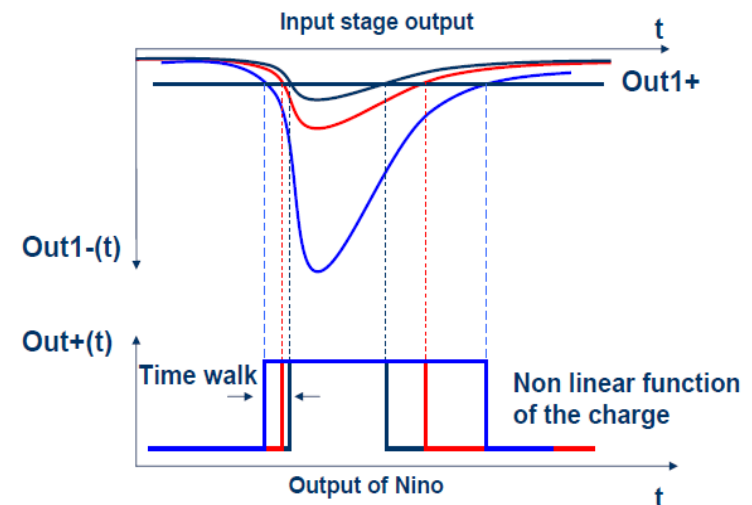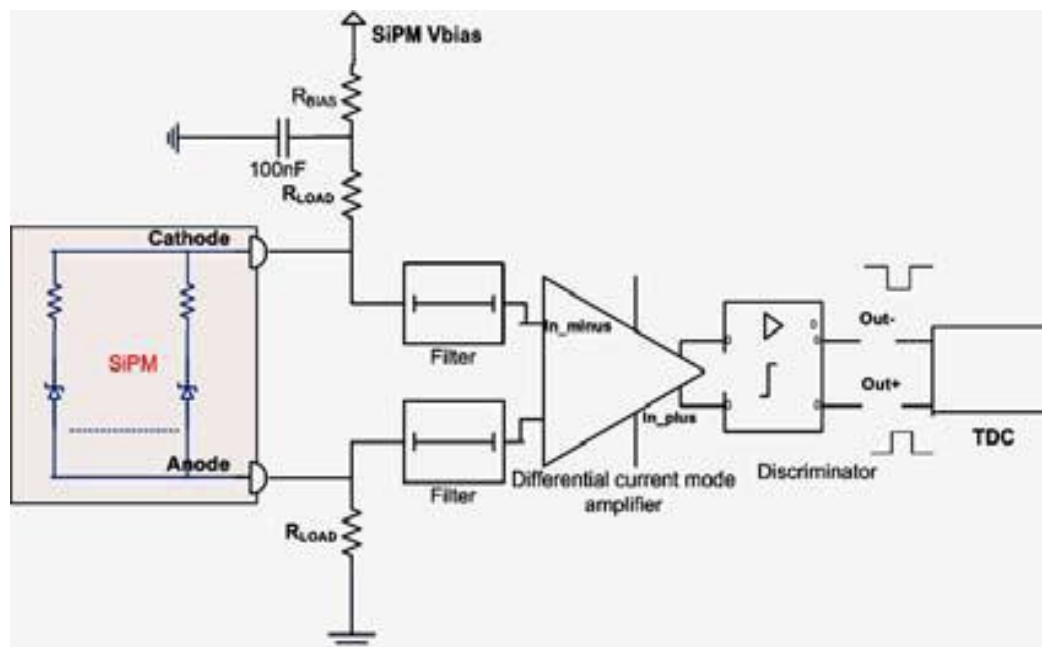III. FE circuits: NINO





- NINO: current mode, binary and quite generic
- Binary: usually connected to TDC for Time-Over-Threshold (ToT) energy
 - Simple discriminator: ToT is not linear
- Differential connection to the SiPM



F. Anghinolfi, P. Jarron et al. NINO, NIM A, 2004, Vol. 533 page 183-187

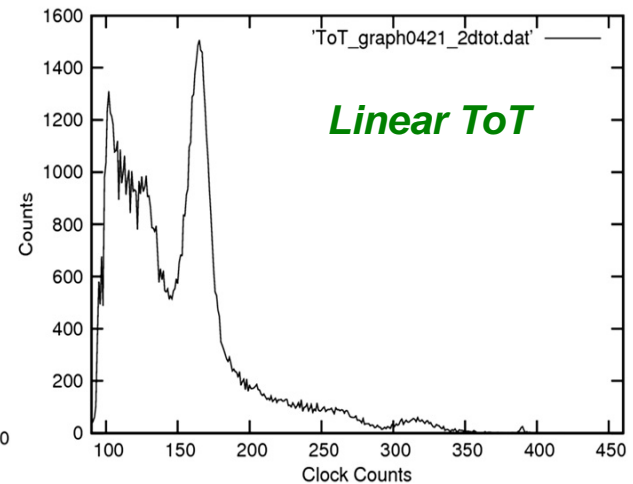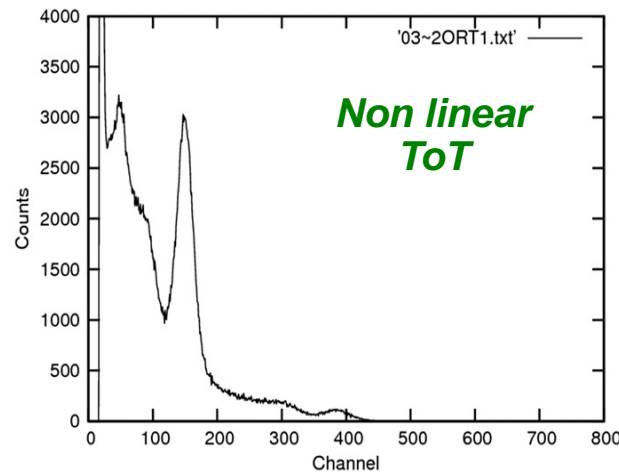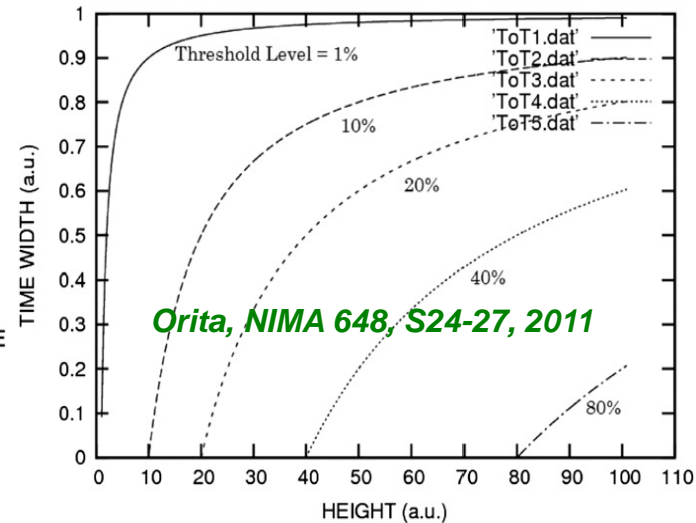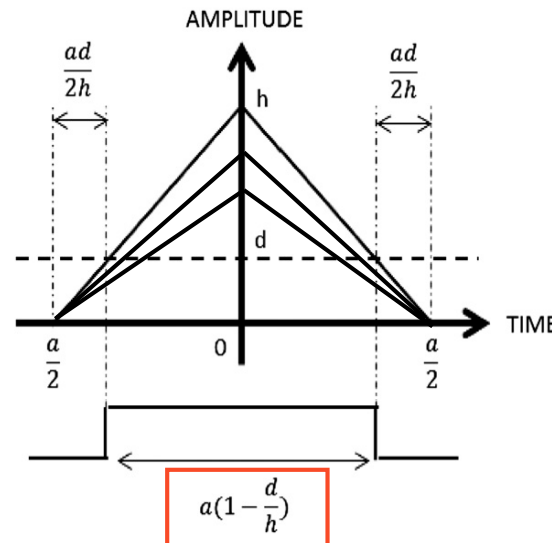
III. FE circuits: NINO

- Classical ToT is non-linear
 - Calibration is possible
 - But not perfect...
- It has an impact on energy resolution
 - Calibration is possible
 - But not perfect...



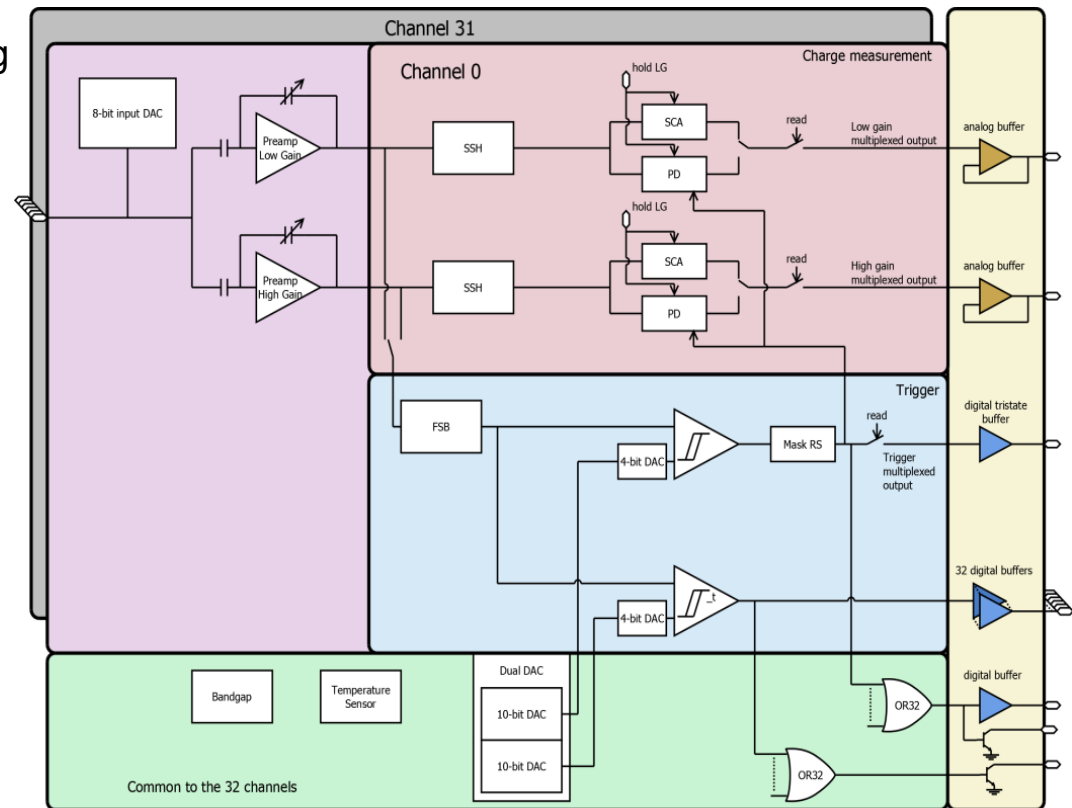III. FE circuits: CITIROC


- CITIROC: voltage mode, analogue and for CTA SSTs ASTRI camera
- Part of Omega/Weeroc family: CITIROC, PETIROC, PETIROC2, TRIROC, etc
- General ASIC
 - 32 channel, charge and trigger outting
 - 6.26mW/Ch. Power pulsed
- Front-end
 - Trigger
 - Fast shaper connected to either low or high gain preamp
 - Two discriminator : one for timing, one for event validation on energy
 - Energy measurement
 - 2 voltage preamplifier (10x gain difference) followed by shaper
 - Analogue memory : track and hold or peak detector
 - Analogue multiplexer
 - **Peaking time between 12.5 and 100 ns**
 - **Valid only for SSTs**



<https://www.weeroc.com/fr/products/citiroc-1a>

III. FE circuits: CITIROC

SAMPLING & HOLD Vs. PEAK DETECTION

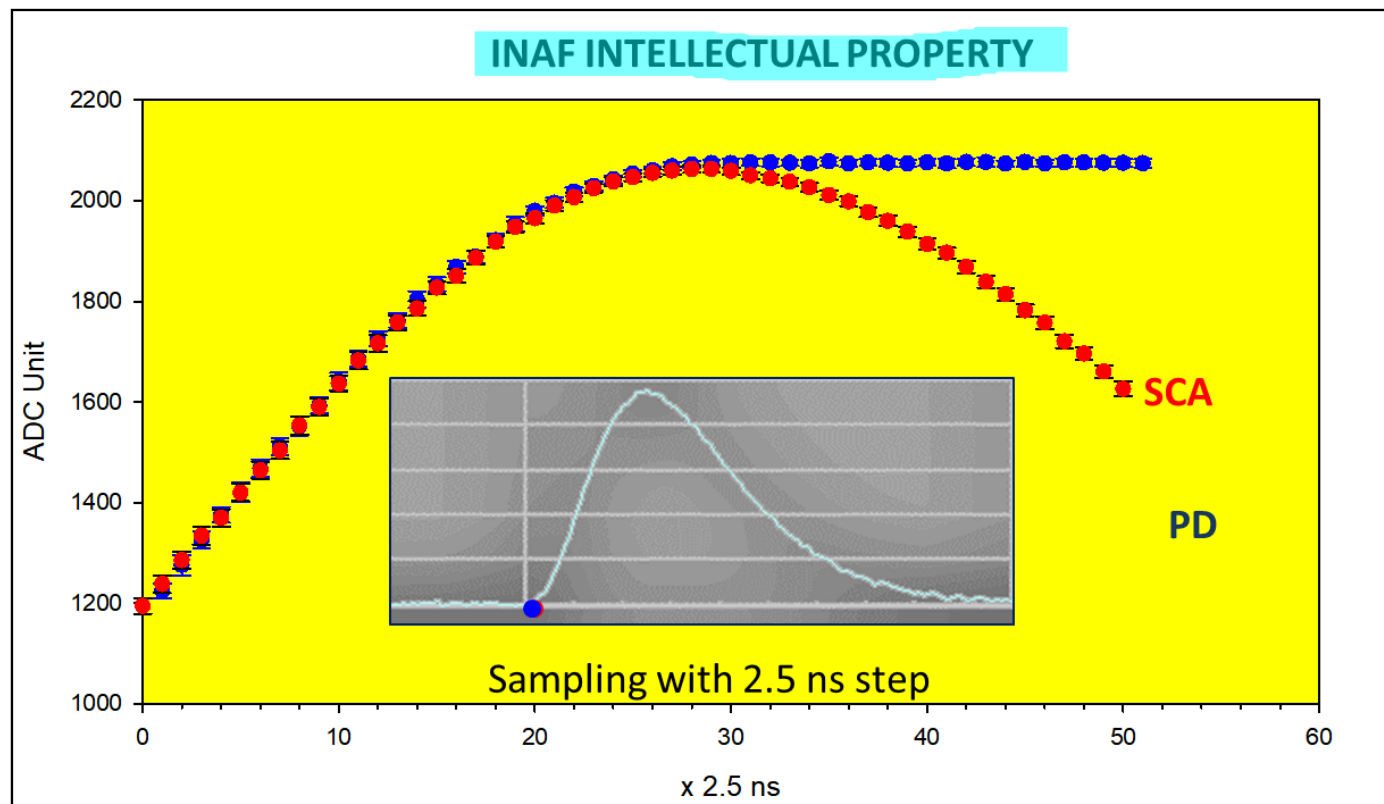

Same pulse measured in SCA and PD mode as a function of delayed HOLD

<https://www.weeroc.com/fr/products/citiroc-1a>




CITIROC SCHEMATIC DIAGRAM



Trigger

HG


LG

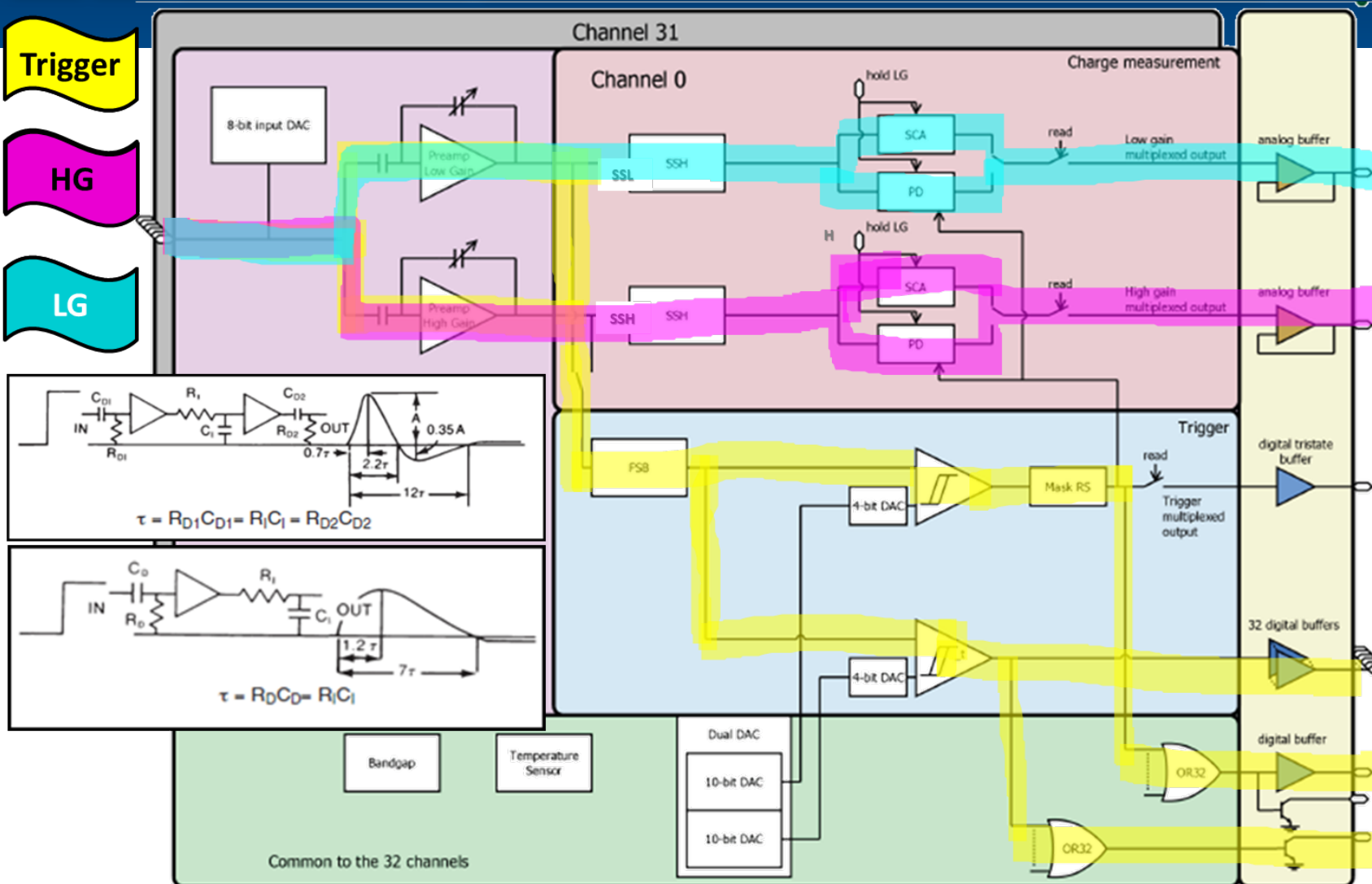

Osvaldo Catalano– 3rd SiPM Advanced Workshop- Palermo 26-28 May 2015



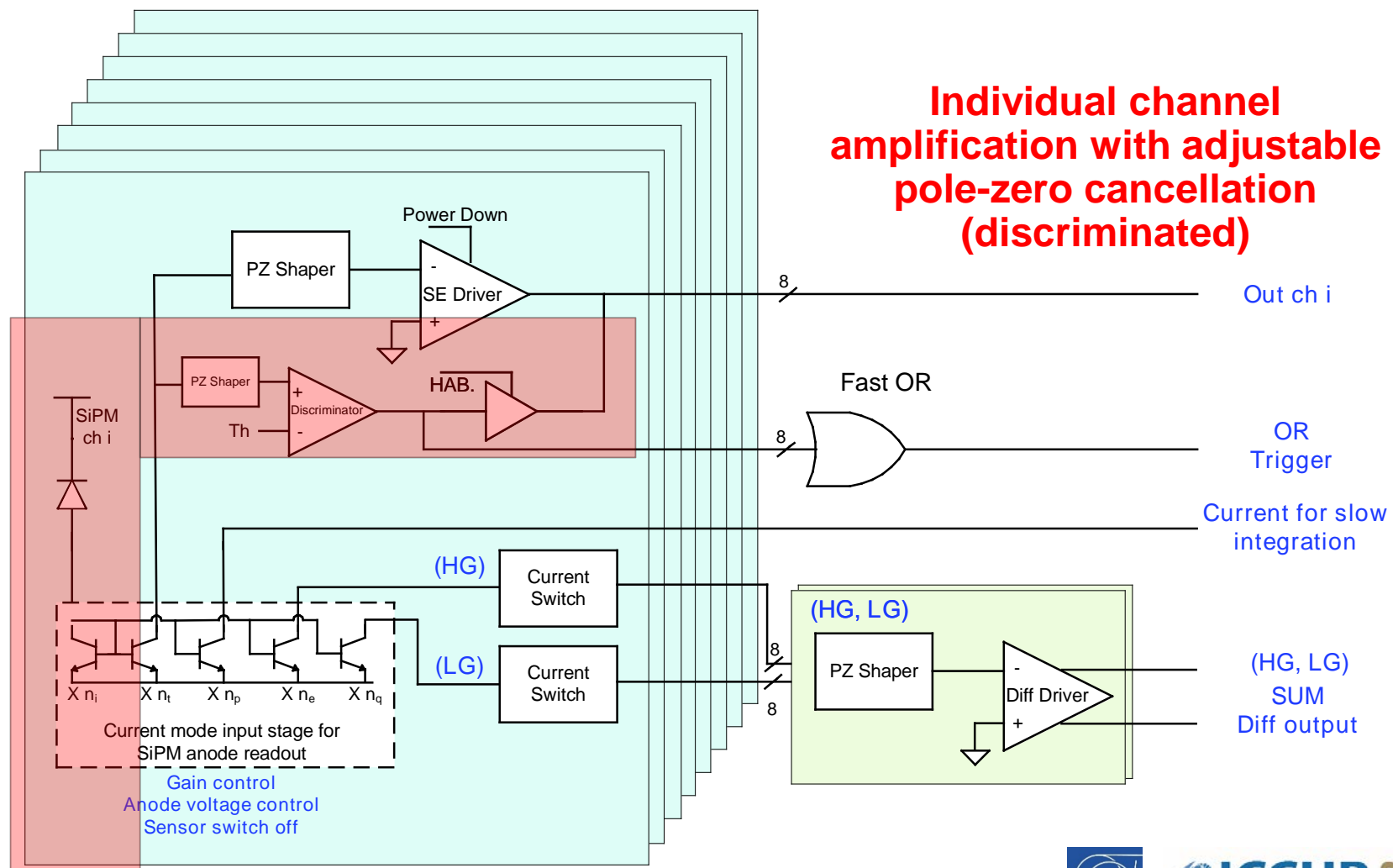
III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- MUSIC 8 ch ASIC integrates all those functionalities



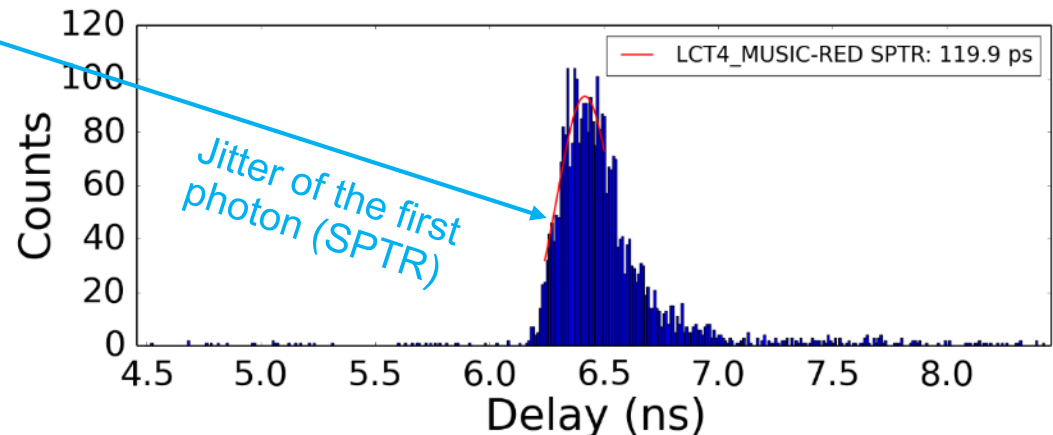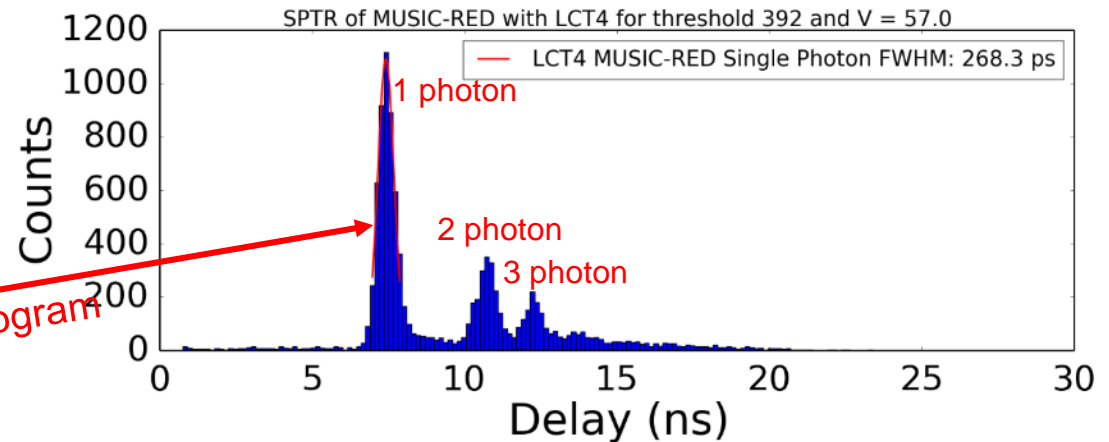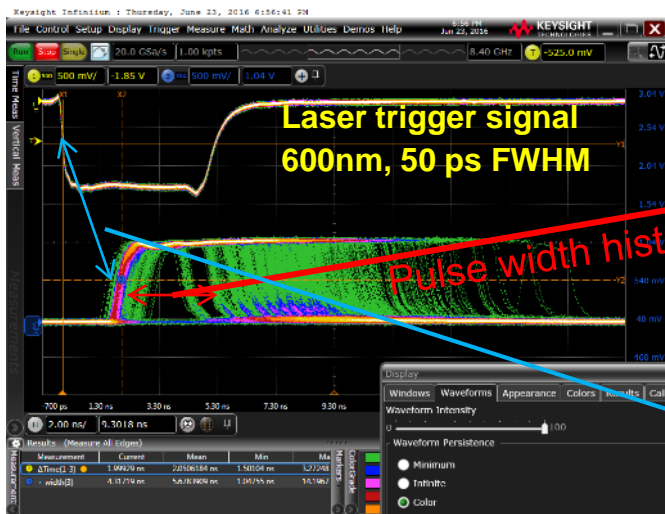
III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- Output for a LCT4 HPKK MPPC (3x3 mm²)
 - Picosecond laser
 - Pole-zero cancellation
 - Single Photon Time Resolution about 100 ps (@ 5V OV)




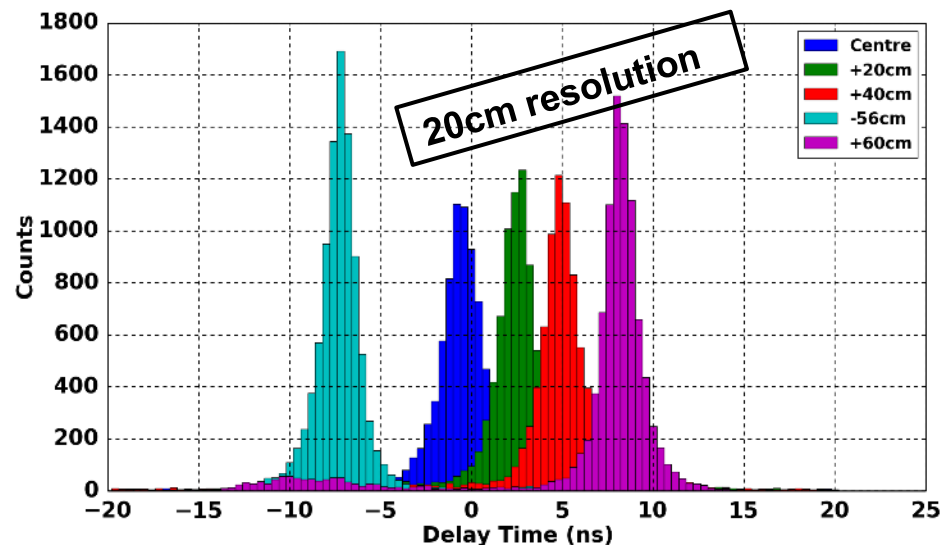III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- Studying the possibility to develop a beam loss monitoring system based on scintillating fibers
 - Collaboration with Alba synchrotron General idea:
 - Fiber along the beam pipe or in selected regions
 - Losses are detected by a rate increase
 - With timing information, additional position information
 - Preliminary results: 20 cm resolution for a 2 m fiber of 1 mm diameter



IV. ASICs for PET: PETIROC

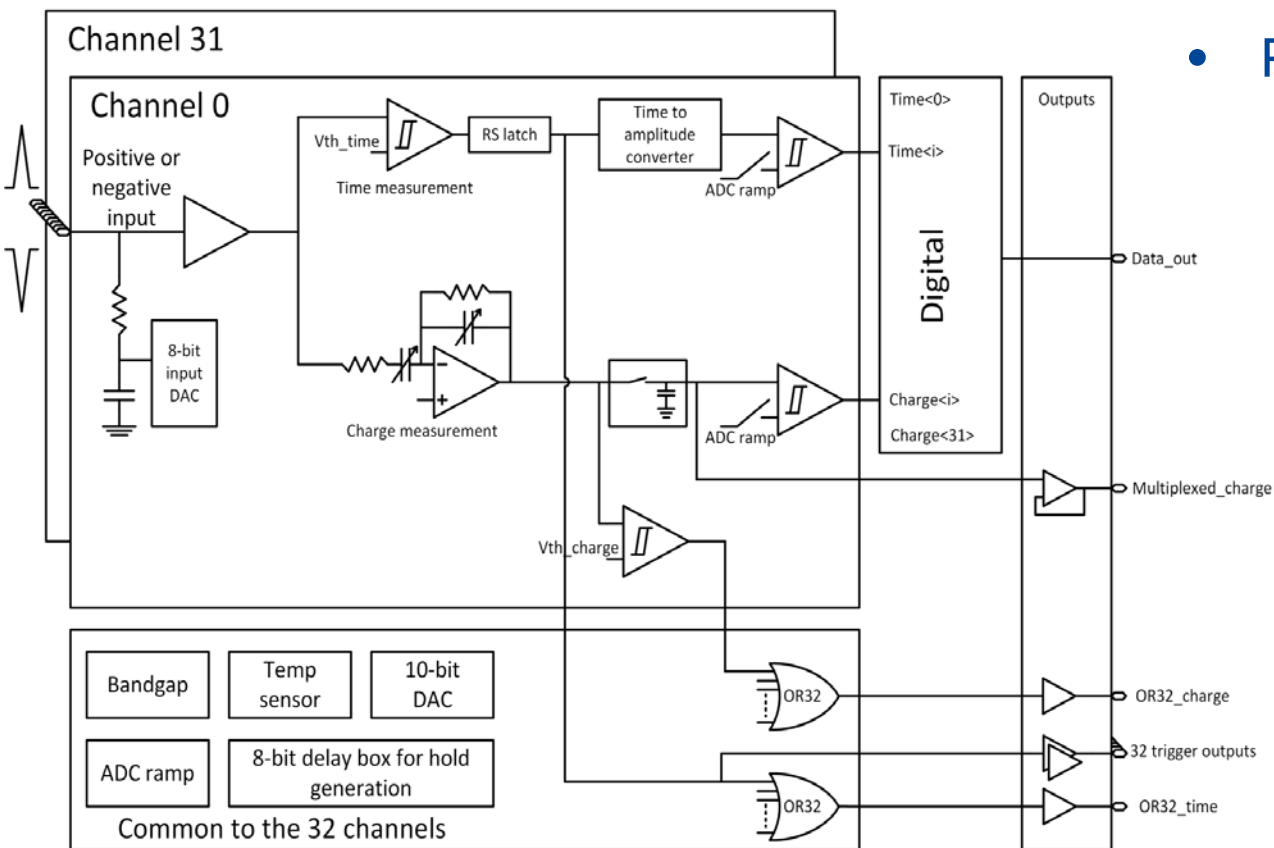

• PETIROC2:

- Voltage mode,
- Configurable: analogue, binary or digital
 - S&H + Wilkinson ADC
- For medical imaging (PET)
- Versatile: analog or digital
- But shaping time > 10 ns
- Max ev. rate is 40 KHz in digital mode
- Power:

<https://www.weeroc.com/fr/products/petiroc-2a>

Detector Read-Out	SiPM, SiPM array
Number of Channels	32
Signal Polarity	Positive or Negative
Sensitivity	Trigger on first photo-electron
Timing Resolution	~ 35 ps FWHM in analogue mode (2pe injected) - ~ 100 ps FWHM with internal TDC
Dynamic Range	3000 photo-electrons (10 ⁶ SiPM gain), Integral Non Linearity: 1% up to 2500 ph-e
Packaging & Dimension	TQFP208 – TFBGA353


IV. ASICs for PET: TOFPET

- Pre-amplifier: low input impedance current conveyor
- Two post-amplifiers (TIA) for time and energy measurements
- Three leading edge discriminators;
 - Very low threshold (1-5 p.e.) for optimum PET time resolution
 - multi-level event rejection

- Time to Amplitude Converter (TAC)
- Charge Integrator (CI)
 - configurable integration windows
 - linear amplitude measurement
 - TAC and Charge Integrator are quad-buffered
 - No dead-time due to Poisson fluctuations

- Two 10-bit ADCs per channel
 - Time and amplitude measurements
 - Optionally: Time-over-Threshold

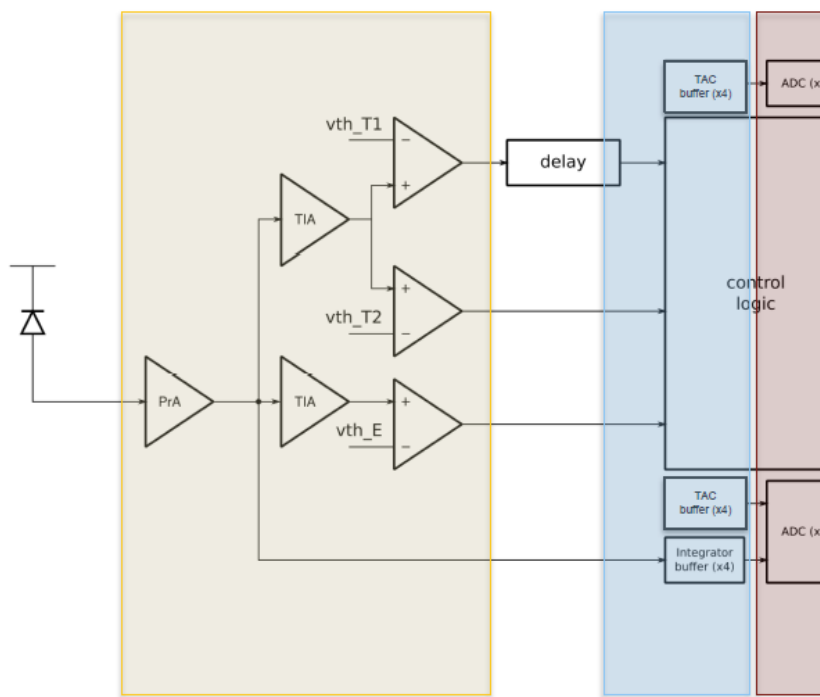- TOFPET2: current mode, digital (linear ToT) and for medical imaging (PET)
 - Power: 8 mW/ch
 - Max rate 200 KHz/ch




J. Varela, "New results with TOFPET2", FAST, Ljubljana, Jan 2018


IV. ASICs for PET: STiC

- STiC: current mode, digital (linear ToT) and for medical imaging (PET)

STiC 2.1
[on test PCB]

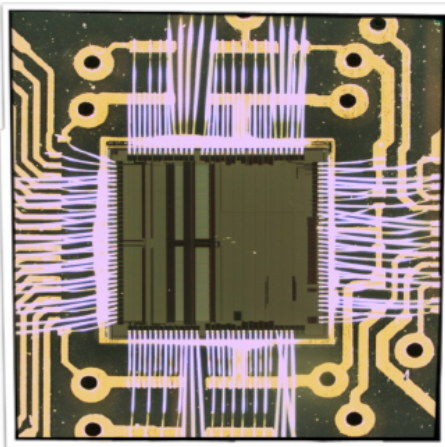

STiC 3.0
[Chip layout]

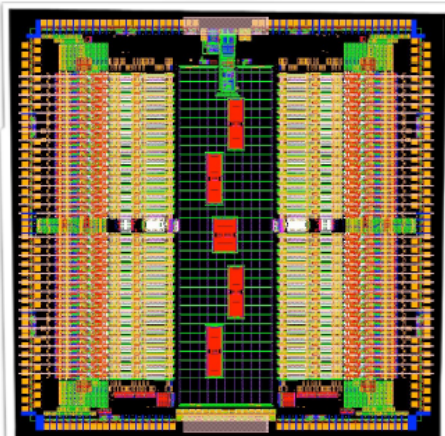

Features:

STiC 2.1: 16 channels

STiC 3.0: 64 channels

Differential and
single-ended readout ...

Integrated TDC [ZITI, Fischer et al.]
and digital data processing ...

Timing and ToT-based
linearized energy measurement ...
[SPTR:180 ps; MPPC S10362-11-100]


SiPM bias tuning ...
[Tuning range: ~ 500 mV]

Serial interface for data
transmission and configuration ...

STiC — a mixed mode silicon photomultiplier readout ASIC for time-of-flight applications
T. Harion et al., 2014 JINST 9 C02003

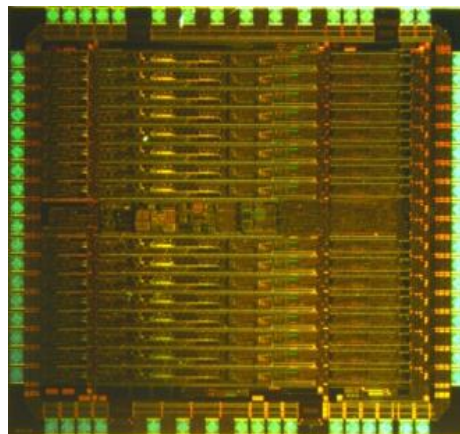IV. ASICs for PET: FlexToT: linearized ToT RO chip

- Joint project with CIEMAT to develop a time-over-threshold ASIC for SiPM based PET
 - ICCUB: expertise on electronics and microelectronics design for detector FE
 - CIEMAT: expertise on PET and medical imaging instrumentation



FlexToT

16 channel

SiGe BiCMOS 0.35um

Austriamicrosystem

10 mm²


3.3 V (10 mW/ch)

QFN 64

IV. ASICs for PET: FlexToT: linearized ToT RO chip



• Spectroscopy with linear ToT

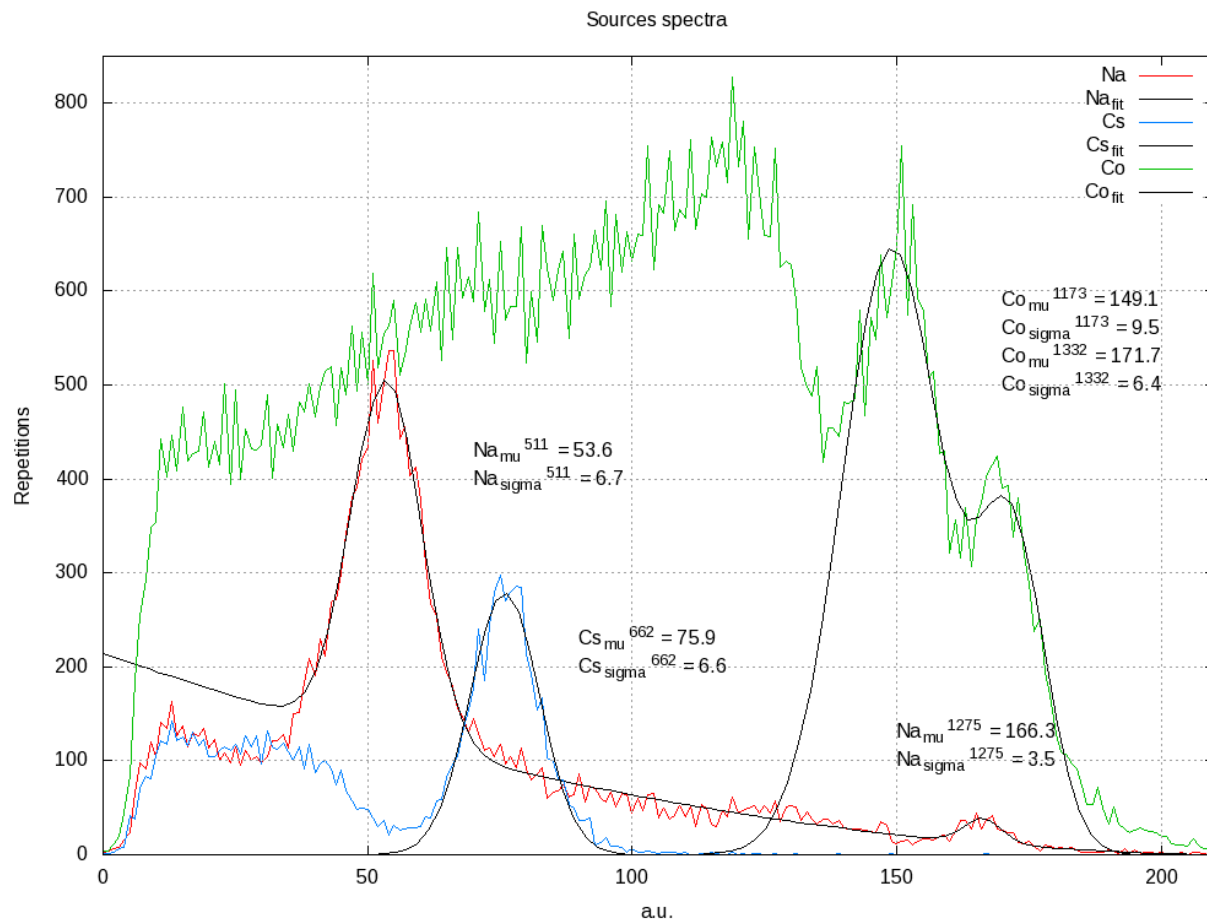


Outlook

- I. Introduction
- II. SiPM model
- III. FE circuits
- IV. Digitization**
- V. System-On-Chip (SoC)
- VI. Emerging technologies

III. Digitization: basic options


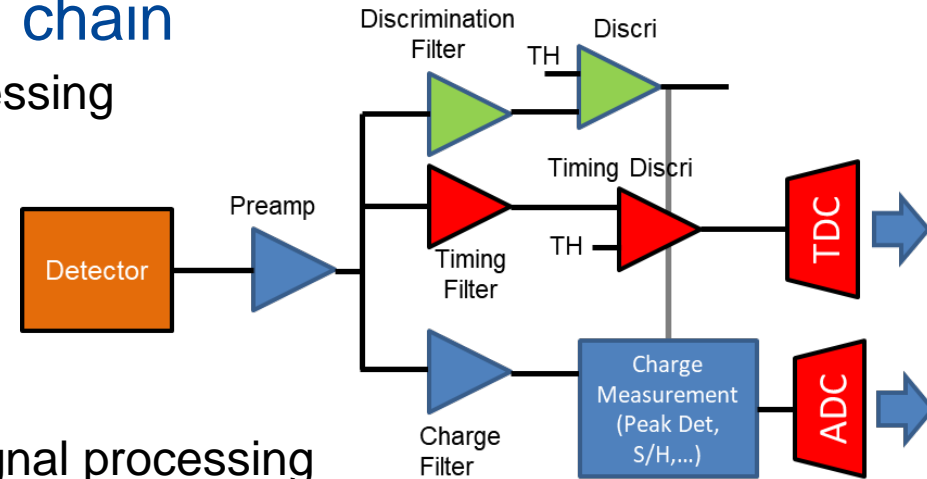
1) “Classical” signal processing chain

- Requires complex analogue processing
- Not so flexible
- Optimal in power for specific app.



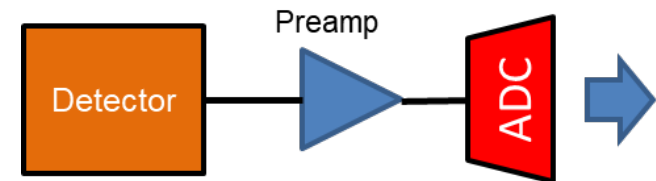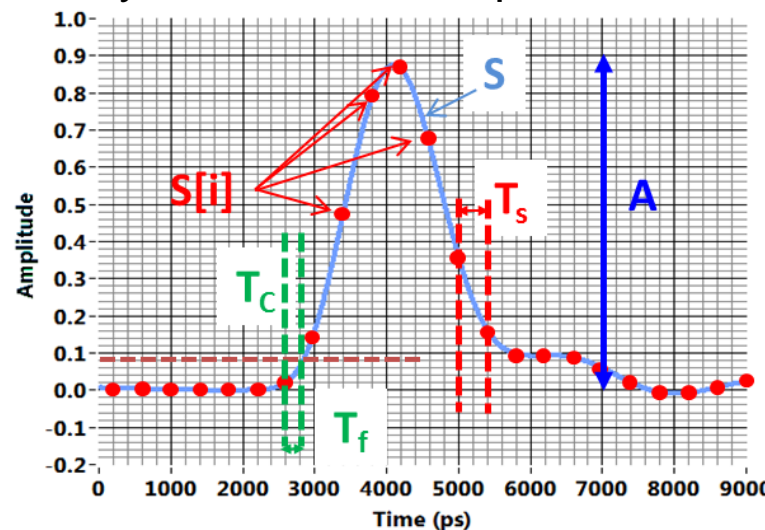2) Digital signal processing


- Waveform sampling and digital signal processing
- Ideally one should sample at $f_s > 2 \times \text{signal BW}$ (x5)



E. Delagnes, “Precise Pulse Timing based on Ultra-Fast Waveform Digitizers”, IEEE NSS 2011

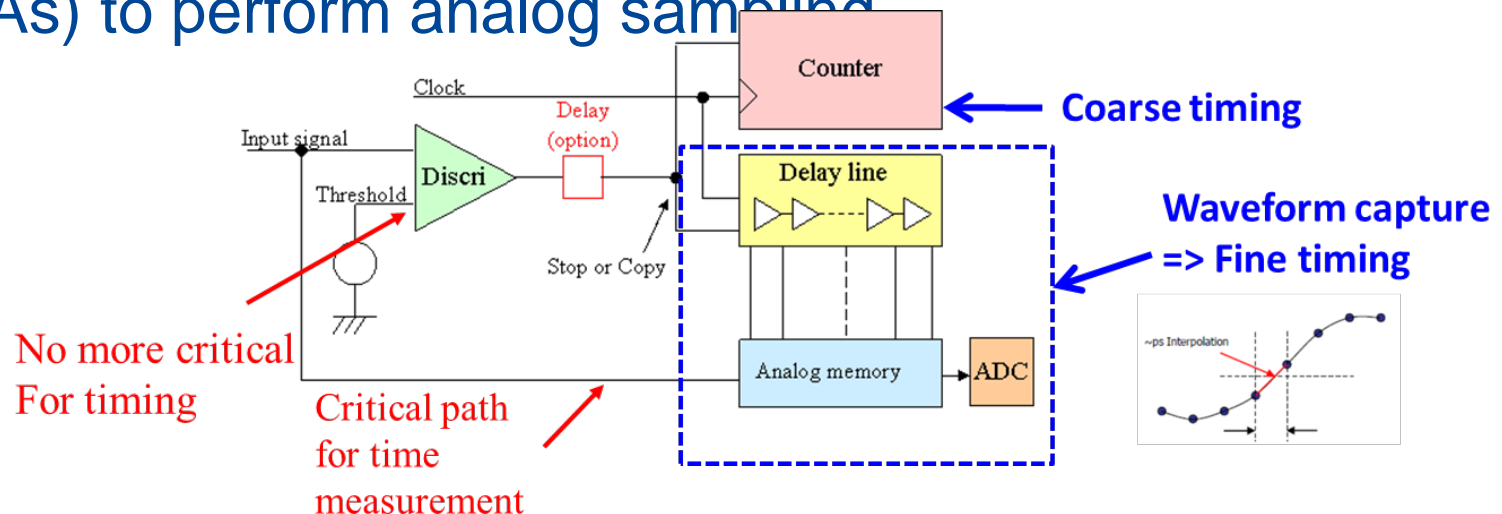III. Digitization: waveform sampling

- Very demanding sampling specs for IACTs
 - Dynamic range of about 12 bits (with several gains)
 - Analog BW > 300 MHz requires 1-2 GS/s
 - Power consumption and ADC cost !
 - Alternative: FlashCAM digitizes at much lower speed and tries to extract signal parameters by signal processing
 - But NSB will be there anyway, so energy threshold will be degraded...
- Many projects have been using Switch Capacitor Arrays (SCAs) to perform analog sampling




E. Delagnes, "Precise Pulse Timing based on Ultra-Fast Waveform Digitizers", IEEE NSS 2011

III. Digitization: waveform sampling

- SCAs sample the signal which is digitized at a lower speed



Switched Capacitor Array (Analog Memory)

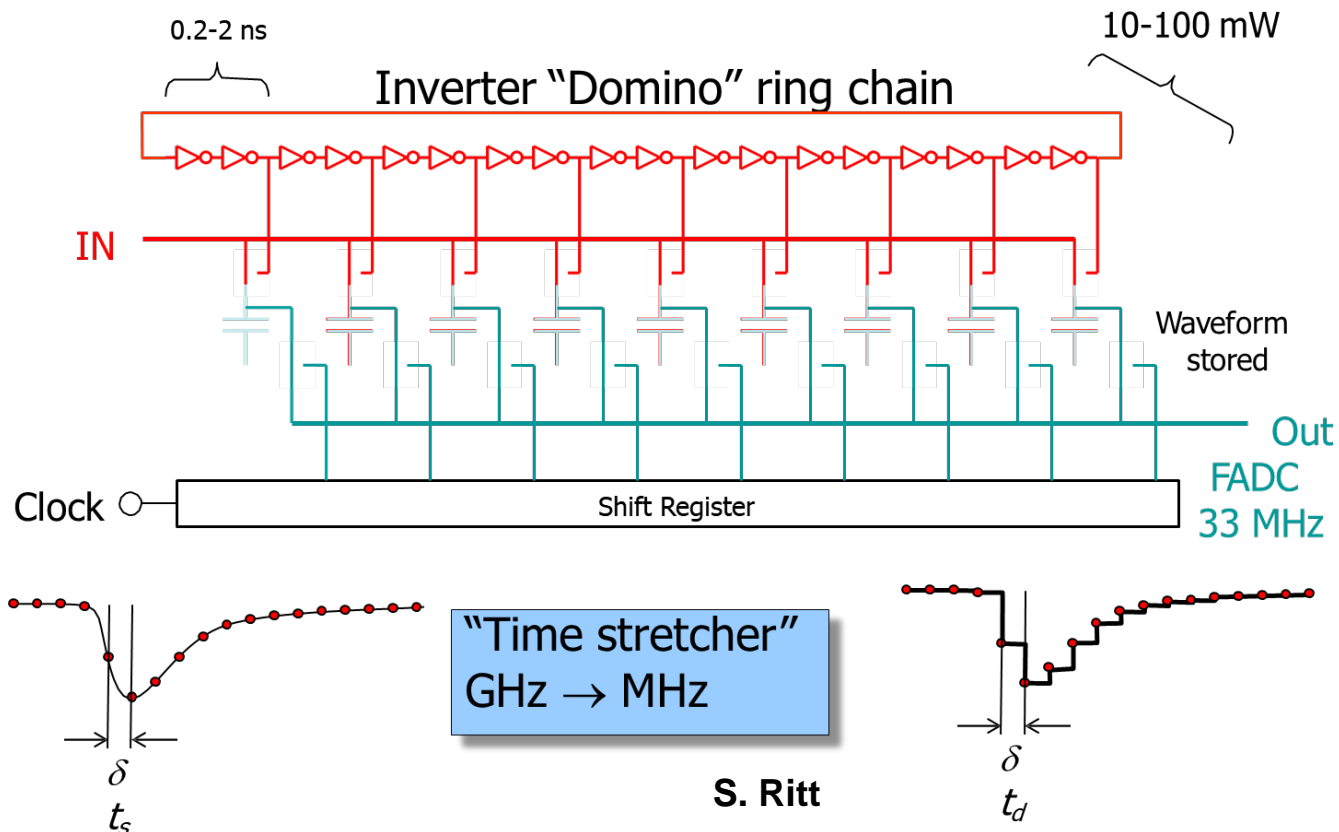

III. Digitization: waveform sampling

G. Varner Univ. Hawaii




TARGET 
CTA SCT and SST


Many chips for different projects
Buffered and unbuffered
Very deep arrays
ADC on chip.
Philosophy => pushing the
limit of the SCA technology




Straw3

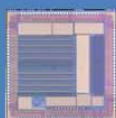


Labrador

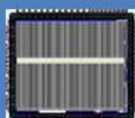

Labrador3

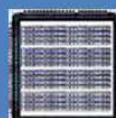

Target

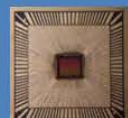

BLAB family

H. Frisch et al., Univ. Chicago



ps family

Goal: reach a 1ps precision !
Pioneering R&D work
130nm IBM
18 GSPS, 256 samples, 6ch
ADC on chip

Initiator of a
networking
activity on SCAs
and ps-timing

S. Ritt, R. Dinapoli PSI



Universal chip for many applications
8 + 1 channels 1024 cells
5GSPS, 950 MHz BW
Low power consumption
Short readout time
Several possible modes of operation




DRS1



DRS2



DRS3

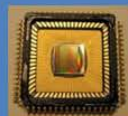

DRS4

DRS4
CTA LST

D. Breton IN2P3/LAL
E. Delagnes CEA/Saclay



NECTAr
CTA MST-
NECTArCAM




ARS



MATAcq



SAM family

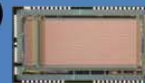


Nectar

More than 120.000 SCAs operating worldwide
Buffered (f_{3dB} 400-500MHz) 3.2GSPS
High dynamic range
Robust (minimum calibration or ext. control)
Conservative technologies
Moderate depth 256-1024 cells/ 2ch
On-chip ADC in the last chip

E. Delagnes, "Precise Pulse Timing based on Ultra-Fast Waveform Digitizers", IEEE NSS 2011

III. Digitization: waveform sampling

SAMPIC Waveform TDC

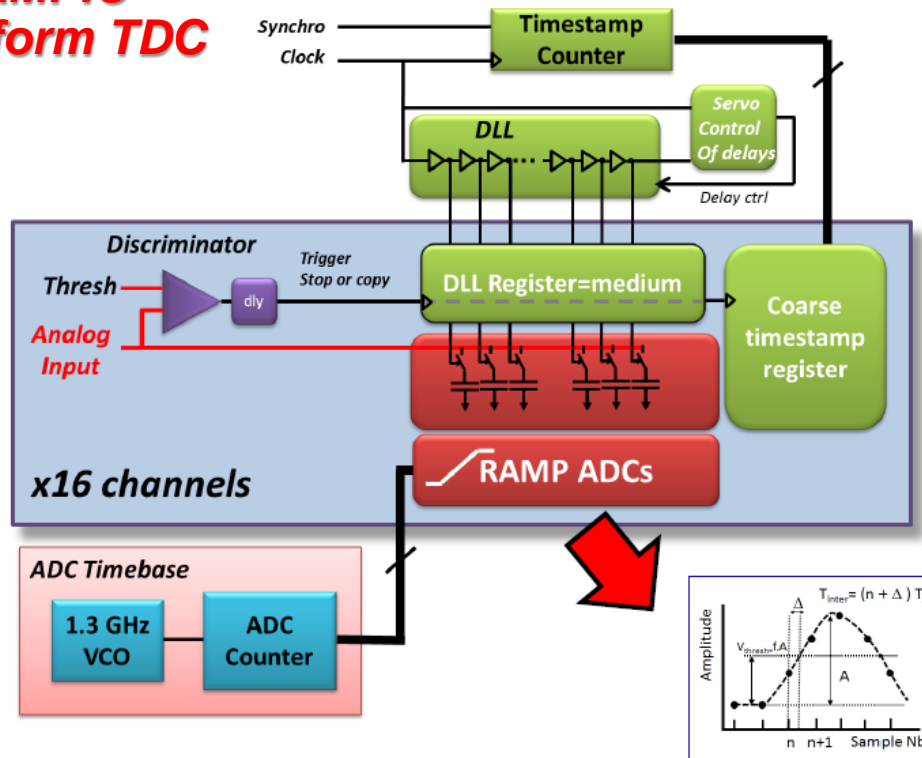

Global time = counter ($\sim 10\text{ns}$) + DLL ($\sim 100\text{ps}$) + waveform ($\sim \text{ps}$)

Waveform is available for extraction of other parameters (Q, A)

- **One Common 12-bit Gray Counter** (FClk up to 160MHz) for Coarse Timestamping.

- **One Common servo-controlled DLL:** (from 1.6 to 10.2 GHz) used for medium precision timing & analog sampling

- **16 independent WTDC channels each with :**

- ✓ 1 discriminator for self triggering
- ✓ Registers to store the timestamps
- ✓ 64-cell deep SCA analog memory
- ✓ One 11-bit ADC/ cell

(Total : $64 \times 16 = 1024$ on-chip ADCs)

- **One common 1.3 GHz oscillator + counter** used as timebase for all the **Wilkinson A to D converters**.

- **Read-Out interface**

- **SPI Link** for Slow Control configuration

D. Breton, 4th FAST WG3/4/5 Meeting, Ljubljana, January 7/8 2018


III. Digitization: waveform sampling

SAMPIC Waveform TDC

SAMPIC_V1 PERFORMANCES


- Power consumption: 10mW/channel →
- 3dB bandwidth > 1 GHz
- Discriminator noise ~ 2 mV rms
- Counting rate > 2Mevts/s (full chip, full waveform),
up to > 10 Mevts/s with Region Of Interest (ROI)

Power
distribution

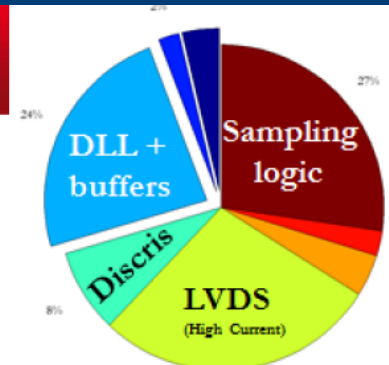


- Wilkinson ADC works with internal 1.3 GHz clock

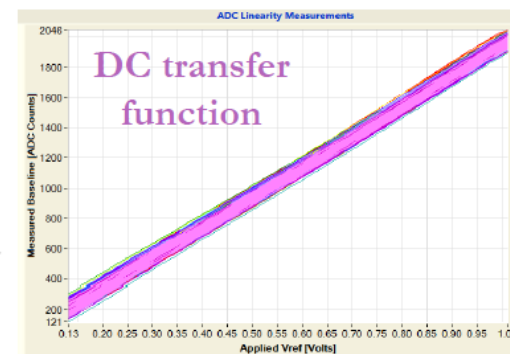- Dynamic range of 1V
- Gain dispersion between cells ~ 1% rms
- Non linearity < 1.4 % peak to peak
- After correction of each cell (linear fit):
noise = 0.95 mV rms



Ex: TDR @ 6.4 GS/s

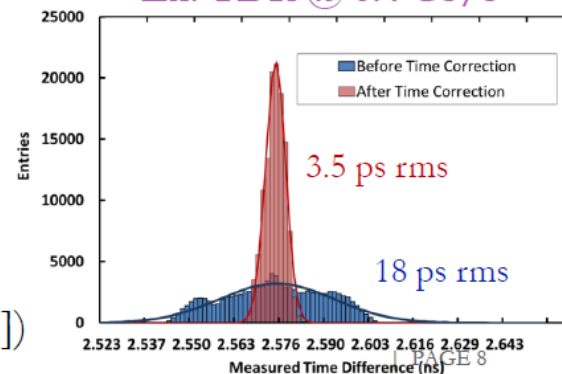


D. Breton, 4th FAST WG3/4/5 Meeting, Ljubljana, January7/8 2018

III. Digitization: waveform sampling

- CHEC camera is an interesting example of compact readout

CTA Application for TARGET

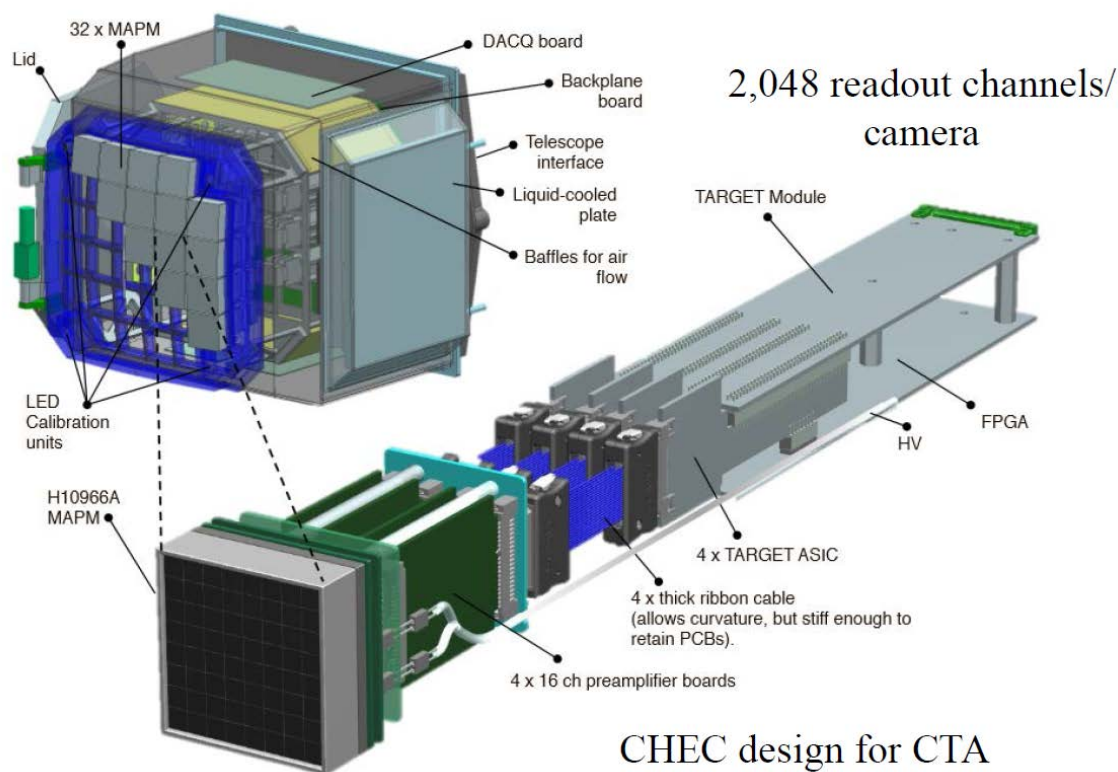

CHEC design for CTA



Gary S. Varner, 2nd Adv SiPM Workshop, Geneva, 2014

III. Digitization: waveform sampling

- Several iterations to have a functional chip: TARGET7

TARGET7 Specification Summary

16384	samples/chan (16-32us trig latency)
16	channels/TARGET ASIC
$\Sigma 4 \rightarrow 4$	Trigger channels (indep. Thr/Width)
~9-10	bits resolution (12-bits logging)
32	samples convert window (~32-64ns)
0.5-1	GSa/s
1	word (RAM) chan, sample readout
<10	us to convert 512 samples (at once)
>100	kHz sustained readout (multibuffer)

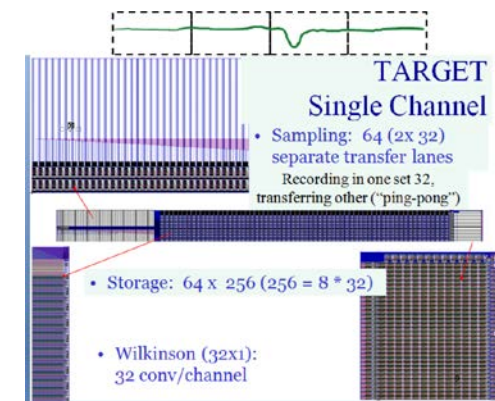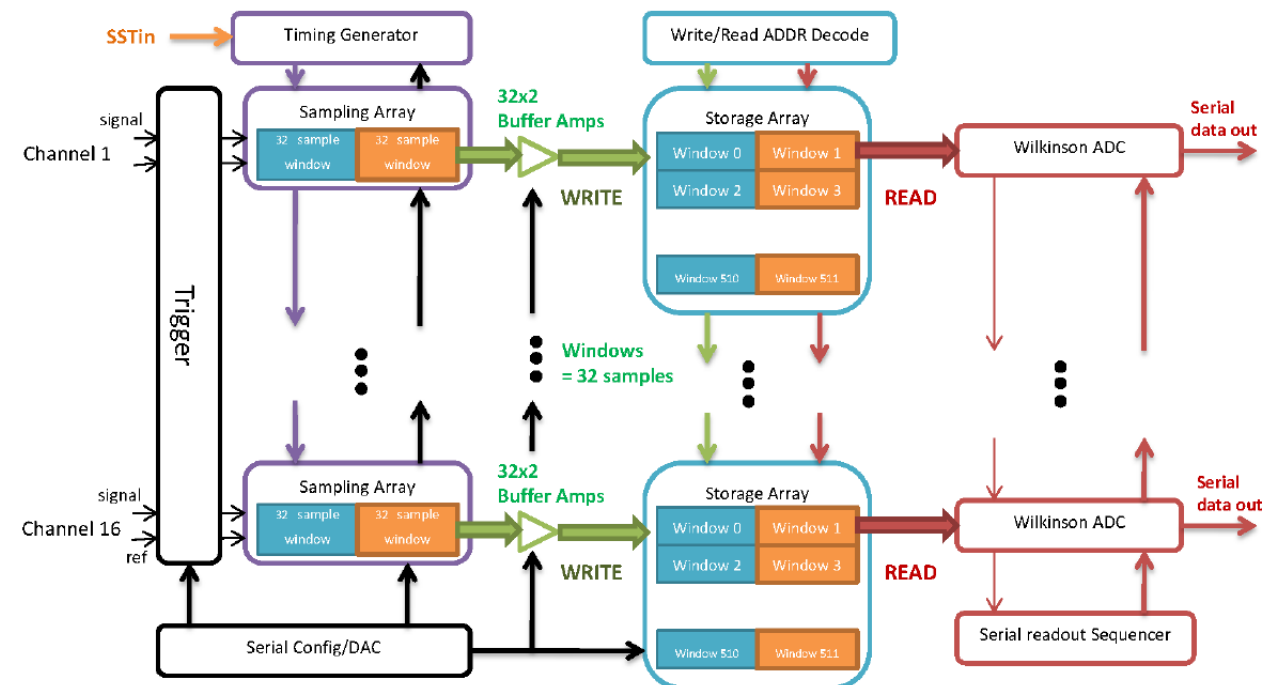


Gary S. Varner, 2nd Adv SiPM Workshop, Geneva, 2014

- I. Introduction
- II. SiPM model
- III. FE circuits
- IV. Digitization
- V. System-On-Chip (SoC)**
- VI. Emerging technologies

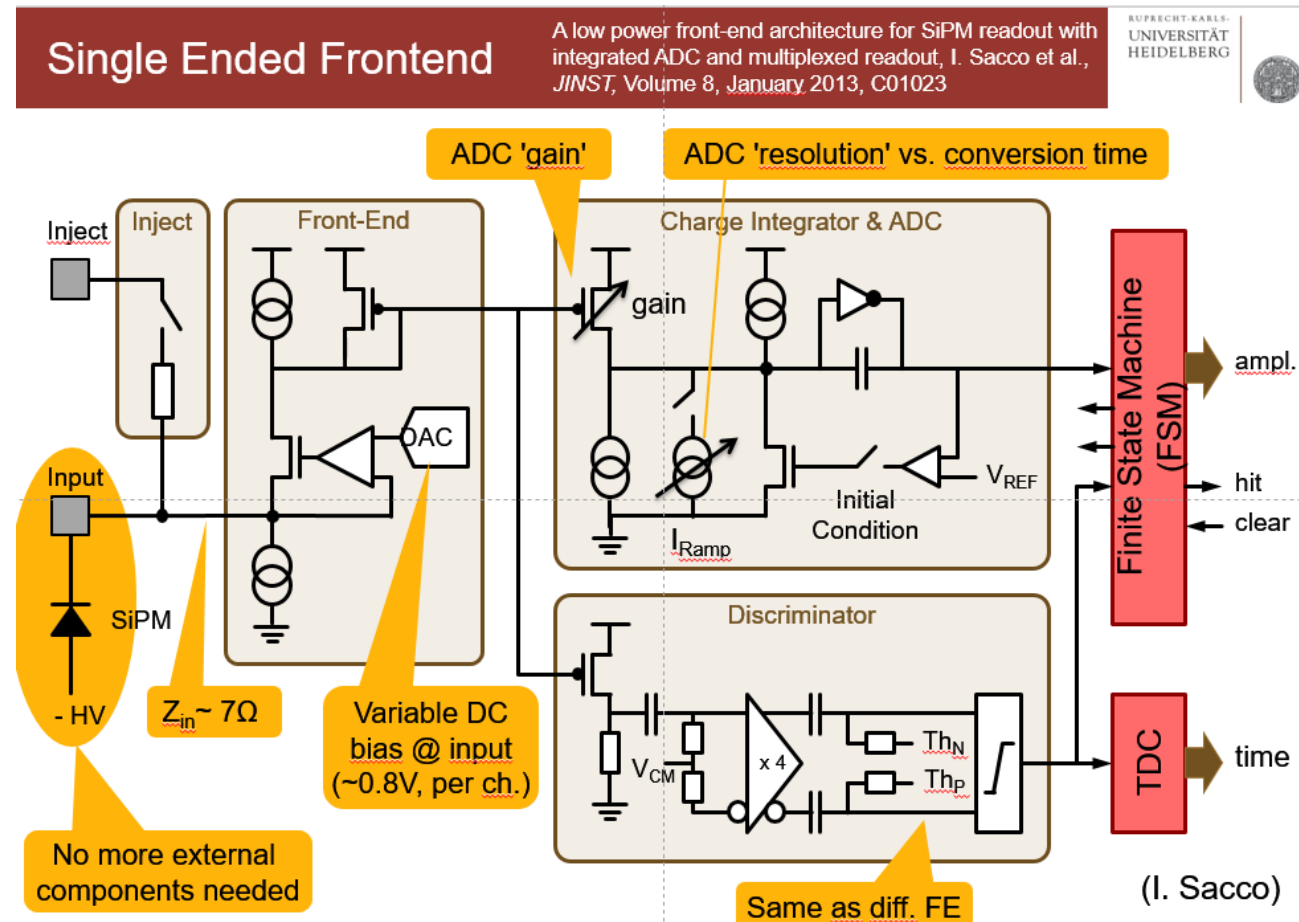IV. ASICs for PET: PETA


- PETA: current mode, charge (ADC) and time (TDC), for PET
 - Choice between Differential FE (both polarities, MRT immune) and Single Ended FE (low Z_{in} , DC bias adjustment, no external coupling parts)
 - Readout rates >200 kHz per channel (in all channels)
 - Power consumption ~30mW / channel



P. Fischer, Heidelberg University, The PETA Chip Family FAST Workshop, FBK 2016

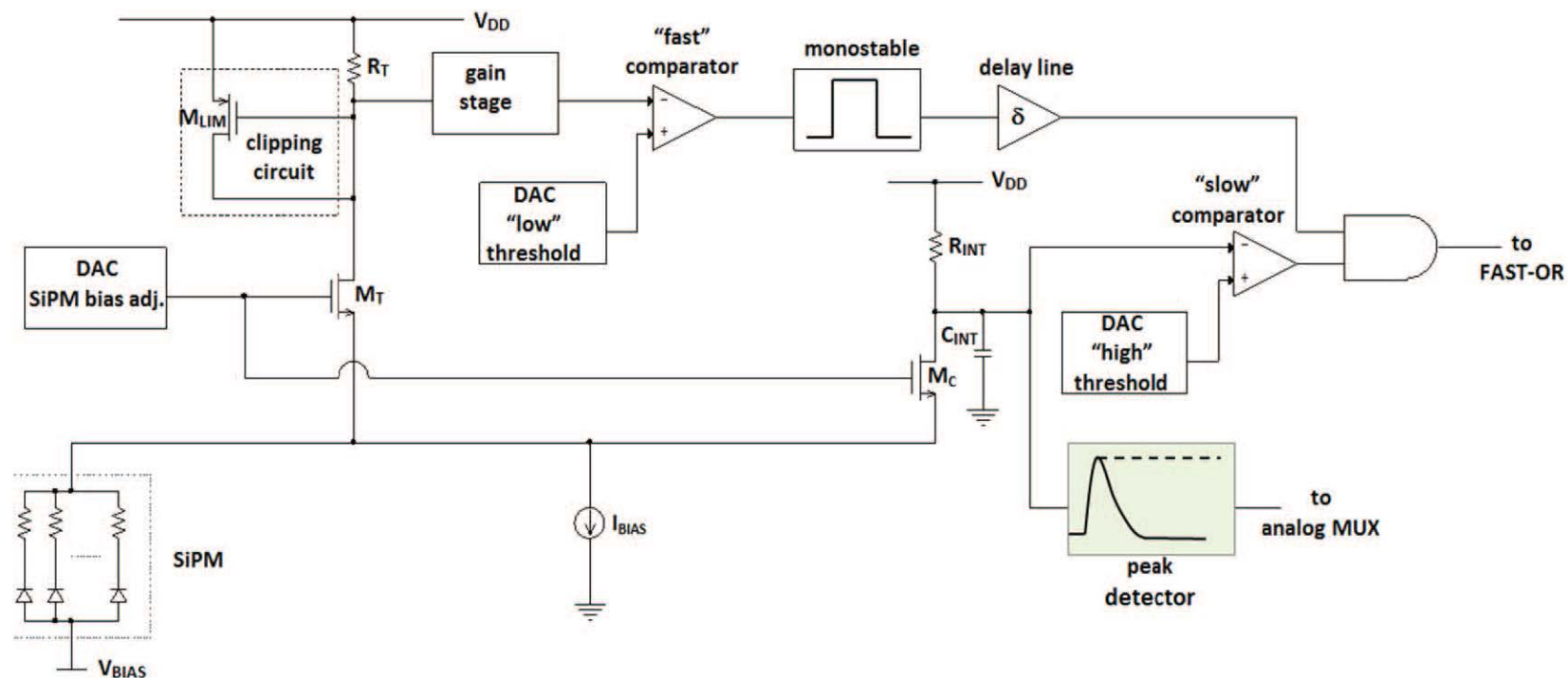IV. ASICs for PET: BASIC64

- BASIC64: current mode, digital (peak detector + ADC) and for PET
 - Power: 10 mW/ch
 - Max rate: 75 KHz/ch
 - No TDC for timing




C. Marzocca et al., "BASIC64: A new mixed-signal front-end ASIC for SiPM detectors," NSS 2016

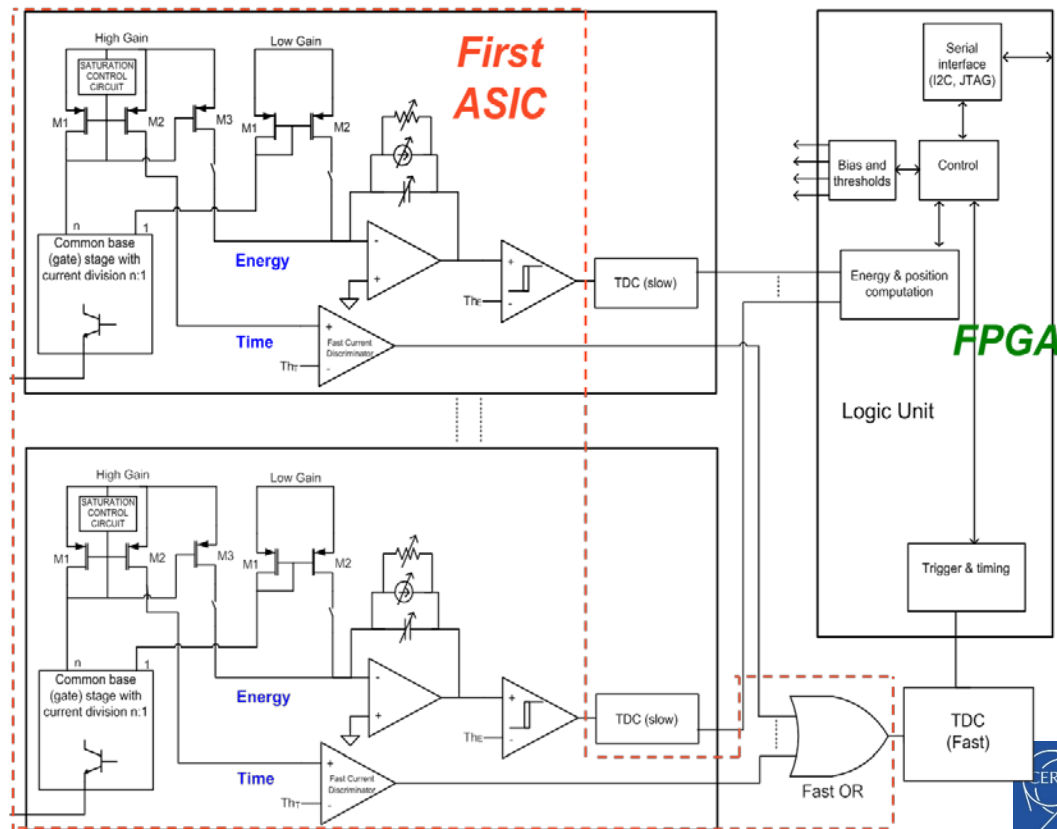IV. ASICs for PET: FlexToT: linearized ToT RO chip

• Why FlexToT is flexible?




- Different scintillator time constants
- Trading-off resolution versus rate
- Accurate analog processing directly connected to FPGA
 - TDCs and signal processing are in FPGA: reconfigurable !



IV. ASICs for PET: FlexToT: linearized ToT RO chip


- No linear ToT may degrade resolution
- Linear ToT is possible
 - Used in Medipix, Timepix, Dosepix ASICs family
 - Also proposed for PET
 - Tuneable feedback current (IFB)

▪ Rate vs resolution

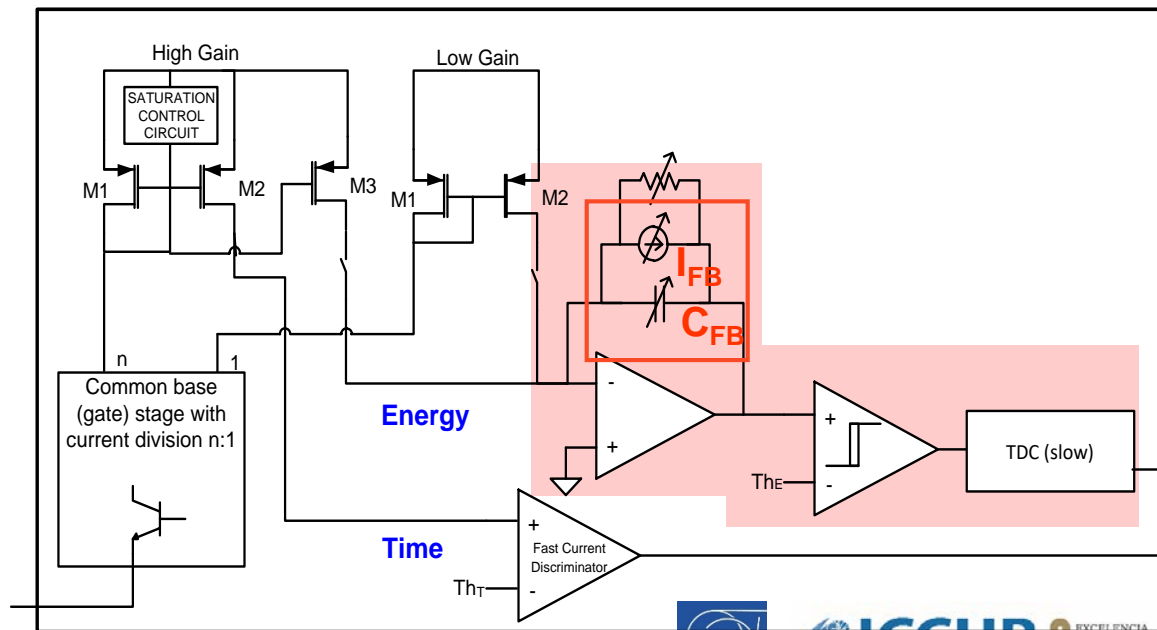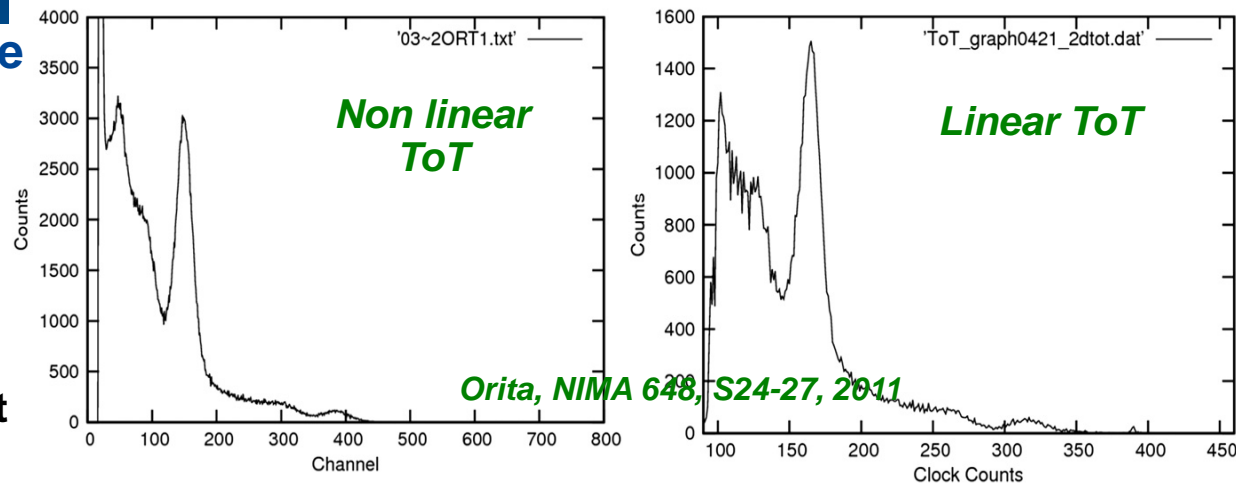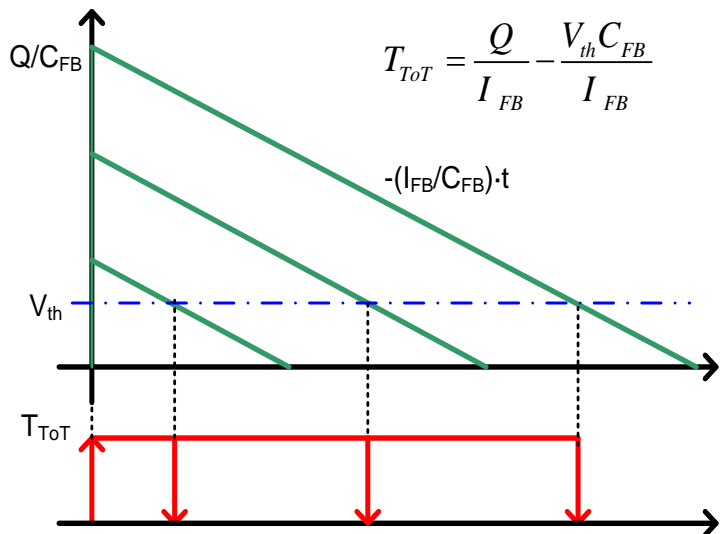


IV. ASICs for PET: HRFlexToT: linearized ToT RO chip

- Preliminary results

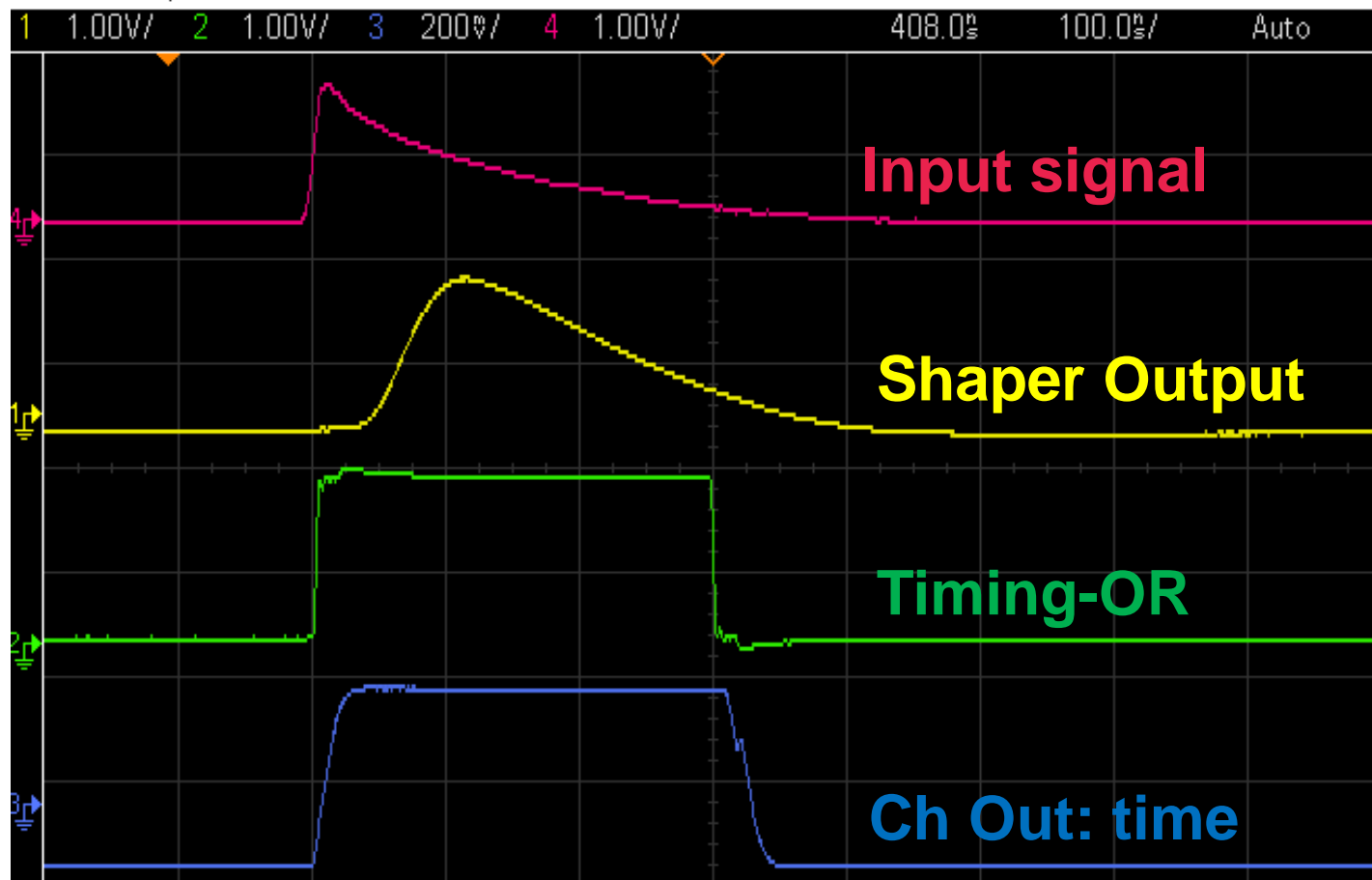


IV. ASICs for PET: HRFlexToT: linearized ToT RO chip

- Preliminary results

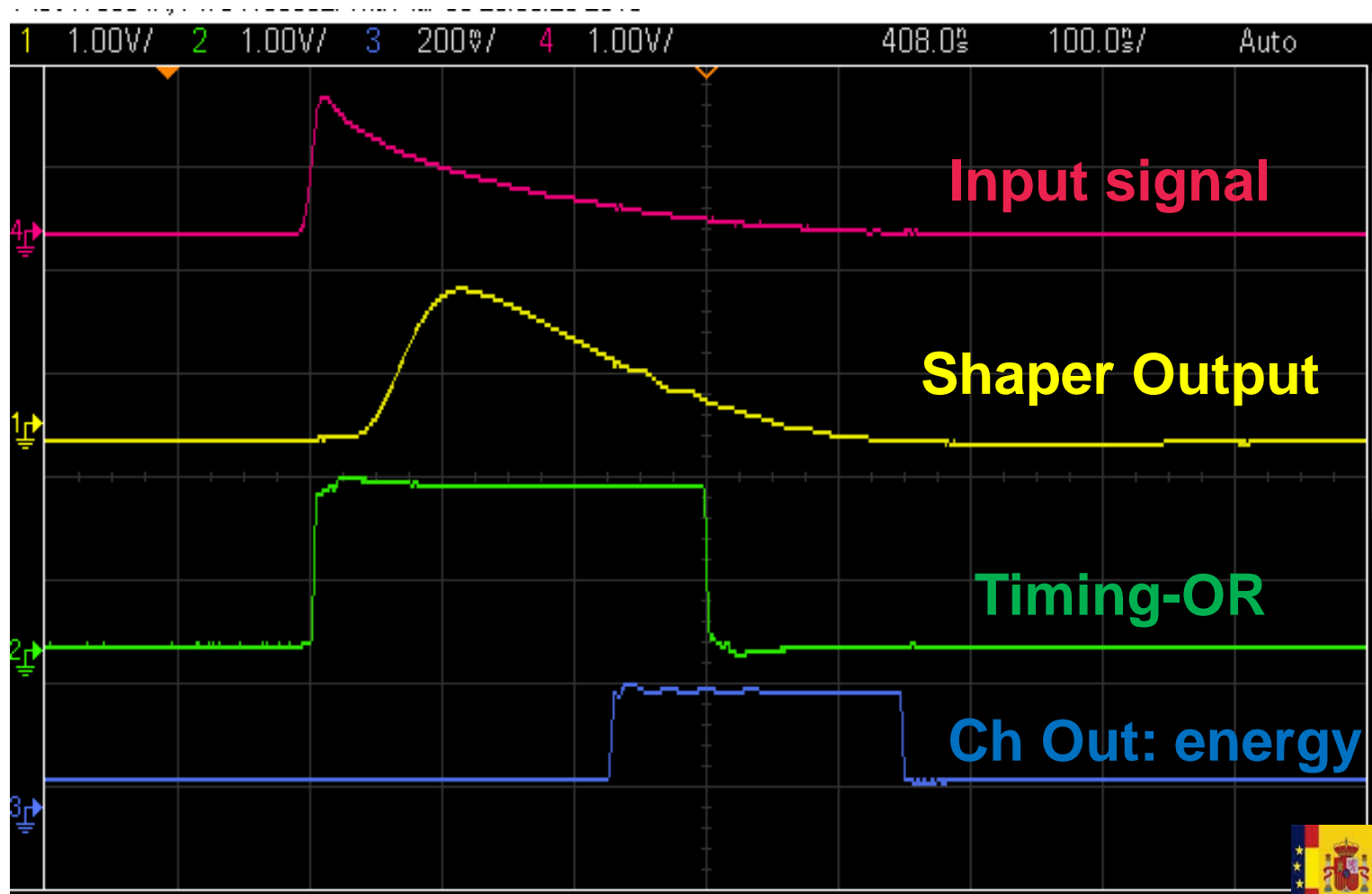

IV. ASICs for PET: HRFlexToT: linearized ToT RO chip


- Preliminary results

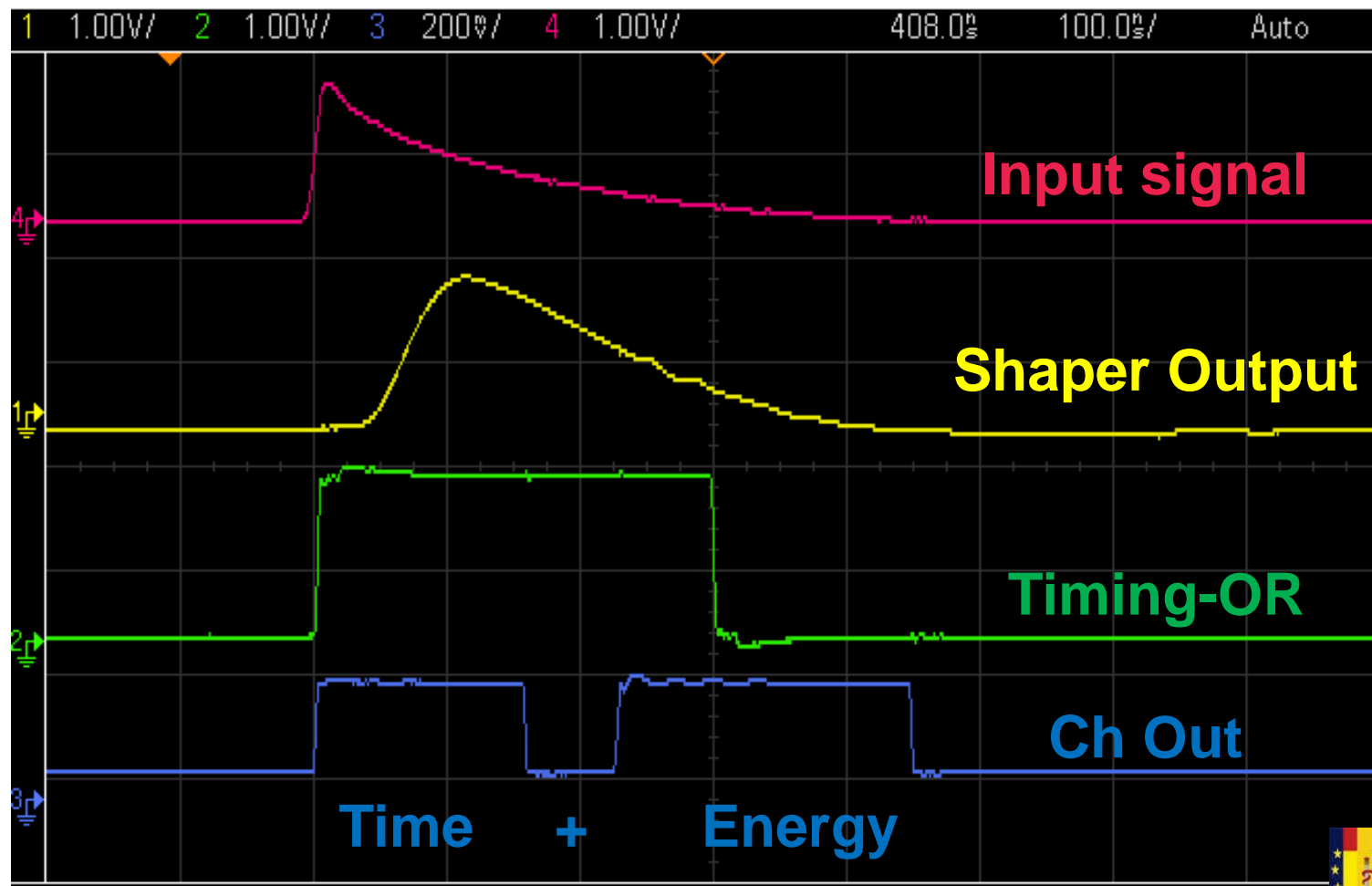

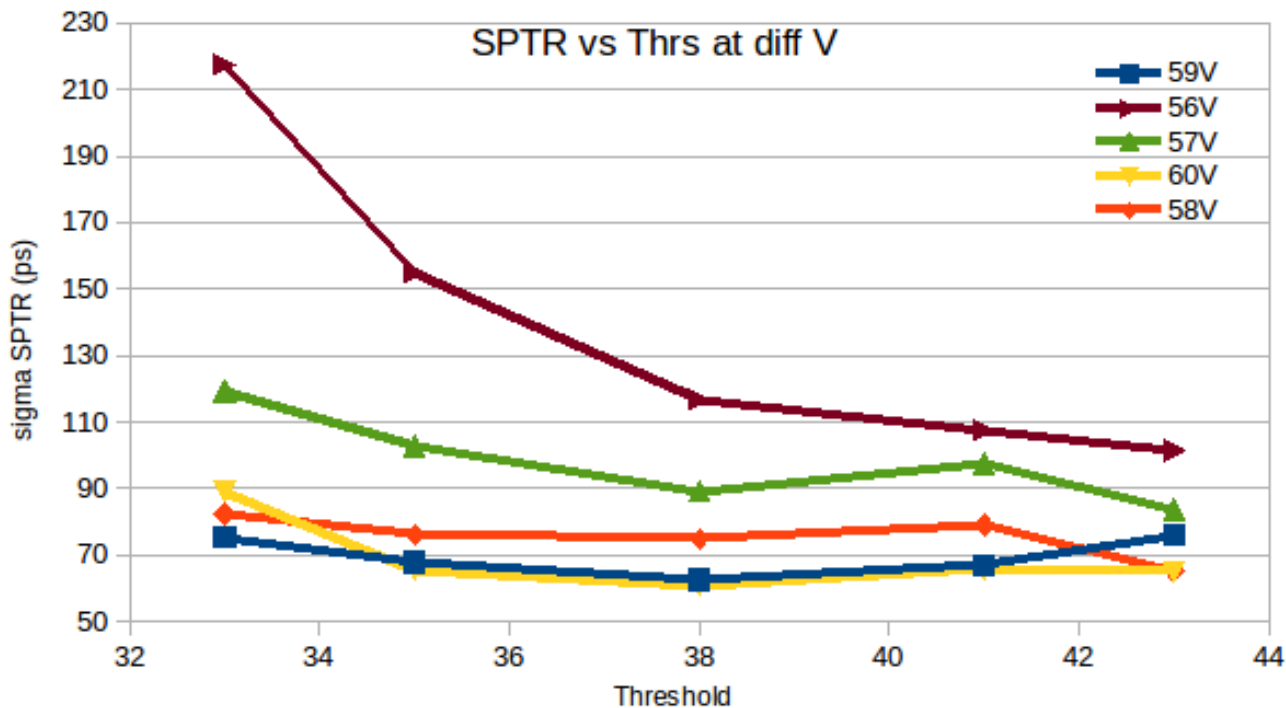IV. ASICs for PET: HRFlexToT: linearized ToT RO chip

- Preliminary result

- **3x3 mm²** HPKK device (75 um) cell, 4 year old.
 - Soon test with more recent devices
- **SPTR** of about 65 ps rms (**150 ps FWHM**)




Inverted logic: low code means high threshold

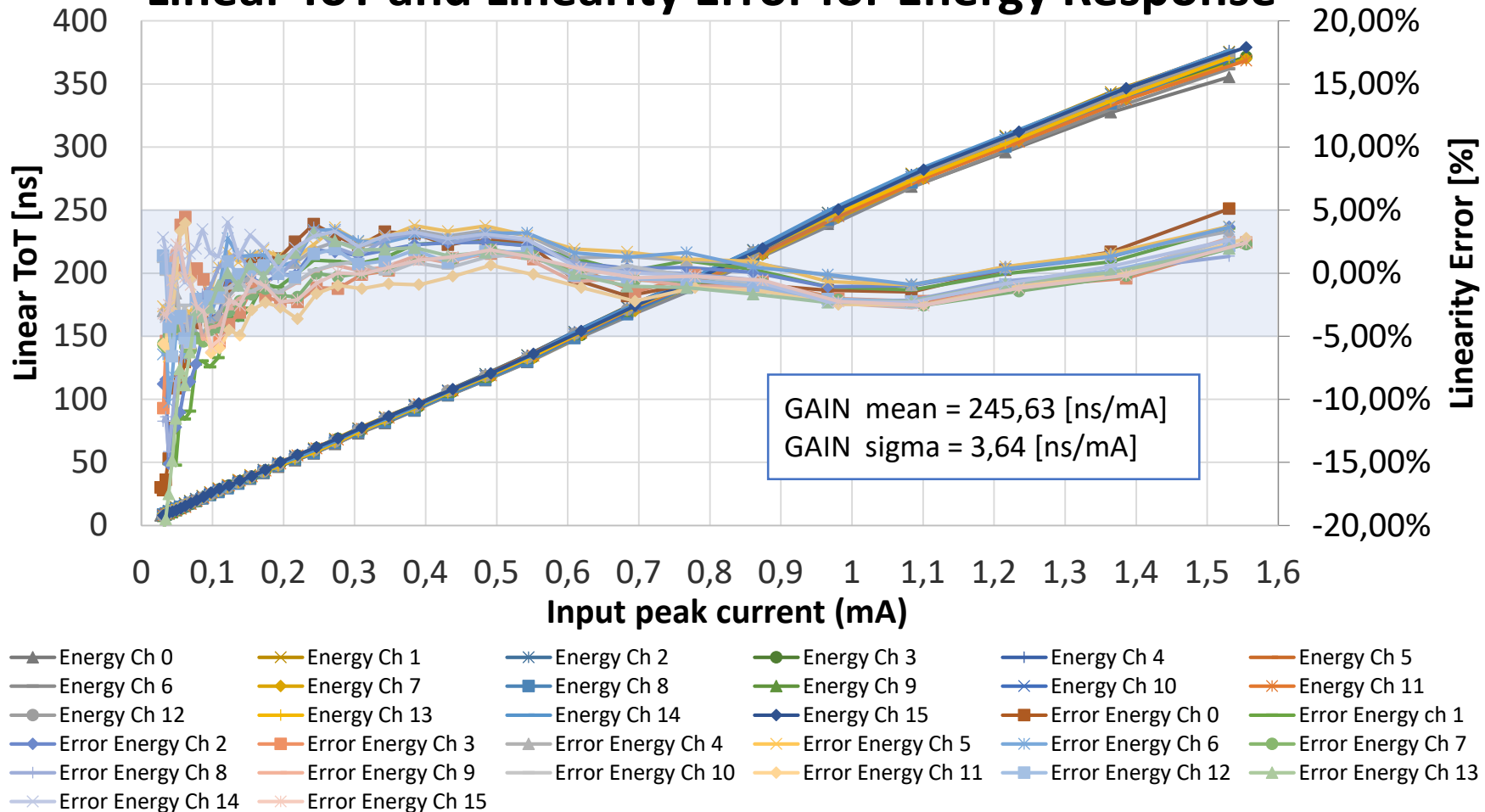IV. HRFlexToT: Linearity analysis: Channel Uniformity

Peak Detector mode and Max Gain (G=3, RL=3)

Linear ToT and Linearity Error for Energy Response



• Maximum current limited by injection system with amplifiers.

14 June 2018

Meeting



IV. ASICs for fast timing: outlook

- In order to improve CTR we need to progress in
 - Crystals: prompt light emission
 - Sensors: SPTR
 - In the the limit, the single SPAD SPTR: 20 ps FWHM ?
- A cost/power effective mixed-mode approach:
 - Use small SiPMs
 - Better SPTR
 - Low power input stage
 - Demonstrated with HRFlexToT chip
 - Fast analog summation
 - Demonstrated with MUSIC chip
 - Multi threshold comparators
 - Provides estimation of the time of arrival of several photons
 - High performance TDCs and synchronization
 - < 10 ps timing resolution demonstrated in 130 nm technology