 




HitDetection ASIC with a CSA Input Stage, an Analogue Memory and a 12 Bit Pipeline ADC - UMC 180 nm Process -

H. Flemming, H. Deppe and P. Wieczorek

GSI Helmholtzzentrum fuer Schwerionenforschung GmbH
Experiment Electronics Department

29. March 2018

Outline

1 HitDetection ASIC Overview



2 Input Stage

3 Analogue Memory

4 12 Bit Pipeline ADC

Outline

  - 1 HitDetection ASIC Overview
 - Design Overview
- 2 Input Stage
- 3 Analogue Memory
- 4 12 Bit Pipeline ADC



- Chip area (4 channels):
 $3250 \mu\text{m} \times 3250 \mu\text{m}$

- Mode of operation

- HitDetection ASIC: Self-triggered analogue transient recorder and a 12 bit pipeline ADC
 - Input stage: differential input buffer or a charge-sensitive amplifier
 - Discriminator as trigger and a differential analogue memory for signal storage
 - On-chip 12 bit pipeline ADC for signal digitalisation

Outline


1 HitDetection ASIC Overview

2 Input Stage

- Analogue Input
- Noise Calculation
- Input Transistor
- Charge Integration

3 Analogue Memory

4 12 Bit Pipeline ADC

 

- Input stage consists of a CSA, single- end to differential stage and differential output

- Noise calculations for the input transistor as dominant noise source

$$ENC_{th}^2[e^2] = \frac{10 \cdot k_B \cdot T}{8 \cdot q^2} \frac{C_T^2}{\tau_s \cdot \sqrt{(k_x \cdot W/L \cdot I_{ds})}} \quad (1)$$

$$ENC_{1/f}^2[e^2] = \frac{4 \cdot K_f}{C_{ox}^2 \cdot q^2} \frac{C_T^2}{W \cdot L} \quad (2)$$

$$ENC_{DET}^2[e^2] = \frac{2}{q} \cdot I_{det} \cdot \tau_s \quad (3)$$


$$ENC_{tot}^2 = ENC_{th}^2 + ENC_{1/f}^2 + ENC_{DET}^2 \quad (4)$$

Const.	Value	Unit
k_B	1.38E-023	J/K
C_{ox}	8.22E-003	F/m^2
q	1.60E-019	C
T	300	K
K_f	5E-027	C^2/m^2
k_x	129E-006	F/Vs


Variable	Description
C_T	sum of all Cs at the input
W	transistor width
L	transistor length
I_{ds}	current through transistor
τ_s	shaping time
I_{det}	detector leakage current

- Set parameters for current design
 - Implement small capacitance for stability in differential OTA
 $\Rightarrow$ integration time $\tau_s = 10 \text{ ns}$
 - Detector leakage current: $I_{det} = 10 \text{ nA} \dots 100 \text{ nA}$

 
- Optimise transistor parameter W/L and I_{ds}
 - Input transistor ratio W/L high $\Rightarrow$ large input capacitance
 - Current through input transistor large $\Rightarrow$ high power consump.





- Optimise parameter $C_T = C_{gs} + C_{det} + C_f$
 - Low noise contribution $\Rightarrow C_T$ as small as possible
 - Detector capacitance C_{det} : is fix
 - C_{gs} increase with the transistor geometrie
 $\Rightarrow$ trade off between transistor width and capacitance
 - Feedback capacitance C_f : $\Rightarrow$ trade off between noise and dynamic range
- $C_{gs}=20\text{ pF}$; $C_{det}=50\text{ pF}$; $C_f=1\text{ pF} \dots 30\text{ pF}$
 $\Rightarrow C_T=71\dots100\text{ pF}$

 

 - Small capacitance for small signals $\Rightarrow$ better SNR



  
- Layout input transistor with $W/L: 35\,556\ (256 \times 25/0.18)$
- Input transistor area on chip: $330\ \mu\text{m} \times 95\ \mu\text{m}$




- Architecture of the programmable feedback
 - Option: Automatic or manual setting of feedback capacitance C_0 to C_4
- Design of the self switching-logic with one comparator

No.		Unit	Area	Unit
C_0	200	fF	220	μm^2
C_1	$4 \times C_0$	fF	880	μm^2
C_2	$16 \times C_0$	fF	3523	μm^2
C_3	$64 \times C_0$	fF	14080	μm^2
C_4	$128 \times C_0$	fF	28160	μm^2

 - Symmetrical layout for small capacitances
- Multiple of a unit $C_0 = 200 \text{ fF}$
- Max. input capacitance is 42.4 pF
(Output $1 \text{ V} \Rightarrow$ max. input charge is 42.4 pC)
- Capacitances placed over active area of the amplifier



- Gain: 5mV/fC and 0.024 mV/fC

 


- Lin. output range up to 42 pC


Outline

- 1 HitDetection ASIC Overview
- 2 Input Stage
- 3 **Analogue Memory**
 - Analogue Signal Storage and Derandomisation
 - Integrator Stage
- 4 12 Bit Pipeline ADC

 - Capacitor array used as analogue memory
- Analogue memory is divided into blocks with configurable size
- Signals from input receiver are sampled and stored at the position of write pointer
- Write pointer rotates inside of one block



 
- Signals from particle energy deposits are detected by the hit detection unit
- Write pointer switches to the next memory block
- Signal transient is stored in previous block
- Analogue readout when shared ADC is available
- Block is available again for signal storage





- Requirements for the integrator stage:
 - Fully differential operation
 - Input DC range: 0 - 1.5V
 - Pulse amplitude: $\pm 1V$
 - High linearity
 - High slew rate
- Use a fast integrator architecture without CMFB
 - Differential input
 - Auto zero circuit
 - Output buffer

Outline

 
- 1 HitDetection ASIC Overview
- 2 Input Stage
- 3 Analogue Memory
- 4 12 Bit Pipeline ADC**
 - ADC Overview
 - 1.5 bit Stage
 - Pipeline ADC Structure
 - ADC Measurement Results
 - Results



  
- Layout of the 12 bit pipeline ADC ($715\ \mu\text{m} \times 930\ \mu\text{m}$)
- Central: 1.5 bit stage (total 10 stages); last stage only comparator
- Voltage references below the pipeline stages
- On top: Digital logic (includes calibration)





 - MDAC works with 3 clock phases (reset/charge/readout)
- Amplifier: fast, stable, precise $\Rightarrow$ switched design



 - ADC measurements and analysis are done by Mainz colleagues



  

- Results of ADC measurements and analysis (carried out by colleagues from Mainz)
 - ADC has an INL of 2.26 LSB
 - ENOB of the ADC: 10
- Results of CSA measurements and analysis
 - ASIC is bonded and will be measured in June
- Results of memory measurements and analysis
 - Measurements and analysis are/will be done by colleagues from Mainz