


Development of 10 bit pipeline ADC and triggerless data processing readout

Marek Idzik
Sz. Kulis, K. Świentek, T. Fiutowski
AGH-UST Kraków


Outline

- Design and measurements of 10 bit pipeline ADC
- Triggerless readout with amplitude and time measurement
 - Simulations
 - Test setup
 - Measurements results





Design of 10 bit pipeline ADC

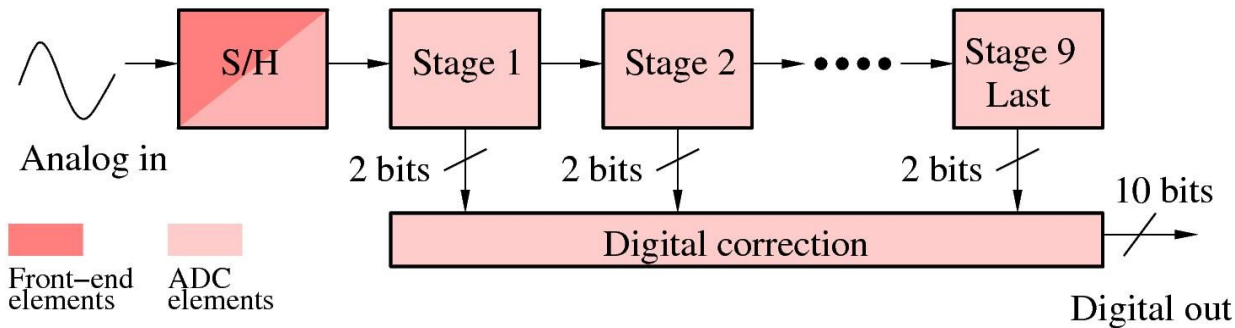

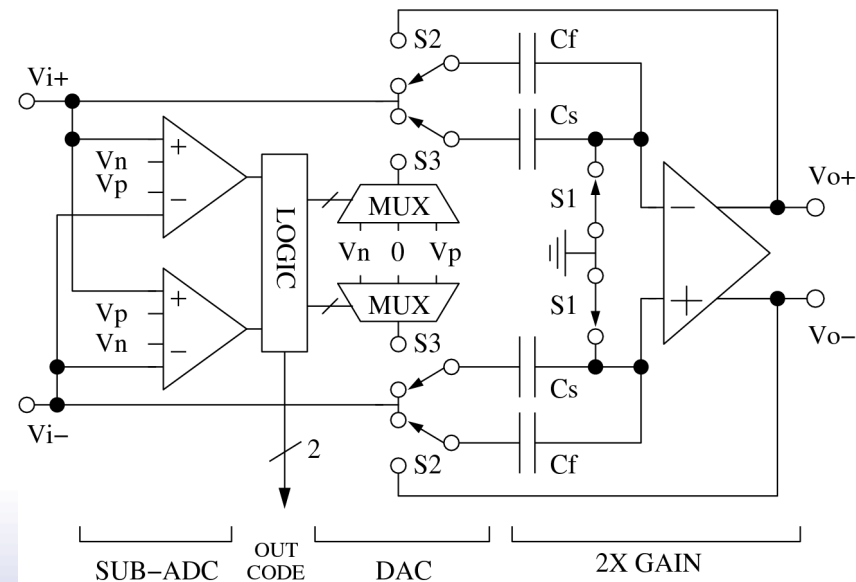- ❑ 10 bit pipeline ADC 1.5 bit/stage
- ❑ Variable sampling frequency up to ~25 Ms/s
- ❑ Scalable power consumption
- ❑ Fully differential
- ❑ Power switching OFF/ON (ILC, CLIC beam timing)
- ❑ Present version in 0.35 μm AMS, smaller size technology soon...




ADC static measurements

    


Very good linearity
 $INL < 1\text{LSB}$, $DNL < 0.5\text{LSB}$

ADC dynamic measurements

 

Good dynamic performance ENOB ~ 9.5 bit



ADC - power OFF/ON

 

Power ON
at t=0

Depending on sampling frequency 8-16 clocks needed for switching ON


ADC power consumption

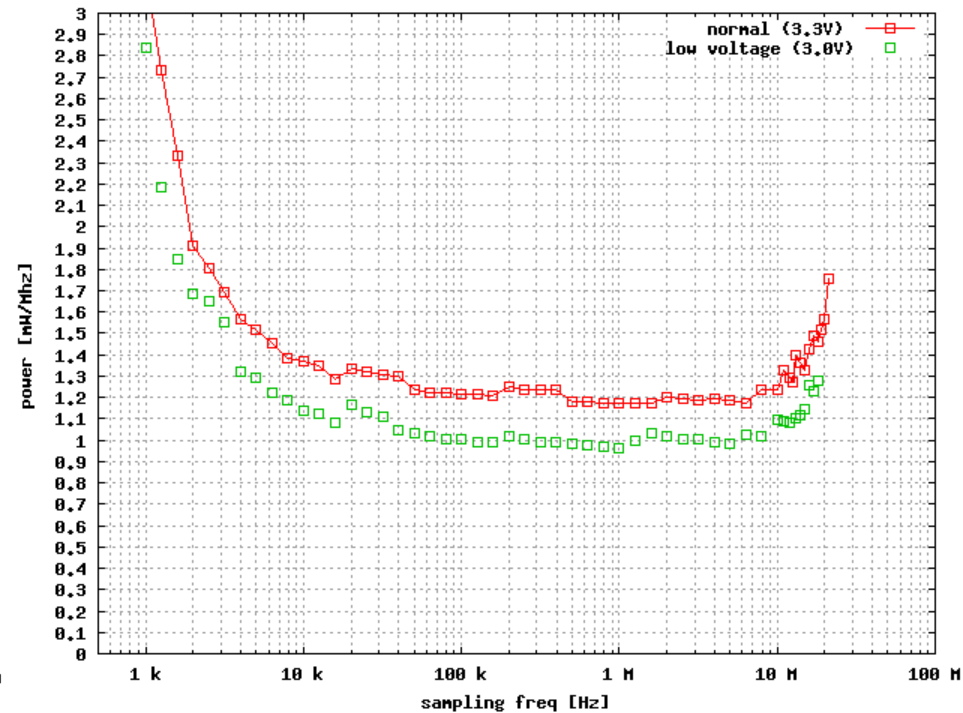 

Presently power consumption about 1-1.5 mW/MHz at worst case
(Nyquist input frequency, output buffers)


We have just submitted 8 channels ADC version layout with a pitch
200 μm per channel

Deconvolution - idea

 

- ❑ No trigger – ADC continuously running
- ❑ Fixed pulse shape at ADC input!!!
- ❑ Very good candidate is a semi-gaussian
1st order CR-RC, only 3 samples are needed
- ❑ Timing and amplitude information are obtained manipulating deconvoluted samples
- ❑ For CR-RC shaping - 100% pileup free if $\Delta T_{\text{pulse}} > 3T_{\text{samp}}$, e.g. $T_{\text{peak}} = 100\text{ns}$,
 $T_{\text{samp}} = 100\text{ns} \rightarrow$ no pileup if $\Delta T_{\text{pulse}} > 300\text{ns}$

 
Simulated example of deconvolution for CR-RC shaping and $T_{\text{peak}} = T_{\text{samp}}$



Amplitude info is obtained from the sum of blue samples and timing info from their ratio (for both lookup tables needed)


Deconvolution after CR-RC

 Deconvoluted samples, their ratio and sum



Simulated

 Timing and Amplitude error vs Sampling time
 $S/N = 25$ was used for this MC




Other than CR-RC shapers are also considered but not shown here
 since no measurements are available



Readout architecture for luminosity detector at ILC/CLIC

Prototypes in AMS
0.35 μm

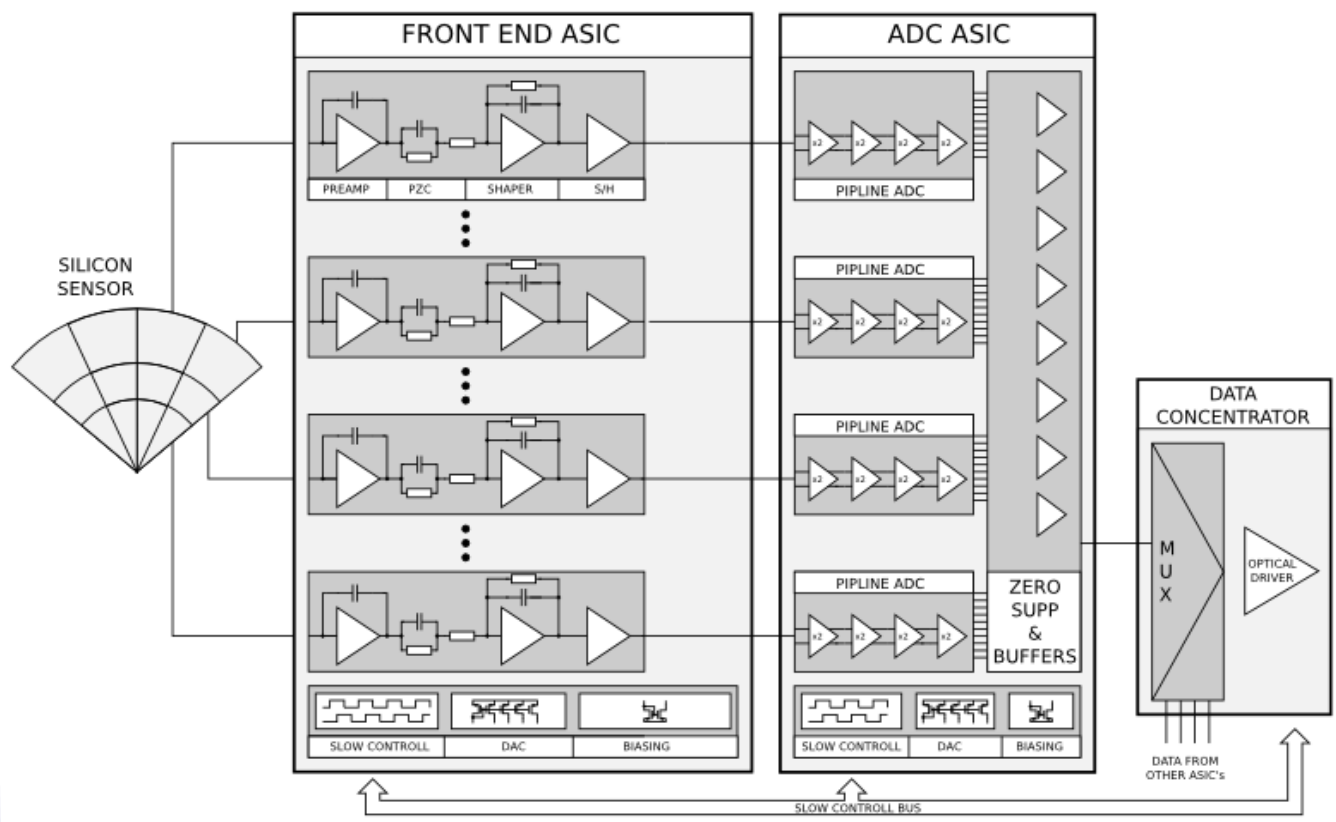
- 8 channels front-end
- 1 channel ADC (no zero suppression)



Preamplifier & PZC & Shaper

 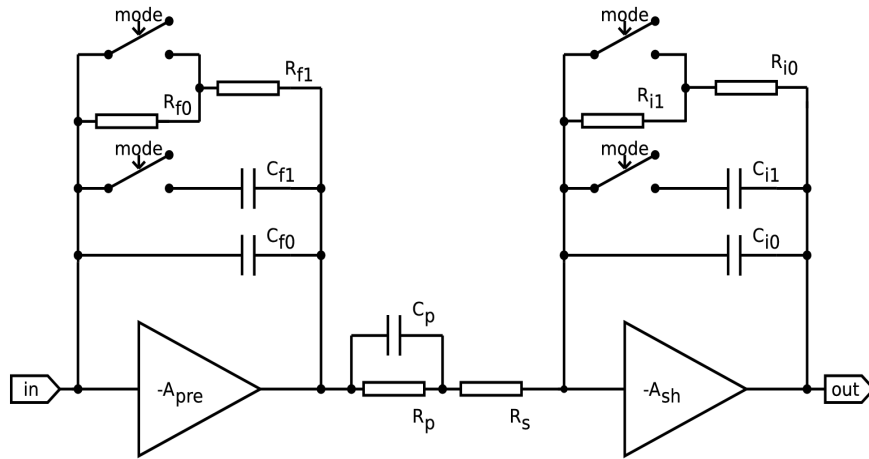


$$\frac{U_{out}(s)}{I_{in}(s)} = \frac{1}{C_f C_i R_s} \cdot \frac{s + 1/C_p R_p}{s + 1/C_f R_f} \cdot \frac{1}{(s + 1/C_i R_i)(s + 1/C_p (R_p || R_s))}$$

 

- ❑ ASIC with 8 channels
- ❑ Variable gain (MIPs and high input charge up to ~ 10pC)
- ❑ C_{det} range ~ 0-500 pF
- ❑ 1st order shaper $T_{peak} \sim 60$ ns
- ❑ Power consumption < 9 mW/chan








Test setup preparation

 - ❑ Dedicated PCB board
- ❑ Silicon sensors for LumiCal
- ❑ Dedicated fanout
- ❑ 8 channel ASICs with preamplifier and shaper plus external buffers
- ❑ At present 8 channels external ADC (CAEN, our prototype has only 1 channel)










The results shown on next slides are obtained with electrical input test pulses - sensor not yet mounted

Measurements for S/N=25

       

$\Delta t / T_{\text{sampling}}$ resolution < 6%, Amplitude resolution ~ 3-4% 13

Measurements for $S/N=70$

       


$\Delta t/T_{\text{sampling}}$ resolution $\sim 4-5\%$, Amplitude resolution $\sim 1.8\%$ 14

Summary


- Works on readout architecture with triggerless data sampling and signal deconvolution started:
 - Simulations studies with different shapers
 - Measurements with CR-RC shaper
- First measurements show promising results regarding timing and amplitude resolution
- Good agreement between simulations and measurements
- To be done:
 - Measurements with prototype multichannel ADC ASIC
 - Further ADC development (for less power)
 - Other shapers...
 - ...
- Thank you

Front-end measurements

Gain

 

Noise

 

Mode	Gain [mV/fC]	Noise@50pF [fC]	Linearity [pC]	Rate [MHz]	Crosstalk [%]
Physics	0.107	0.62	10	3	≈1
Calibration	≈20	0.28	0.035	2.5	≈0.1